

# Automated PCB Parasitics Extraction from EDA Tools for Power Electronics Design Support

Sven FIEßER, PhD student, Technical University Ilmenau

# Personal Introduction



**Sven Fießer**

**PhD Student:** Research in HV-SMPS for magnetron applications and SMPS/PCB design at the Technical University Ilmenau

**In cooperation with:**  
University of Applied Sciences  
Fulda, Germany



**Prof. Dr.-Ing.  
Ulf Schwalbe**



University of Applied  
Sciences Fulda

- Renewable Energies
- E-Mobility
- Power Electronics
- Energy Storage  
Systems for Grid  
Integration

# Agenda

1. Background Information
2. Methods for Parasitic Extraction
  - a. Inductances and Resistances
  - b. Capacitances
3. Verification
4. Automated Parasitic Extraction
5. Simplification by Critical Path Extraction
6. Conclusion

# Background Information

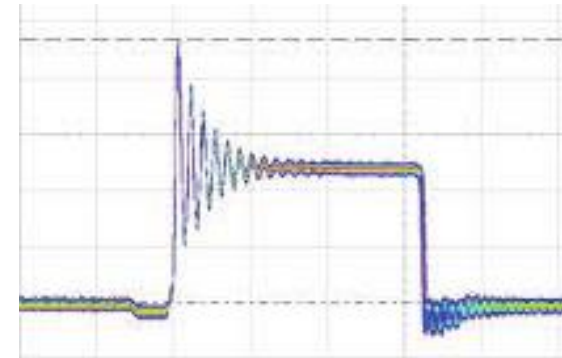 


Source: R. Taylor 2012

Parasitic components in every power converter

Results in unwanted ringing in the switching elements

- Increasing the power density by higher switching frequencies (e. g. with GaN and SiC semiconductors)
  - Low parasitic PCB components are necessary
  - Several design iterations until a good layout is created
  - Reduce design process by evaluating its effects while routing the PCB

# Method for Parasitic Extraction

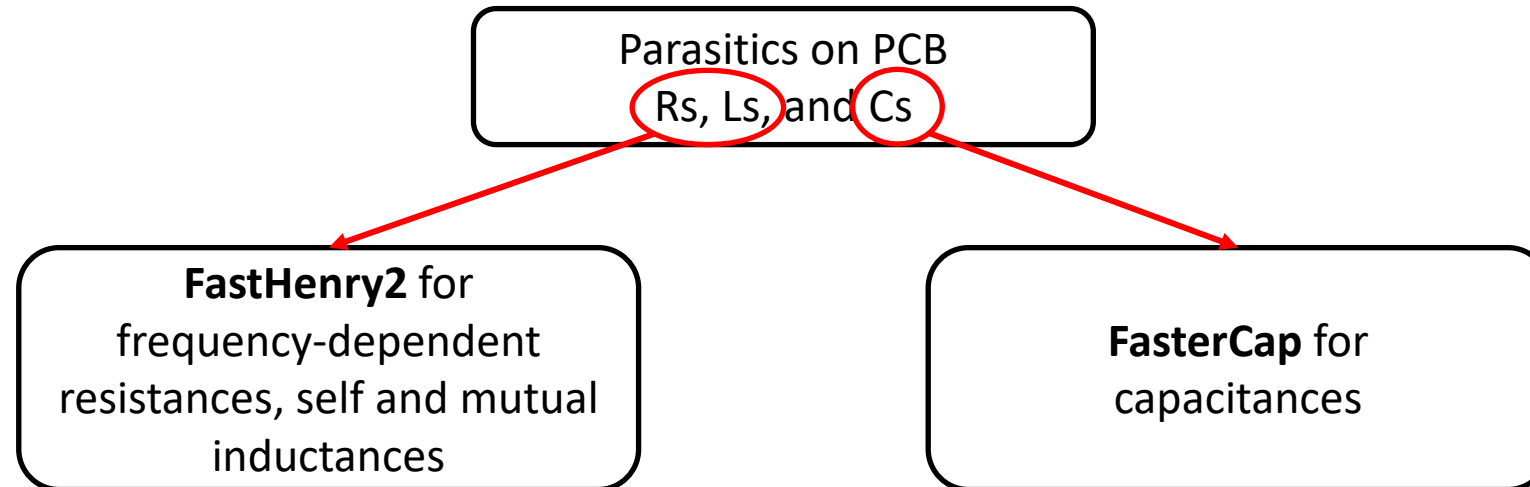

# Method for Parasitic Extraction

## FastHenry

- Developed at M.I.T. on Unix platform
- For the solution of Maxwell equations and extraction of **inductances** and **resistances** (includes **coupling** effects) in 3D
- FastHenry2 as a Windows porting

## FastCap

- Developed at M.I.T. on Unix platform
- For the solution of Maxwell equations and extraction of **capacitances** in 3D
- FastCap2 as a Windows porting
- FasterCap with several improvements (lossy dielectrics, automatic mesh refinement, ...)

→ FOSS

Source: [fastfieldsolvers.com](http://fastfieldsolvers.com)

# Method for Parasitic Extraction


## FastModel

Windows 3D viewer and text editor for  
FastCap2, FasterCap and FastHerny2

Download:

[www.fastfieldsolvers.com/download.htm](http://www.fastfieldsolvers.com/download.htm)

(contact form can be left empty)

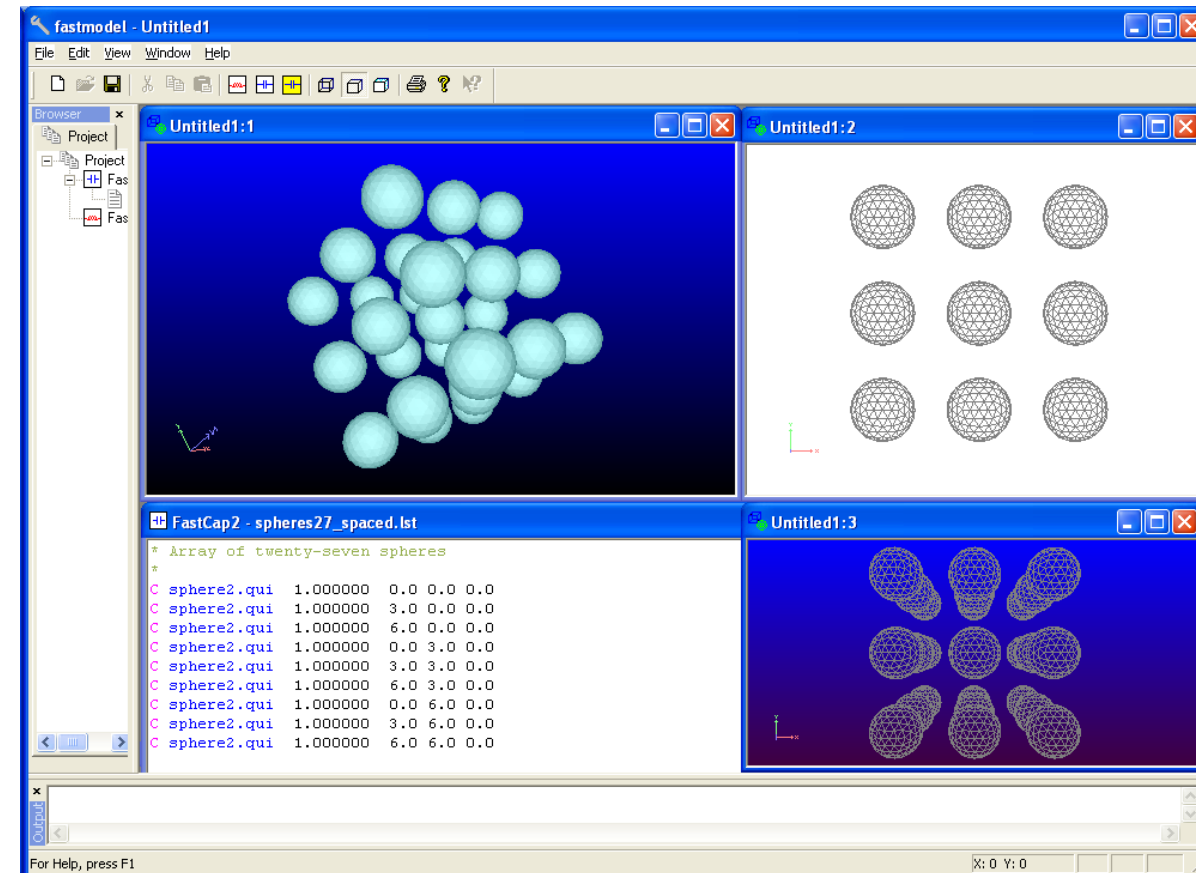

# Method for Parasitic Extraction

## Converter for FastHenry2

### Input

- Geometry of the *copper traces* in 3D using
  - Elements (connection between two Nodes) → Wires
  - Planes (incl. Holes) → Planes
- Frequency range
- Material properties of the copper (conductivity)

### Output


- Maxwell matrix for each frequency
- SPICE model



# Method for Parasitic Extraction

## FastHenry2 Inputfile Example

## Converter for FastHenry2

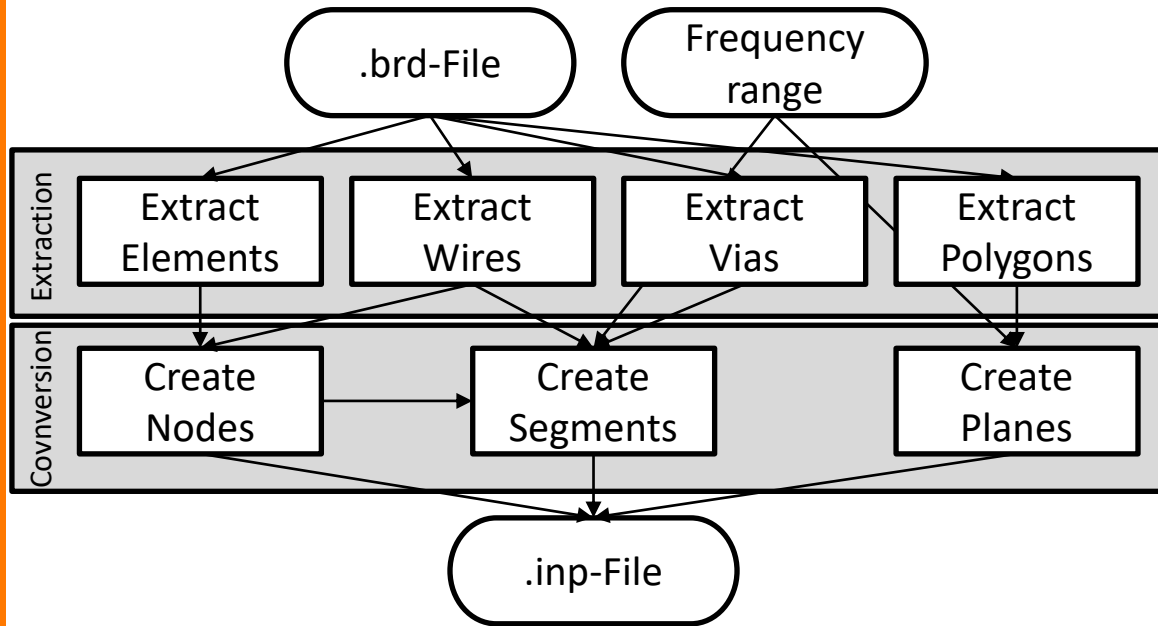

```

.Units MM
.Default z=0 sigma=5.8e4


*NODES
*=====
N1_X16_1 x=23.025 y=53.5611 z=1.6
N2 x=38.5889 y=53.5611 z=1.6
N3_C12_+ x=39.0 y=53.15 z=1.6
...

*ELEMENTS (== wires)
*=====
E1 N1_X16_1 N2 w=2 h=0.035 nwinc=15 nhinc=4
E2 N2 N3_C12_+ w=2 h=0.035 nwinc=15 nhinc=4
...

*PLANES
*=====
g1N$27 x1=69.0 y1=23.0 z1=1.6 x2=69.0
+y2=58.0 z2=1.6 x3=121.0 y3=58.0 z3=1.6
+thick=0.035 seg1=100 seg2=100
+nQ6_2 (100,28,1.6)
+nD3_1 (118,48,1.6)
+hole rect (115,29,1.6,121,23,1.6)
+hole rect (112,26,1.6,115,23,1.6)
...

*START- AND ENDPOINTS
*=====
.external nQ6_2 nD3_1
...

 *FREQUENCY RANGE
*=====
.freq fmin=100 fmax=100e6 ndec=1
.end
  
```



Source: M. Kamon 1996

$$\delta > \begin{cases} \frac{W}{2 \sum_{i=0}^{nwinc/2-1} r^i} & \text{if } nwinc = \text{even,} \\ \frac{nwinc - 1}{r \frac{1}{2} + 2 \sum_{i=0}^{(nwinc-1)/2-1} r^i} & \text{if } nwinc = \text{odd.} \end{cases}$$

# Method for Parasitic Extraction

## Converter for FasterCap

### Input



- Geometry of the *copper traces* and *PCB* in 3D using
  - Triangles or Squares
- Material properties of the PCB (relative permittivity)
  - for FR4 approx. 4 (see datasheet)

### Output

- Maxwell matrix

# Method for Parasitic Extraction

## Converter for FasterCap

 
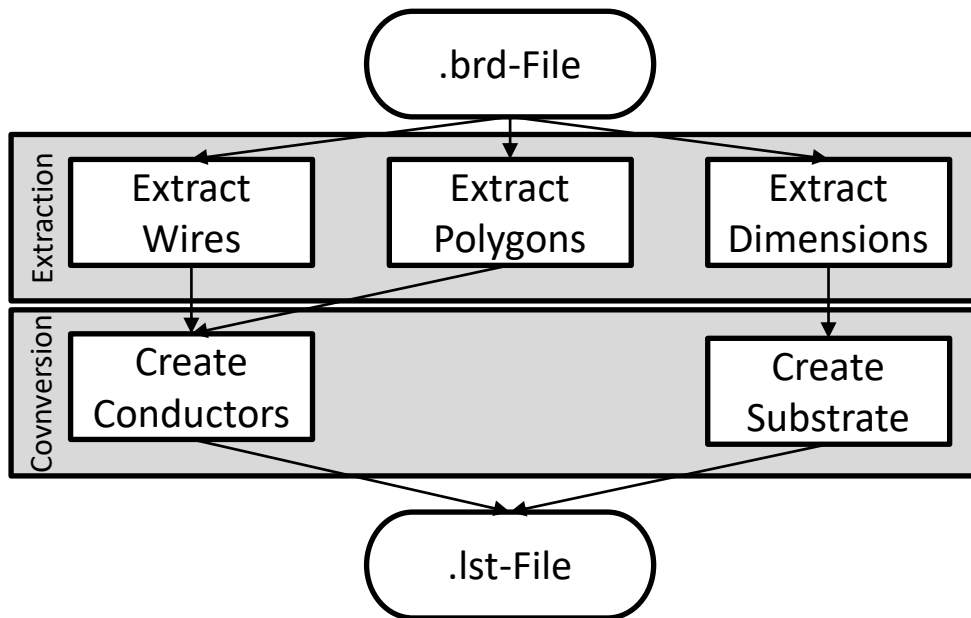


- For FasterCap only a rough mesh is needed → FasterCap does the mesh refinement (FastCap needs this to be done by hand)
- The meshing is done using **Gmsh**  
[www.gmsh.info](http://www.gmsh.info)

# Method for Parasitic Extraction
  
## Example FastHenry2 - Backend

Boost-Converter – w/o Plane – w/o GND-Plane




### Maxwell-Matrix for each given frequency

```

Computed matrices (R+JL)
Row 0: n4 to n5      *C1_+ - L1_2
Row 1: n9 to n10    *L1_1 - Mittelpunkt
Row 2: n10 to n16   *Mittelpunkt - Q1_2
Row 3: n10 to n12   *Mittelpunkt - D1_1
Row 4: n25 to n26   *D1_2 - C3_+
Row 5: n45 to n46   *Q1_3 - Punkt zu GND
Row 6: n35 to n46   *C3_- - Punkt zu GND
Row 7: n46 to n42   *Punkt zu GND - C1_-
Freq = 1e+06
Row 0: 0.0075634+1.80117e-08j 1.35612e-06+2.03218e-09j 5.33902e-07-1.16422e-12j 1.03529e-06+7.08856e-10j 3.14947e-07+3.42858e-10j 2.31339e-07-1.70688e-12j -3.34644e-06-1.18411e-09j 7.25318e-07-3.00028e-09j
Row 1: 1.3411e-06+2.03233e-09j 0.00812196+2.01008e-08j 9.88968e-08-1.15908e-12j 3.56848e-05+2.80854e-09j 3.69332e-07+6.55626e-10j 2.00173e-07-2.01634e-12j -5.90326e-06-1.86375e-09j -1.16568e-05-3.28489e-09j
Row 2: 5.25811e-07-1.12886e-12j 9.68636e-08-1.11943e-12j 0.00748078+1.8141e-08j 2.45561e-06+5.13625e-11j 3.40801e-07-2.96845e-13j 1.78785e-06+8.99193e-10j -3.58937e-07+1.99873e-09j -2.23086e-06-1.40691e-09j
Row 3: 1.05978e-06+7.22454e-10j 3.56755e-05+2.80852e-09j 2.4586e-06+5.1317e-11j 0.00507248+1.08617e-08j -1.25971e-06+7.13035e-10j 3.7836e-07+8.71661e-12j -4.08145e-06-1.31808e-09j -7.36468e-06-1.76729e-09j
Row 4: 3.29958e-07+3.47244e-10j 3.59011e-07+6.5567e-10j 3.45459e-07-3.1816e-13j -1.26473e-06+7.1307e-10j 0.00367591+7.27724e-09j 4.13288e-08-3.5601e-13j -3.67522e-06-1.00109e-09j -3.35448e-06-9.59923e-10j
Row 5: 2.16733e-07-1.73563e-12j 2.07737e-07-2.0763e-12j 1.79547e-06+8.99142e-10j 3.77779e-07+8.72701e-12j 4.05103e-08-3.55199e-13j 0.00293433+5.30378e-09j -6.51506e-05+7.08669e-10j 5.63014e-05-3.93222e-10j
Row 6: -3.56666e-06-1.19742e-09j -6.05793e-06-1.86264e-09j -3.87833e-07+1.99894e-09j -4.17694e-06-1.31733e-09j -3.75499e-06-1.00048e-09j -6.51656e-05+7.08807e-10j 0.0233713+6.46531e-08j -0.000127451+5.44038e-09j
Row 7: 5.48584e-07-2.99955e-09j -1.19656e-05-3.28263e-09j -2.34312e-06-1.40628e-09j -7.55533e-06-1.7827e-09j -3.49382e-06-9.53236e-10j 5.63034e-05-3.93169e-10j -0.000128158+5.44779e-09j 0.0307431+8.87394e-08j
    
```


### SPICE model

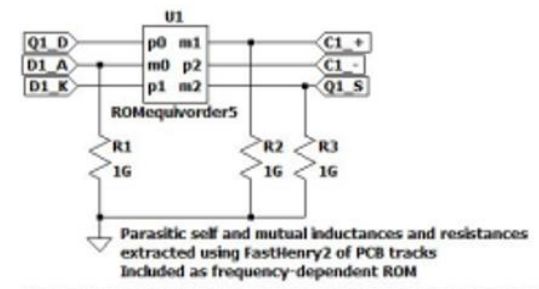

# Method for Parasitic Extraction
 
## Example FastHenry2 - Frontend


Boost-Converter - w/o Plane - w/o GND-Plane



Name	L	R	$\Delta L$	$\Delta R$
Cond1	10 nH	1 m $\Omega$	- 10 %	- 11 %
Cond2	15 nH	2 m $\Omega$	+ 15 %	+ 16 %
Cond3	20 nH	3 m $\Omega$	- 10 %	- 11 %
...	...	...	...	...



## SPICE model

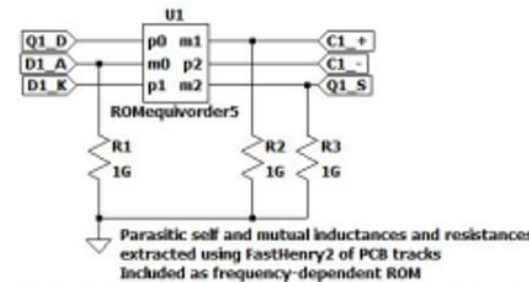


Extraction process for FasterCap is similar


# Method for Parasitic Extraction
 
## Optimization Process

Boost-Converter – w/ Plane – w/o GND-Plane



 Boost-Converter – w/ Plane – w/ GND-Plane



### Exemplary optimization by

1. Insertion of a plane in the critical path


2. Insertion of a ground plane

→ Evaluation of the parasitic components and its influences


# Verification

1. Autodesk EAGLE
2. RCL extraction from EAGLE
3. Boostconverter-PCB verification setup

Boostconverter in EAGLE:

 


Boostconverter-PCB for verification:

 




# Verification

4. SPICE simulation
  - a. Parasitic RCL included
  - b. Switch/Diode models included
5. Comparison simulation and actual board

Comparison simulated and measured data:

 

 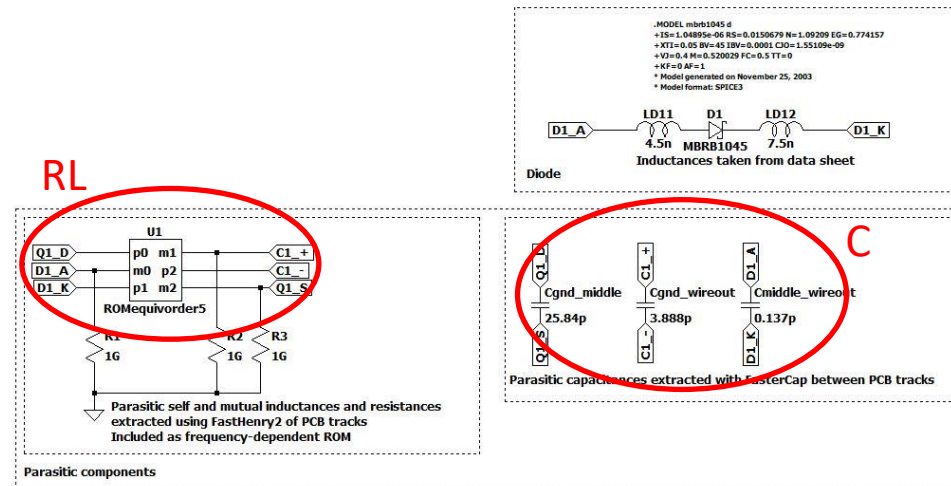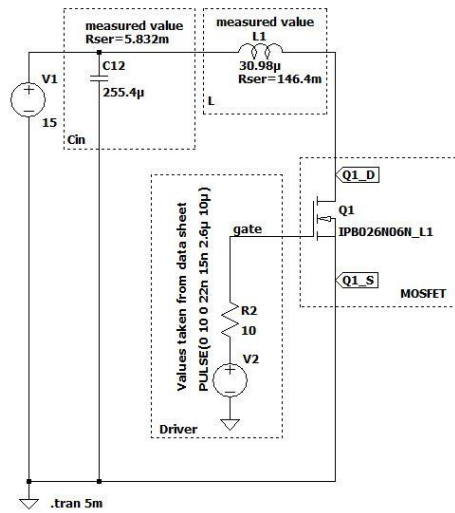SPICE simulation including PCB parasitics:






  
# Verification

Measurement of the parasitic capacitances between the wires using the **Bode 100** from Omicron Lab.

Parasitic Capacitances between each conductor



→ Measured capacitances match quite the simulated values.

# Benefits

- Why go through so much trouble?
- Why not use the rule of thumb for inductance of PCB tracks? →  $8 \text{ nH/cm}$

## Pro:


+ easy

## Con:

- Width and height neglected
- No skin effect ( $f_{\text{ringing}} > f_s$ )
- No coupling effects (e. g. GND-planes)

- Proper selection of switching components ( $V_{\text{ds\_max}}$  and  $P_{\text{v\_max}}$ )
- Proper dimensioning of snubber elements


Example of one PCB track

 

Source: [www.powersystemsdesign.com/articles/pcb-layout/22/5871](http://www.powersystemsdesign.com/articles/pcb-layout/22/5871)
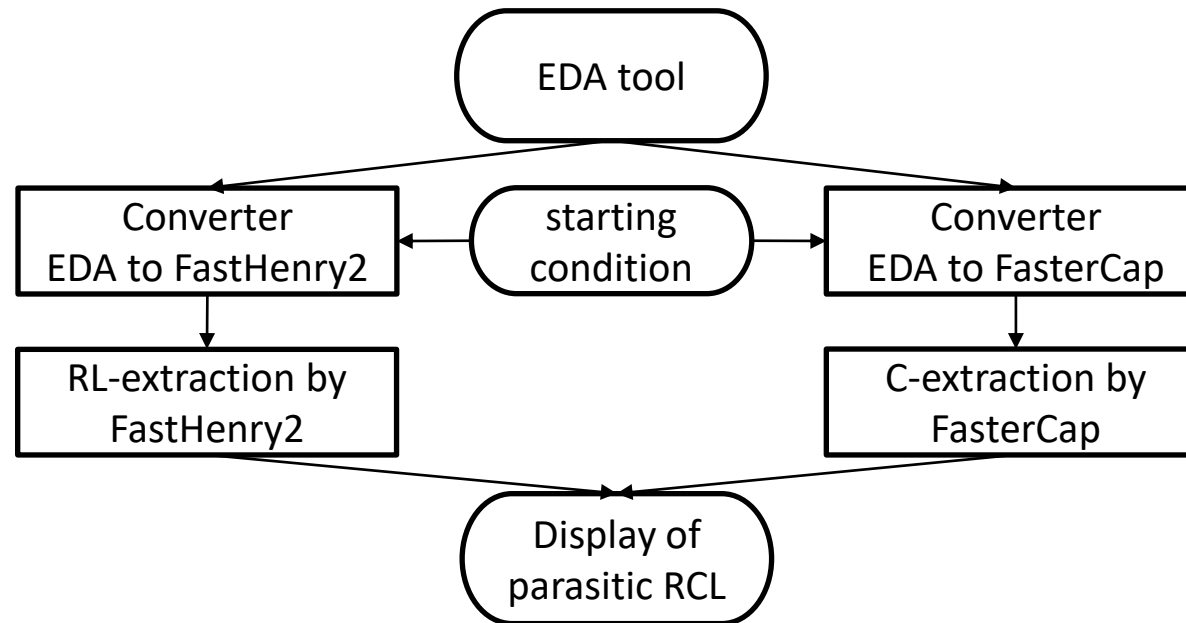
# Automated Parasitic Extraction

Second program for continuous RCL extraction



# Simplification by Critical Path Extraction

Problem so far: The converters convert every wire on the PCB

Solution: Tell the converters which wires to extract

→ only in the critical path

Not everyone knows where the critical path in every converter is

→ Calculate it

# Simplification by Critical Path Extraction


## Extraction using SPICE

- 1) Creation of a (ideal) SPICE file.
- 2) Run the simulation and parse the waveform file.
- 3) Calculate  $di/dt$  and  $du/dt$  of every waveform according to equation 1.
- 4) Calculate the rms value of the differentiated waveforms according to equation 2. The highest values indicate the critical path.


$$\frac{\Delta x}{\Delta t} = x_{t+1} - x_t \quad (1)$$

$$\text{RMS of diff. waveform} = \sqrt{\frac{\sum_i^n \left(\frac{\Delta x_i}{\Delta t_i}\right)^2}{n}} \quad (2)$$
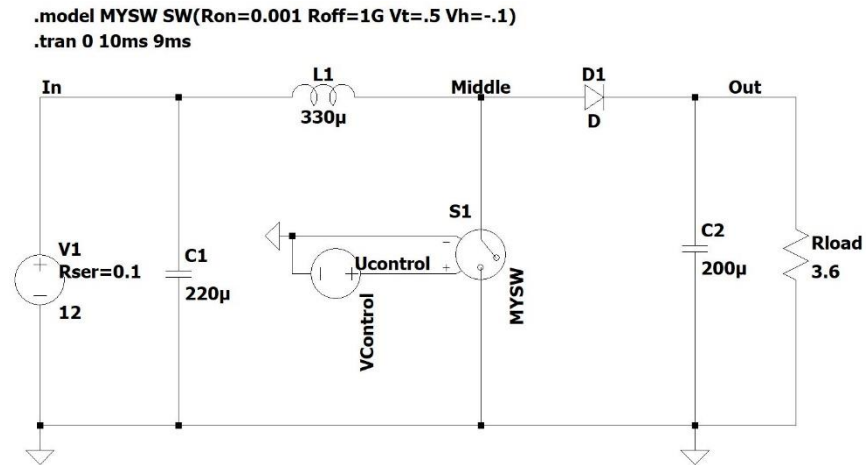
# Simplification by Critical Path Extraction



 
Ideal boost converter used for the critical path extraction




Graphical output of each element from the Simulation color-coded (red: critical path)

# Simplification by Critical Path Extraction

## FastHenry2

 

## FasterCap

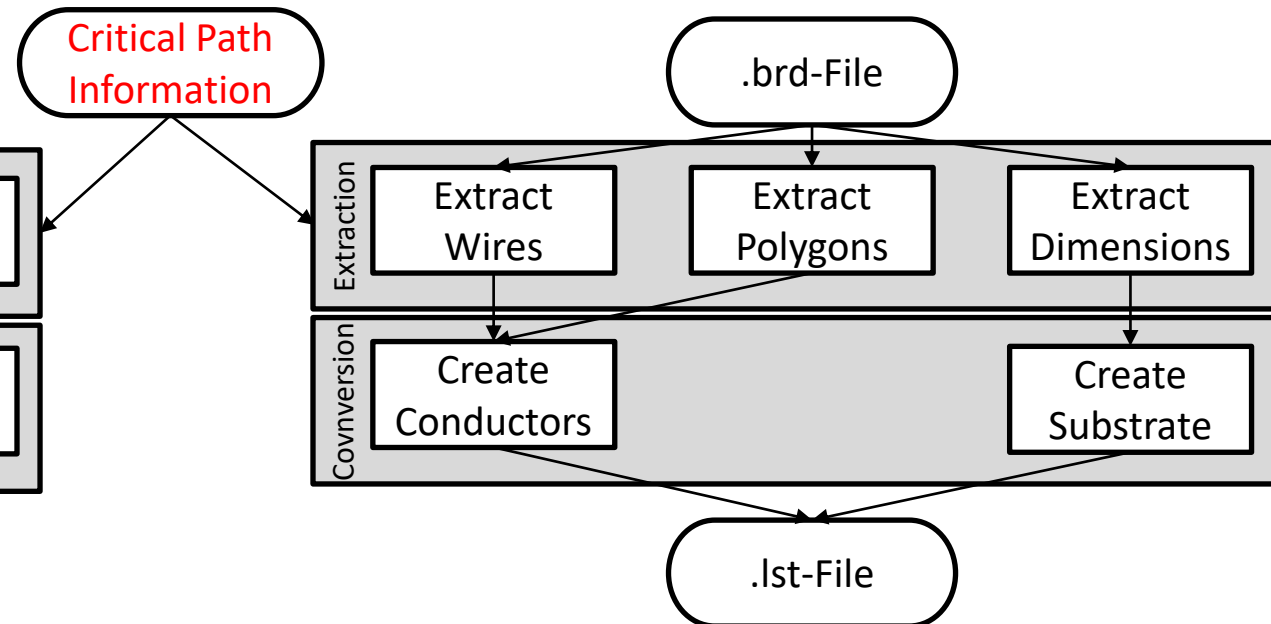

# Current and Future Works and Limitations

- Parasitic extraction works well with “easy” geometries
- Wires and planes on top of each other not supported yet
- How to prevent GIGO:
  - PCB must be modelled correctly
  - Correct SPICE models of switching elements
  - ESR/ESL of capacitances must be modelled correctly (→ e. g. with the Bode 100)
- Publication of the tool as soon as every bug is fixed



# Conclusion

The critical path in any given power converter can be found.

The parasitic components can be simulated before the PCB is manufactured.

Especially in the high-frequency switching domain this evaluation comes in handy to shorten the PCB design process by reducing the design and testing iterations.

# Contact

## **M.Sc. Sven Fießler**

Technical University Ilmenau  
Ehrenbergstraße 11  
98693 Ilmenau, Germany  
sven.fiessler@tu-ilmenau.de

## **Prof. Dr.-Ing. Ulf Schwalbe**

University of Applied Sciences Fulda  
Building 33, Room 113  
Leipziger Straße 123  
36037 Fulda, Germany  
ulf.schwalbe@et.hs-fulda.de

