

# A Power Supply Filter for On-board Voltage Socket with 12V 10A

Omicron-Lab: 13th Power Analysis & Design Symposium

2024-04-17



12V 10A

???

# How did it start?

- My customer offers 12V battery powered systems for portable application.
- An opportunity raised to sell it for a vehicle application.
- He did it and told us: „I need a power supply cable for a On-board Voltage Socket.“



# Now the trouble started!

- Supply track extended from 0.25m to 5m
  - 20 times longer
  - Supply impedance increased
- Input voltage varies
  - Battery had controlled 12V output
  - Car supply ranges from 10 ... 14V with intermediate drops
- Additional interference sources
  - Other devices in the car may introduce noise on supply line
  - Our system may impact other devices via shared supply



# We need a power supply filter!


## Requirements on power supply filter

From User:

- Allow an easy integration
- Do not delay system delivery!

From System:

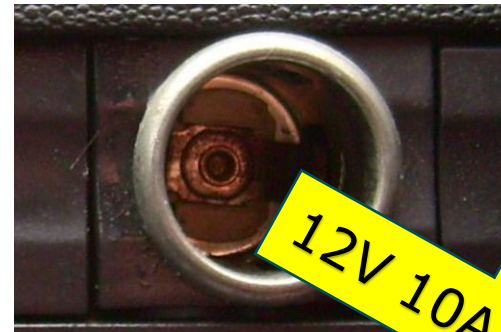- Block noise and interference
- Buffer fast voltage drops
- Lower supply impedance



12V 10A

**Filter**

**System**

# Let's be more specific

## Interference


- Isolation: > 40dB
- Frequency: 1kHz ... 10MHz

## Housing

- For dry environment (IP20)
- Easy mounting
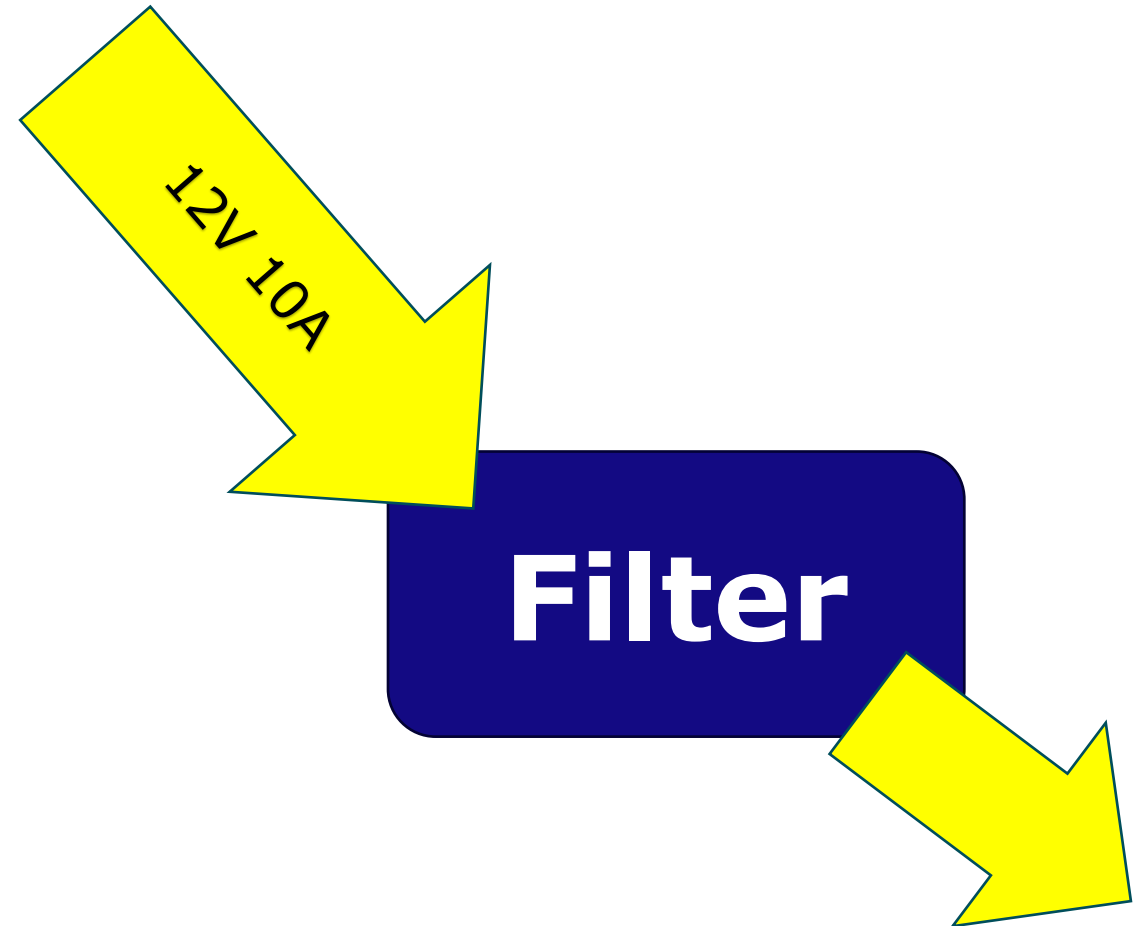
## Electric

- Voltage: 8 ... 16V
- Current: 0 ... 12A
- DC +/- runs through Filter




# Low impedance requirement (1)

Inside our system there are many DC/DC converters.

- Known and unknown ones.
- All of them require a low source impedance.


Middlebrook Criteria:

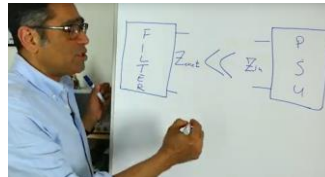- $Z_{\text{source}} \ll Z_{\text{in}}$
- Valid for loop frequency range



Assumption:

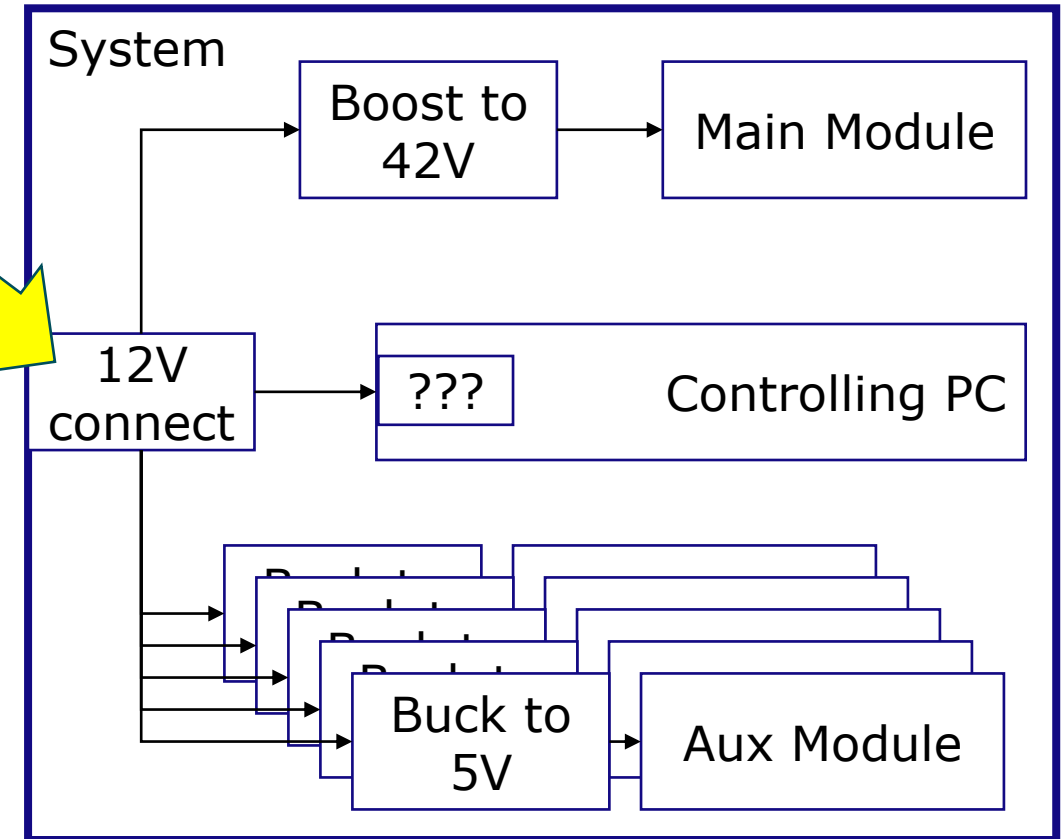- Max. switching: 2MHz
- Max. loop: 200kHz (=2MHz/10)



# Low impedance requirement (2)

Peak load is 120W

$$\begin{aligned} &= 12V * 10A && (R_{in} = 1.2\Omega) \\ &= 10V * 12A && (R_{in} = 0.82\Omega) \\ &= 14.4V * 8.3A && (R_{in} = 1.73\Omega) \end{aligned}$$

Dynamic input resistance (est.)

$$R_{Dyn} = 0.82\Omega - 1.73\Omega = -0.91\Omega$$

Supply wire inductance

length = 10m (2x5m)

$\varnothing = 4\text{mm}$

$L = 215\mu\text{H}$  (<https://chemandy.com>)

Supply impedance with wire


- $500\Omega$  @ 400kHz ✗
- $50\Omega$  @ 40kHz ✗
- $5\Omega$  @ 4kHz ✗
- $0.5\Omega$  @ 400Hz ✗
- $0.15\Omega$  @ 100Hz ✓

Only at frequencies **below 100Hz** supply impedance is low enough to fulfill Middlebrook criteria!
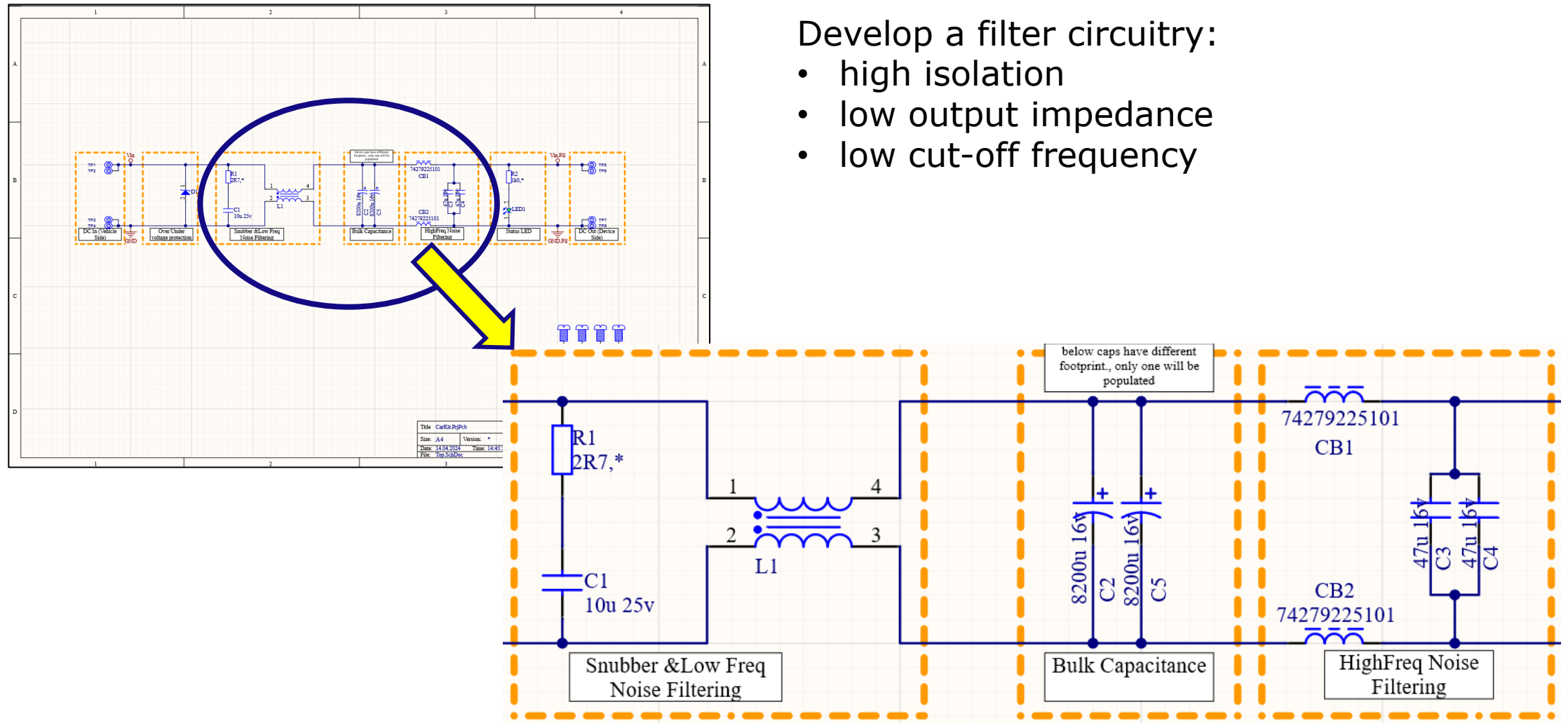
# Developing schematic




Develop a filter circuitry:

- high isolation
- low output impedance
- low cut-off frequency







# Verify with simulation

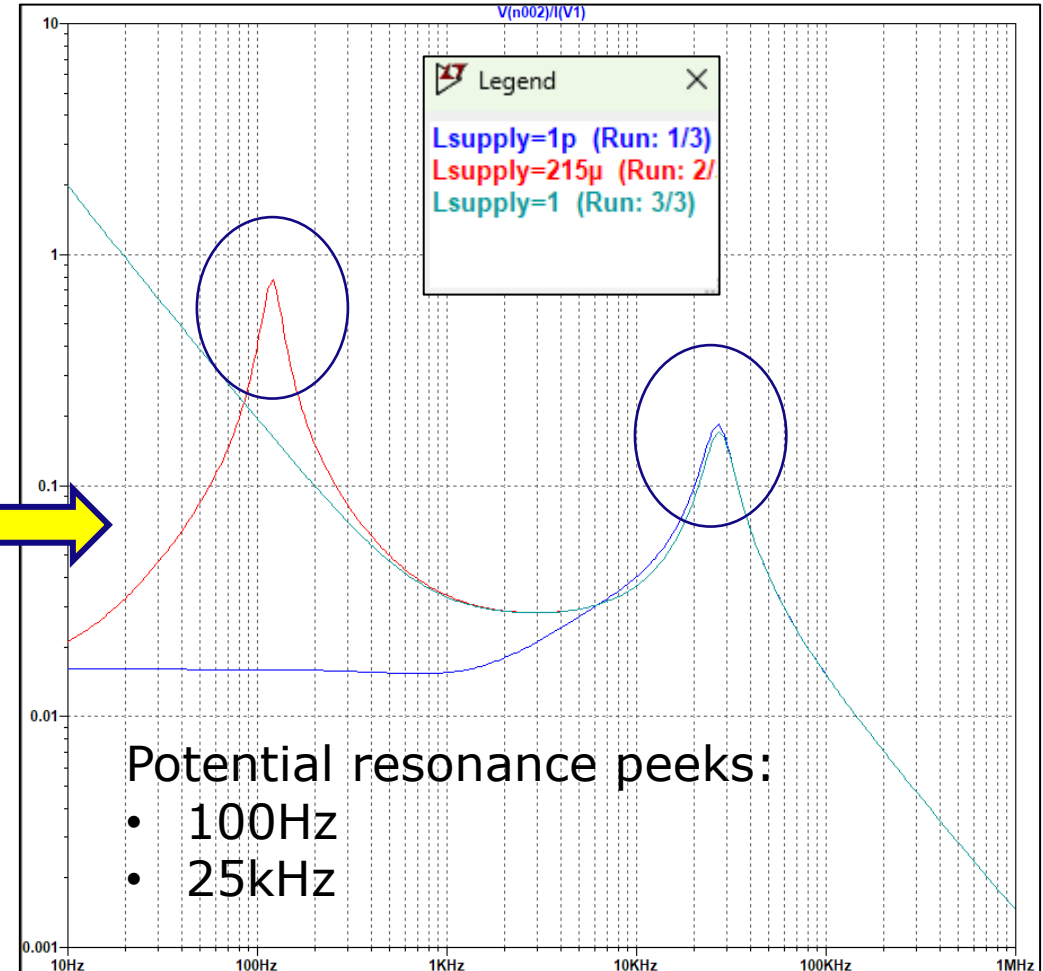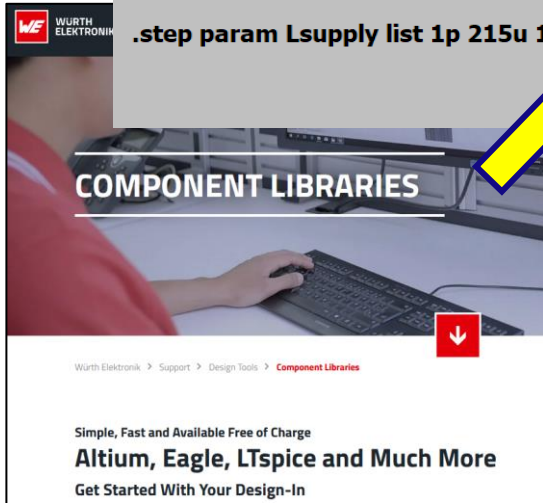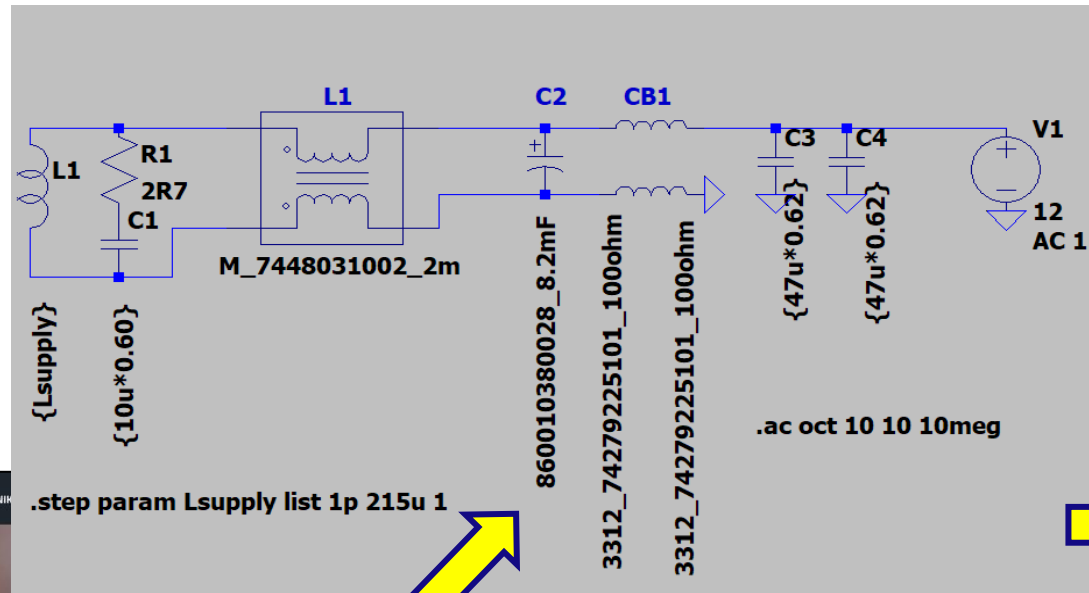

# Layout

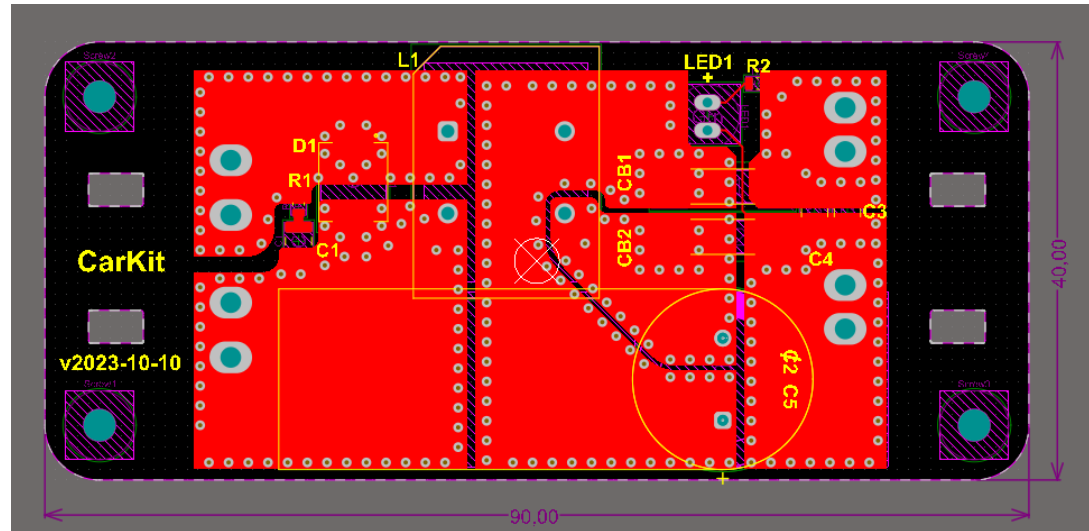

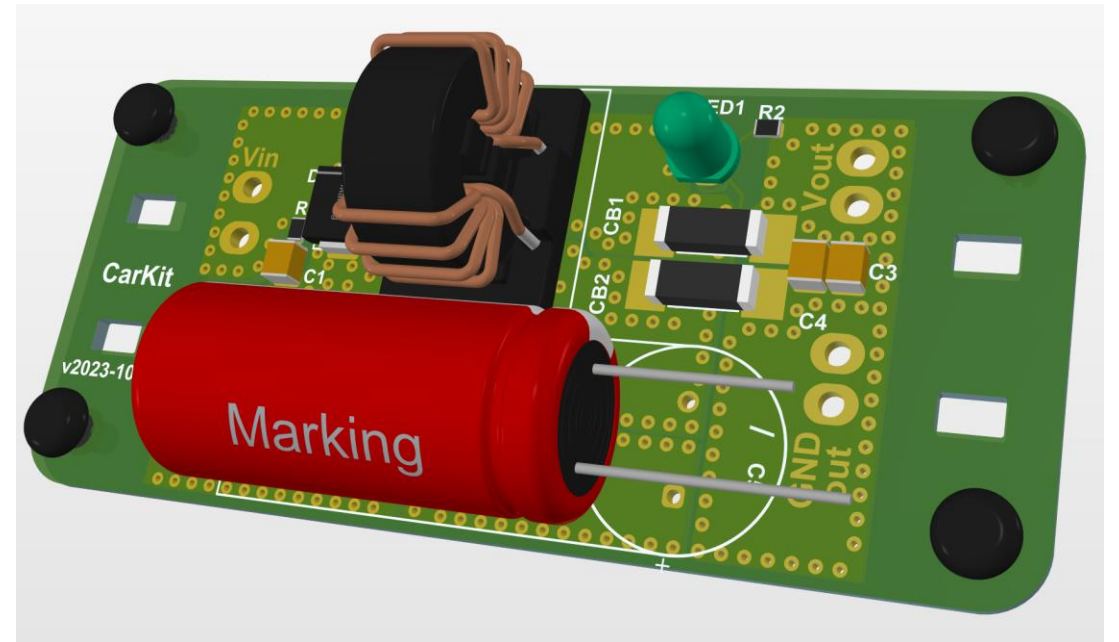PCB: FR4, 2 layer, 1.6mm  
Population: one side, SMT&THT  
Compact!




# Housing (1)

## Specification


- Easy to mount
- IP20

## Implementation

- 3D-Print
- Snap Rivets, no screws



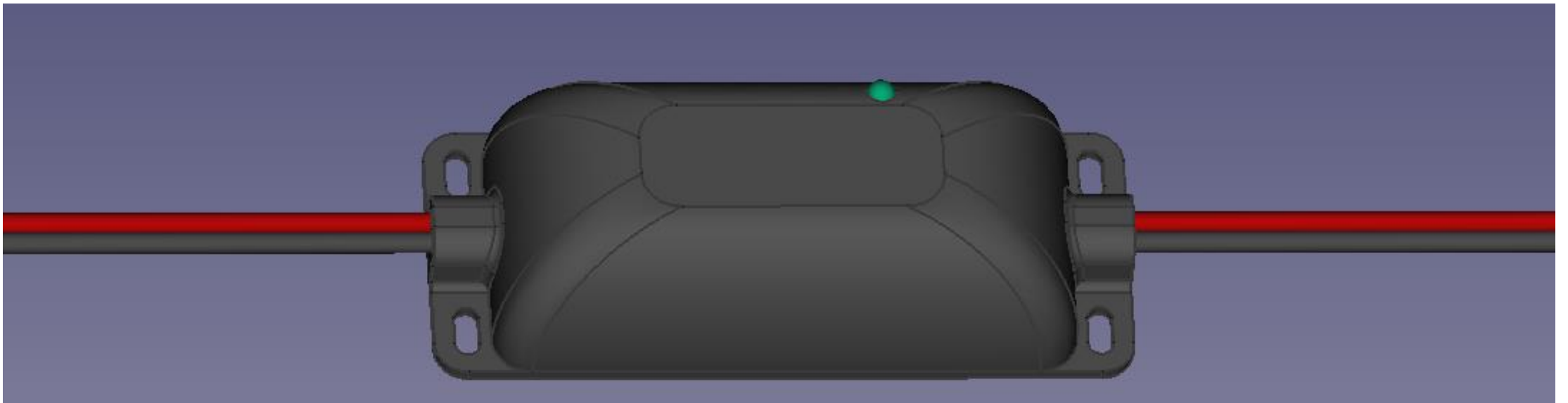


# Housing (2)


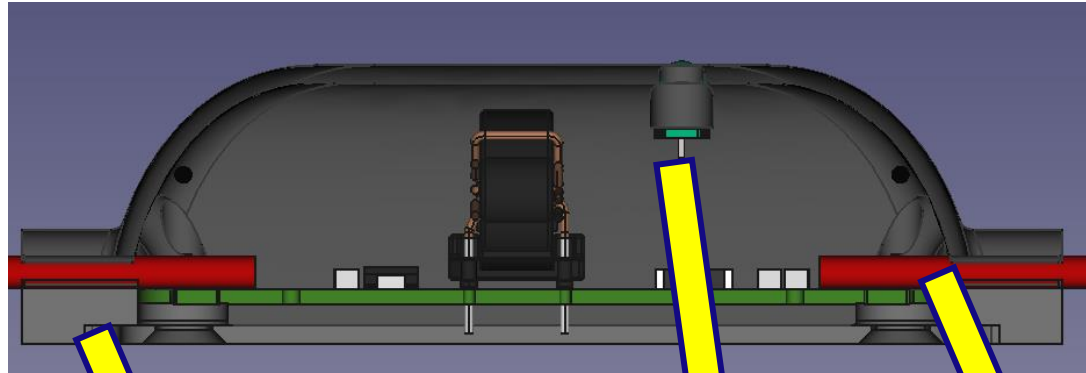

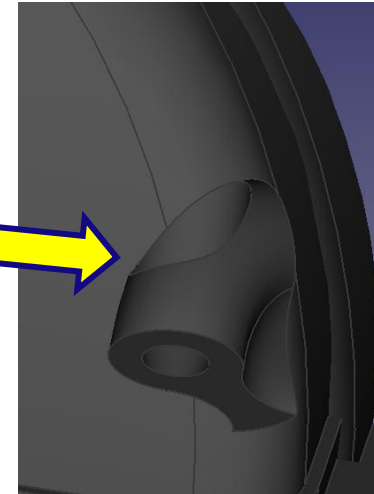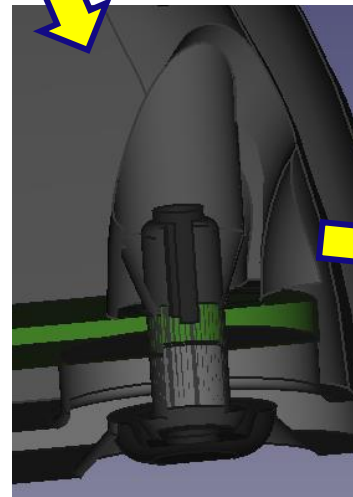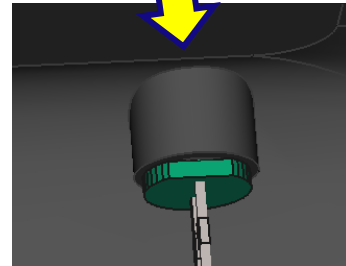
## 3D-Print housing

- Cable clamp
- LED protection
- Snap rivet holder




# Final Product

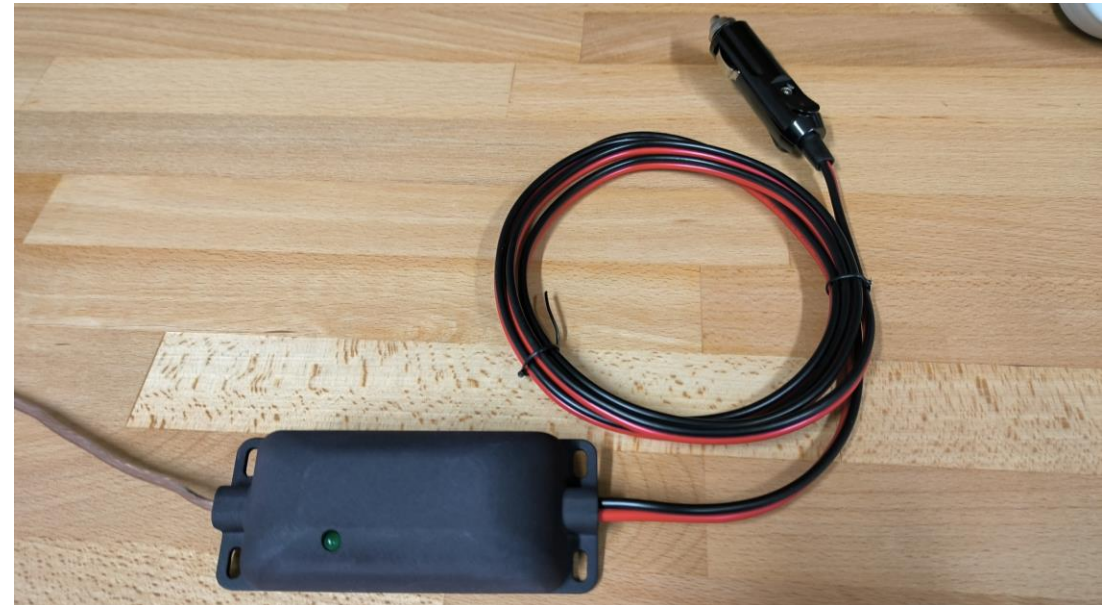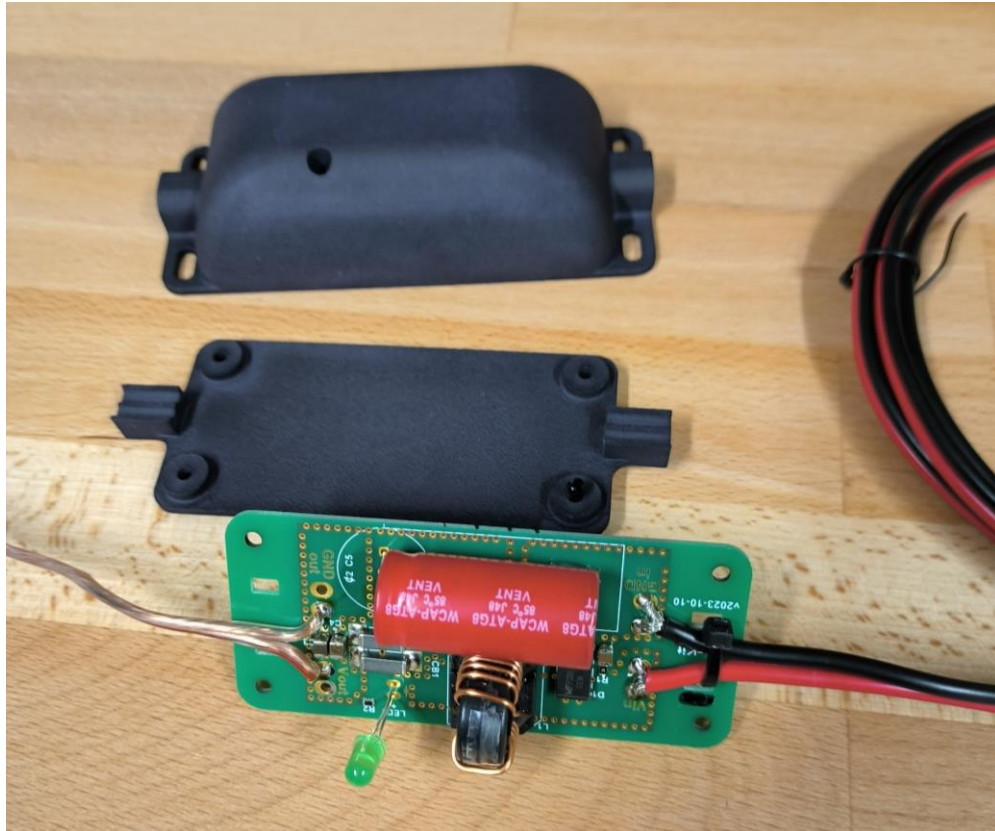

We made it in time. How good is it?



# Put it under test!

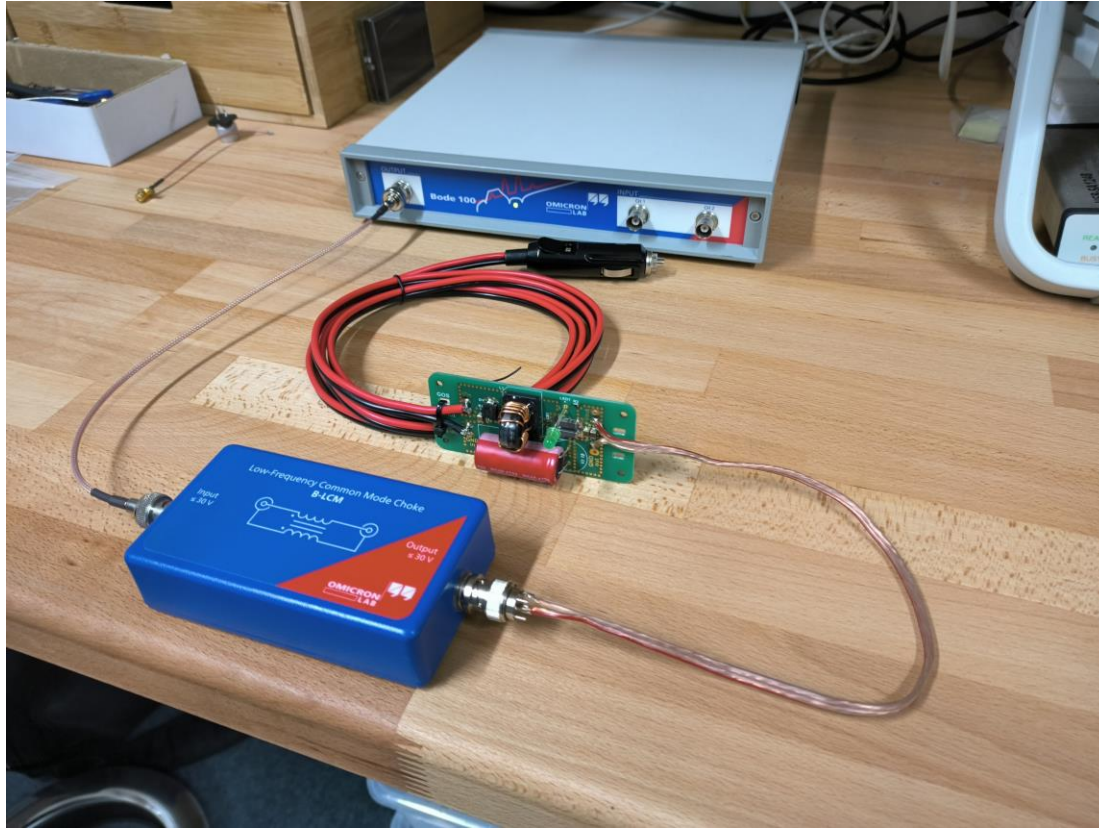

Use Bode 100!

Add B-LCM:


- Low-frequency common mode choke
- Differential measurement
- No common ground
- 100 Hz to 10 MHz

Start measure:

- Impedance (S11)
- Blocking (S21)

# Results (1), Output Impedance

Cursor 1	18,575 kHz	382,353 mΩ	396,16 mΩ	🗑️
Cursor 2	98,39 Hz	255,065 mΩ	261,839 mΩ	🗑️
Cursor 3	200,889 kHz	568,006 mΩ	567,158 mΩ	🗑️

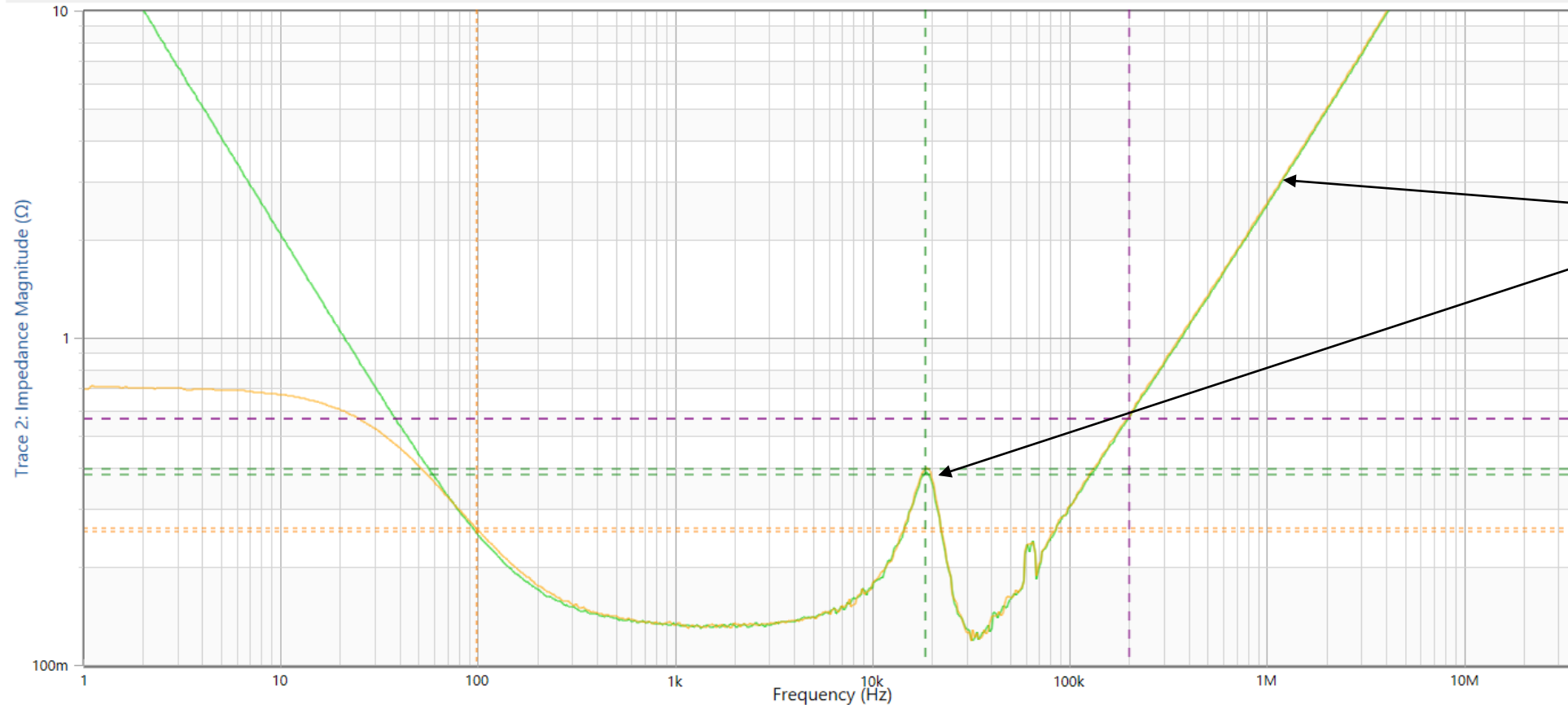

Connecting cable


Filter resonance



Compensated by system input capacitor

# Results (2), Blocking

Cursor 1	19,441 kHz	-49,547 dB	🗑️
Cursor 2	86,18 Hz	-39,903 dB	🗑️
Cursor 3	29,121207 MHz	-39,553 dB	🗑️

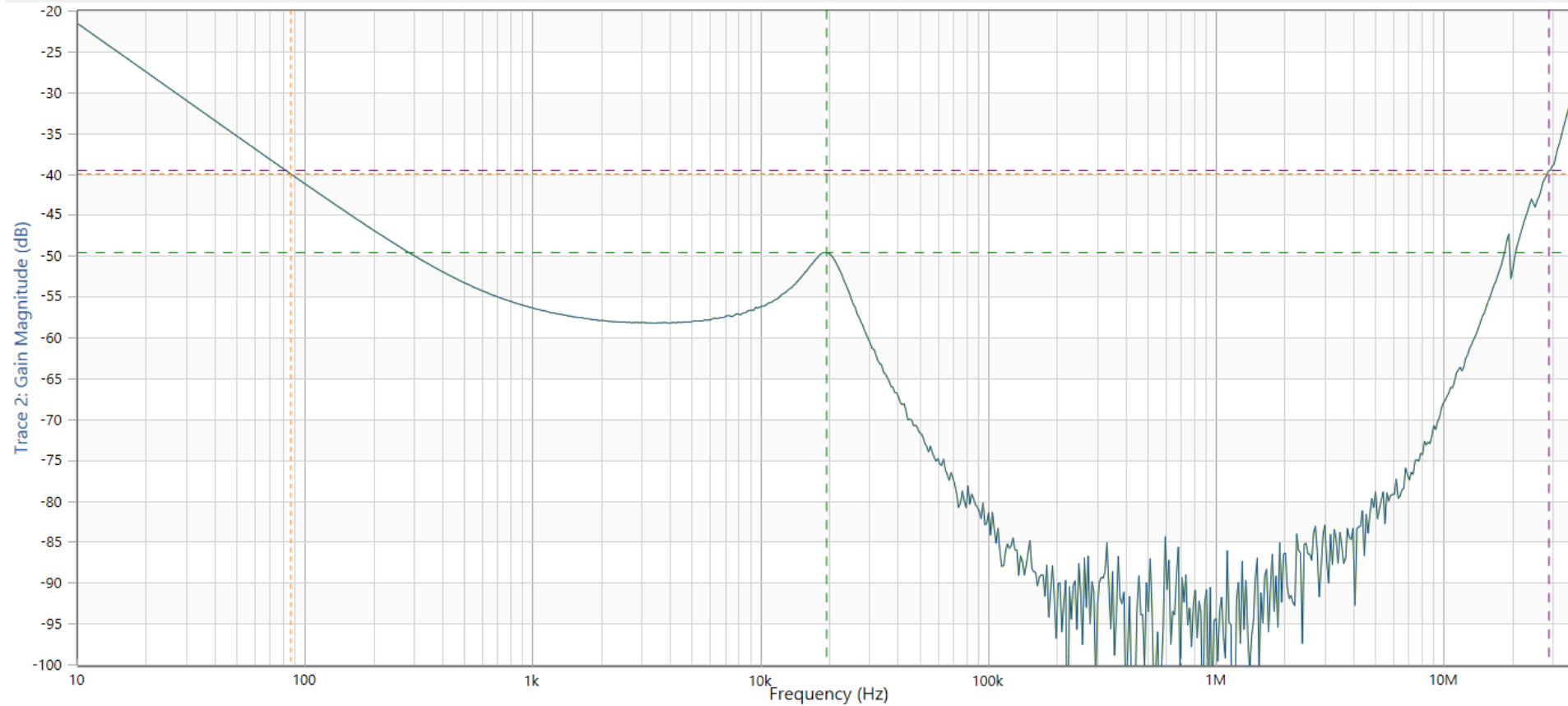




# Results (3)

**It worked!**  
**Customer is happy!**



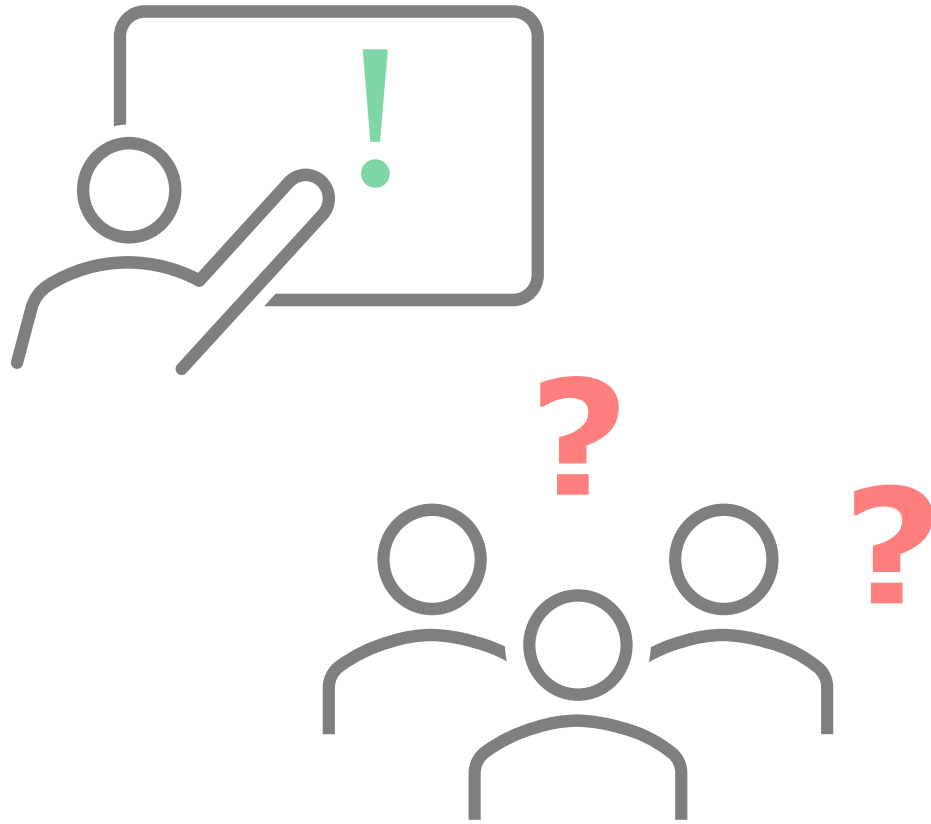

Contact:

Günther Klenner

[www.kk-prime.com](http://www.kk-prime.com)

+49 8031 20 80 555

[g.klenner@kk-prime.com](mailto:g.klenner@kk-prime.com)

# Picture reference



[https://de.wikipedia.org/wiki/Bordspannungssteckdose#/media/Datei:12volt-socket\\_21mm.jpg](https://de.wikipedia.org/wiki/Bordspannungssteckdose#/media/Datei:12volt-socket_21mm.jpg)



<https://www.msdirect.com/product/details/70461538>



<https://www.pngall.com/suv-png/download/67907>



<https://www.youtube.com/watch?v=zPcMNpyavMw>



<https://www.we-online.com/en/support/design-tools/libraries>

On all other pictures contact [g.klenner@kk-prime.com](mailto:g.klenner@kk-prime.com)