



Passive Component Analysis

OMICRON Lab Webinar Nov. 2015

Webinar Hints

Activate the chat function

The screenshot displays the Cisco WebEx Meeting Center interface. The main window shows a presentation slide featuring an OMICRON Bode 100 device. The interface includes a top menu bar with 'File', 'Edit', 'Share', 'View', 'Audio', 'Participant', 'Meeting', and 'Help'. Below the menu, there are tabs for 'Quick Start', 'Meeting Info', and 'OMICRON C...'. A toolbar contains icons for 'New Whiteboard', 'Participants', 'Chat', and 'Notes'. The 'Participants' panel on the right lists 'Speaking: Bernhard Baumgartner, Doc Brown' and shows 'Doc Brown (me)' with a mute icon. The 'Chat' panel shows a conversation between 'Bernhard Baumgartner' and 'Doc Brown (me)'. A 'Send' button is visible at the bottom of the chat window. The status bar at the bottom indicates 'Connected'.

We will record the presentation such that you can view it again later

Please mute yourself by clicking on this icon!

Send questions via chat to Bernhard Baumgartner

Agenda

- Why do we analyze passive components
- How to measure component impedance
- A detailed look at a capacitor
- Inductor and transformer
- Filter simulation vs. real world
- Summary



Passive Components

- Essential parts in analog circuits
- Inductor and capacitor used e.g. to store energy or to create filter circuits



$$\text{Inductor: } v(t) = L \frac{di(t)}{dt} \quad X_L = \omega L \quad \frac{V}{I} = Z_L = j\omega L$$



$$\text{Capacitor: } i(t) = C \frac{dv(t)}{dt} \quad X_C = \frac{-1}{\omega C} \quad \frac{V}{I} = Z_C = \frac{1}{j\omega C}$$

Theory and Reality

- Theoretically inductor and capacitor are purely **reactive** elements → No resistive behavior and therefore **lossless**
- In reality **parasitics** can strongly influence the real behavior especially at higher frequencies

Examples:

Inductor:

- Wire has resistance
- Windings form electric field
- Core is not lossless




Capacitor:

- Plates are resistive
- Rolling of foils creates inductance
- Insulator not lossless




Equivalent Circuits

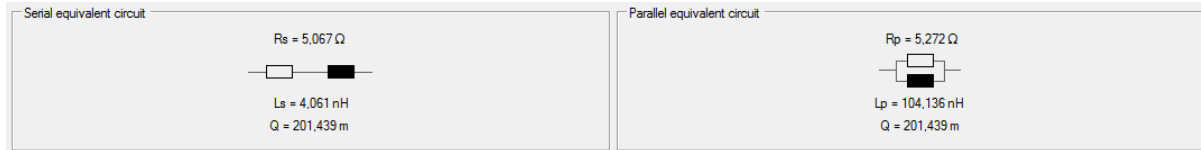- Are used to model the real behavior of the components
- Different complexity of models
 - 1st order models are valid for one frequency
 - Single Frequency Mode in BAS calculates R, L and C



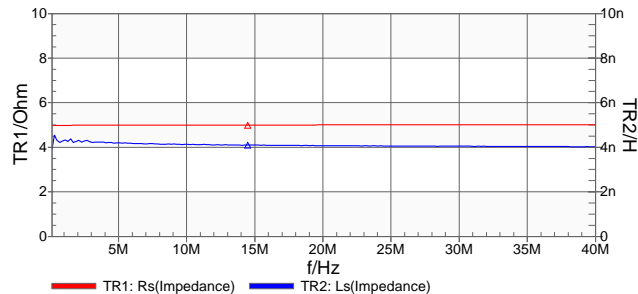- Frequency Sweep Mode calculates R, L and C over frequency




Equivalent Circuits



- Higher complexity models are valid for a frequency range
 - 2nd Order equivalent circuits for inductor and capacitor



≅

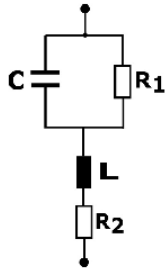

≅

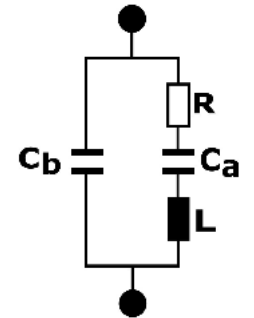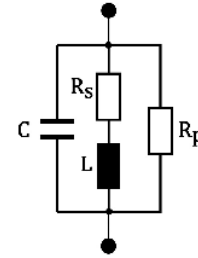

- 3rd Order models (e.g. quartz crystal or piezo element)



see Application Note:

Equivalent Circuit Analysis of Quartz Crystals

<https://www.omicron-lab.com/application-notes/>


- Parameter identification requires manual work or e.g. curve-fitting procedure

Bode 100 Impedance Measurement Methods

- Direct Measurements
 - One-Port Reflection
 - Impedance Adapter (3-port technique)
 - External bridge (e.g. high impedance bridge)
- Indirect Measurements (via Gain)
 - Shunt-Thru (2-port technique)
 - Series-Thru (2-port technique)
 - Voltage-Current Gain (3-port technique)


Direct Measurement Methods

One-Port

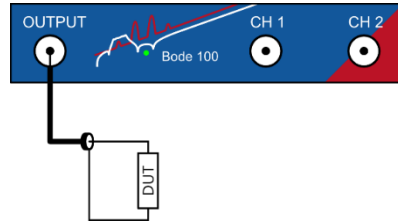


Recommended for $0.5 \Omega - 10 \text{ k}\Omega$

Impedance Adapter

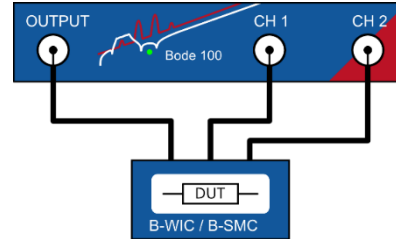

Recommended for $20 \text{ m}\Omega - 600 \text{ k}\Omega$

External Bridge / Coupler

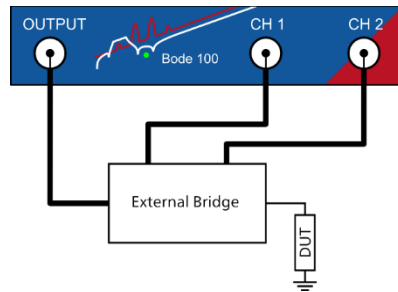


Range depends on bridge

Indirect Measurement Methods

Shunt-Thru

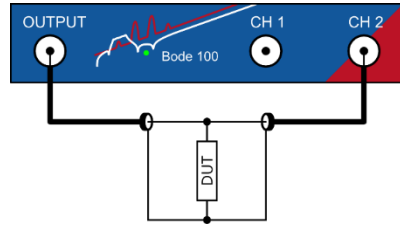
$$Z_{DUT} = 25\Omega \cdot \frac{S_{21}}{1 - S_{21}}$$



Recommended for 1 mΩ - 10 Ω

Series-Thru

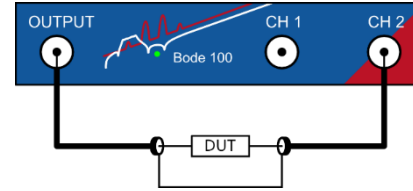
$$Z_{DUT} = 100\Omega \cdot \frac{1 - S_{21}}{S_{21}}$$




Recommended for 1 kΩ < 10 MΩ

Voltage Current Gain
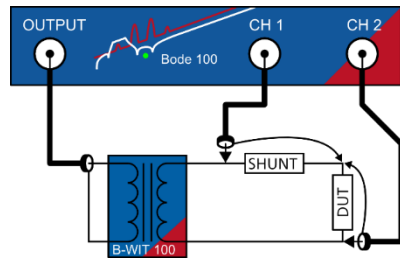
$$Gain = \frac{V_{CH2}}{V_{CH1}} = \frac{V}{I} = Z_{DUT}$$



Impedance Range Overview

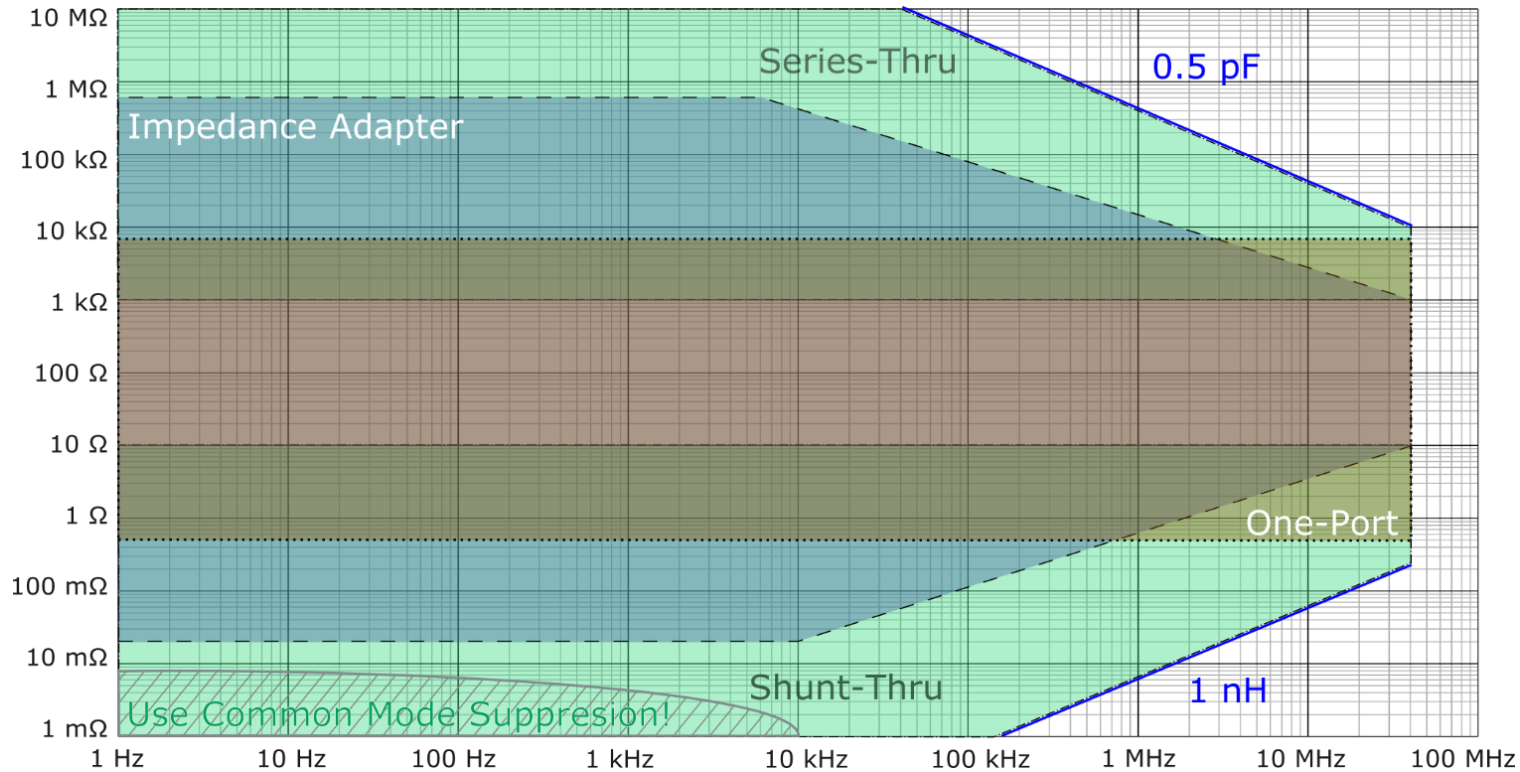


Why is it important to measure capacitors?

- A capacitor is **NEVER** just a capacitor
- Capacitor ESR influences the phase margin of power supplies
- Capacitor ESR influences the output ripple at the switching frequency of a SMPS
- ESR can change over Frequency
- Capacitors are inductors above their resonance frequency



What does the data sheet tell us?

220 μ F aluminum capacitor

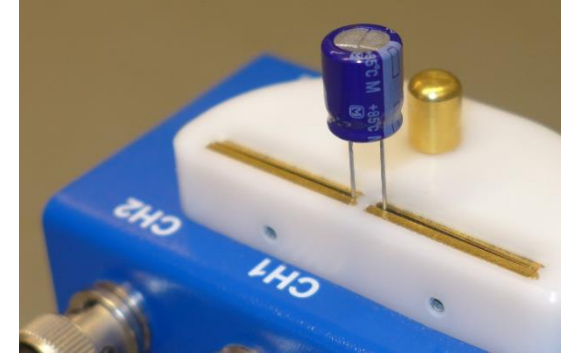





■ Standard Products

W.V.	Cap. ($\pm 20\%$)	Case size		Specification		Lead Length			Part No.	Min. Packaging Q'ty	
		Dia.	Length	Ripple Current (120 Hz) (+85 °C)	$\tan \delta$ (120 Hz) (+20 °C)	Lead Dia.	Lead Space			Straight Leads	Taping
							Straight	Taping *B			
(V)	(μ F)	(mm)	(mm)	(mA r.m.s.)		(mm)	(mm)	(mm)		(pcs)	(pcs)
	220	10	12.5	400	0.12	0.6	5.0	5.0	ECA1HM221()	200	500

$$C = 220\mu\text{F} (\pm 20\%)$$

$$ESR = \frac{\tan(\delta)}{\omega C} = \frac{0.12}{2\pi \cdot 120\text{Hz} \cdot 220\mu\text{F}} = 0.72 \Omega @ 120 \text{ Hz}$$



This is what the measurement tells us

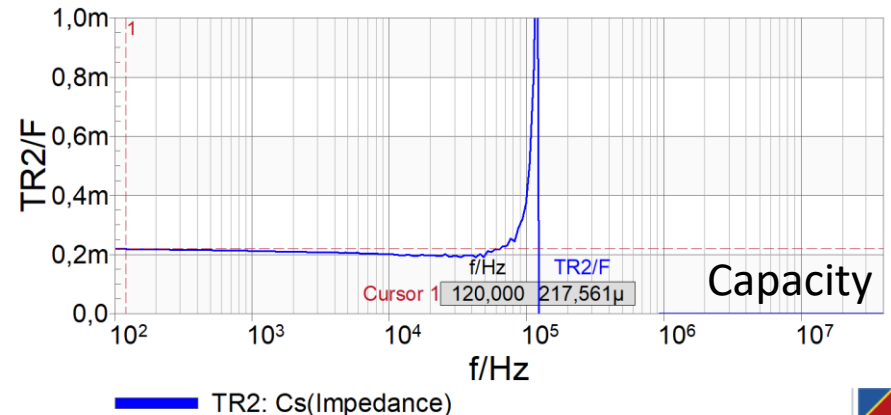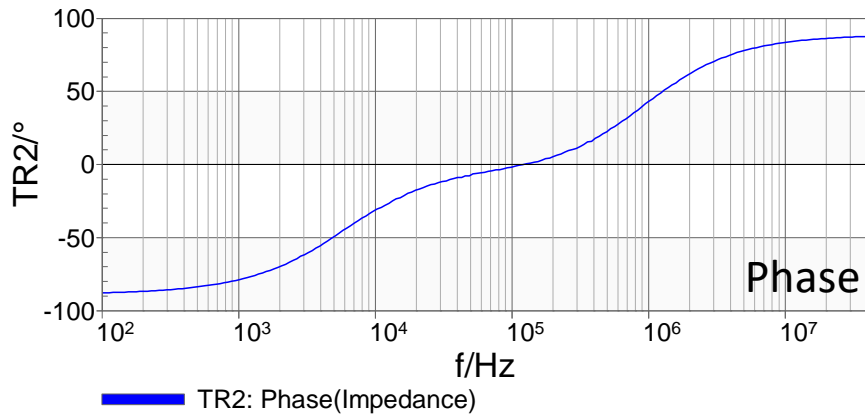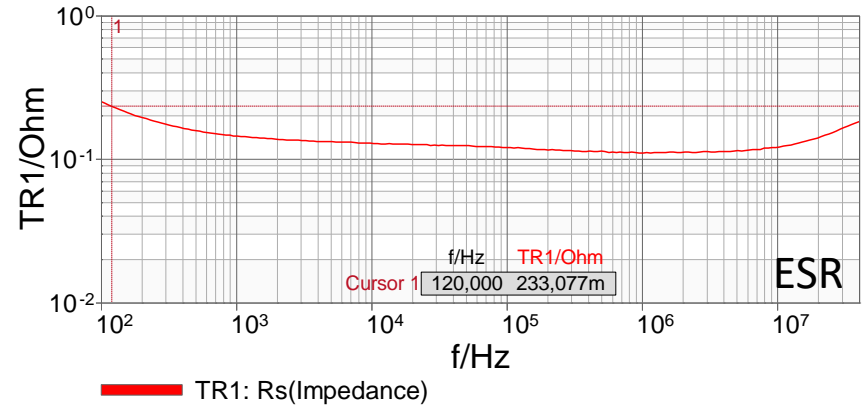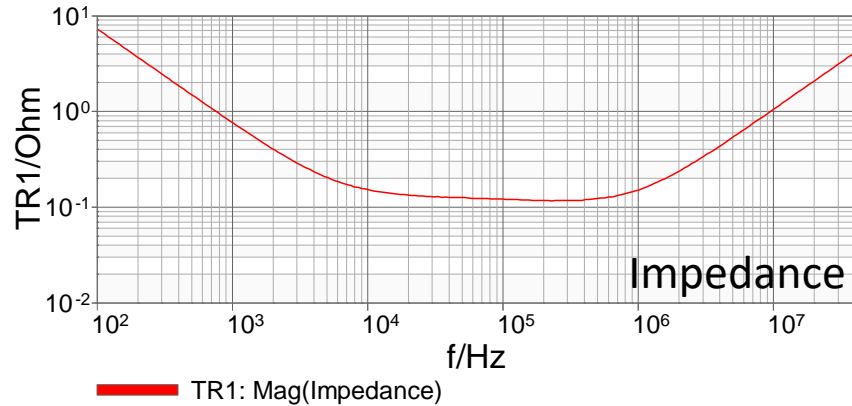


Calibration



Open

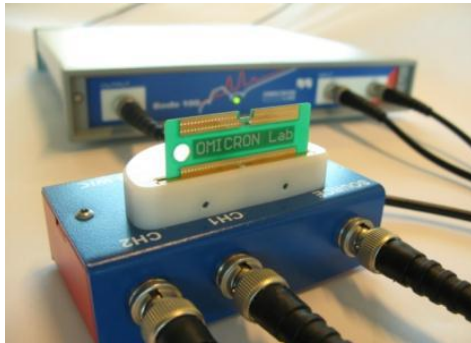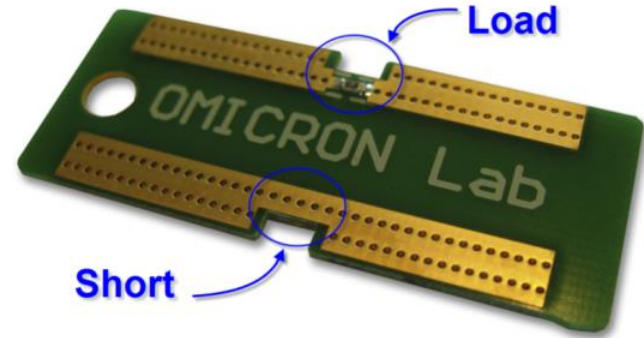


Short

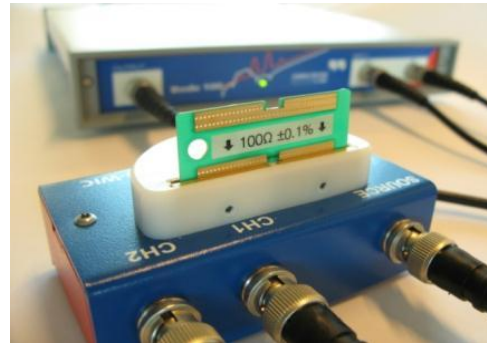


Load

User Calibration / Probe Calibration


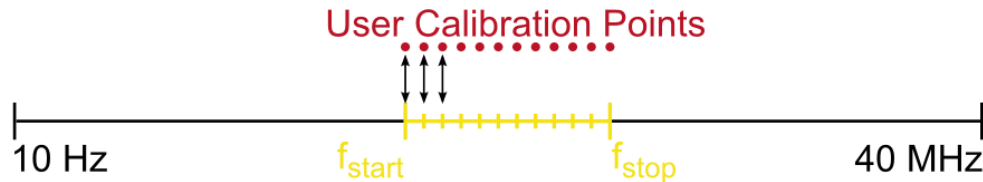
- User Calibration (User Range Calibration)
Calibrates at exactly the frequencies that are currently measured
+ No interpolation, suitable for narrowband probes



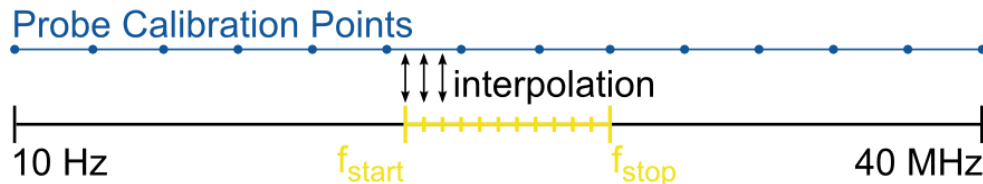- Probe Calibration (Full Range Calibration)
calibrates at pre-defined frequencies and interpolates in-between
+ Calibration does not get lost when frequency range is changed



Detailed Example available

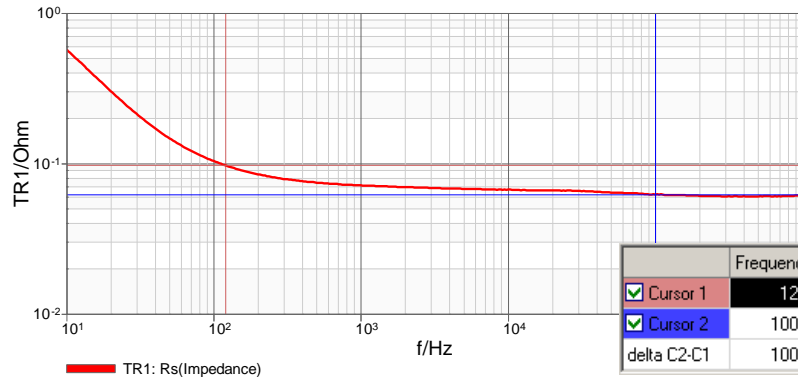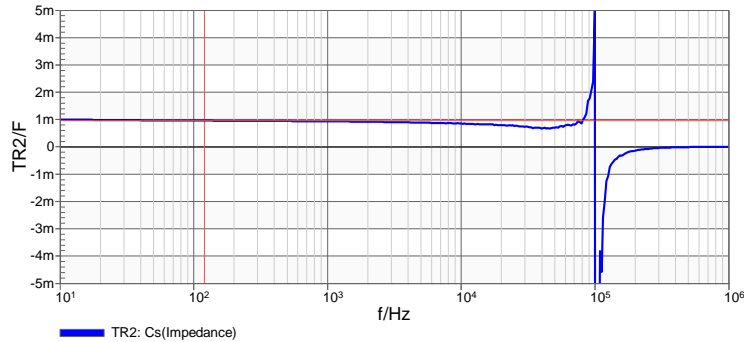

	Frequency	Trace 1	Trace 2
<input checked="" type="checkbox"/> Cursor 1	120,000 Hz	97,200 mΩ	951,758 μF
<input checked="" type="checkbox"/> Cursor 2	100,436 kHz	62,273 mΩ	-42,824 mF
delta C2-C1	100,316 kHz	-34,927 mΩ	-43,776 mF




see Application Note:

Capacitor ESR Measurement with Bode 100 and B-WIC

<https://www.omicron-lab.com/application-notes/>






Fitting Model to Measured Impedance


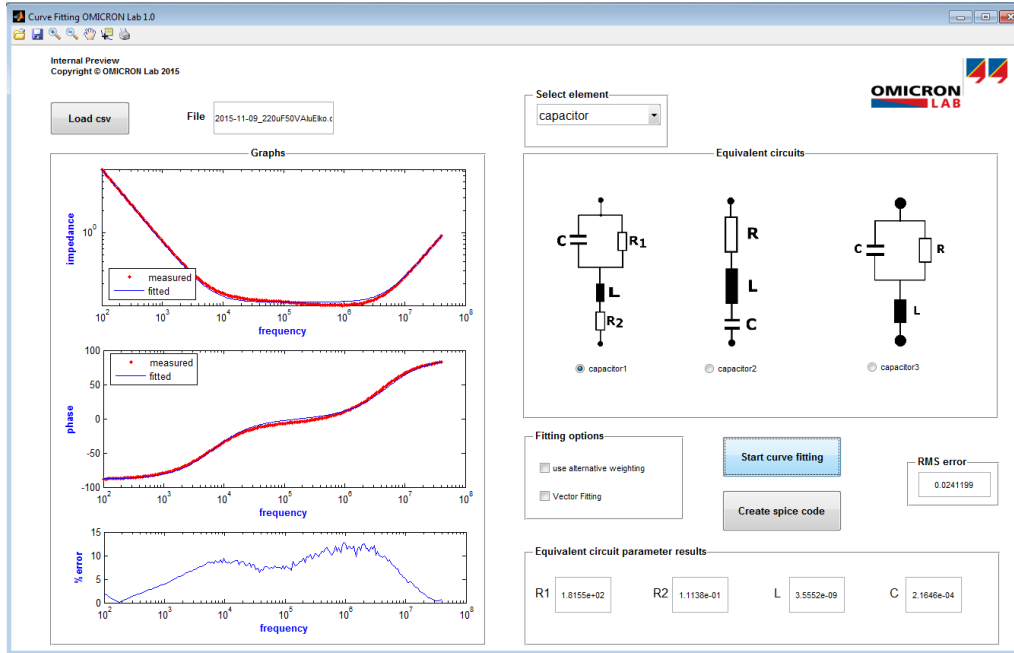


- Various methods available
- We use curve-fitting
- A Preview tool is available on request

Simulation vs. Measurement

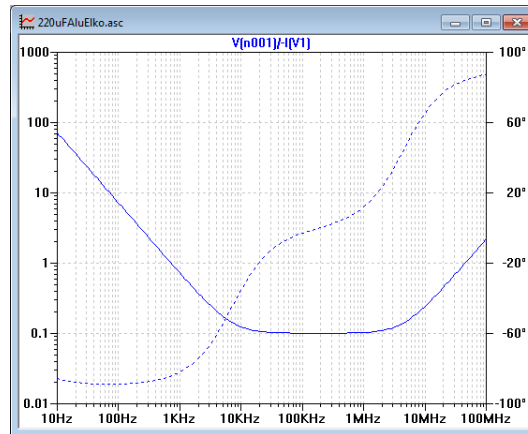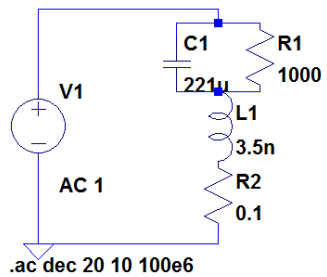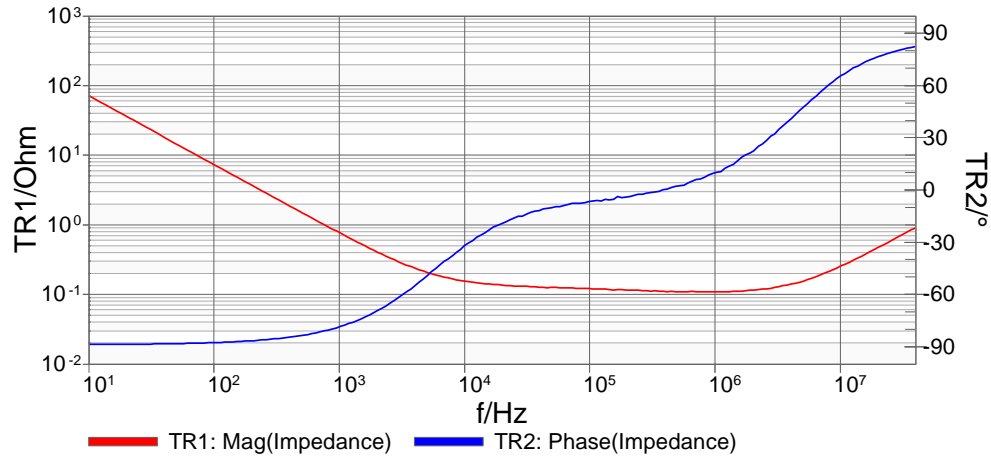

Voltage sensitivity of capacitors

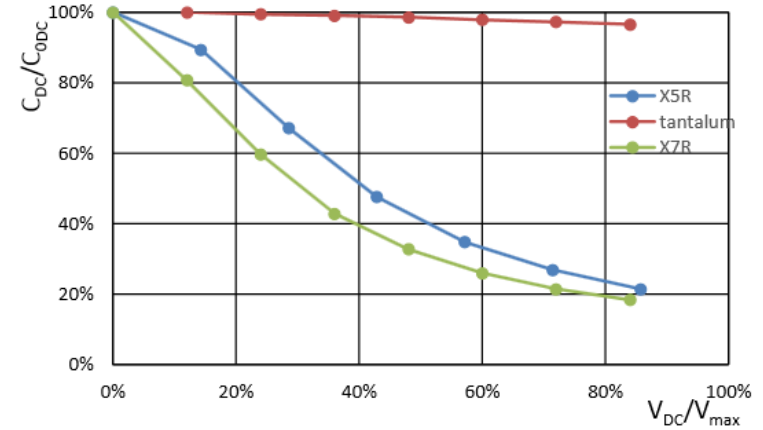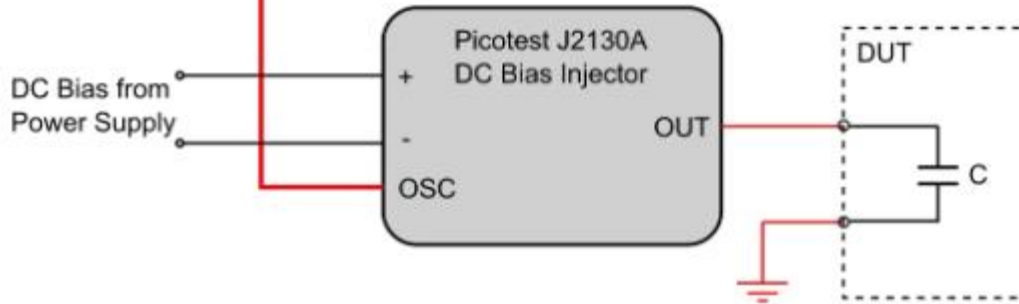

see Application Note:
DC Biased Impedance Measurements
<https://www.omicron-lab.com/application-notes/>


Why should we measure inductors?

- An inductor is **NEVER** just an inductor
- AC resistance \leftrightarrow DC resistance
 - skin effects
 - “Eddie Currents”
- Inductors have resonance frequencies
- Inductors with magnetic cores can have core losses

What does the data sheet tell us?

33 μH shielded power inductor

Properties	Test conditions		Value	Unit	Tol.
Inductance	1 kHz/ 250 mV	L	33	μH	$\pm 20\%$
Rated current	$\Delta T = 40 \text{ K}$	I_R	2.68	A	max.
Saturation current	$ \Delta L/L < 10\%$	I_{sat}	3.00	A	typ.
DC Resistance	@ 20°C	R_{DC}	0.049	Ω	typ.
DC Resistance	@ 20°C	R_{DC}	0.057	Ω	max.
Self resonant frequency		f_{res}	11	MHz	typ.

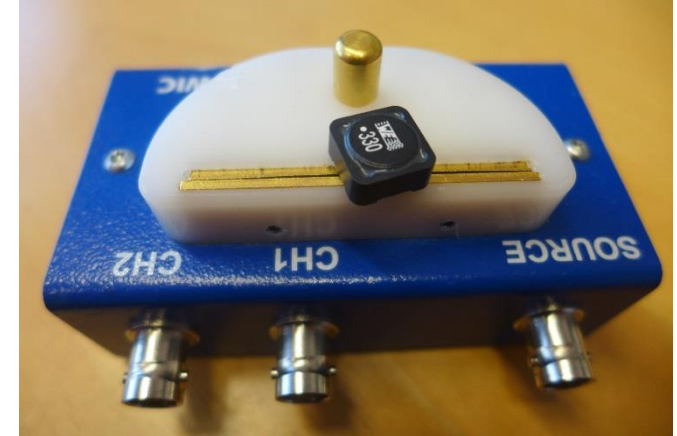





$H = 33\mu\text{H} (\pm 20\%) @ 1 \text{ kHz}$

$R_{\text{DC}} = 0,049 \Omega$ (typ.)

$R_{\text{DC}} = 0,057 \Omega$ (max.)


$f_{\text{res}} = 11 \text{ MHz}$

This is what the measurement tells us

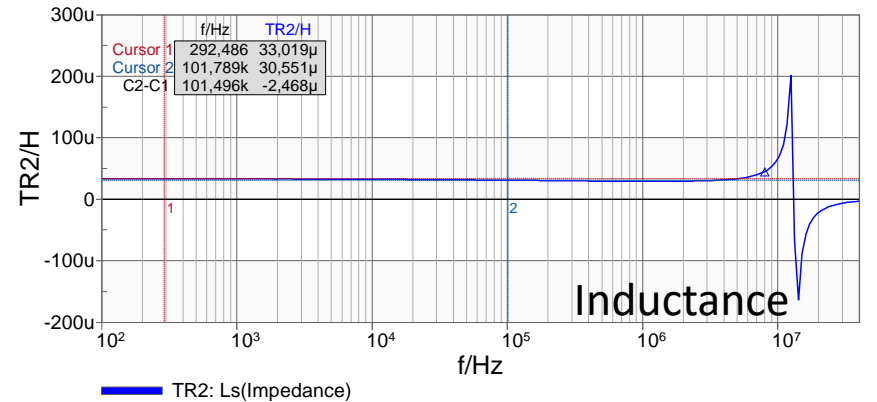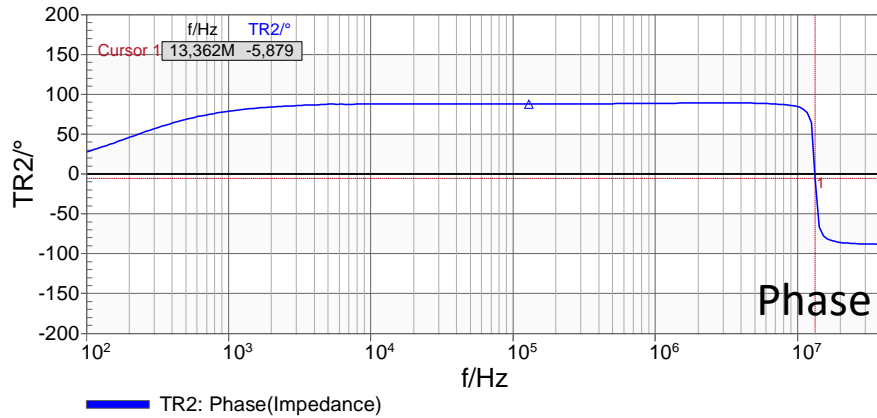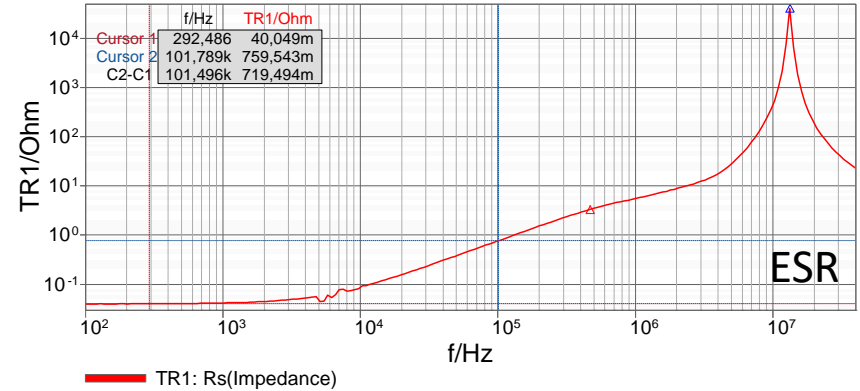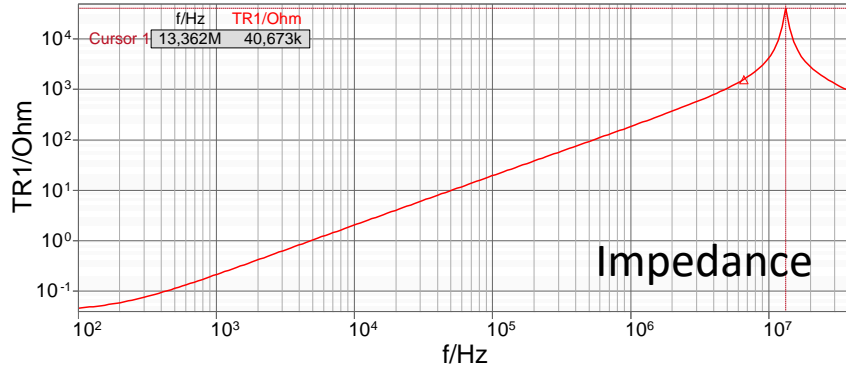


Flyback Transformer Leakage Inductance

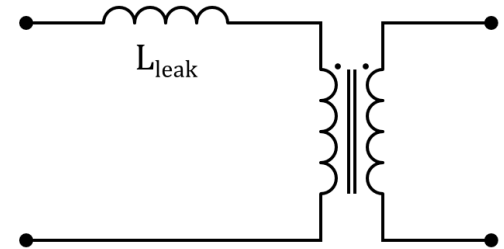- Not all flux generated by the primary winding is coupled to the secondary winding
 - some flux leaks
 - some contributes to core losses
- Represented by a series inductance in the circuit
- Leakage inductance creates a voltage spike when turning off current through primary side (flyback converter)




Measuring Leakage Inductance

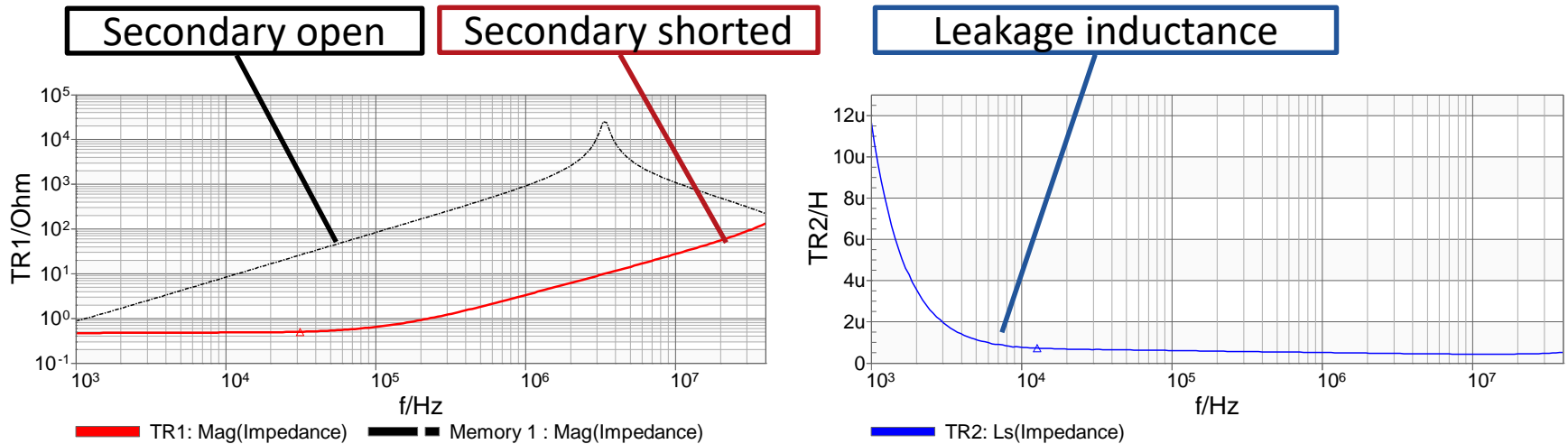Leakage inductance is measured by shorting all other windings except the primary winding



→ Leakage inductance is not constant over frequency


LC Filter Bode Diagram

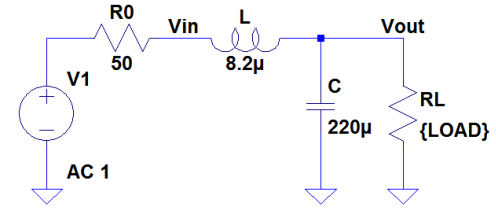


```
.ac dec 20 10 40meg
```

```
.step param LOAD list .5 1 5 500
```


Simulation in LTSpice:

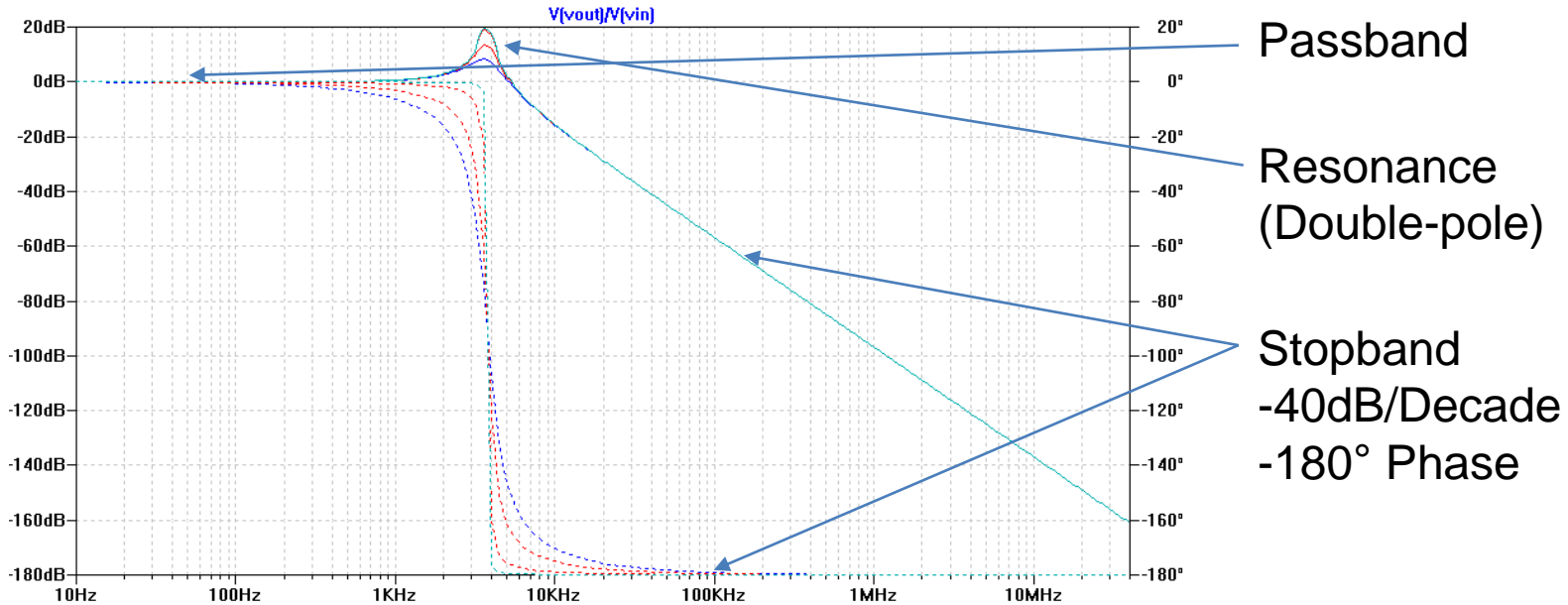


LC Filter Test board

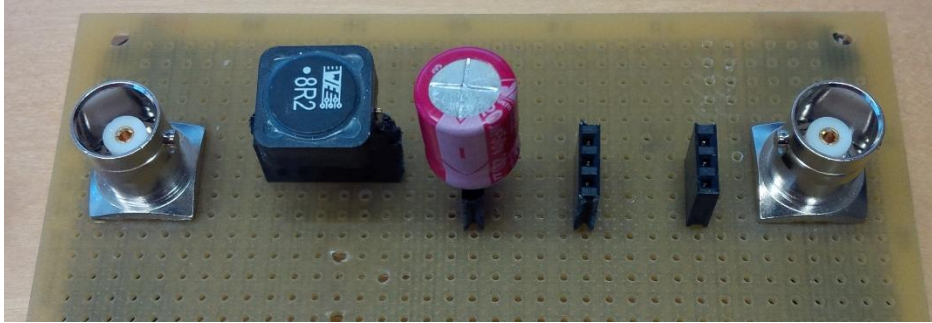

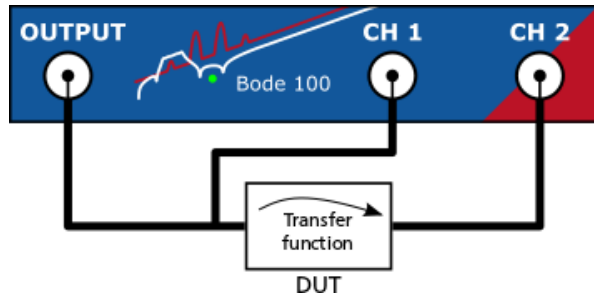Measuring the voltage transfer function $H(j\omega) = \frac{V_{out}}{V_{in}}$





Measurement vs. Simulation

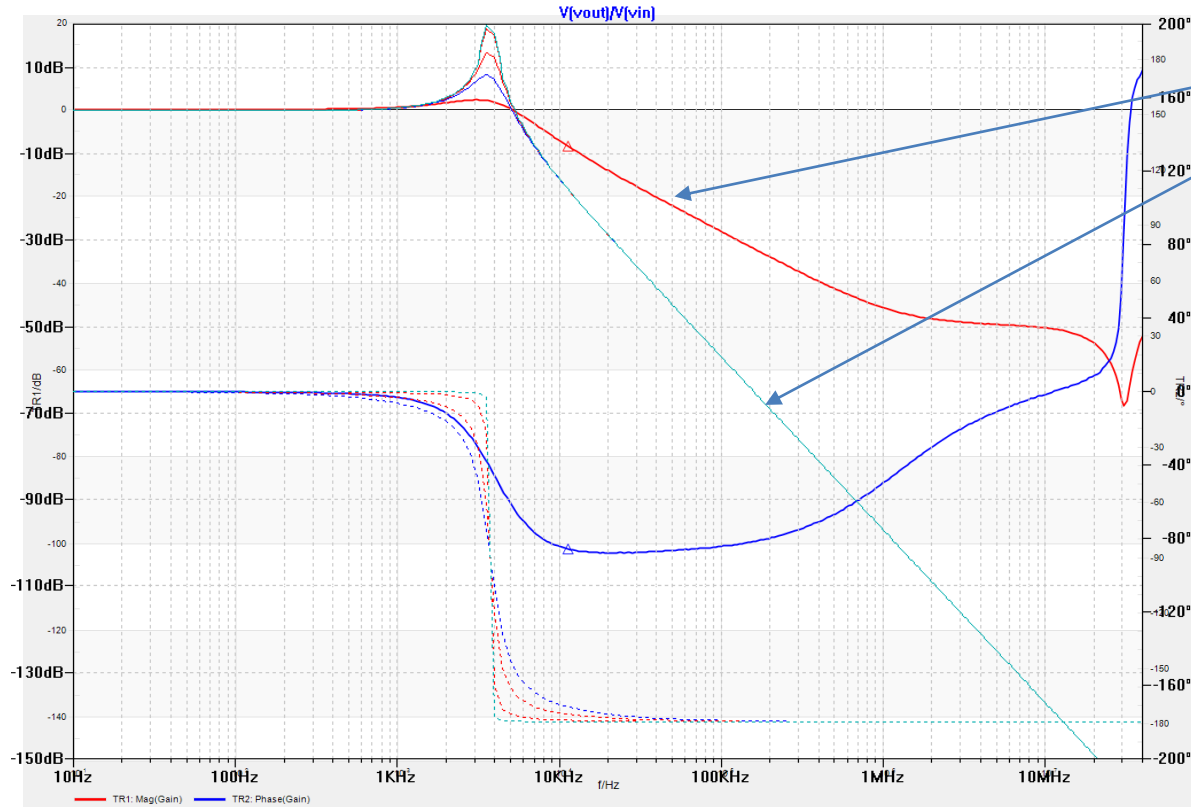

Measurement
Simulation

- Stopband is different
 - Phase does not reach -180°
 - Second resonance at 30 MHz
- parasitic effects


LC Filter Including Parasitics

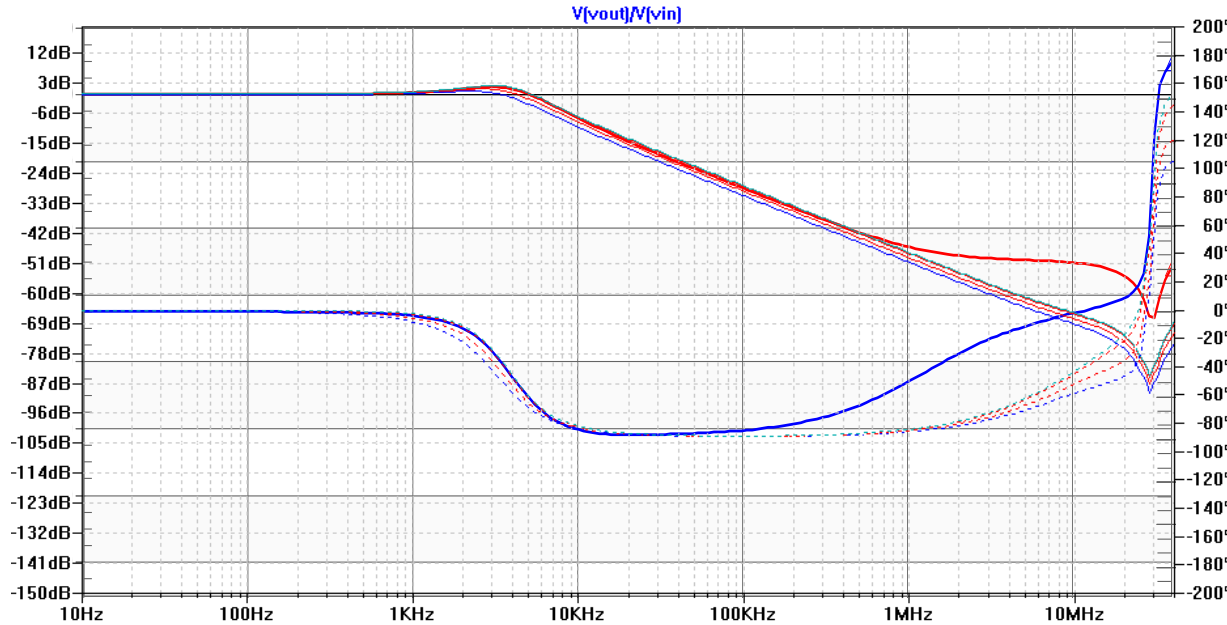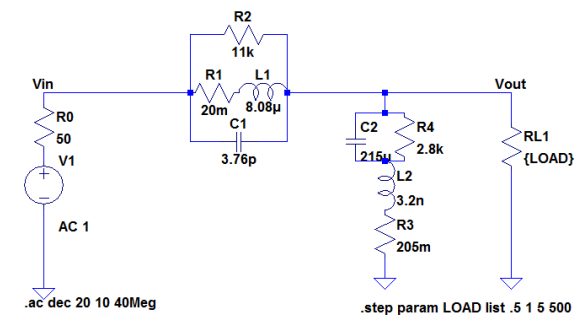

- much better fit between simulation and measurement
- Could be further improved by better component models

Reducing Output Ripple

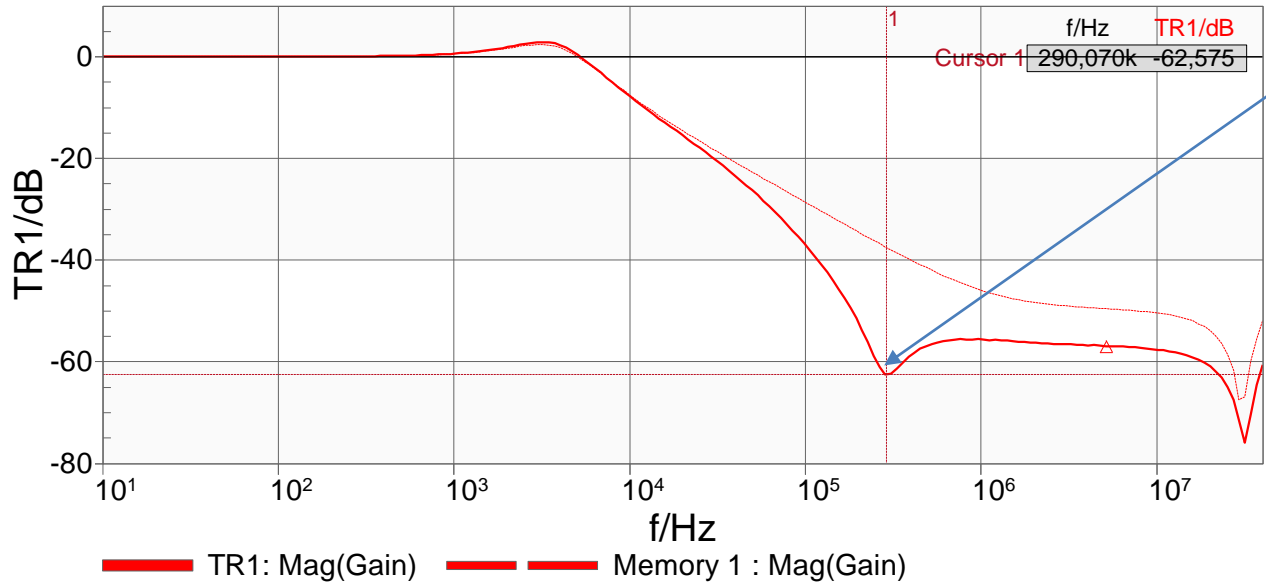→ 2 x 10 μ F ceramics adds 20dB attenuation at 300 kHz



Improved stop band performance at 300 kHz (e.g. switching frequency)

Summary

- Component parasitics are important to understand real life circuit behavior
- Models considering parasitics allow better simulation
- Measuring components can tell us more than the data sheet says





Feel free to ask questions via the chat function...

If time runs out, please send us an e-mail and we will follow up.

You can contact us at: info@omicron-lab.com

Thank you for your attention!