



10th Power Analysis & Design Symposium


March 10th, 2021 - Worldwide (Virtual)

The Search for the Best DC-Bias Components

by Melanie Klenner (K&K Prime Engineering) & Joanne Wu (Würth Elektronik)

The search for the best DC-Bias components

more
than you
expect

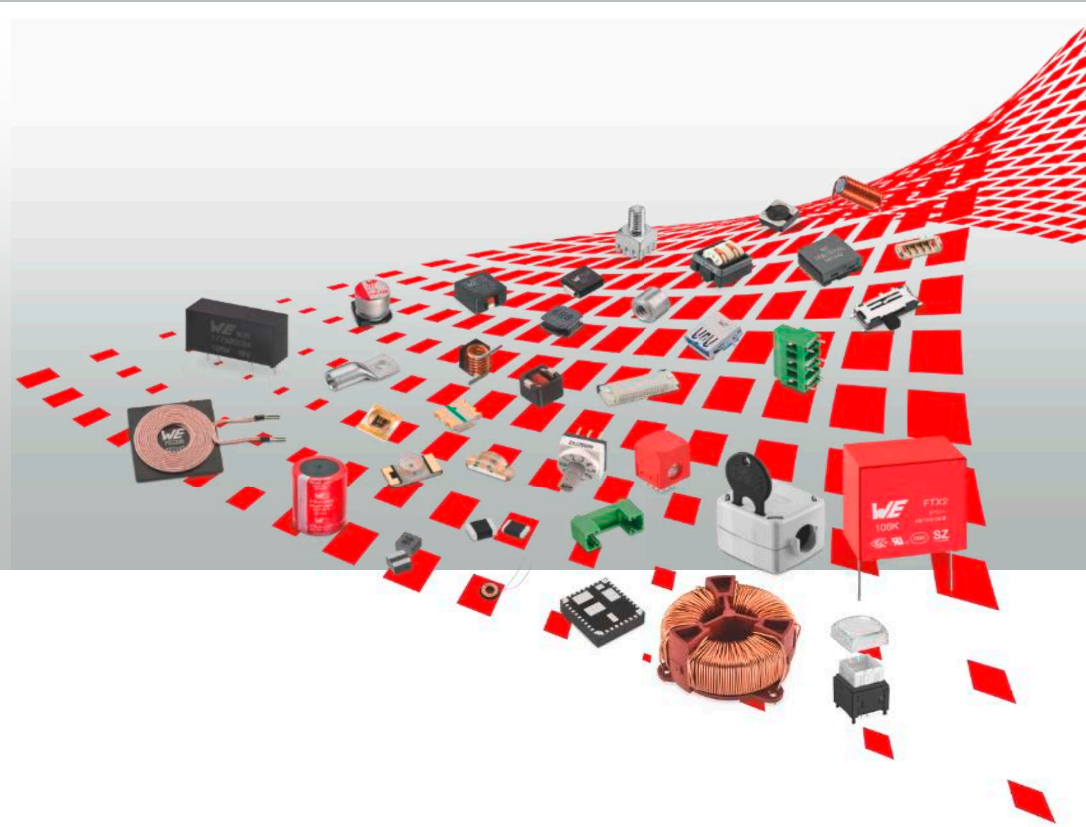

Joanne Wu
WE eiSos
&
Melanie Klenner
K&K Prime

Agenda

- Introduction
- Low Current
- High Current
- DC-Block
- Measurement to Simulation
- Final Summary



Introduction

Use-Case – Narrowband



➤ Applications combining RF & DC

➤ GPS



© Garmin

➤ Satellite communication

➤ Low Noise Block (LNB)



© Summitsource.com

➤ Wireless LAN (WiFi)



© pngimage.net

Introduction

Use-Case – Narrowband




➤ Applications combining RF & DC

➤ Camera system in vehicles



© Komando.com


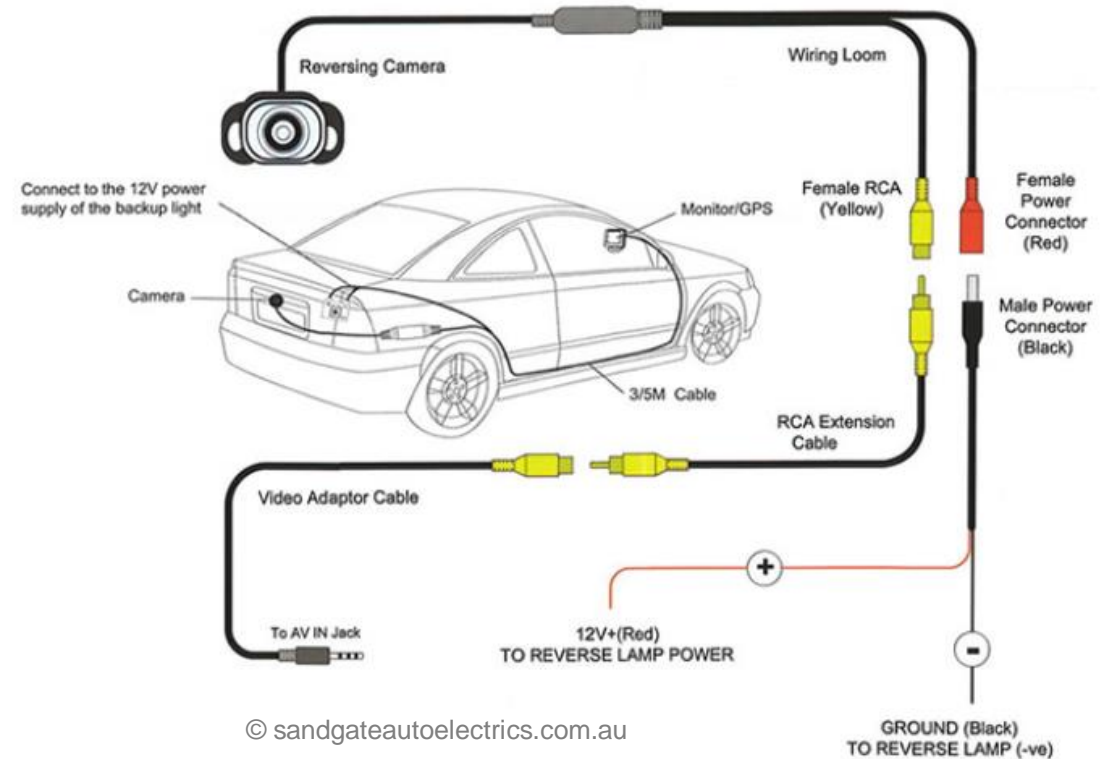


Introduction

Use-Case – Broadband



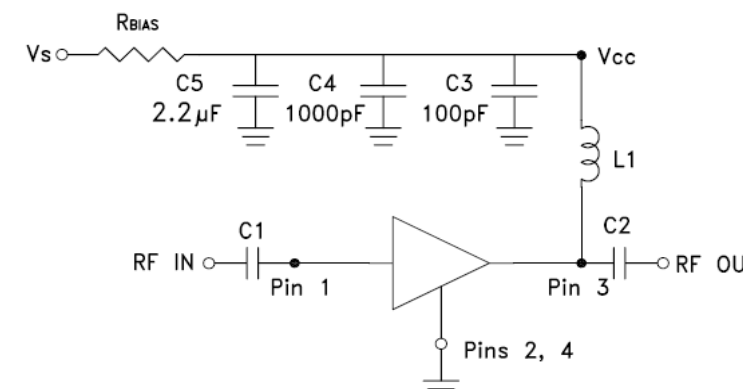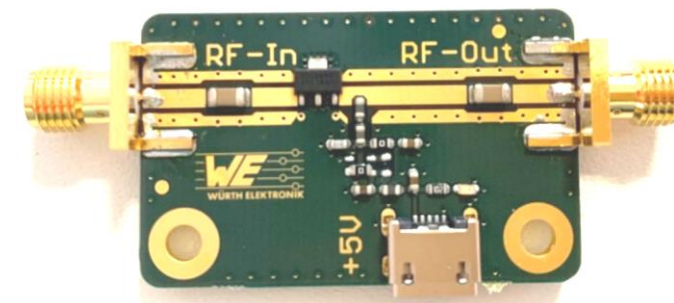- **Gain amplifier:**
 - Broadband amplifiers needed for signal generators
 - Bias network within RF circuit design is crucial for overall performance
 - Limited or only narrowband literature



Recommended Component Values

| Component | Frequency (MHz) | | | | |
|-----------|-----------------|--------|--------|--------|--------|
| | 50 | 900 | 1900 | 2200 | 2400 |
| L1 | 270 nH | 56 nH | 18 nH | 18 nH | 15 nH |
| C1, C2 | 0.01 μF | 100 pF | 100 pF | 100 pF | 100 pF |

© Analog Devices, HMC311ST89

➤ Question:

How to achieve good RF throughput for broadband applications?

Introduction

Summary



General Information

- **Wrong DC-biasing:**
 - RF signal loss
 - RF signal within power line
- **Limited literature about broadband DC-Biasing**



Main categories

- **Low current**
 - **Up to 1A**
- **High current**
 - **More than 1A**
- **DC Block**



➤ Low Current

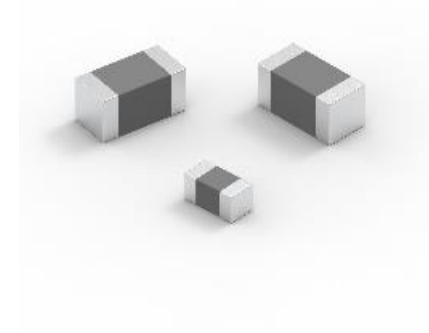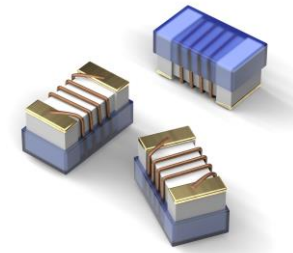- *Combining RF+DC*
- *Standard Approach*
- *Unconventional Approach*
- *Selecting the best fit*



Low Current

Combining RF+DC



➤ RF Trace:



- Check line impedance
- Avoid solder mask & Use via fence

➤ Components:

- Minimize stray parasitics
- Good GND for SMA connectors

➤ S-Parameters:

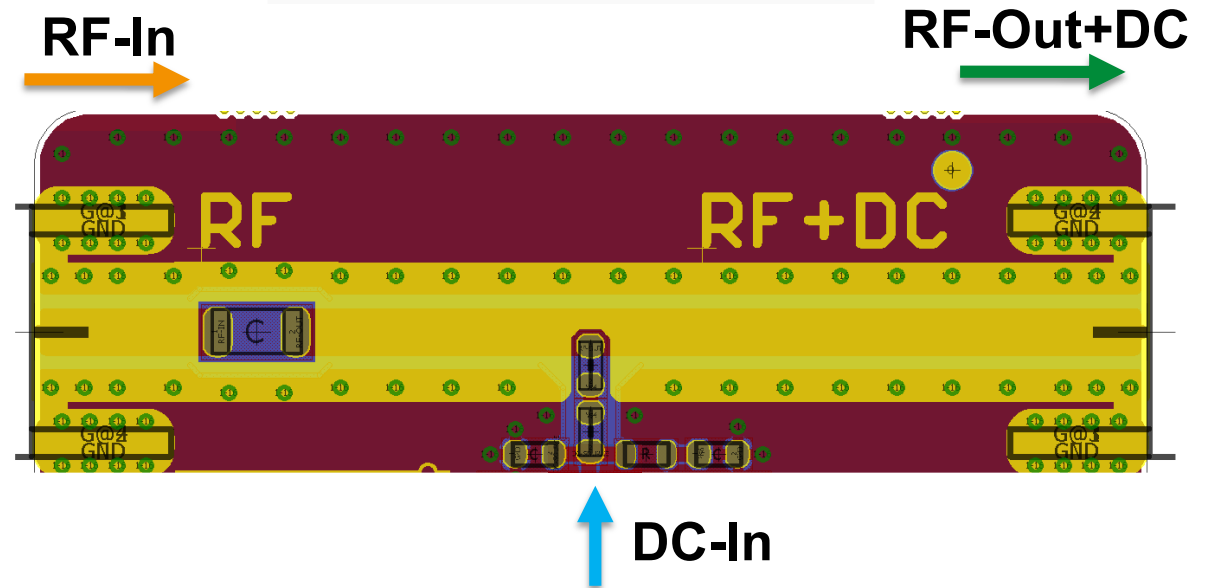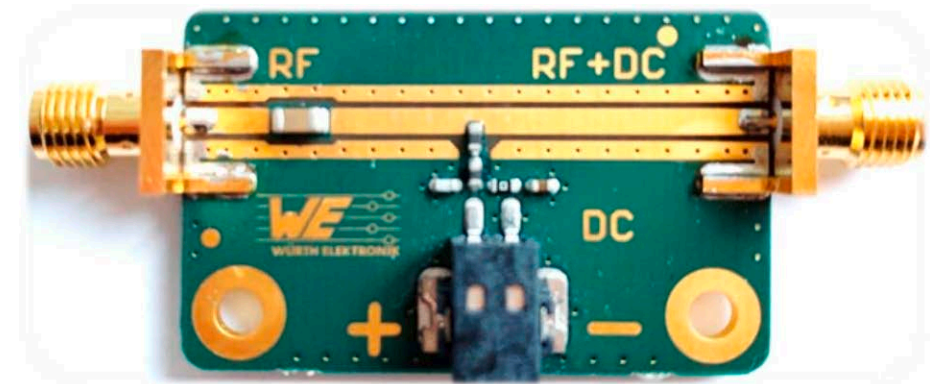- S11: Reflection at RF-In
- S21: Throughput from RF-In to RF-Out




Low Current

Standard approach – Wire wound ceramic




➤ WE-KI:

- 744761156A - 56nH

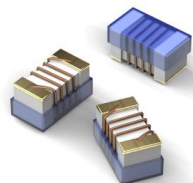

➤ Pros & Cons:

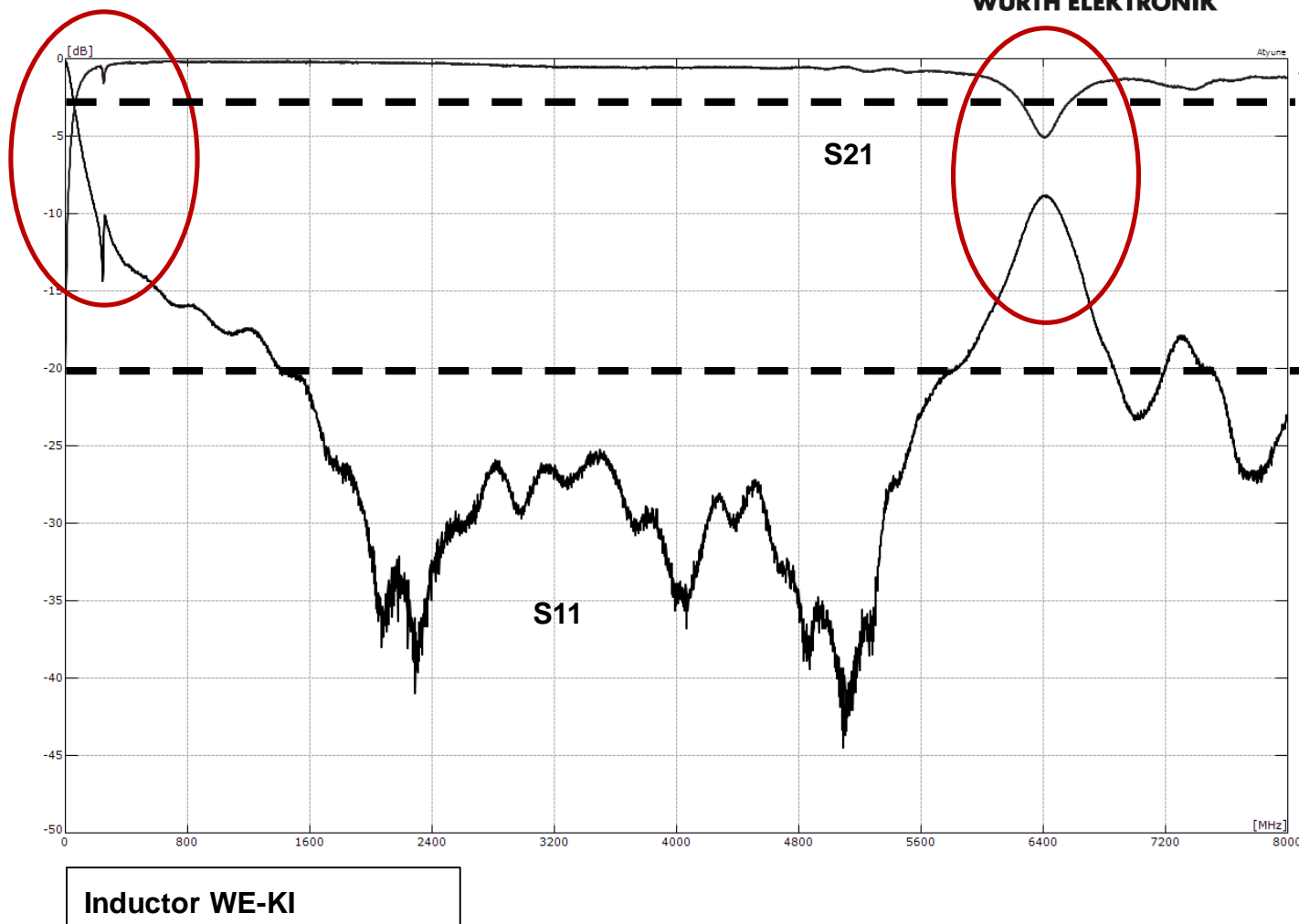- + Broadband
 - 400 MHz to 6 GHz
- – Resonate with filter capacitors
- – Self resonance with high Q
- – Not for low frequency <400 MHz




Low Current

Unconventional approach – Ferrite beads



➤ WE-CBF HF:

➤ 742863160 - 600Ω

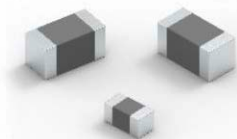

➤ Pros & Cons:

- + Very broadband
 - 30 MHz to 7 GHz
- + Low frequencies
- – Low current rating
- – Bead saturation



Inductor WE-KI

Ferrite bead WE-CBF HF

Low Current

Unconventional approach – Ferrite beads 0.1A




➤ Conclusion:

- Ferrite saturation
 - ↓ Impedance

- Use two ferrite beads in series
 - Doubles impedance

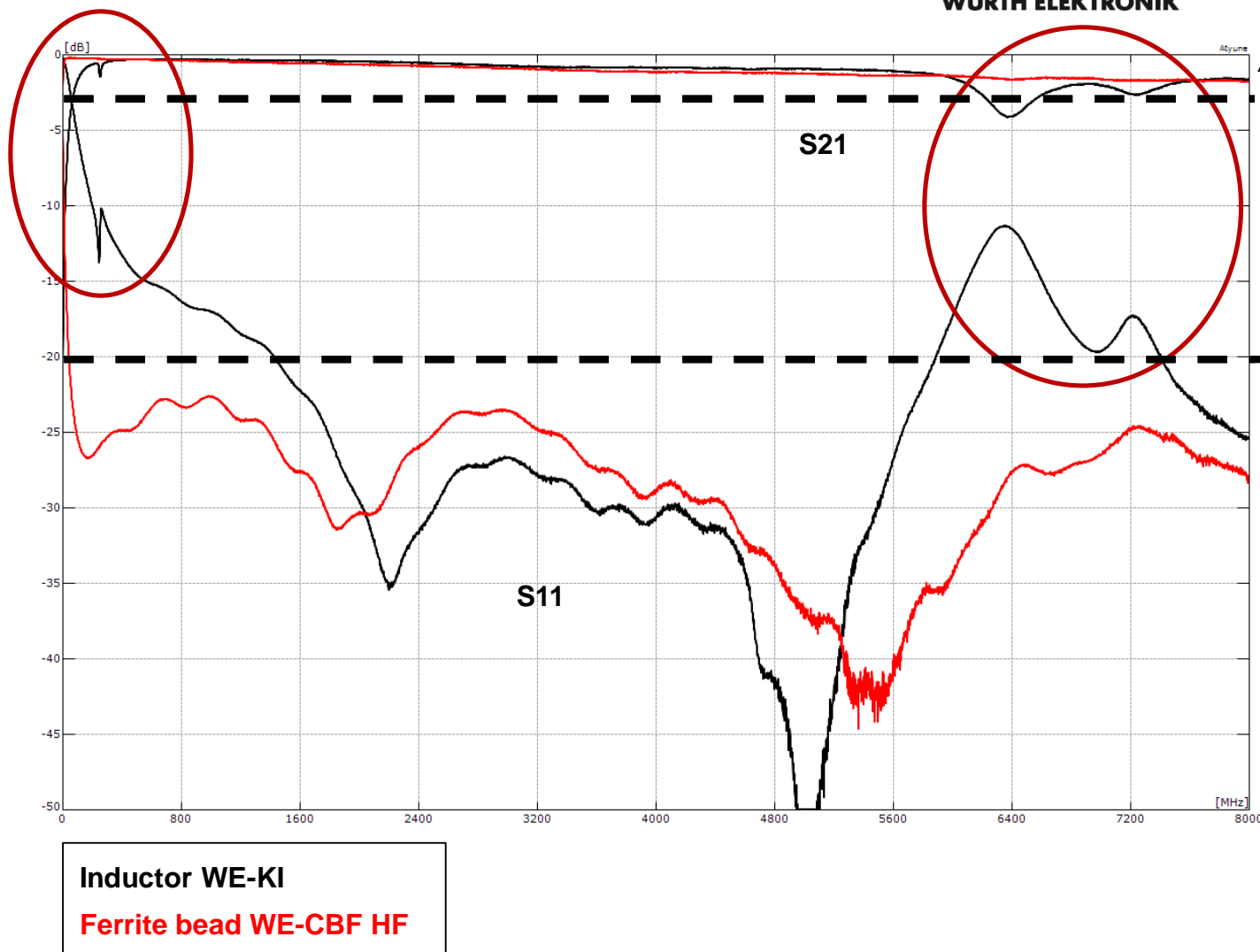- Choose the right component
 - High impedance
 - Saturation current



Low Current

Selecting the best fit




➤ Used chip beads:

- CBF HF – 742863160
- CBF – 742792656
- TMSB – 74269262601

➤ Results:

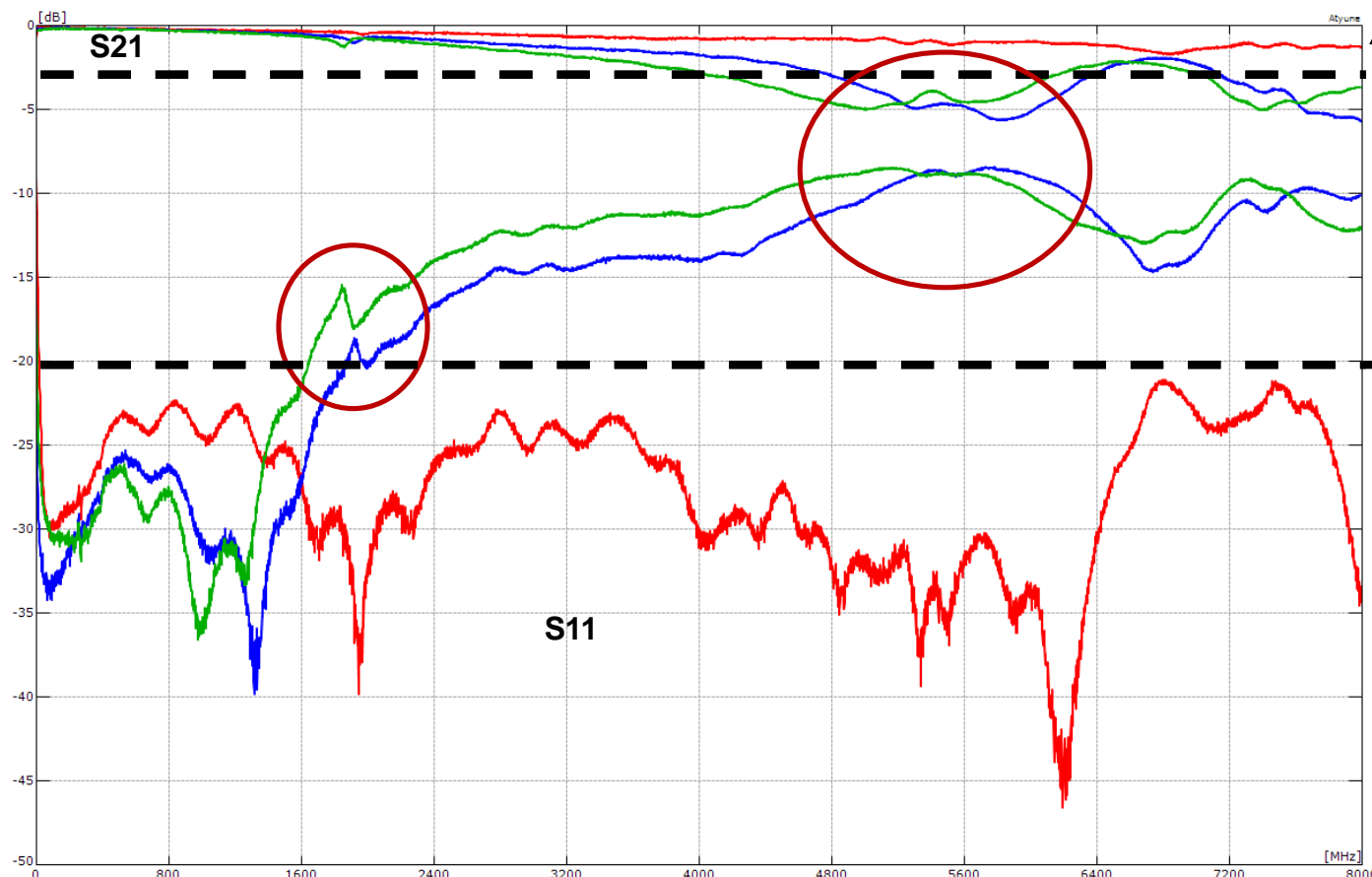- All broadband & good for LF
- Freq. restriction due to:
 - Parasitic capacitances
 - Resonances



Ferrite bead WE-CBF HF
 Ferrite bead WE-CBF
 Ferrite bead WE-TMSB

Low Current

Choosing the right component



REDEXPERT® FERRITES FOR PCB ASSEMBLY | APPLICATIONS | HOW TO | SHARE

ITEMS MELANIE

100 / 360 items




| System | Order Code | Series | Size | Spec | Type | Z@100MHz | Z _{max} | R _{DC} | I _R | L | W | H | Pin L... | Lines | Assembli... | AEC |
|--------|-------------|---------|------|------|--------------|----------|------------------|-----------------|----------------|---------|----------|----------|----------|-------|-------------|-----|
| | 74269262601 | WE-TMSB | 0603 | | High Current | 600 Ω | 634 Ω @184 MHz | 89.0 mΩ | 1.50 A | 1.60 mm | 0.800 mm | 0.800 mm | | 1 | SMT | |
| | 74273001 | WE-MLS | 7650 | | 3 lines | 264 Ω | 264 Ω @100 MHz | 2.00 mΩ | 4.00 A | 7.62 mm | 5.08 mm | 10.0 mm | 5.80 mm | 3 | THT | |
| | 74273002 | WE-MLS | 1111 | | 4 lines | 249 Ω | 260 Ω @300 MHz | 2.00 mΩ | 4.00 A | 10.9 mm | 5.49 mm | 10.0 mm | 3.19 mm | 4 | THT | |
| | 742730021 | WE-MLS | 1111 | | 4 lines | 170 Ω | 200 Ω @1.00 GHz | 2.00 mΩ | 4.00 A | 11.2 mm | 11.2 mm | 5.00 mm | 4.25 mm | 4 | THT | |
| | 742730022 | WE-MLS | 1111 | | 4 lines | 248 Ω | 275 Ω @400 MHz | 2.00 mΩ | 4.00 A | 11.2 mm | 11.2 mm | 8.00 mm | 2.75 mm | 4 | THT | |

742863160 WE-CBF HF · 0603 600 Ω


742792656 WE-CBF · 0603 750 Ω

74269262601 WE-TMSB · 0603 600 Ω

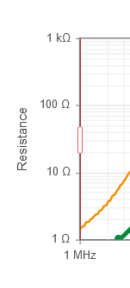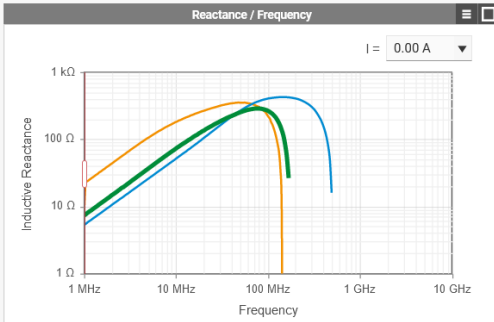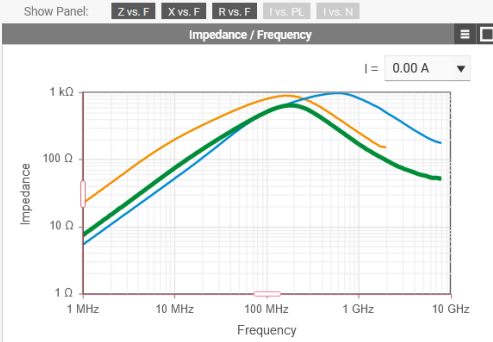Click and type or drop an Order Code here



ABOUT WÜRTH ELEKTRONIK | SITEMAP | CONTACT | IMPRINT | COPYRIGHT © 2020 WÜRTH ELEKTRONIK GMBH. ALL RIGHTS RESERVED.

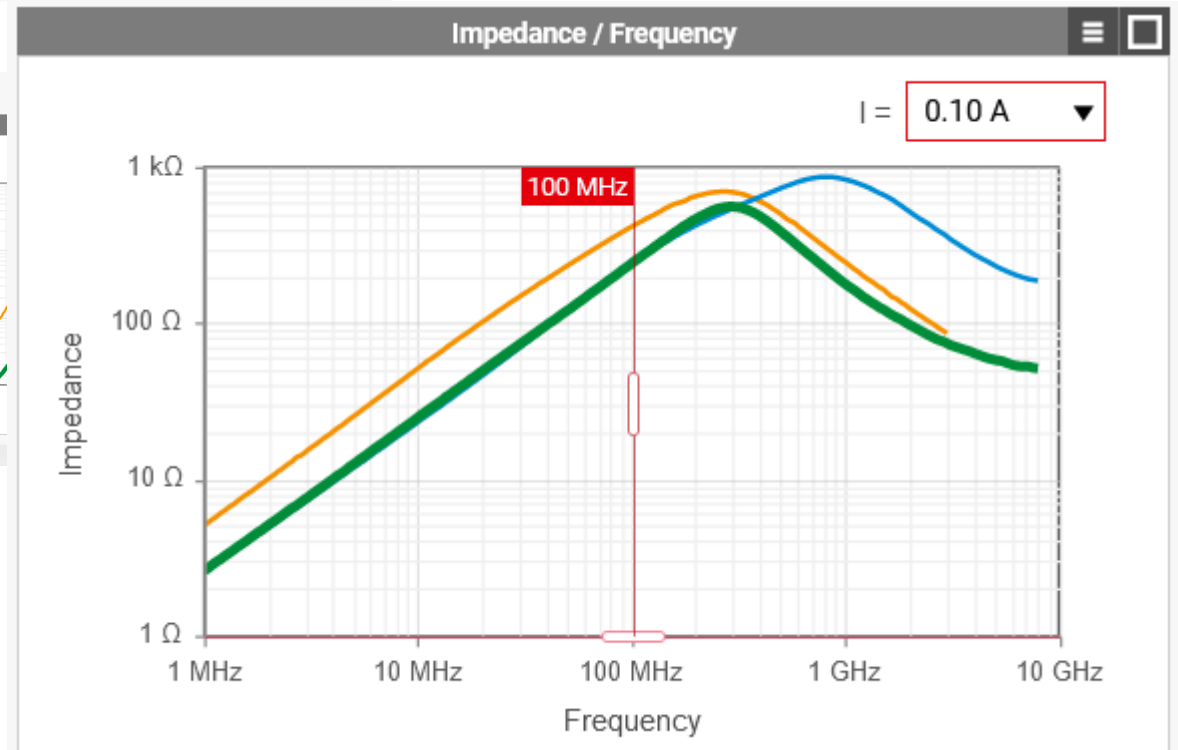


Low Current Summary




Components

➤ Coil – WE-KI

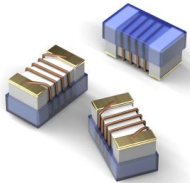

- Resonances
- Not for low freq.

➤ Ferrite – WE-CBF HF

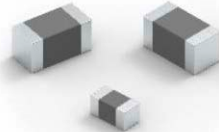

- No resonances
- Broadband


Conclusion

- Compare different inductors and ferrites
- Measurement data with DC-Bias available
- Ferrites improve broadband RF throughput



➤ High Current

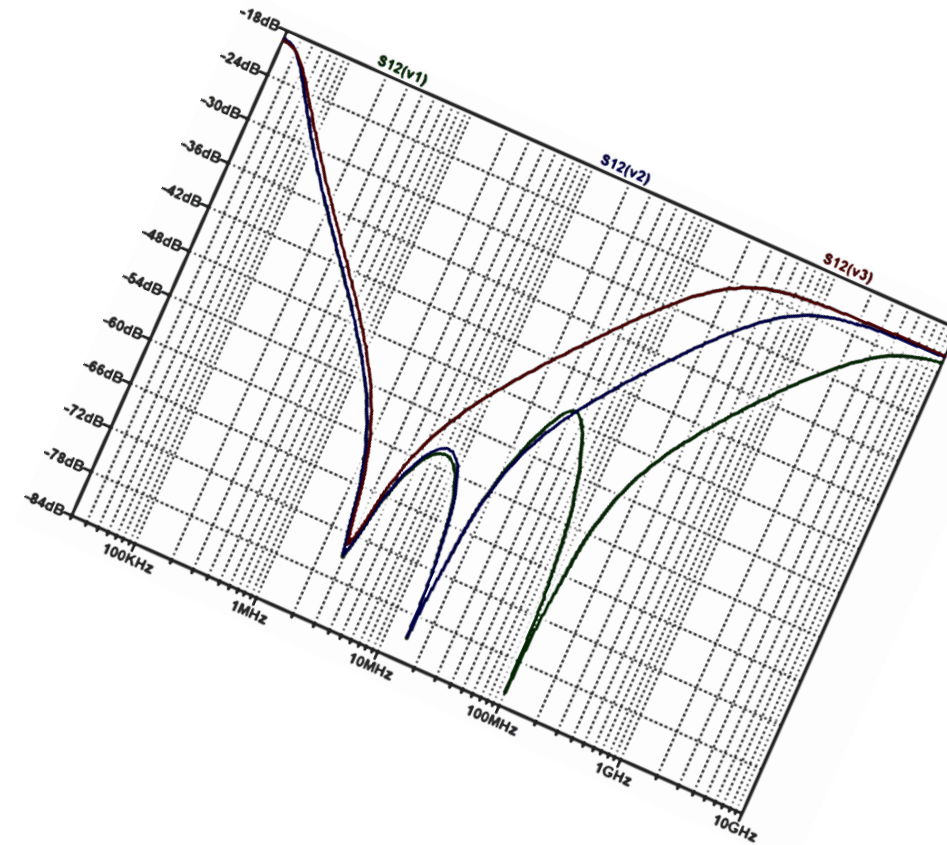- *Concept*
- *Simulation example*
- *Components*



High Current

Concept – Bias Tee (1)



➤ Theory:


- DC-Block & RF-Block

➤ Characteristic RF-Block:

- DC: Low $R = R_{DC}$
- RF: High Z


➤ Broadband:

- Cascade RF-Block

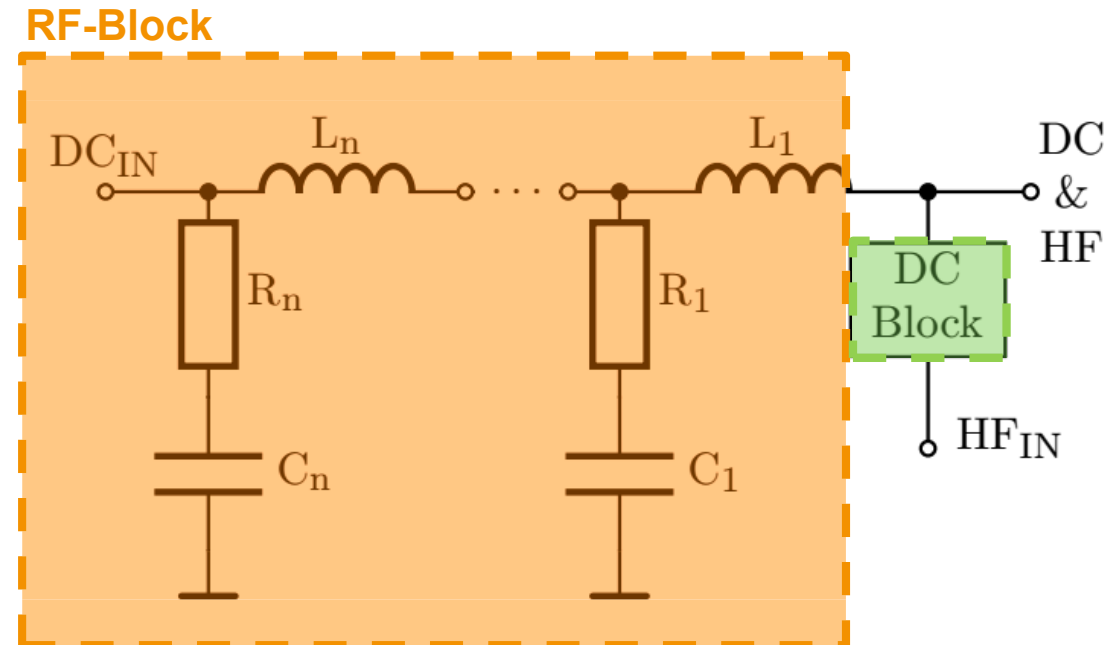

High Current

Concept – Bias Tee (2)

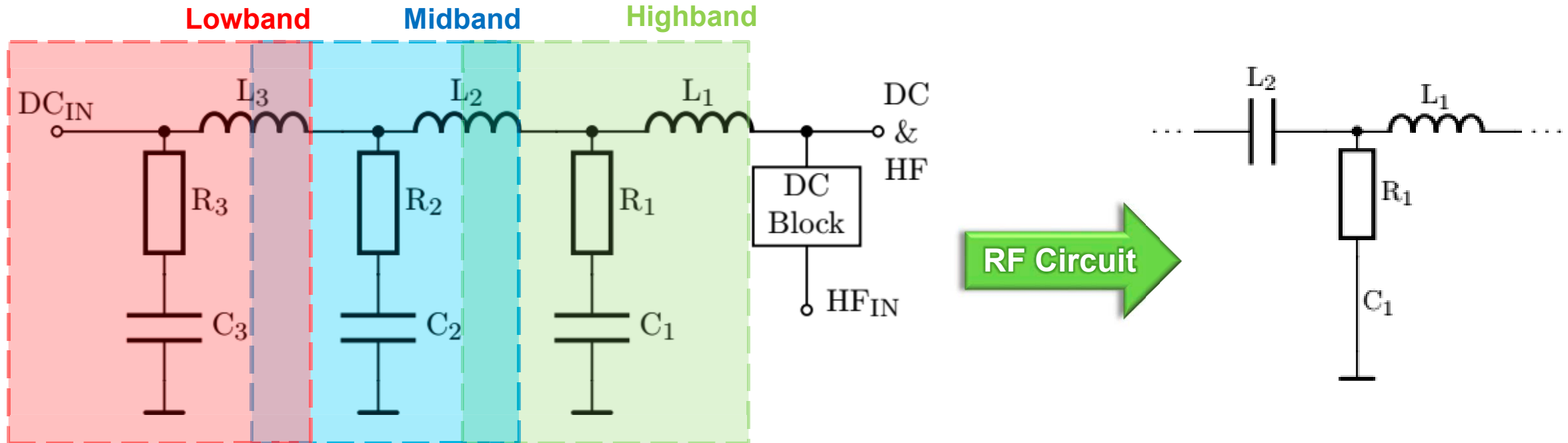

➤ Capacitors & Inductors

- $C_3 > C_2 > C_1$
- $L_3 > L_2 > L_1$





➤ Resistors

- Low $R_3 \rightarrow$ low Z_{DCin}
- $R_3 \ll R_2 \leq R_1$
- accordingly to Z_{ind}

➤ At resonance frequency

- $L_1 \rightarrow$ ind. & $L_2 \rightarrow$ cap.
- $C_1 \rightarrow$ short
- R_1 damps Q_{L1L2}

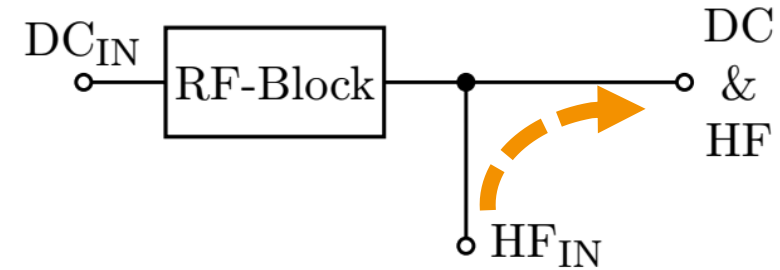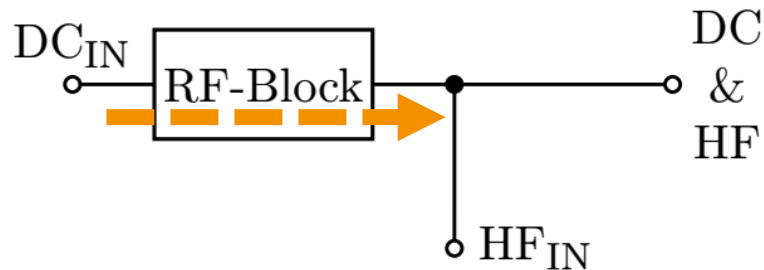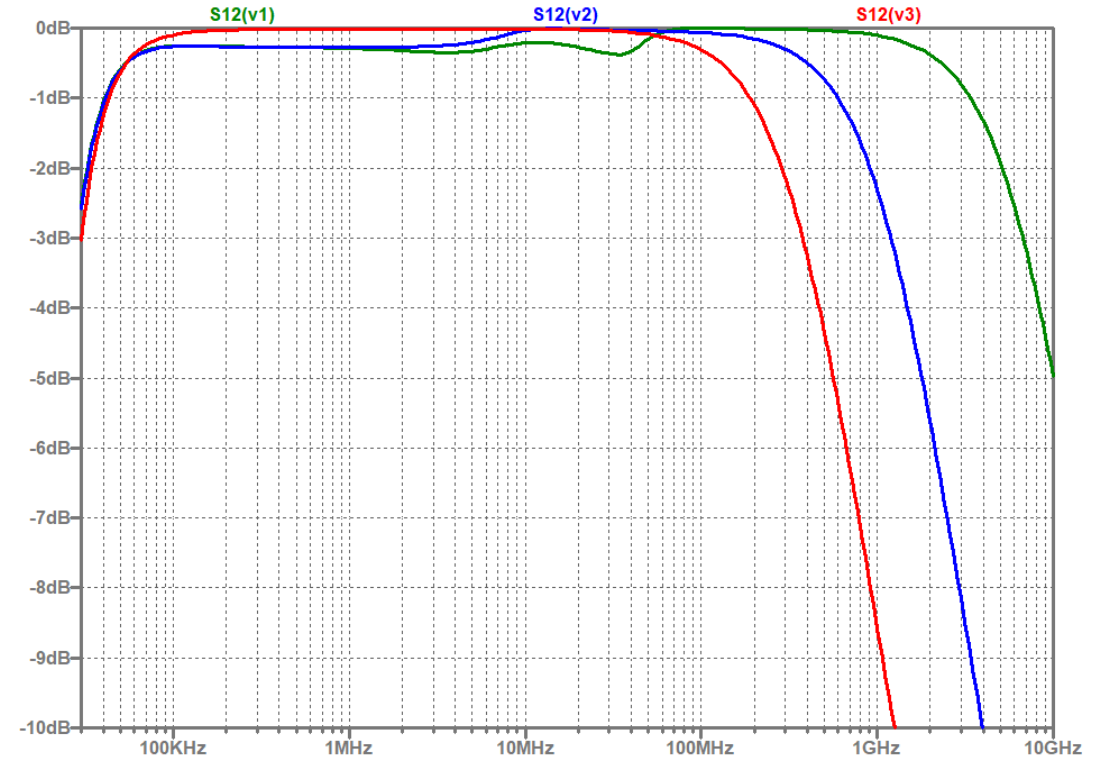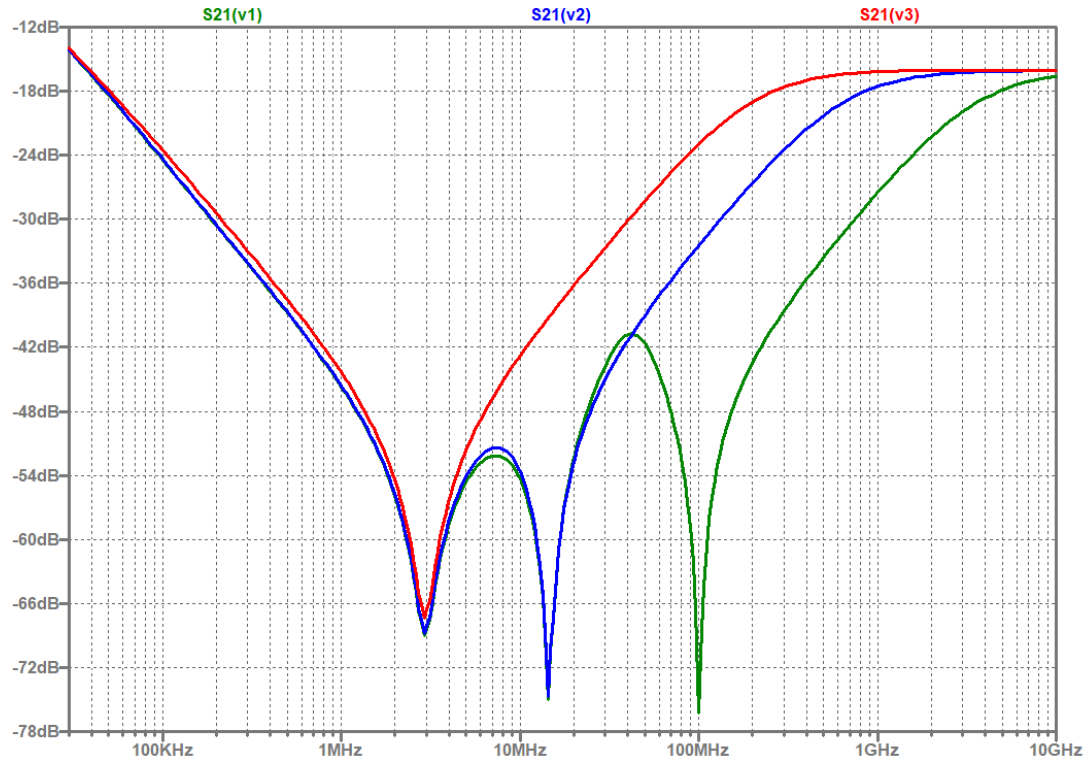High Current Simulation – 3rd order Bias-Tee



High Current Components




➤ Inductors:

- Unshielded & Semishielded for high current
 - Constant L → No saturation over current
 - Very low R_{DC} → small voltage drop
 - E.g: PD2, PD4, HCF or SD
- Be aware of coupling

Smaller H-Field



Wider H-Field

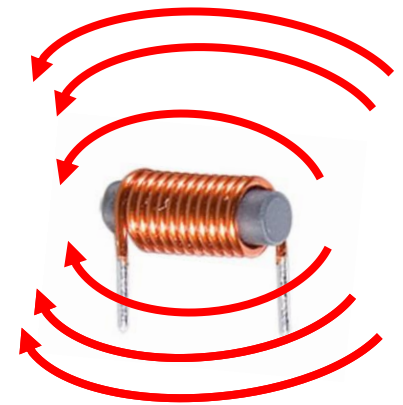

➤ Capacitors:

- Stable over voltage
- MLCC: e.g. NP0
- Electrolytic: not for bipolar applications



High Current

Summary



Theory – RF-Block

- For DC: lowest possible R_{DC}
 - For RF: high impedance
 - Broadband: cascading
- Values:
 - $C_3 > C_2 > C_1$
 - $L_3 > L_2 > L_1$
 - $R_3 \ll R_2 \leq R_1$

Components

➤ Inductor



- Semi & Unshielded
- Low R_{DC}
- Coupling!

➤ Capacitor




- MLCCs – NP0
- Electrolytics
 - Polarisation!



➤ DC-Block

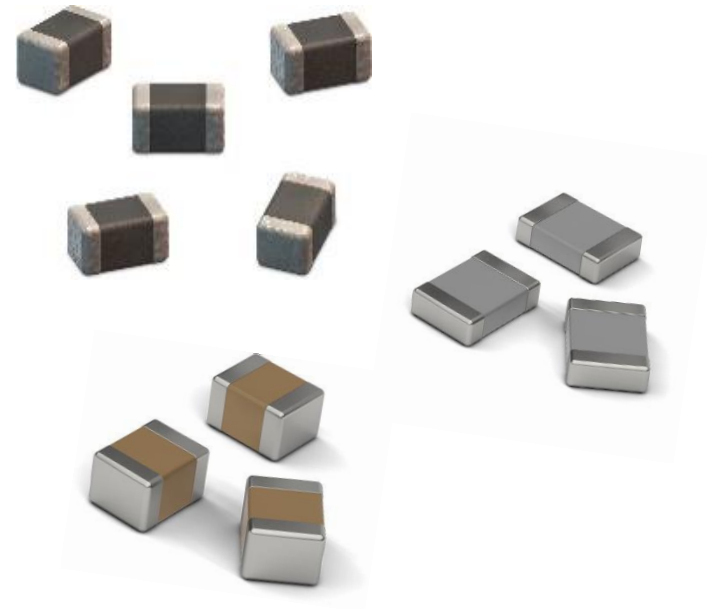- *Concept*
- *Standard*
- *Extreme Range*



DC Block

Concept




➤ Capacitor:

- Blocks DC to RF Source
- Determines voltage & frequency range

➤ ESD-Protection:

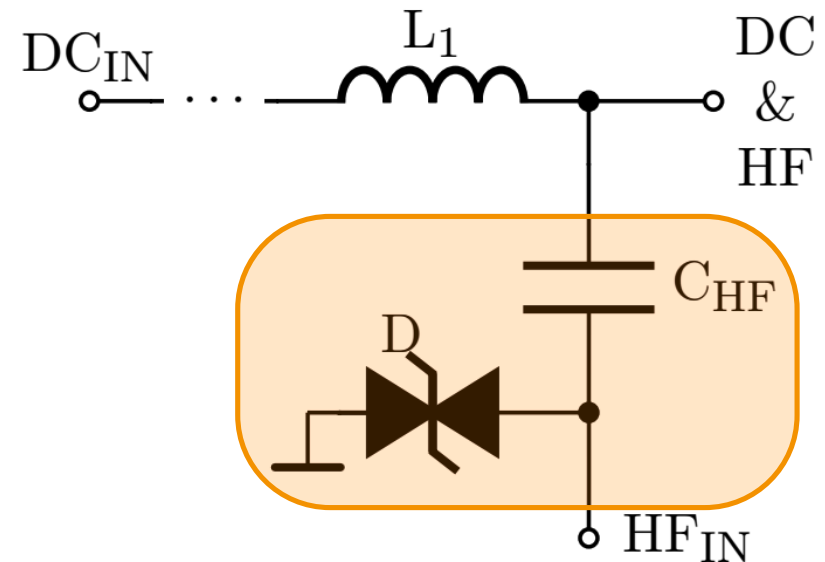- Needed if separate input or output
- E.g. bidirectional





DC Block

Standard



➤ MLCCs:

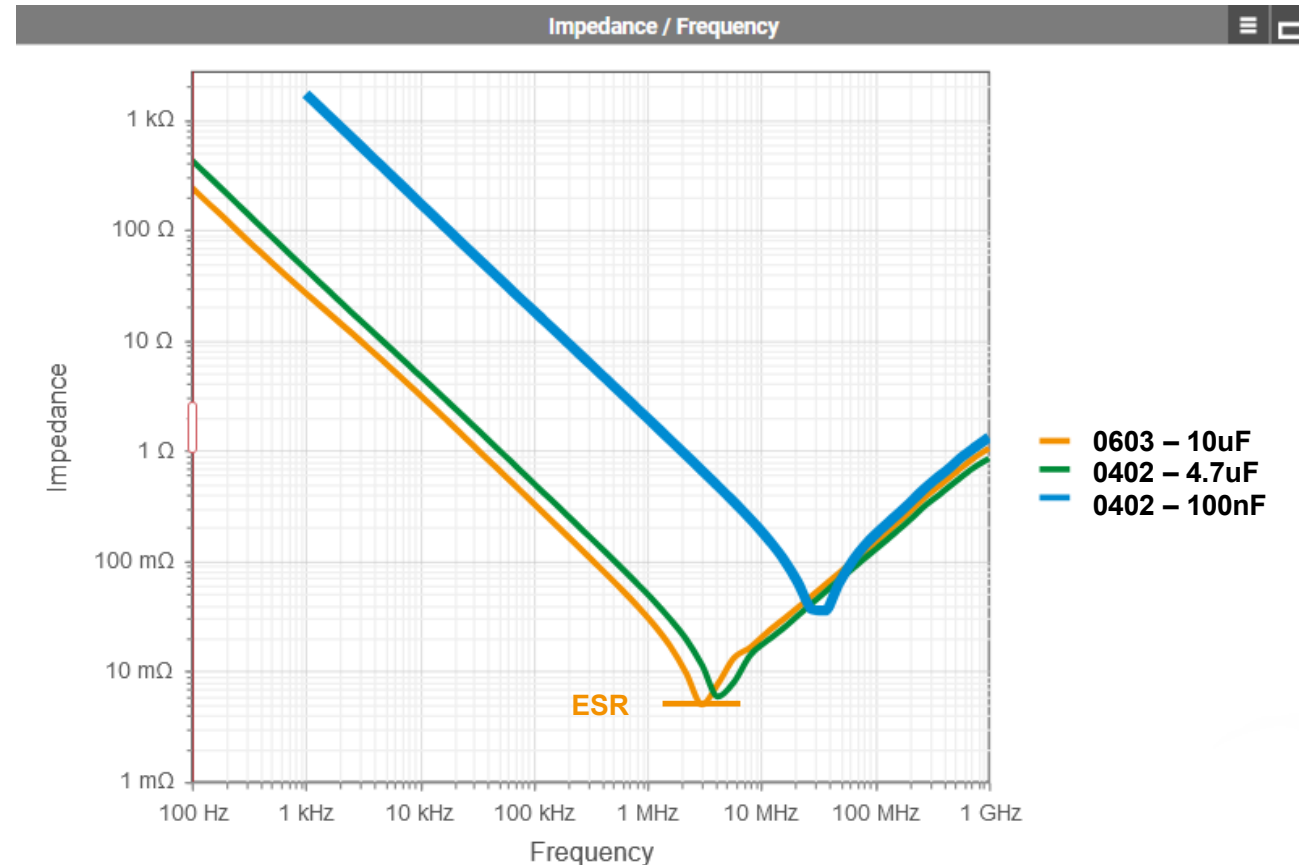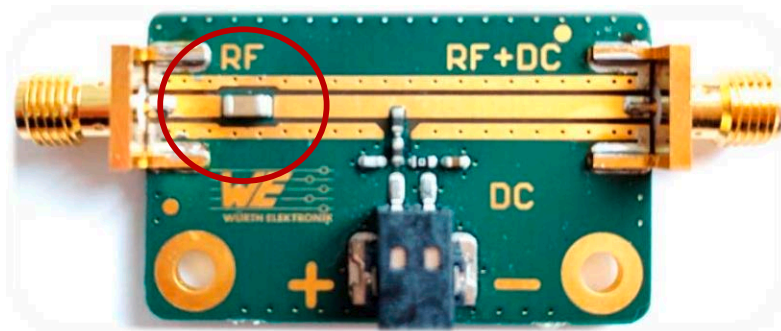- Broadband needed → used above SRF
- Use highest value of biggest possible size
 - Low ESR
 - Low ESL




DC Block

Extreme Range



➤ High voltage:

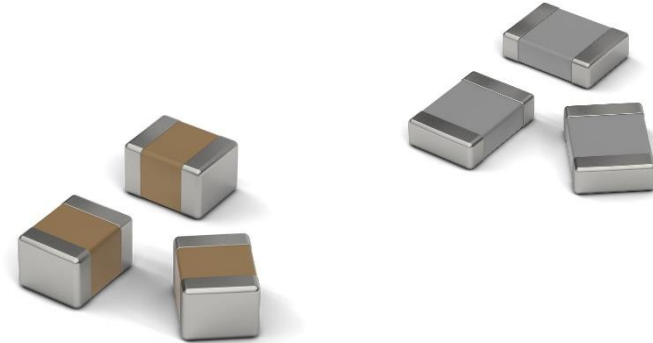- Safety & High Voltage Types MLCCs like *CSMH* or *CSSA*
- Bigger in size → Line impedance!



➤ Extreme broadband:

- Combine two different capacitors
 - E.g. MLCCs and electrolytic
 - Be aware of resonances



- Use special capacitor types

DC Block

Summary



Overview

➤ Blocks DC to RF Source

➤ Low ESR

➤ Low ESL




MLCCs

Use highest value of
biggest possible size

Extreme Range


➤ High Voltage

➤ High Voltage MLCCs

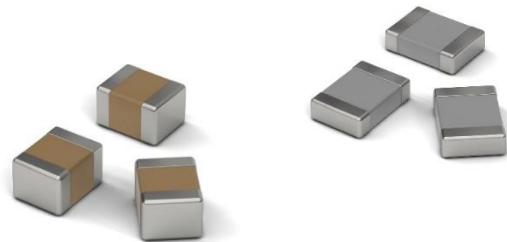


➤ Extreme broadband

➤ Two Capacitors


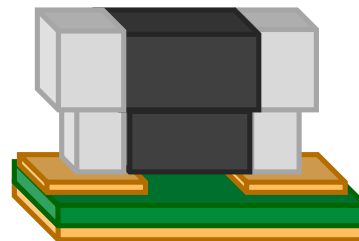


➤ **Measurement to simulation**

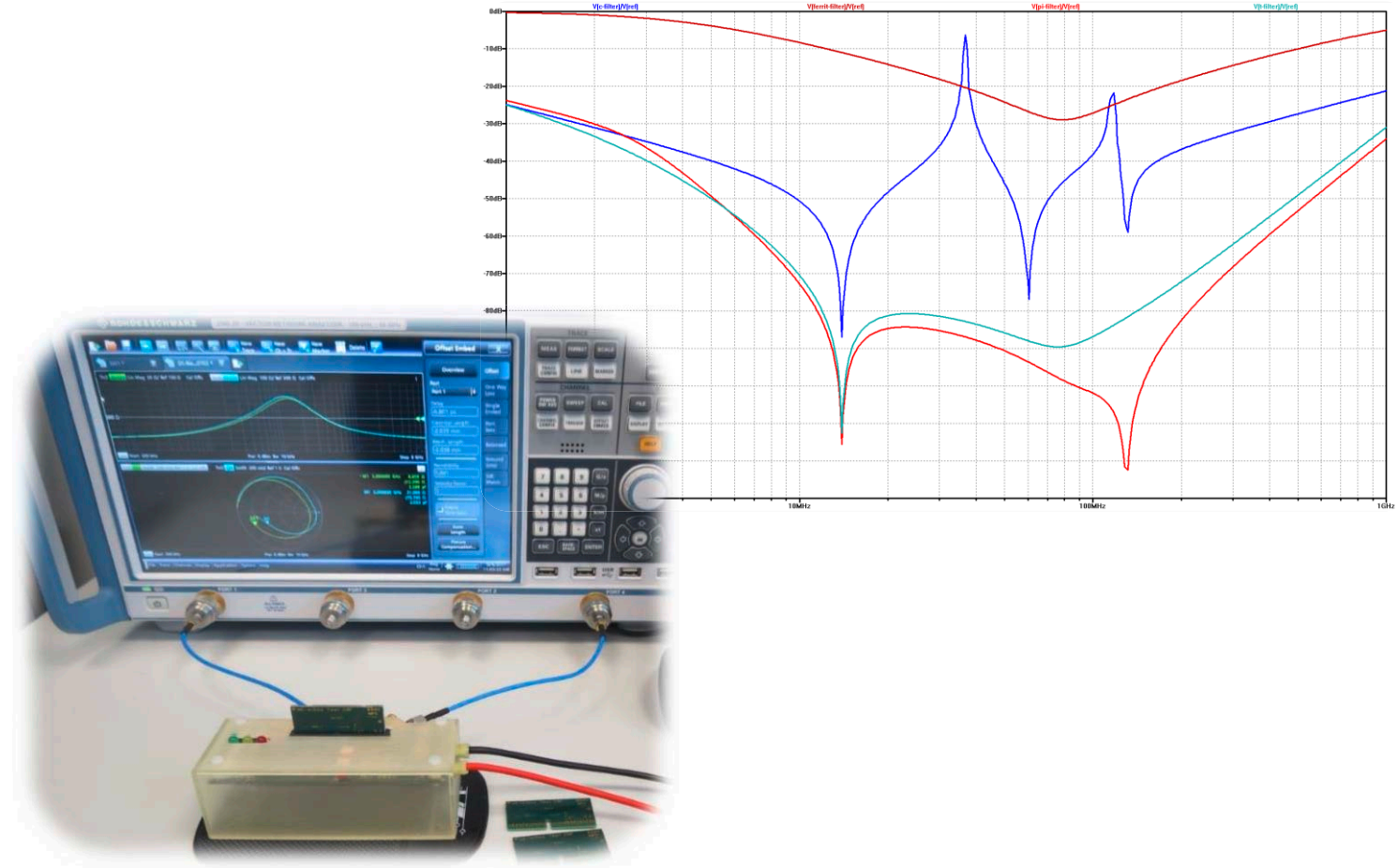

Measurement to simulation

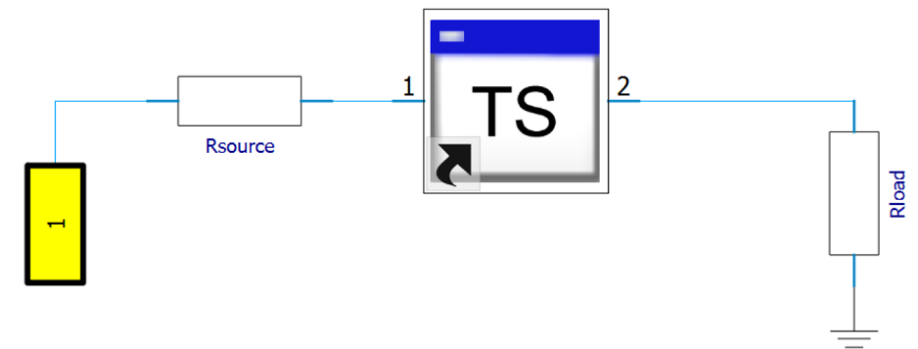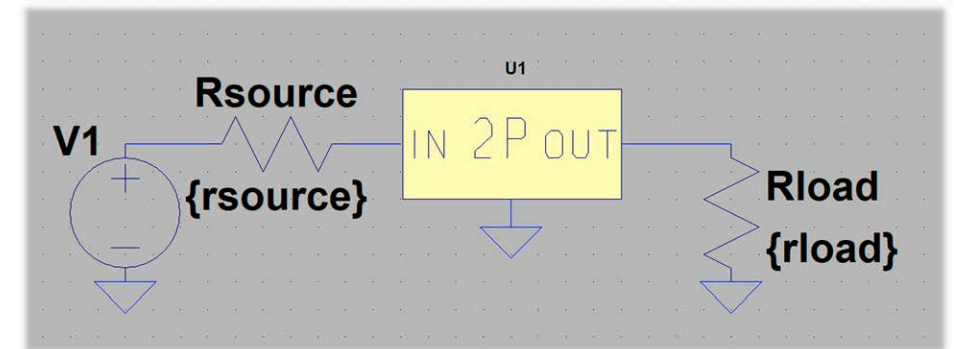- Include measurement data e.g. touchstone (s1p,s2p...)
- Simulate load & source impedance change
- Behaviour with other modules






➤ Final Summary




Final Summary

Low Current

- **RF Coil** 
 - Resonances
 - Not for low freq.
 - **Ferrite** 
 - No Resonances
 - Broadband
- Ferrites improve broadband RF throughput

High Current

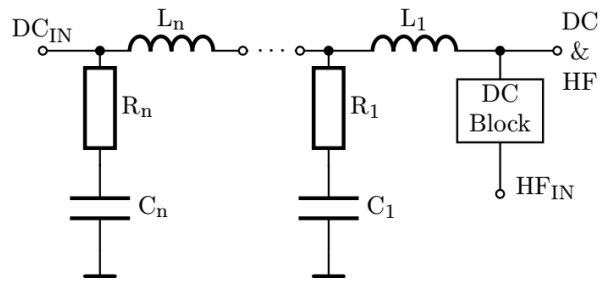- **Cascading** → broadband
- 
- **Inductors**
 - Semi & Unshielded
 - Low RDC
 - **Capacitors**
 - Stable over voltage

Great RF throughput &
Disturbtion free power line



