
IMPEDANCES IN DC-MICROGRIDS FROM OFFLINE TO ONLINE MEASUREMENTS

Raffael Schwanninger: raffael.schwanninger@fau.de

Bernd Wunder: bernd.wunder@iisb.fraunhofer.de



Friedrich-Alexander-Universität
Technische Fakultät



Fraunhofer


IISB




Agenda

- *Introduction to the DC-Microgrid*
- *Opportunities for Impedance Measurements in DC-Microgrids*
- *Droop-Controlled DC-Microgrids*
- *Stability Investigation through Impedance Measurements*
- *Bode 100 Testbench*
 - *Output-impedance of a constant-current source*
 - *Output-impedance of a constant-voltage source*
 - *Output-impedance of a droop-controlled converter*
 - *Input-impedance of a constant-power load*
- *Online Measurement with Pseudo-Random-Binary-Sequences*
- *Advanced Data Analytics for Grid Layout and Stability Optimization*
- *Stabilization of DC Networks Applying Artificial Intelligence*
- *Summary*


Introduction to the DC-Mircrogrid

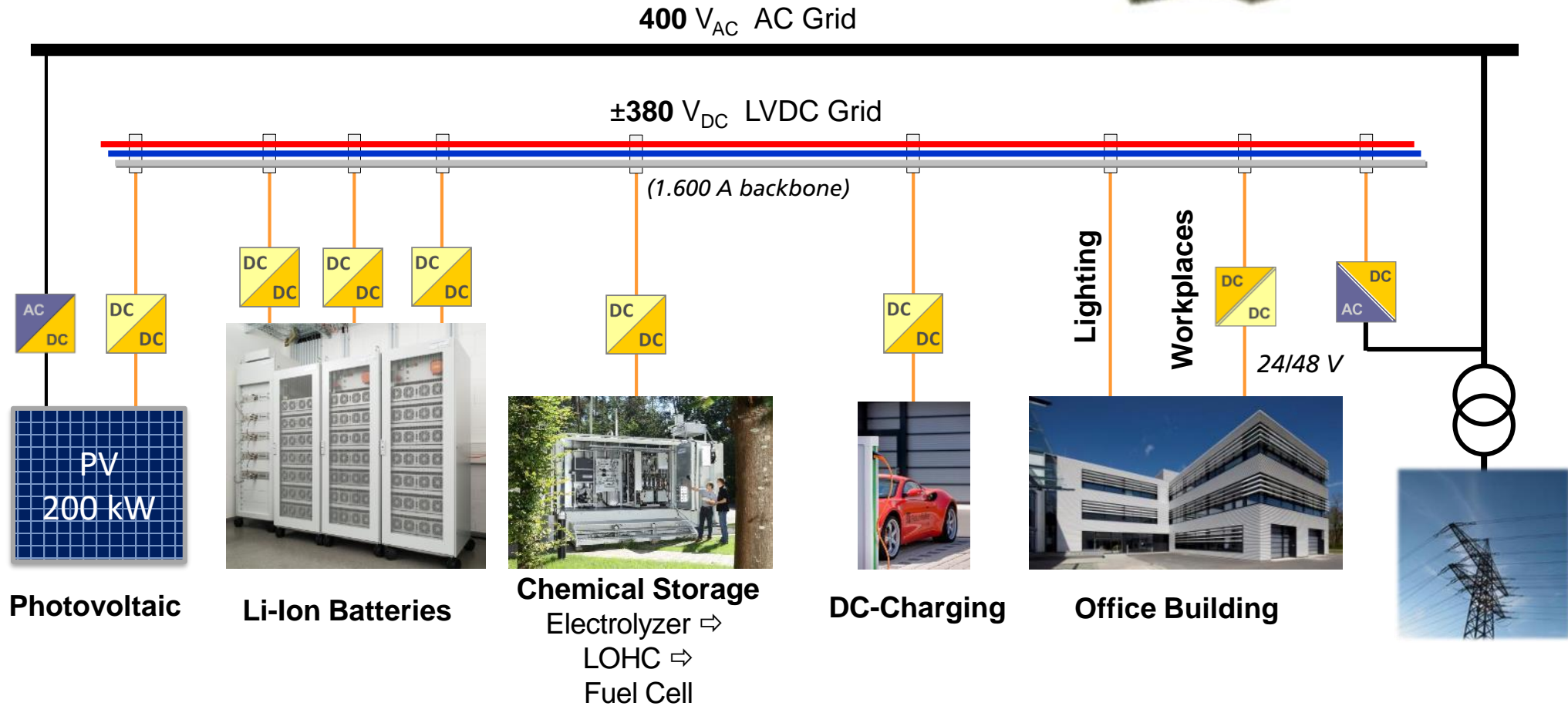

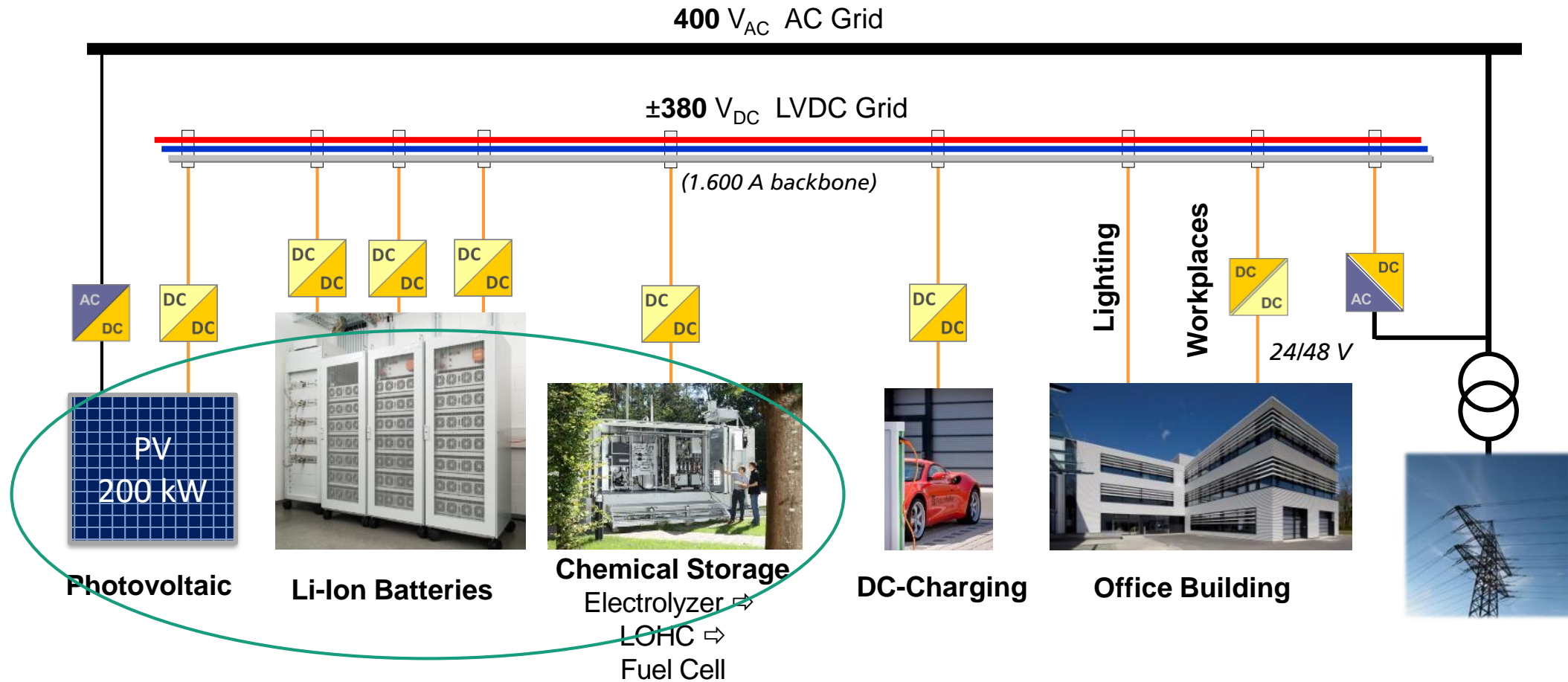Opportunities for Impedance Measurements in DC-Microgrids



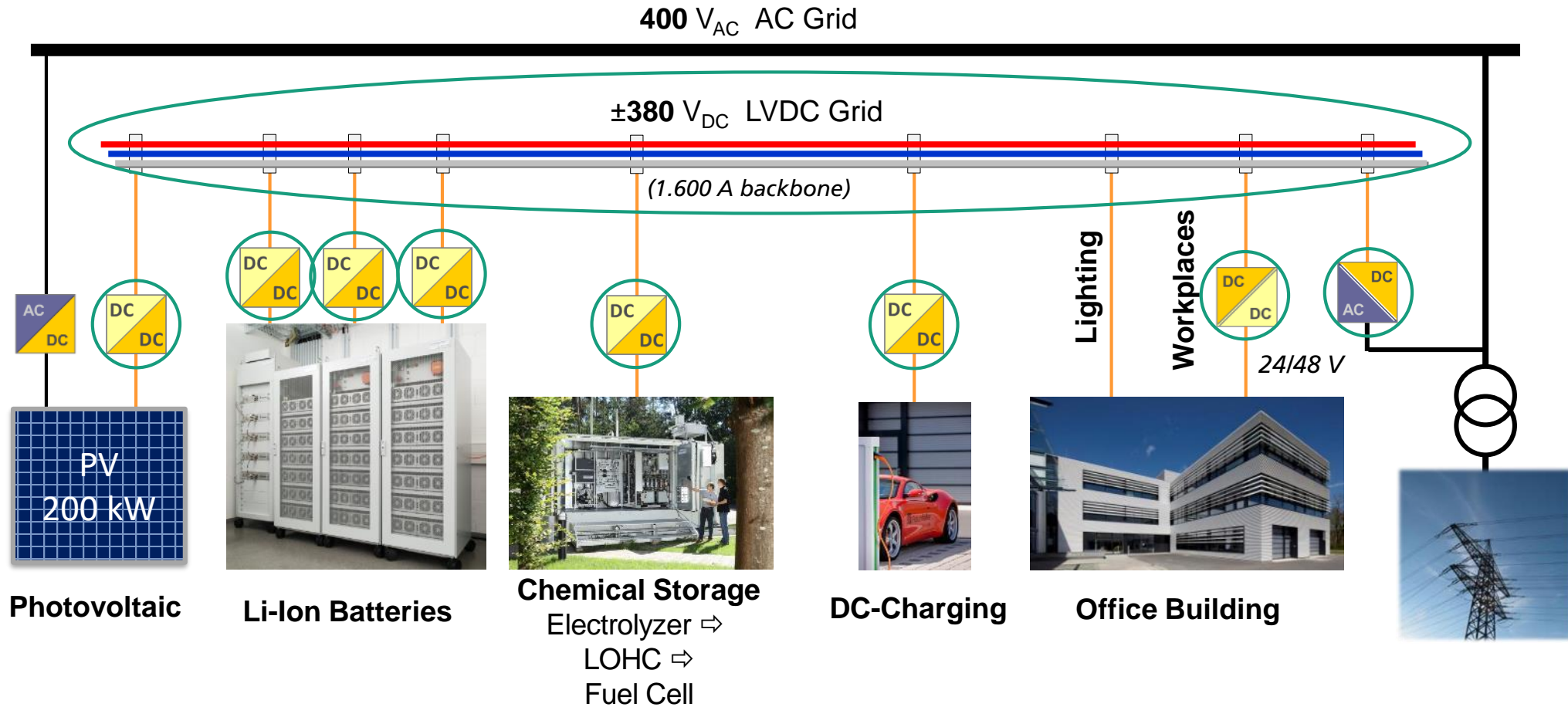
Opportunities for Impedance Measurements in DC-Microgrids



Opportunities for Impedance Measurements in DC-Microgrids

■ Why online measurements?

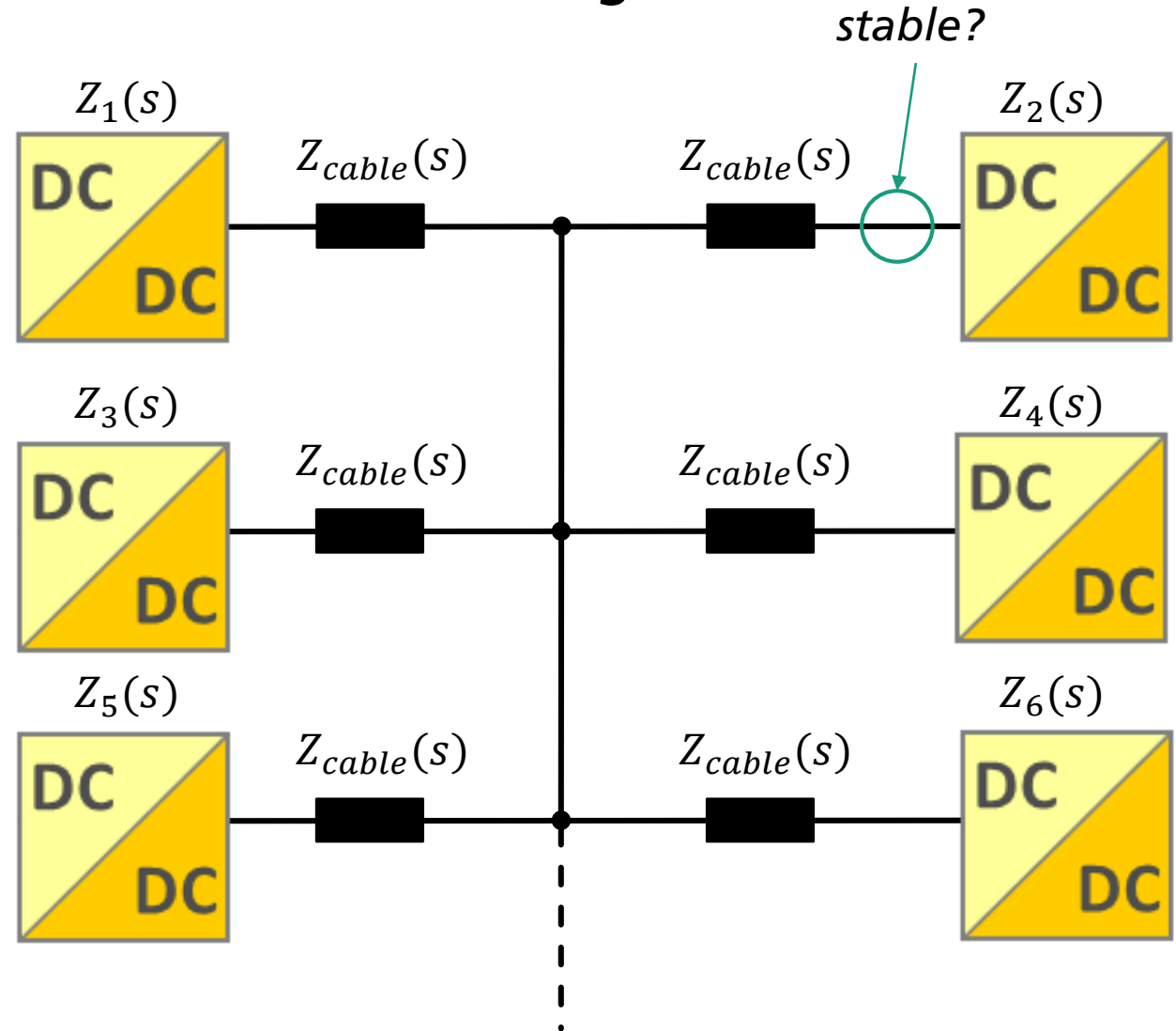
- Real grids are complex
- Converters are nonlinear
- Adjustable parameters:
 - Control
 - Mode of operation
 - Controller
 - Digital filter
 - Droop-curve
 - Slope
 - Shape
 - Offset



Agenda


- *Introduction to the DC-Microgrid*
- *Opportunities for Impedance Measurements in DC-Microgrids*
- ***Droop-Controlled DC-Microgrids***
- *Stability Investigation through Impedance Measurements*
- *Bode 100 Testbench*
 - *Output-impedance of a constant-current source*
 - *Output-impedance of a constant-voltage source*
 - *Output-impedance of a droop-controlled converter*
 - *Input-impedance of a constant-power load*
- *Online Measurement with Pseudo-Random-Binary-Sequences*
- *Advanced Data Analytics for Grid Layout and Stability Optimization*
- *Stabilization of DC Networks Applying Artificial Intelligence*
- *Summary*

Droop-Controlled DC-Microgrids


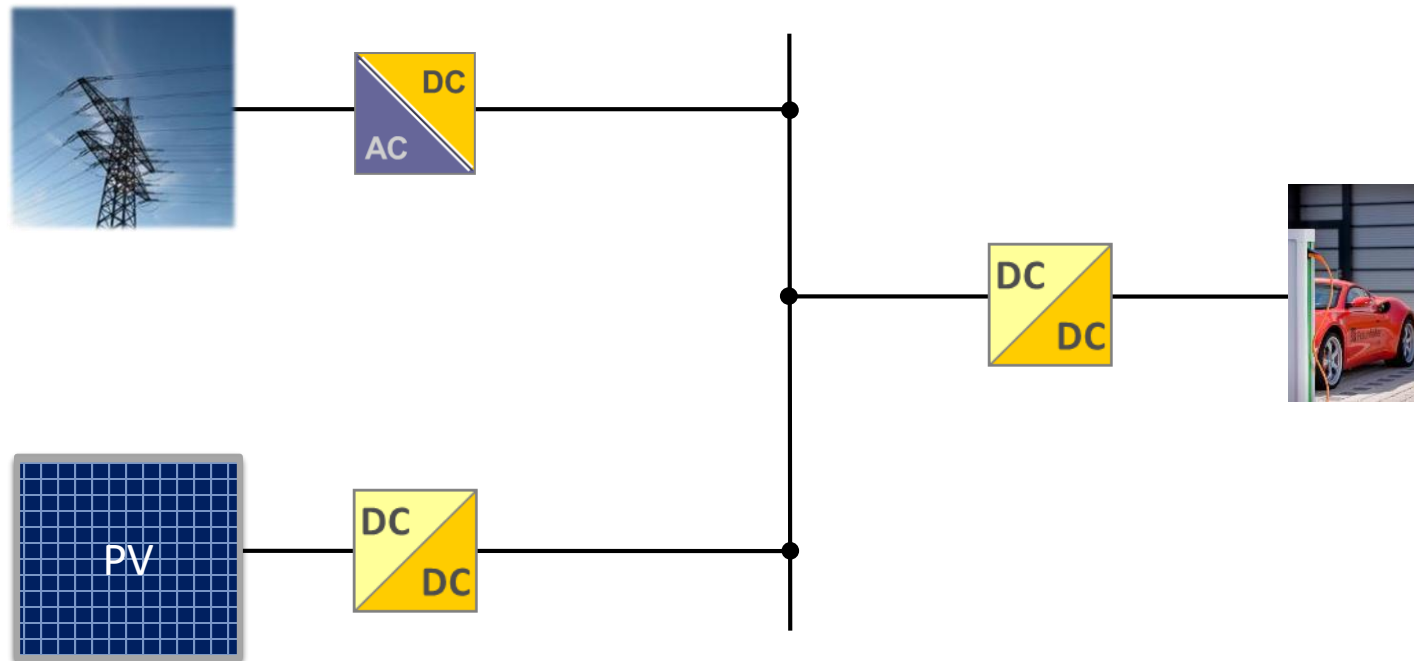


Droop-Controlled DC-Microgrids

- Voltage Control:

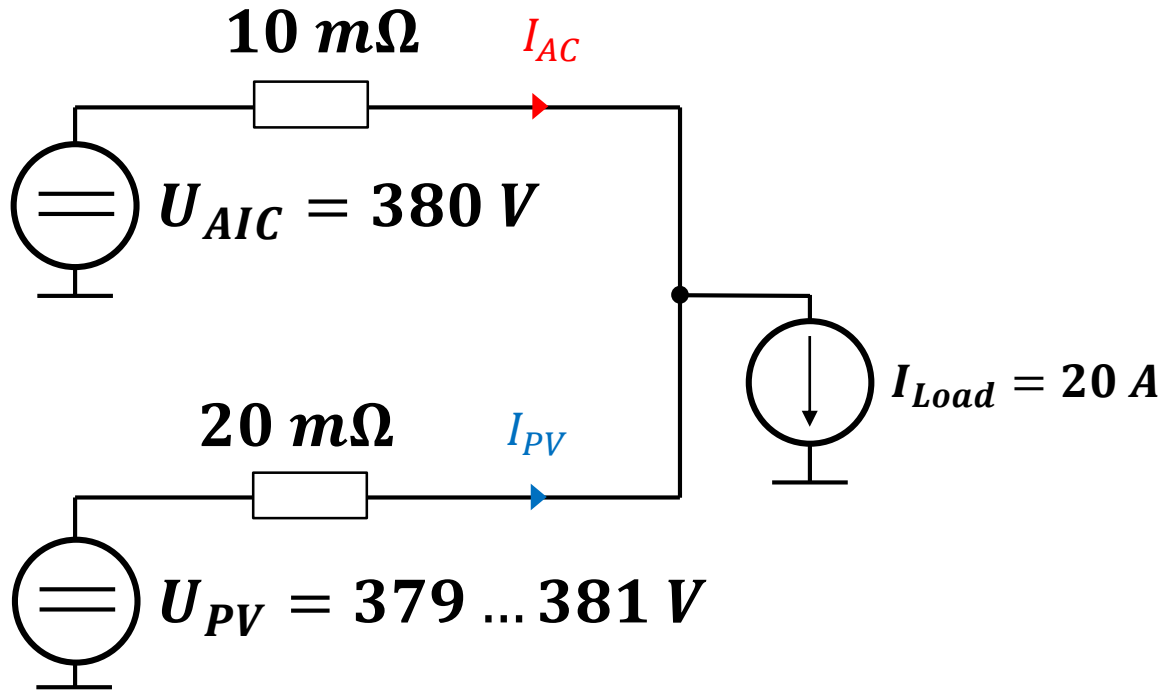


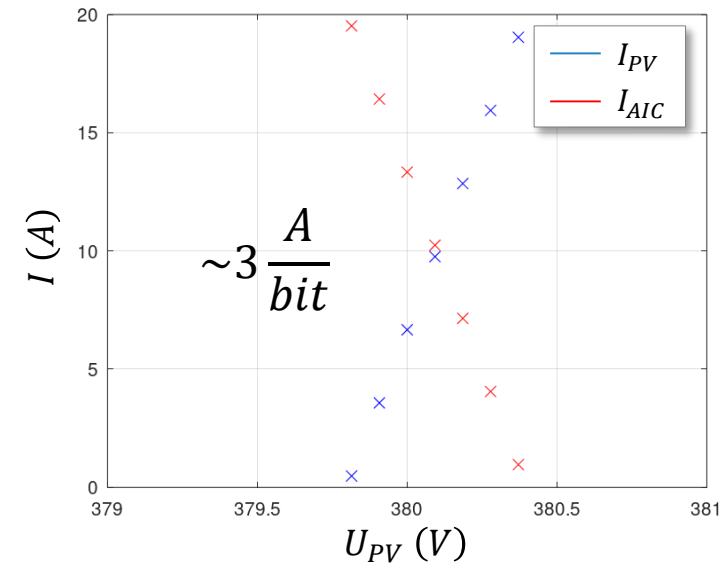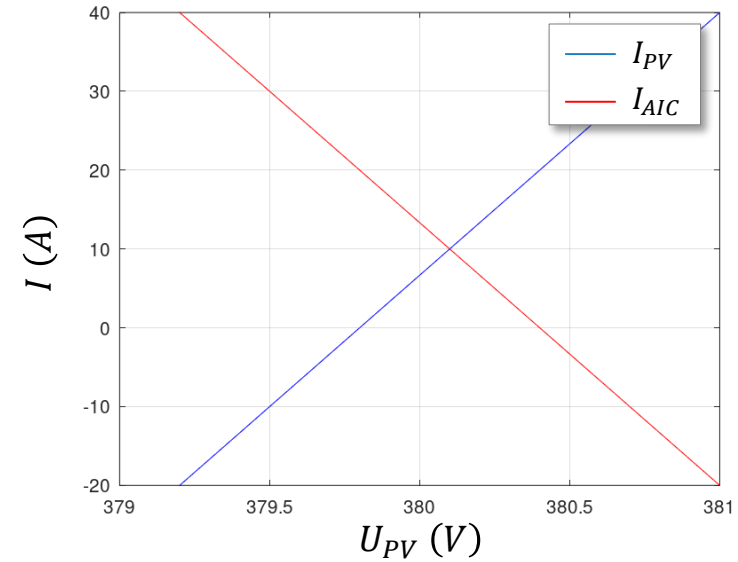- Voltage sources need fine tuning
- Load sharing is nearly impossible with a 12-bit ADC



Droop-Controlled DC-Microgrids


- *Master-Slave Control:*

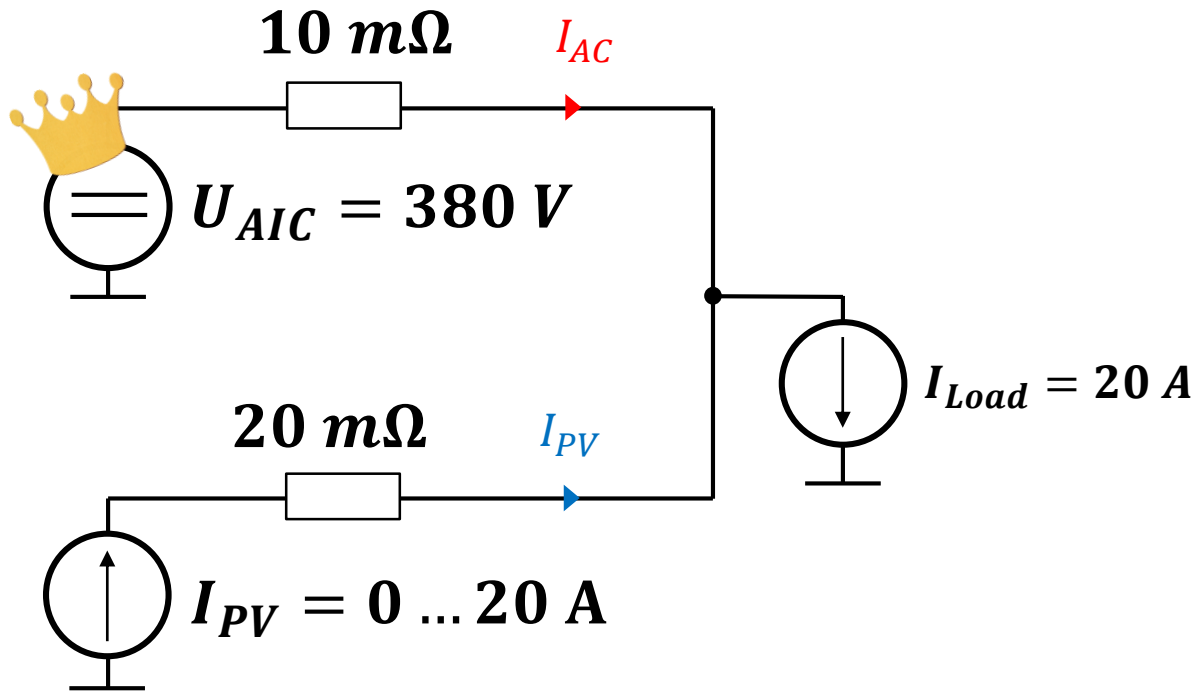



- *Less communication is required*
- *Master must be a bidirectional source*
- *Master must not be turned off*

Droop-Controlled DC-Microgrids

■ *Transition to droop-control:*

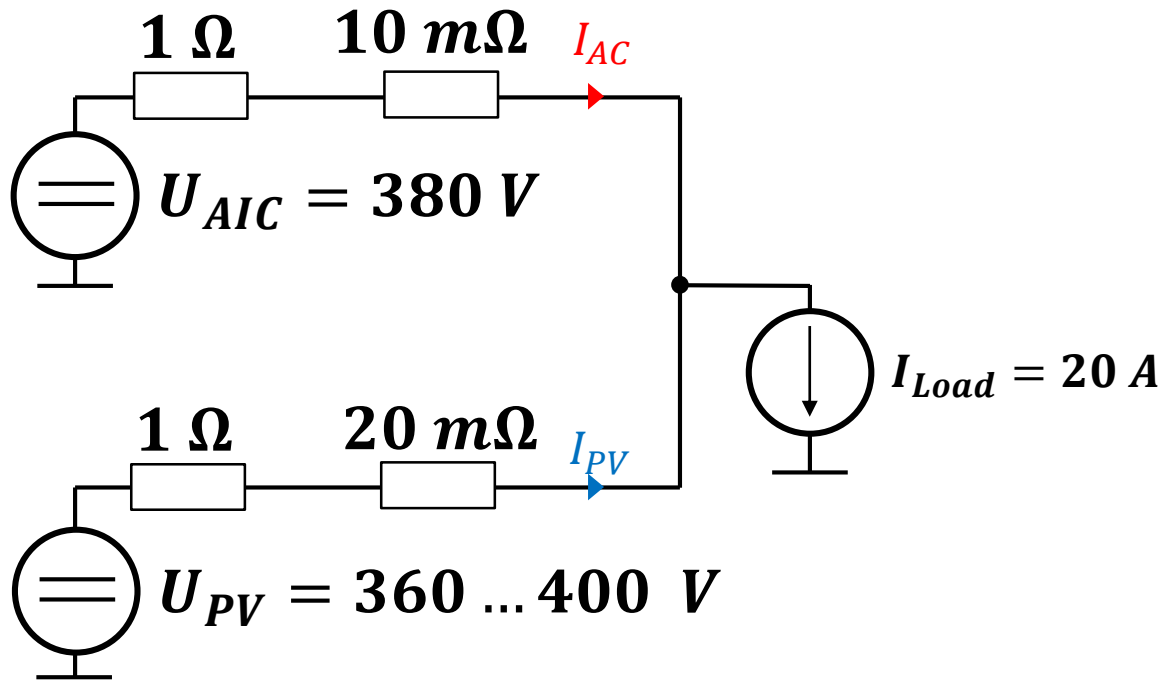

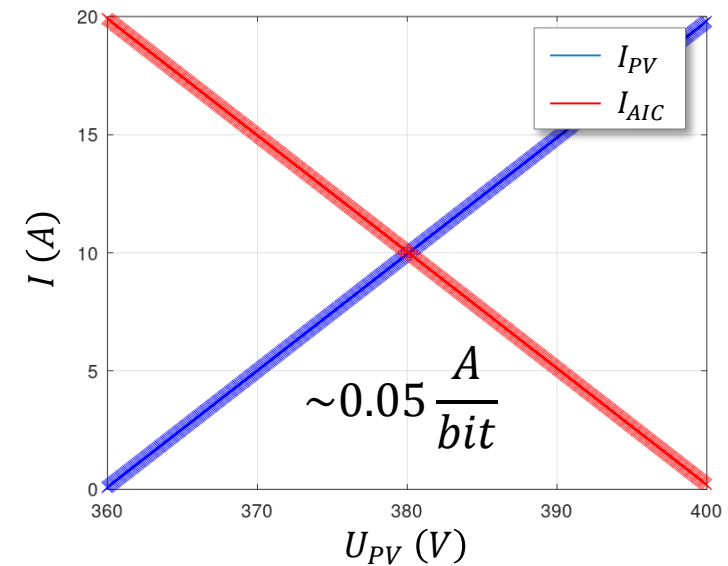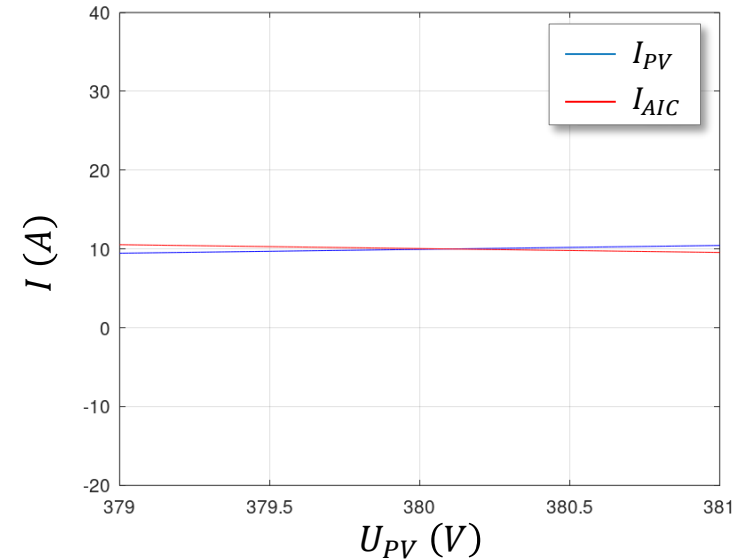- *No communication is required*
- *A defined additional resistance helps with load sharing*
- *Use a virtual droop-resistance*






Droop-Controlled DC-Microgrids

- Load sharing can be accomplished by droop-curves
- The droop-curve is defined by a small signal R_{Droop}
- For each linear interval I_O can be expressed as:

- $I_O = \frac{U_{Grid} - \tilde{U}_0}{R_{Droop}} + \tilde{I}_0$

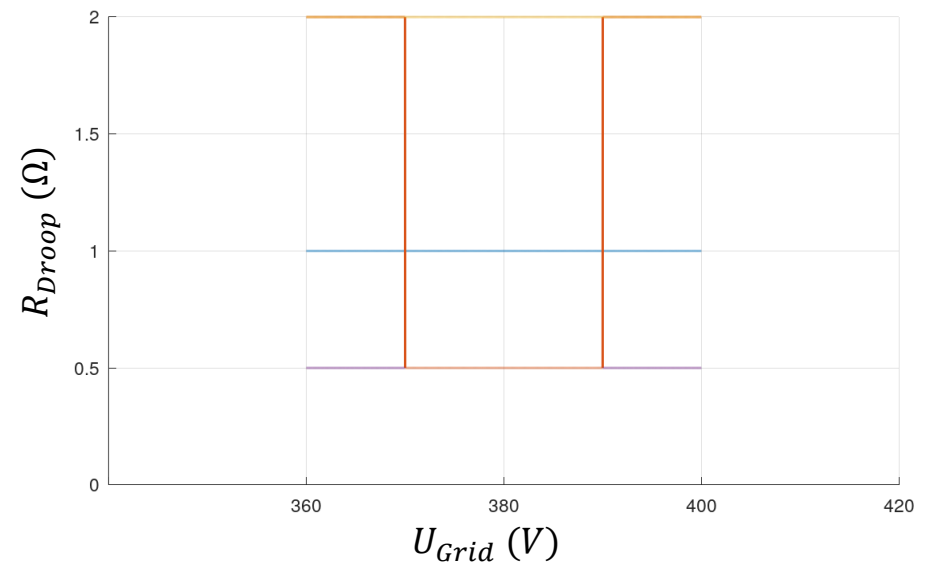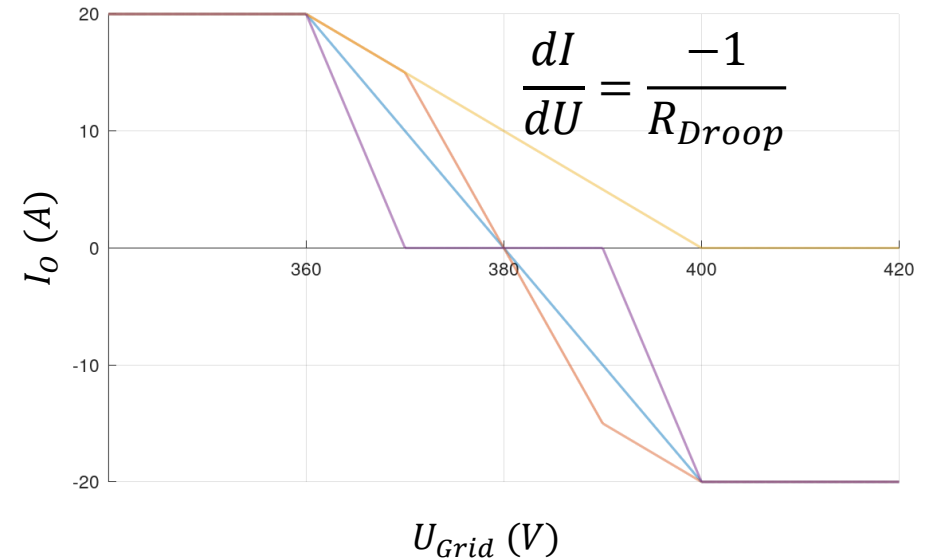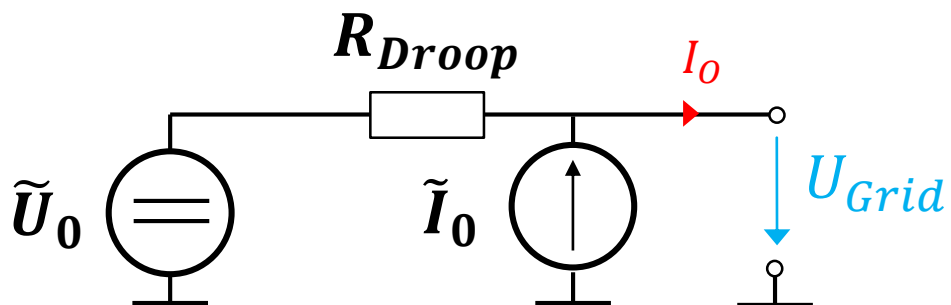- Example (blue curve from 360 V to 400 V)

- $I_O = \frac{U_{Grid} - 380\text{ V}}{1\ \Omega}$






Droop-Controlled DC-Microgrids

- Load sharing can be accomplished by droop-curves
- The droop-curve is defined by a small signal R_{Droop}
- Droop-curves can also be nonlinear
- Constant-power-loads have a negative R_{Droop}
- Example (blue curve at 380 V):

$$\blacksquare I_O = \frac{P_O}{U_{Grid}} = \frac{5 \text{ kW}}{380 \text{ V}}$$

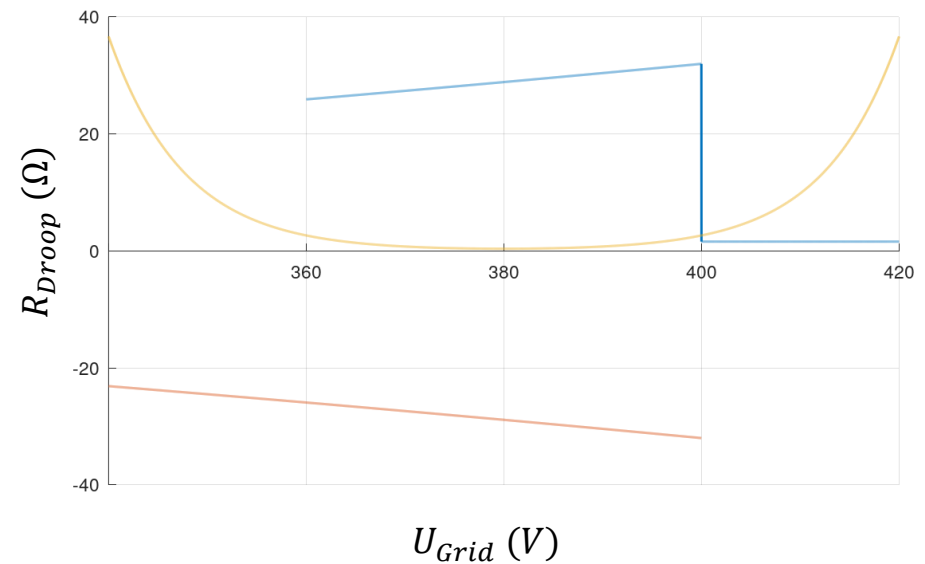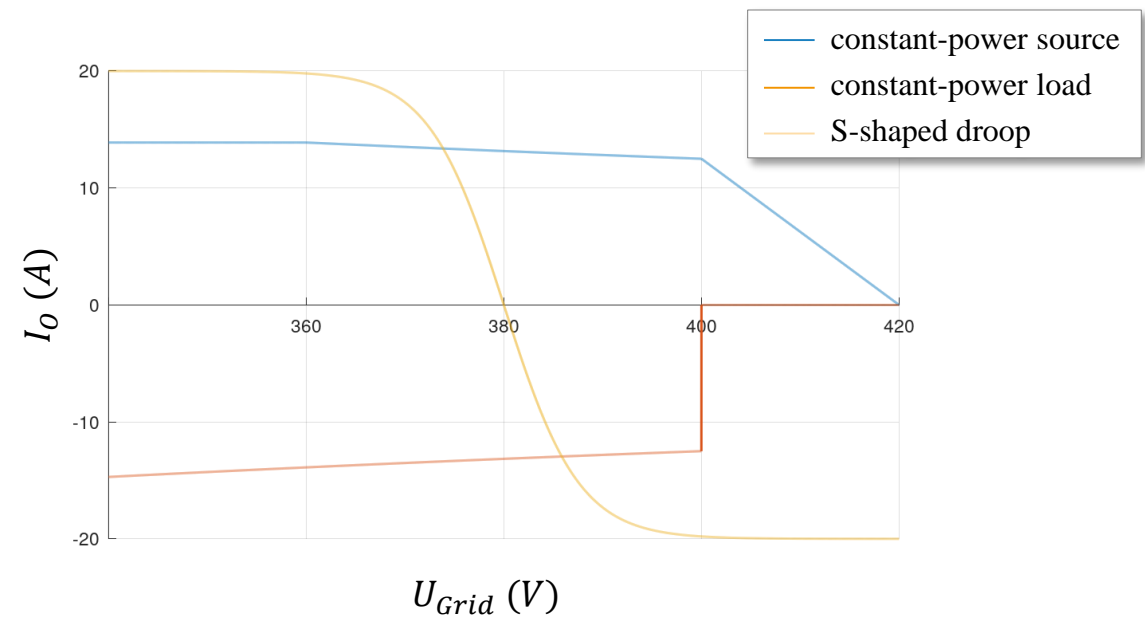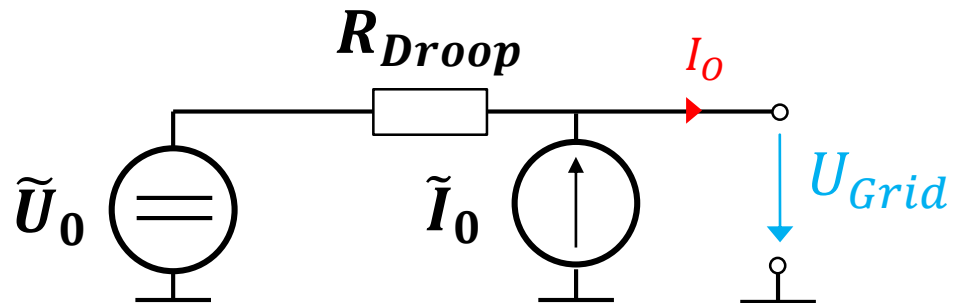
$$\blacksquare R_{Droop} = \frac{U_{Grid}^2}{P_O} = \frac{(380 \text{ V})^2}{5 \text{ kW}} = 28.88 \ \Omega$$




Droop-Controlled DC-Microgrids

Small-signal modeling:

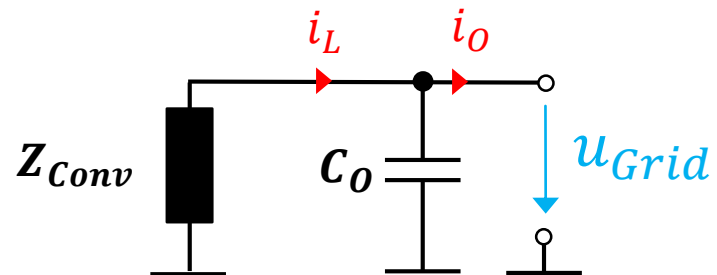- *Converter is current controlled*
- *Converters impedance Z_{Conv} can be separated from C_0*



Droop-Controlled DC-Microgrids

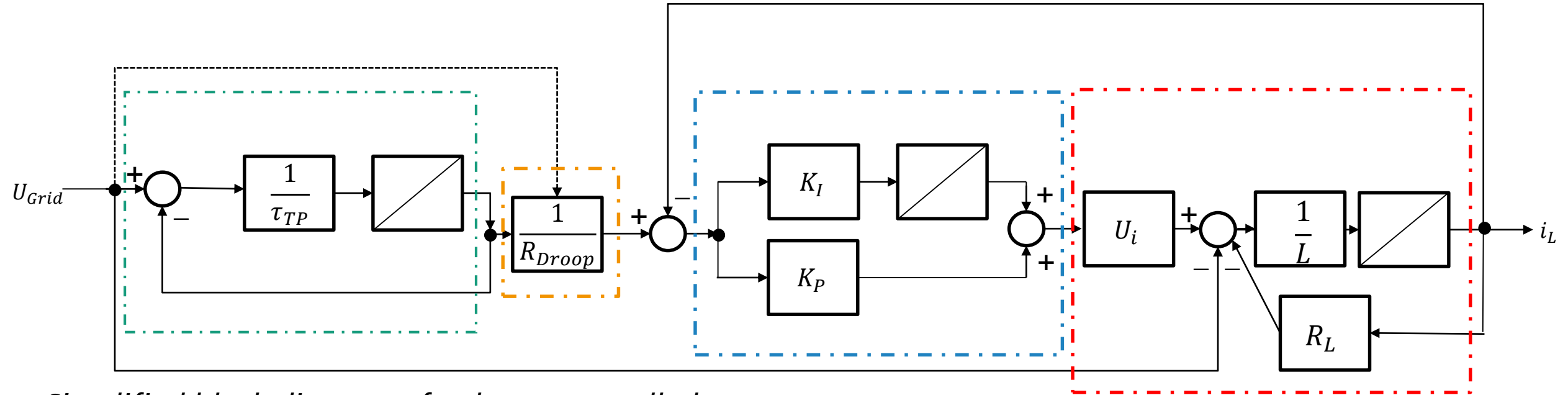

Simplified block diagram of a droop controlled converter:

- *Measurement filter*
- *Droop-resistance*
- *PI-controller*
- *Buck-converter*

Droop-Controlled DC-Microgrids

Small-signal modeling:

- *Converter is current controlled*
- *Converters impedance can be separated from C_0*
- *In many cases the current control acts like a low pass of 1st order*
- *Converter can be modeled as R-L-C*





Droop-Controlled DC-Microgrids

Small-signal modeling:

■ Converter can be modeled as R-L-C

■ L is part of the low pass $L_{LP} = \frac{R_{Droop}}{2\pi \cdot f_c}$

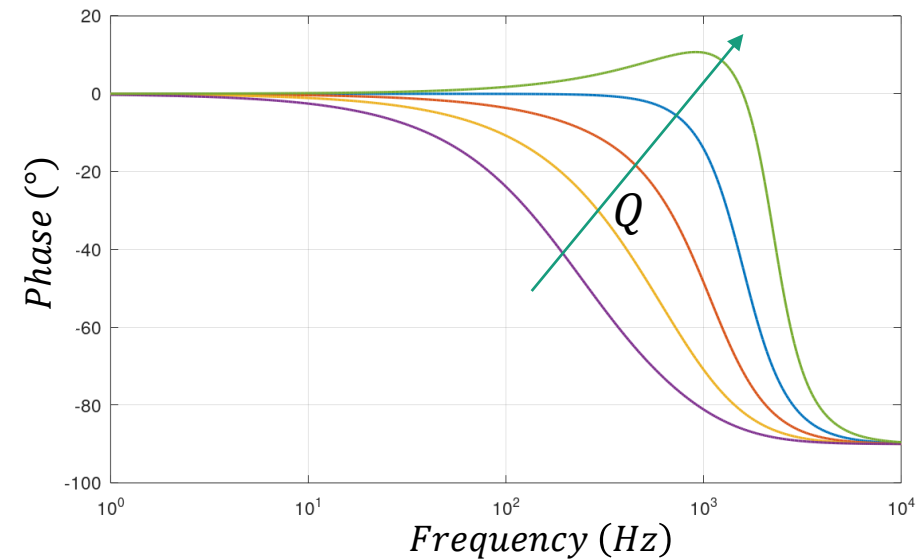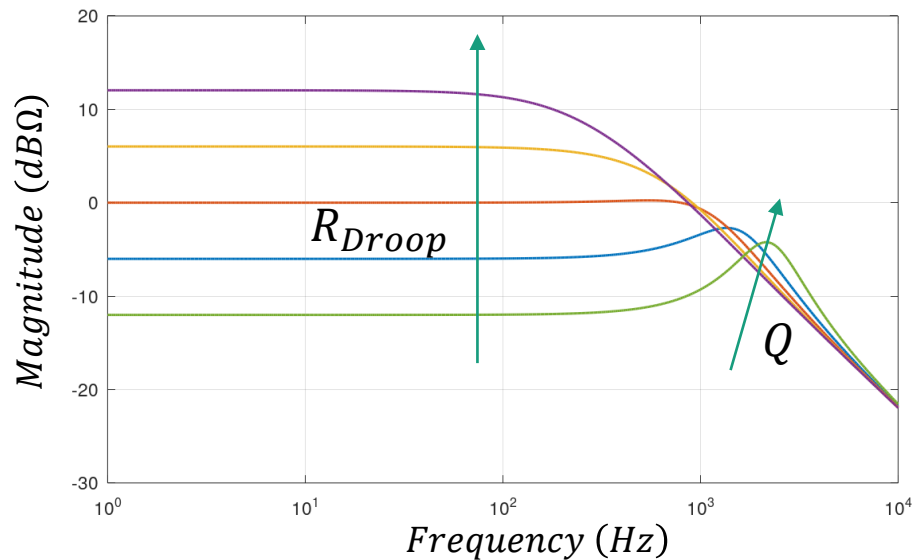■ Resonant circuit has a Quality factor $Q = \frac{1}{R_{Droop}} \sqrt{\frac{L_{LP}}{C_O}} \sim \frac{1}{\sqrt{R_{Droop}}}$




Agenda

- *Introduction to the DC-Microgrid*
- *Opportunities for Impedance Measurements in DC-Microgrids*
- *Droop-Controlled DC-Microgrids*
- ***Stability Investigation through Impedance Measurements***
- *Bode 100 Testbench*
 - *Output-impedance of a constant-current source*
 - *Output-impedance of a constant-voltage source*
 - *Output-impedance of a droop-controlled converter*
 - *Input-impedance of a constant-power load*
- *Online Measurement with Pseudo-Random-Binary-Sequences*
- *Advanced Data Analytics for Grid Layout and Stability Optimization*
- *Stabilization of DC Networks Applying Artificial Intelligence*
- *Summary*

Stability Investigation through Impedance Measurements

Stability Criteria


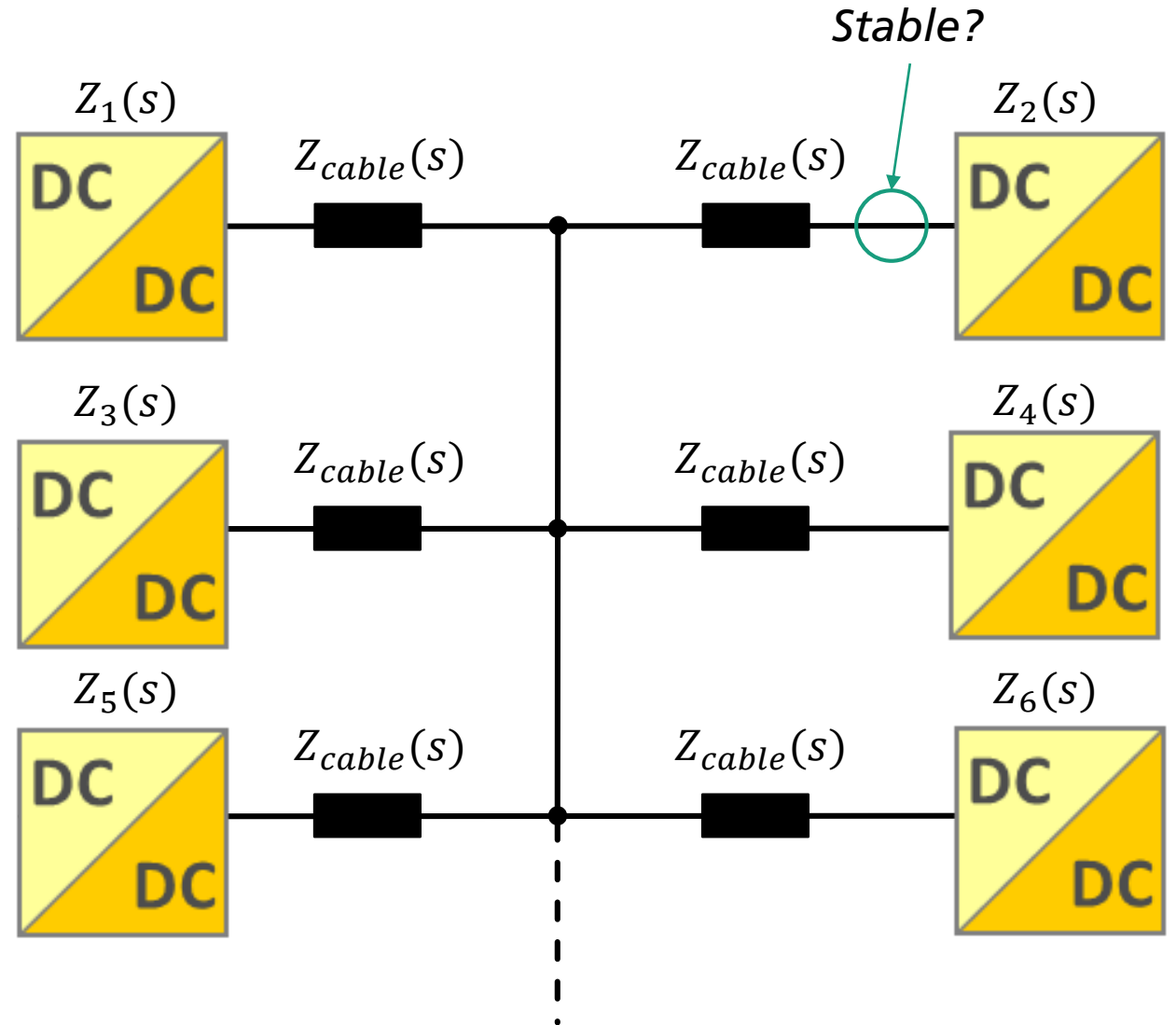
- **Passivity Criterion**
- **Minor Loop Gain Criterion**
 - Middlebrook Criterion
 - **Gain-Margin-Phase-Margin**
 - Opposing Argument Criterion
 - ESAC Criterion
 - RESC Criterion
 - ...



Stability Investigation through Impedance Measurements


■ Passivity Criterion

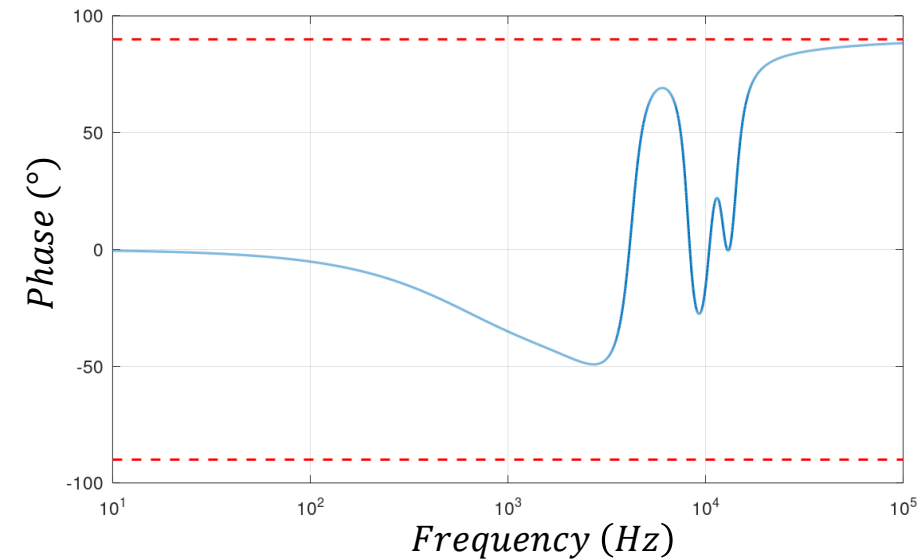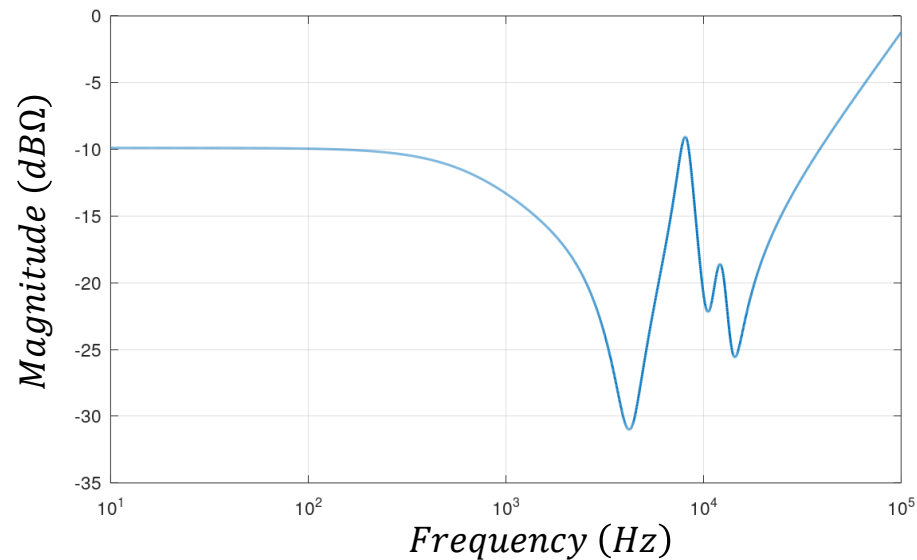- A passive system must have no RHP-poles
- The phase φ of a passive system must be $-90^\circ \leq \varphi \leq 90^\circ$
- Can be used for design of a converter or the whole system



Stability Investigation through Impedance Measurements

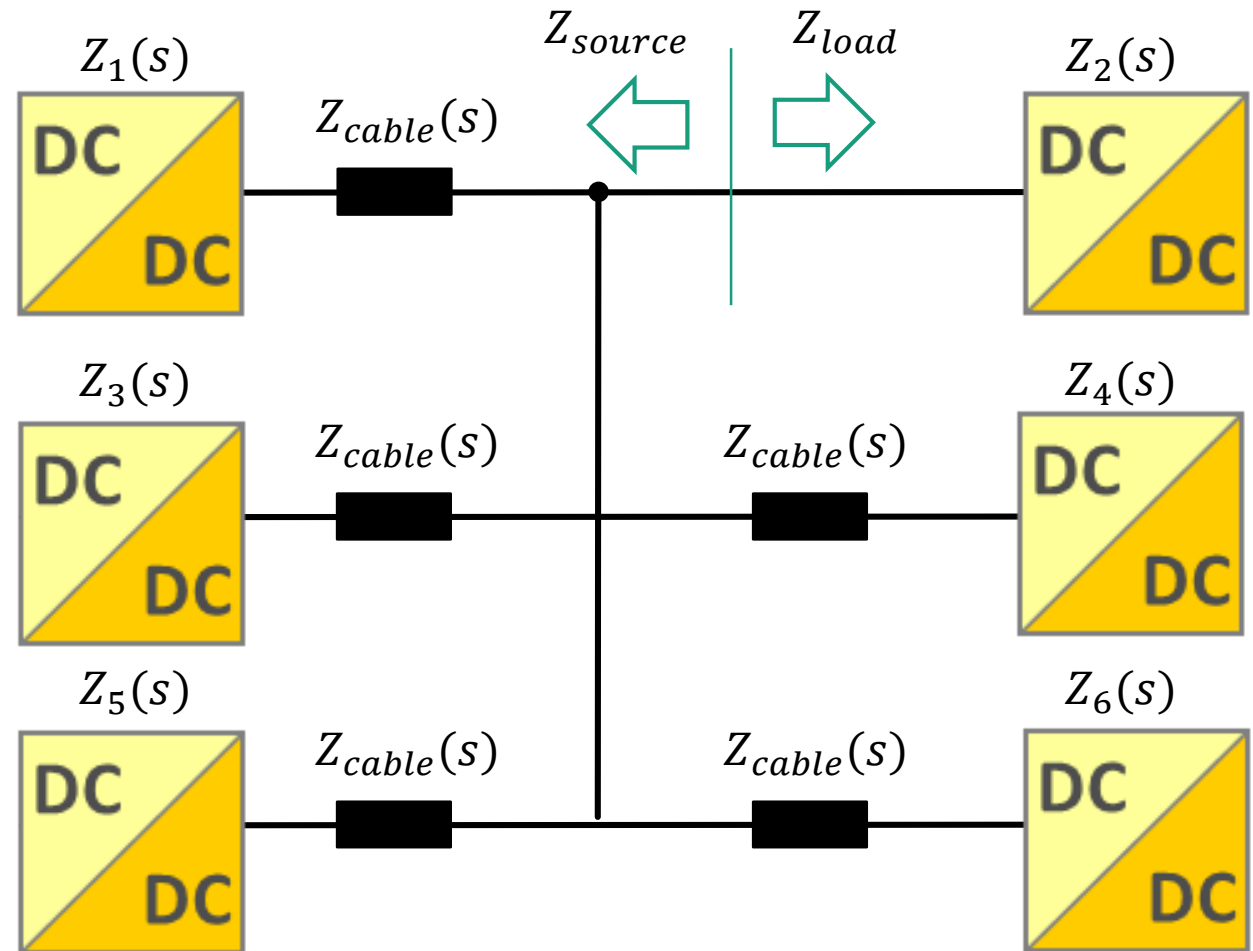- **Minor Loop Gain Criterion**
 - Take an initially stable grid
 - Add a new load converter
 - Measure Z_{source} and Z_{load}
 - We apply a MLGC
 - Repeat for every new load



Stability Investigation through Impedance Measurements


■ Gain-Margin-Phase-Margin

- To form the whole grid Z_{source} and Z_{load} are paralleled

- $$Z_{Grid} = \frac{Z_{source} \cdot Z_{load}}{Z_{source} + Z_{load}} = \frac{Z_{source}}{1 + \frac{Z_{source}}{Z_{load}}}$$

- Z_{source} is stable

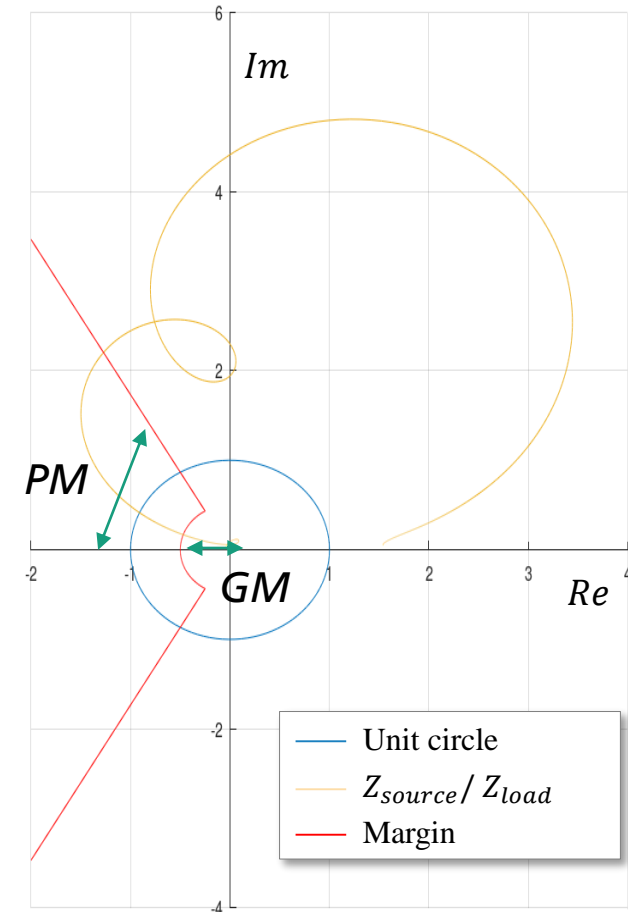- $1 + \frac{Z_{source}}{Z_{load}}$ must not destabilize





Frequency (Hz)

Stability Investigation through Impedance Measurements

■ Gain-Margin-Phase-Margin (GM-PM)

- Compare both Z_{source} and Z_{load}
- For each frequency one of two conditions must apply
 - $|Z_{source}| \cdot GM \leq |Z_{load}|$
 - $\arg(Z_{source}) - (180^\circ - PM) \leq \arg(Z_{source}) \leq \arg(Z_{source}) + (180^\circ - PM)$

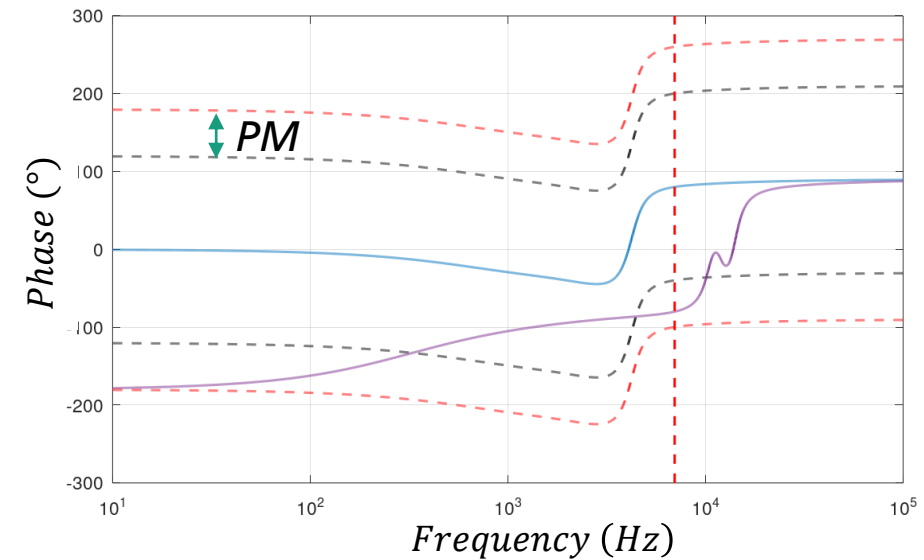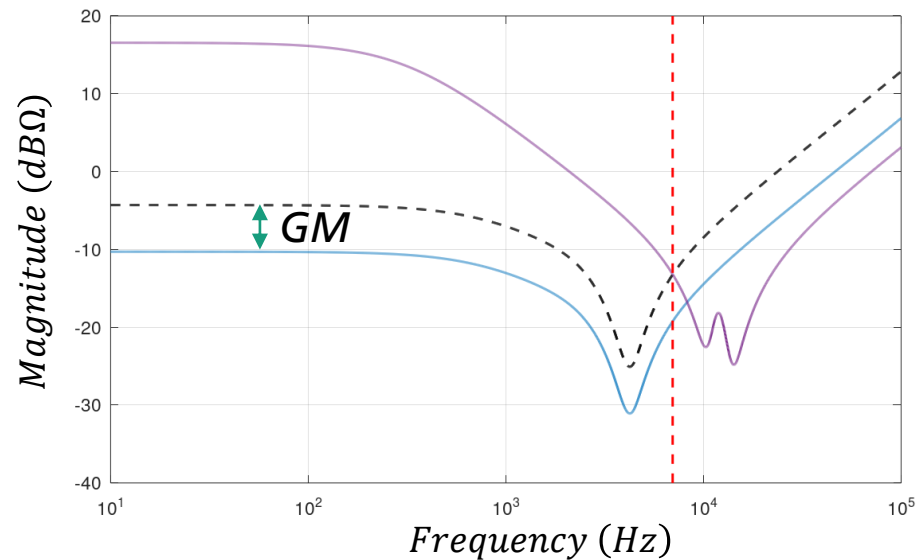

Agenda

- *Introduction to the DC-Microgrid*
- *Opportunities for Impedance Measurements in DC-Microgrids*
- *Droop-Controlled DC-Microgrids*
- *Stability Investigation through Impedance Measurements*
- *Bode 100 Testbench*
 - *Output-impedance of a constant-current source*
 - *Output-impedance of a constant-voltage source*
 - *Output-impedance of a droop-controlled converter*
 - *Input-impedance of a constant-power load*
- *Online Measurement with Pseudo-Random-Binary-Sequences*
- *Advanced Data Analytics for Grid Layout and Stability Optimization*
- *Stabilization of DC Networks Applying Artificial Intelligence*
- *Summary*

Bode100 Testbench

■ Bode 100



- Generation of the test signal (max 13dBm)
- Gain-Phase measurement

■ Wide Band Amplifier

- Amplification by 13 dB
- 0.2 Ω output resistance

■ Coupling Transformers

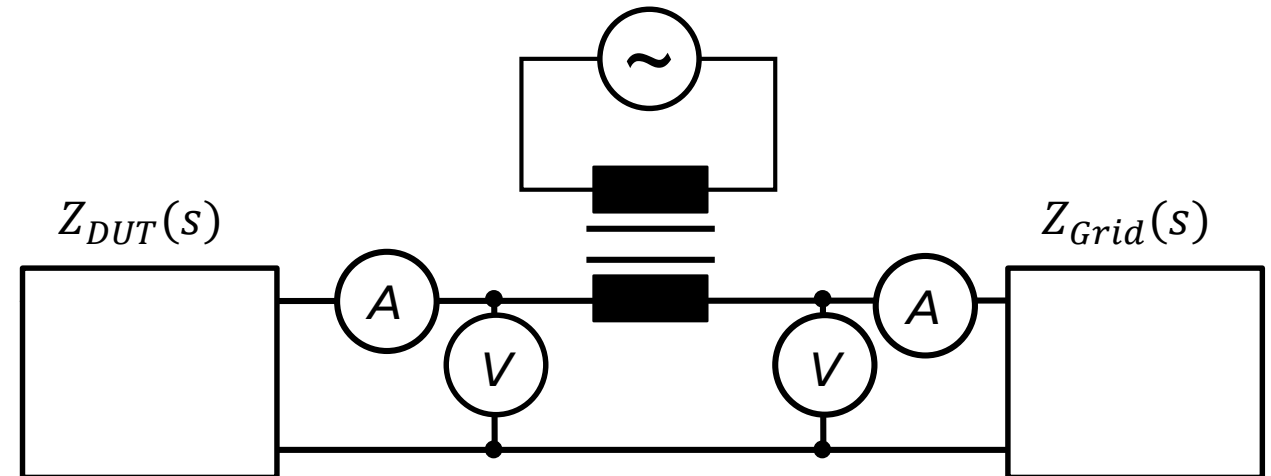
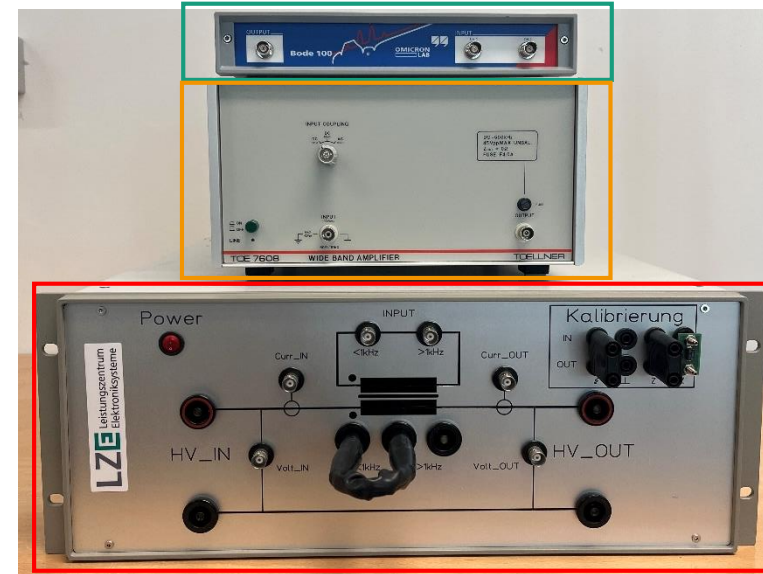
- Isolated coupling
- Isolated measurement
- Maximum DC-current:
 - 25 A for 10 Hz-Transformer
 - 50 A for 100 Hz-Transformer



Bode 100 Testbench


■ Passive converter:

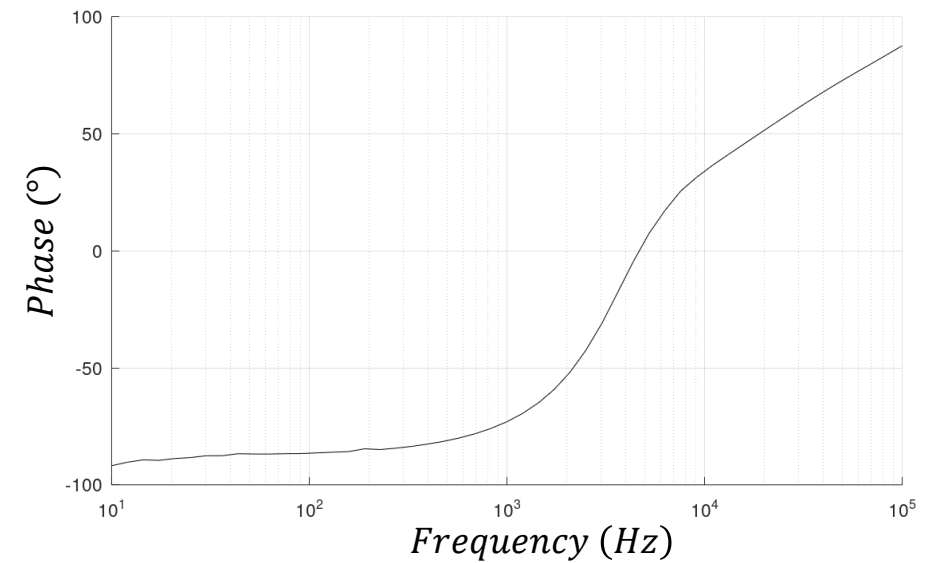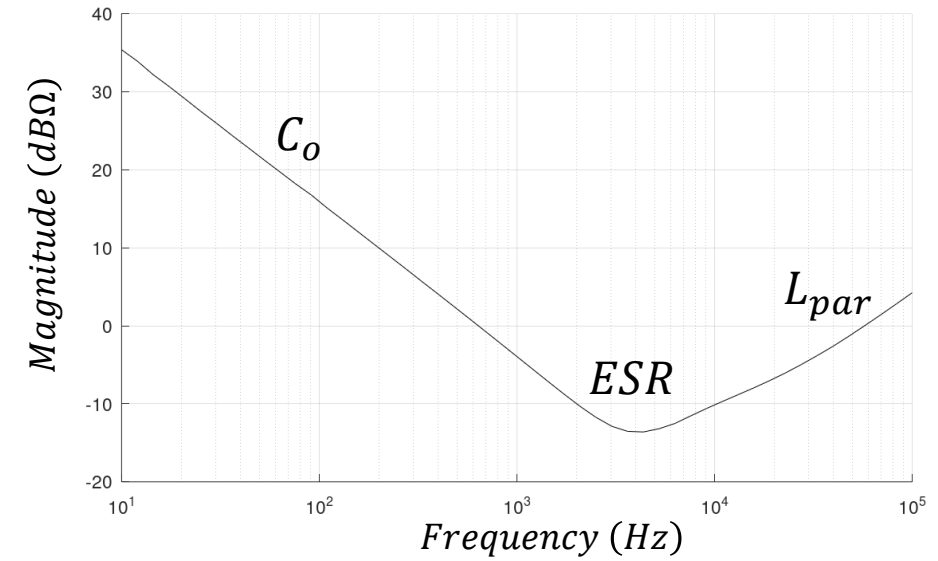- $C_o \approx 260 \mu F$
- $ESR \approx 20 m\Omega$




Bode 100 Testbench

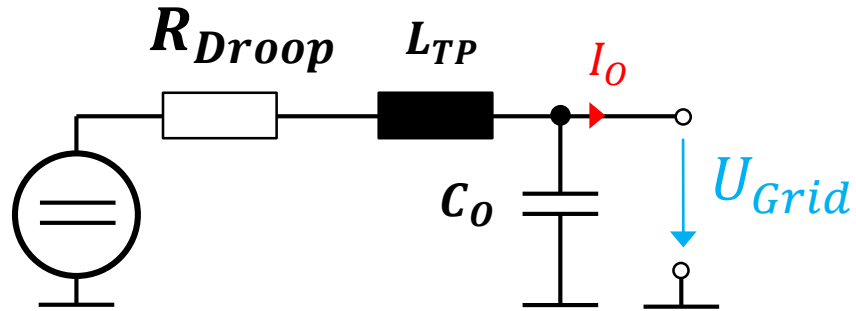- Droop-controlled converter
 - Converter can be modeled as R-L-C





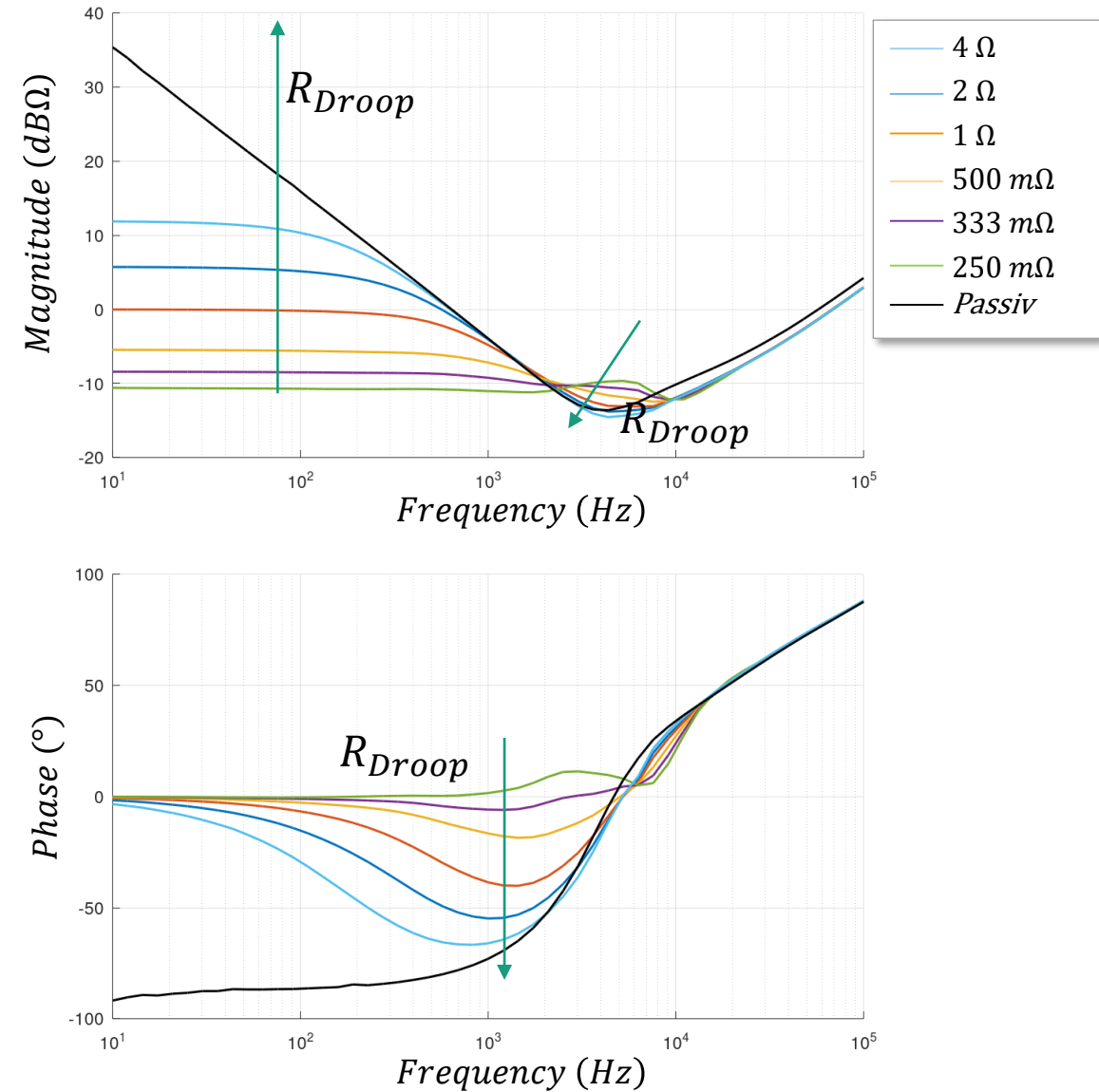- Increase in R_{Droop} leads to:
 - Higher Z at low frequencies
 - Lower Z at „resonance frequency“





Bode 100 Testbench

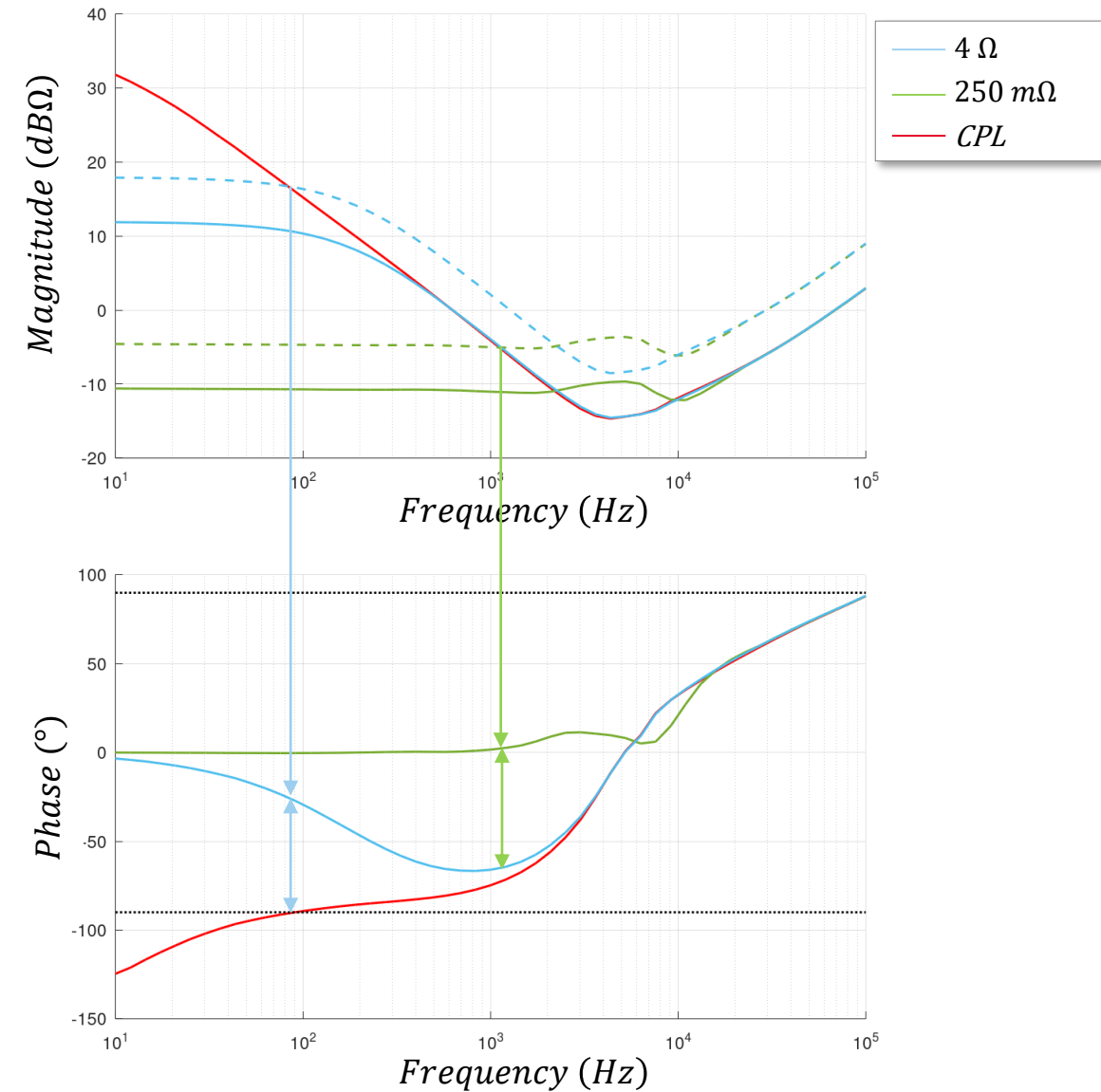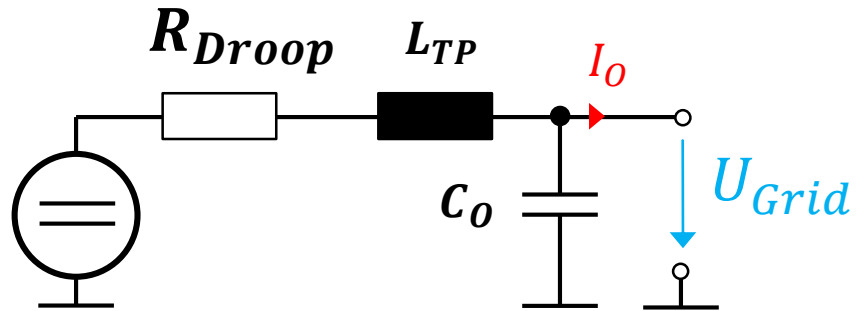- Constant-power load (CPL)
 - Typically high R_{Droop}
 - Violates passivity at low frequencies





Bode 100 Testbench

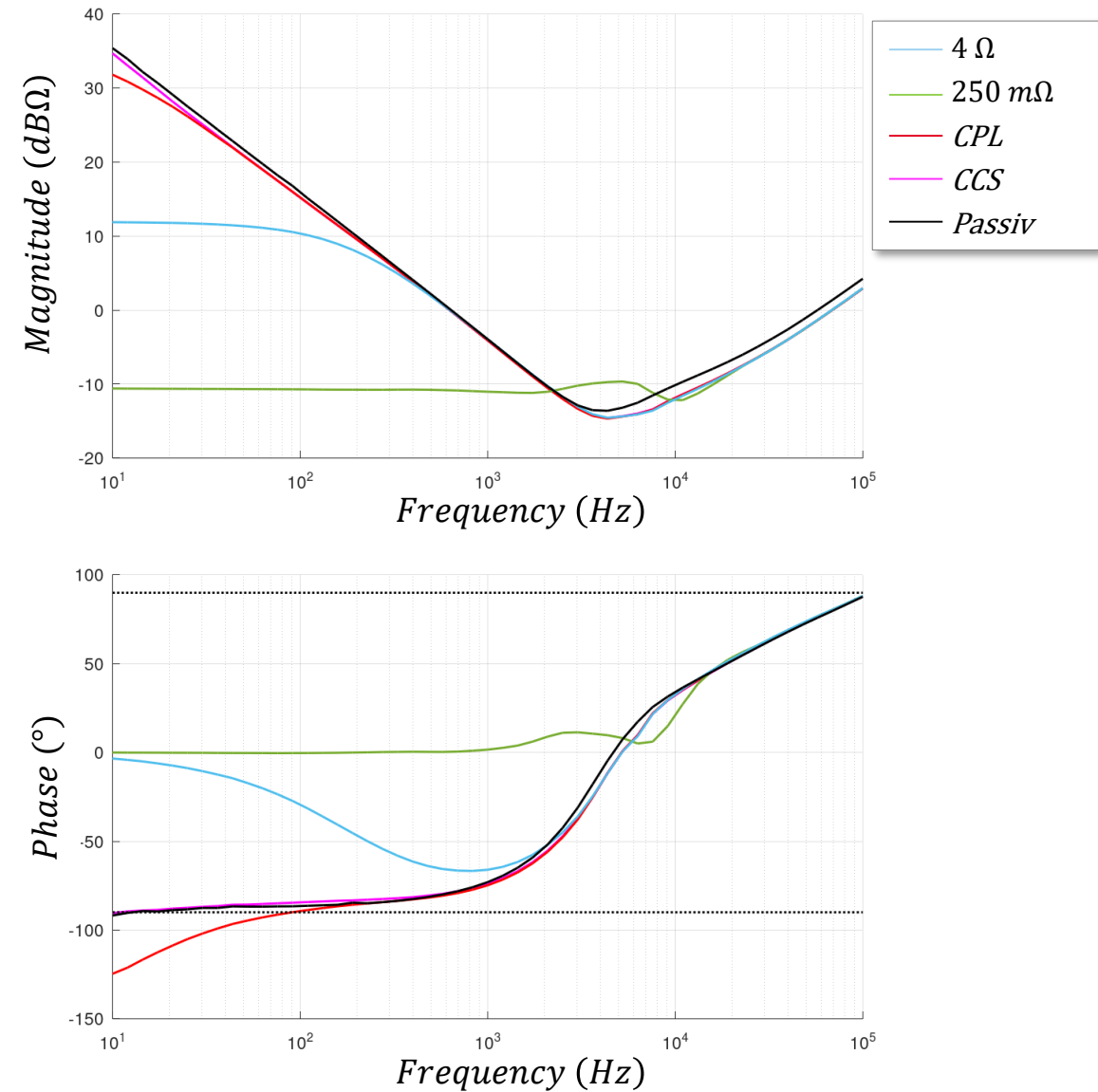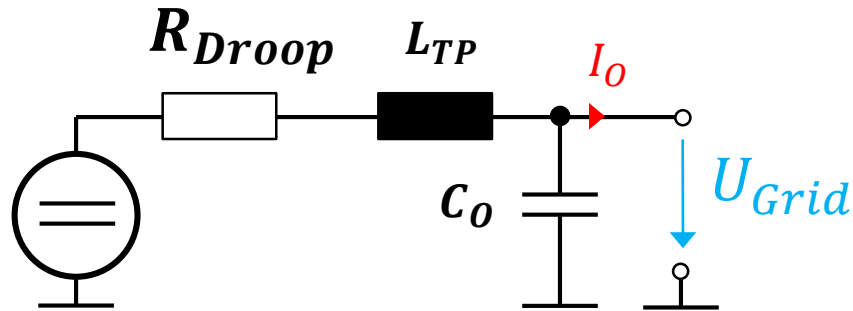- Constant-current source (CCS)
 - Acts like a passive converter ($R_{Droop} = \infty$)
 - Can not stabilize a constant power load



Bode 100 Testbench

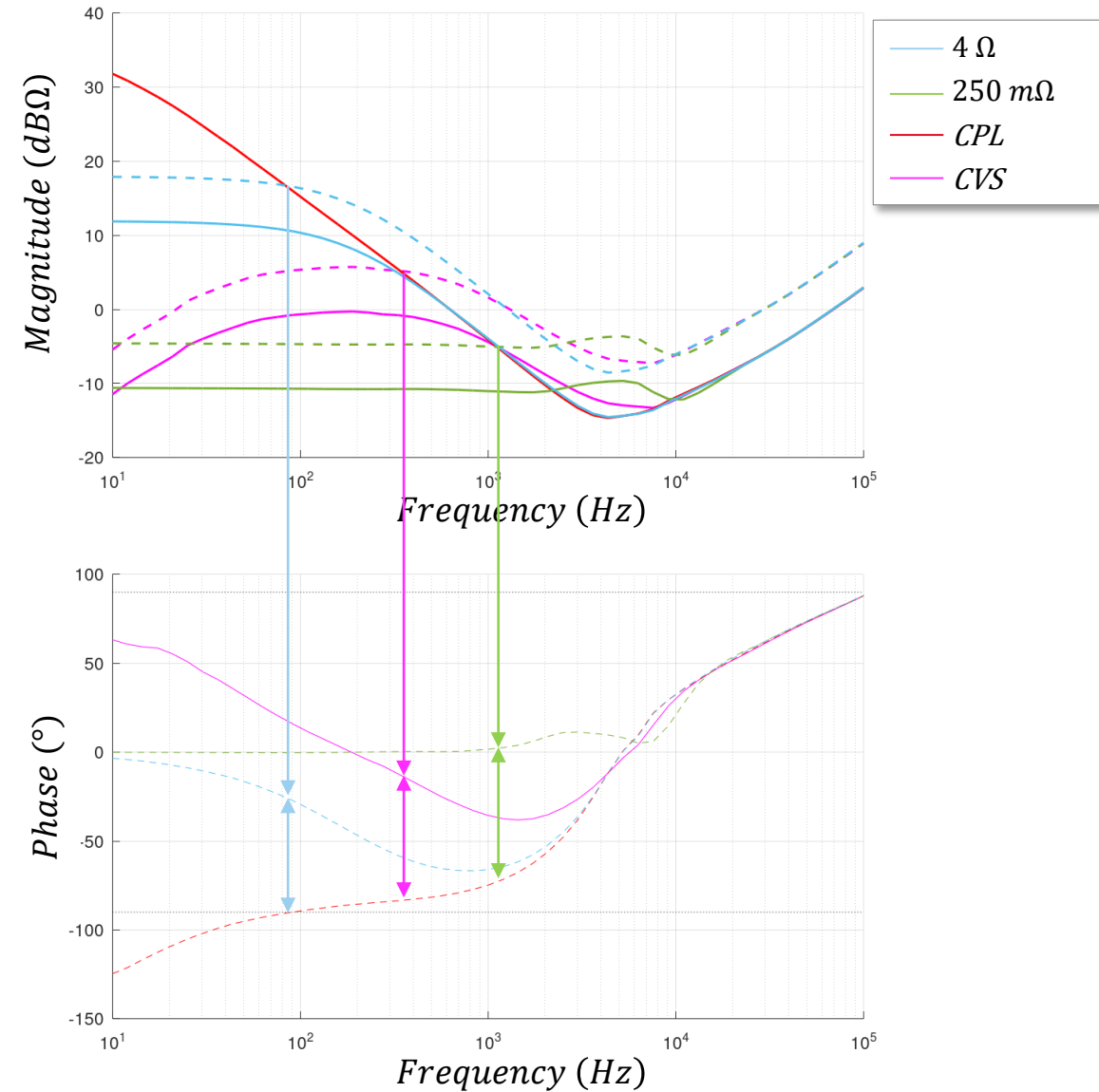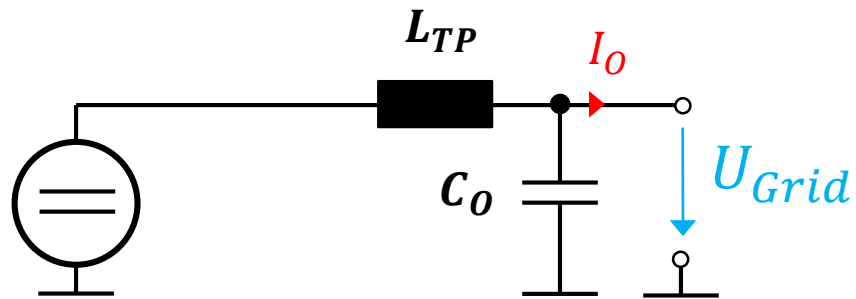- Constant-voltage source (CVS)
- No droop-resistance
- "Resonance" at lower frequencies



Agenda

- *Introduction to the DC-Microgrid*
- *Opportunities for Impedance Measurements in DC-Microgrids*
- *Droop-Controlled DC-Microgrids*
- *Stability Investigation through Impedance Measurements*
- *Bode 100 Testbench*
 - *Output-impedance of a constant-current source*
 - *Output-impedance of a constant-voltage source*
 - *Output-impedance of a droop-controlled converter*
 - *Input-impedance of a constant-power load*
- *Online Measurement with Pseudo-Random-Binary-Sequences*
- *Advanced Data Analytics for Grid Layout and Stability Optimization*
- *Stabilization of DC Networks Applying Artificial Intelligence*
- *Summary*

Online measurement with Pseudo-Random-Binary-Sequences

- *Pseudo-Random-Binary-Sequences (PRBS)*



- *Length L*

- *Bit-Duration τ_B*

- *White noise Approximation*

- $f_{min} = \frac{1}{\tau_B \cdot L} = \Delta f$

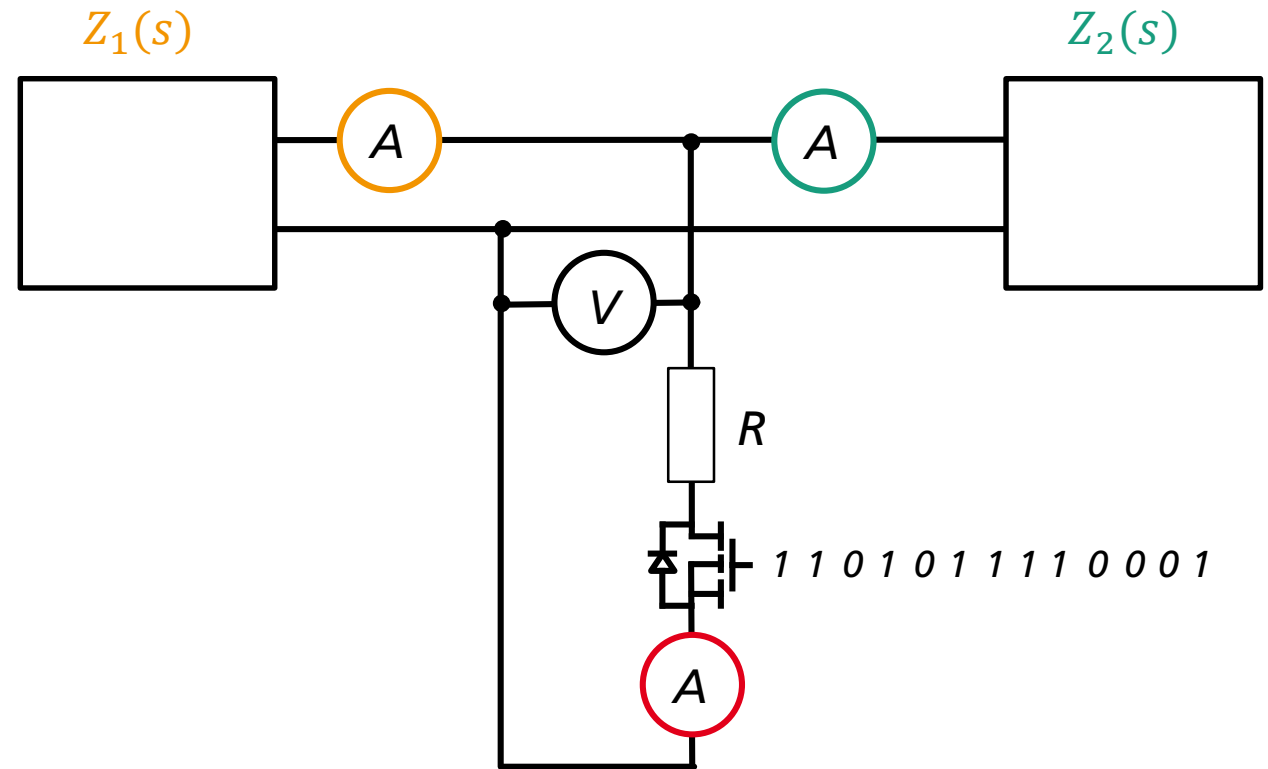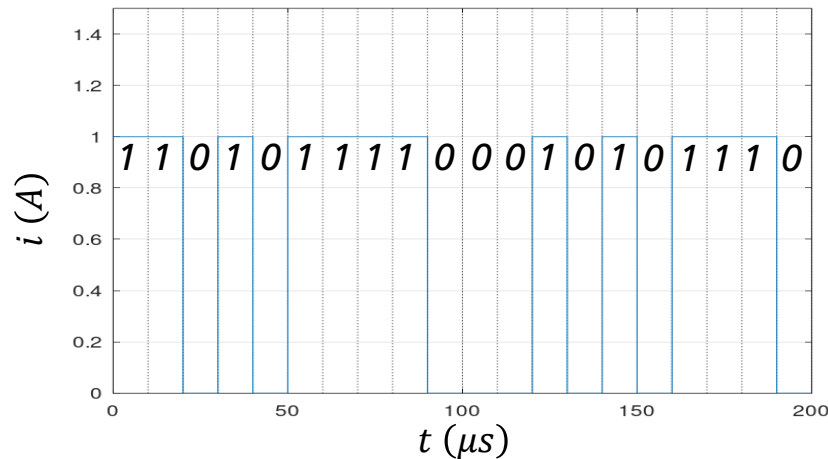- $f_{max} \approx \frac{1}{3 \tau_B} \dots \frac{1}{2 \tau_B}$





Online measurement with Pseudo-Random-Binary-Sequences

■ Pseudo-Random-Binary-Sequences (PRBS)

- Length L
- Bit-Duration τ_B
- White noise Approximation


- $f_{min} = \frac{1}{\tau_B \cdot L} = \Delta f$

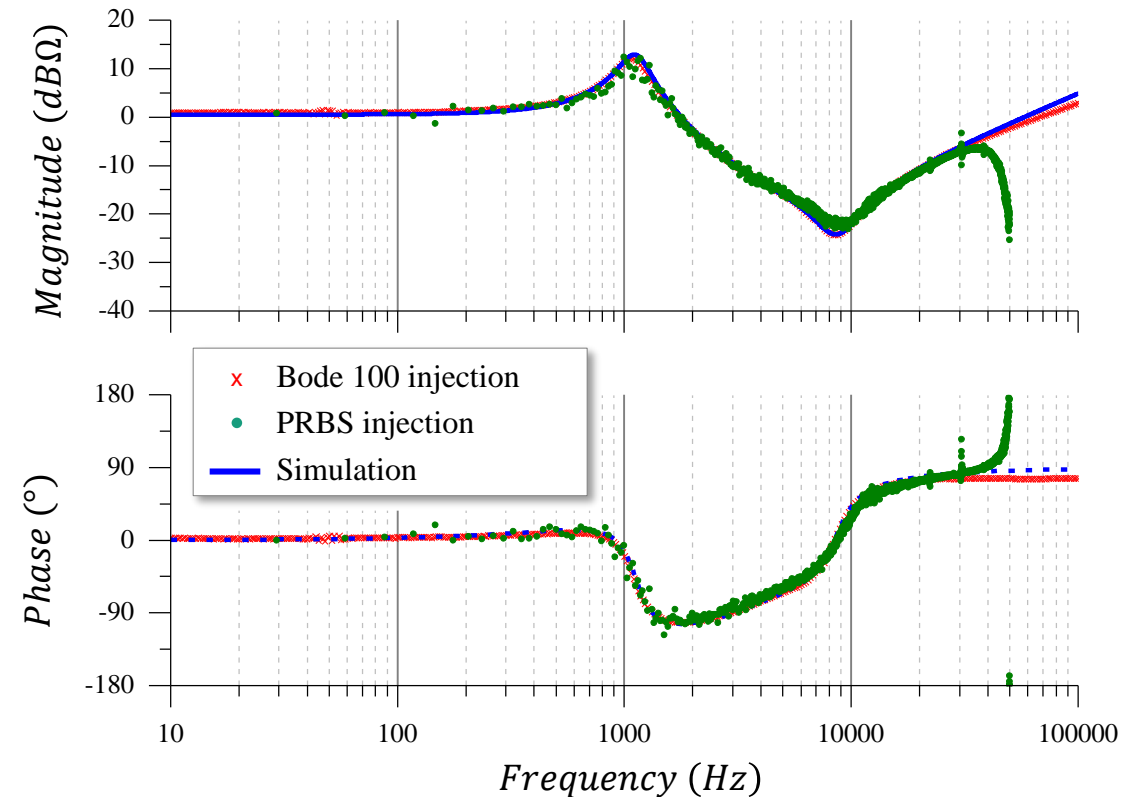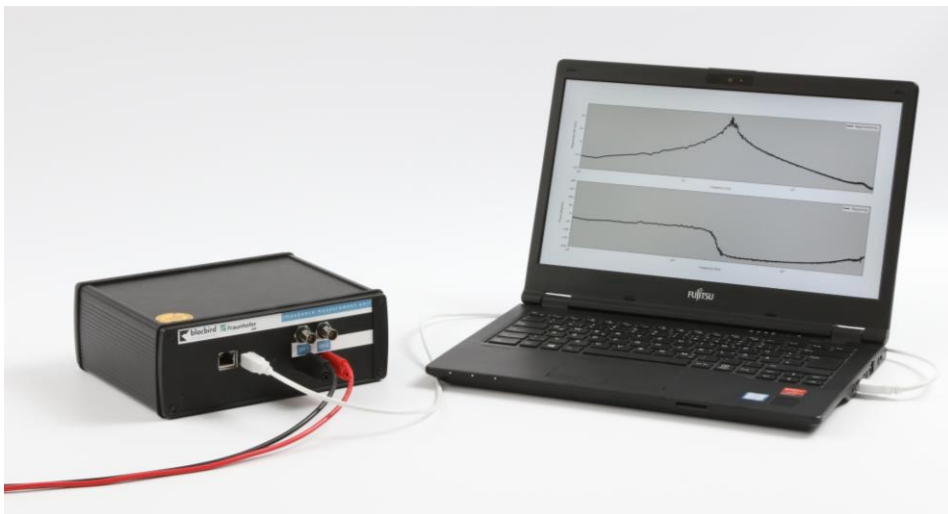- $f_{max} \approx \frac{1}{3 \tau_B} \cdots \frac{1}{2 \tau_B}$




Advanced Data Analytics for Grid Layout and Stability Optimization


Setup of the Example DC Network

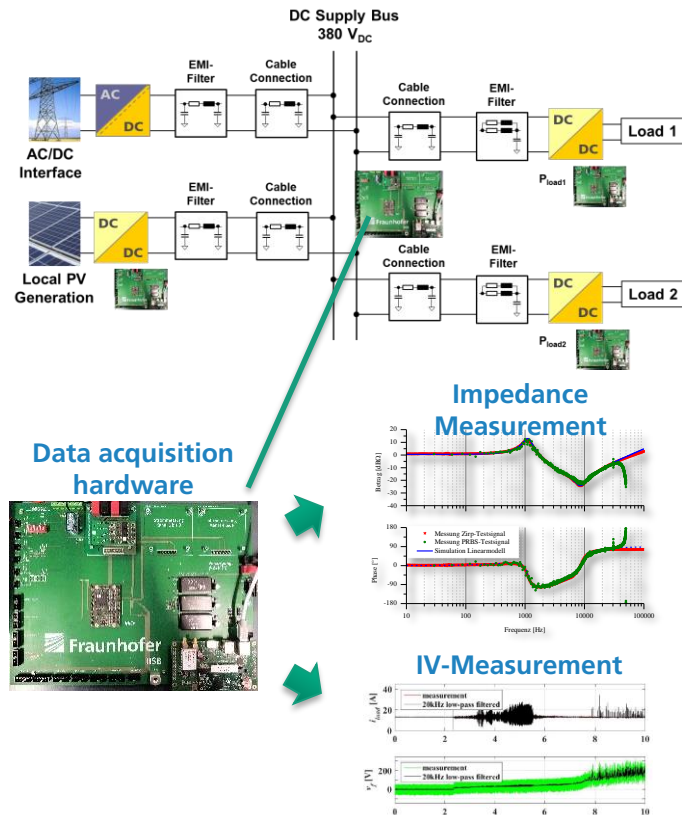

AI Use Cases

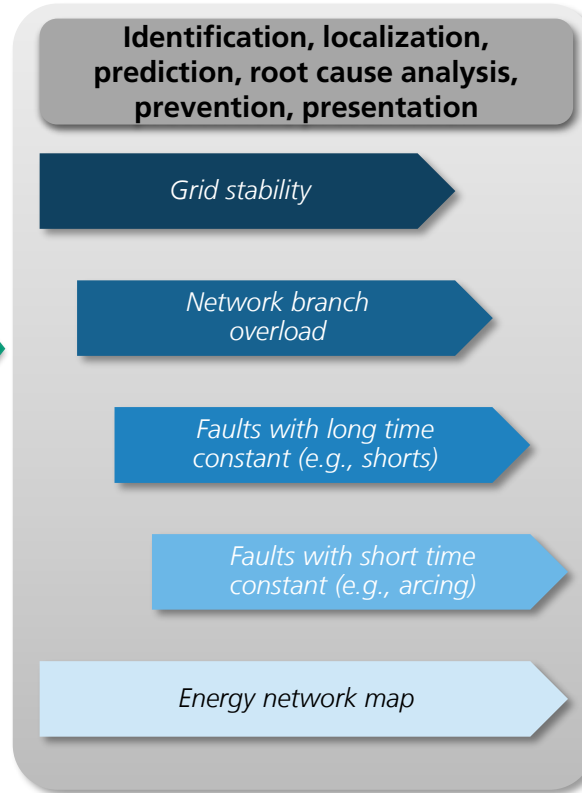


Applications and Benefits

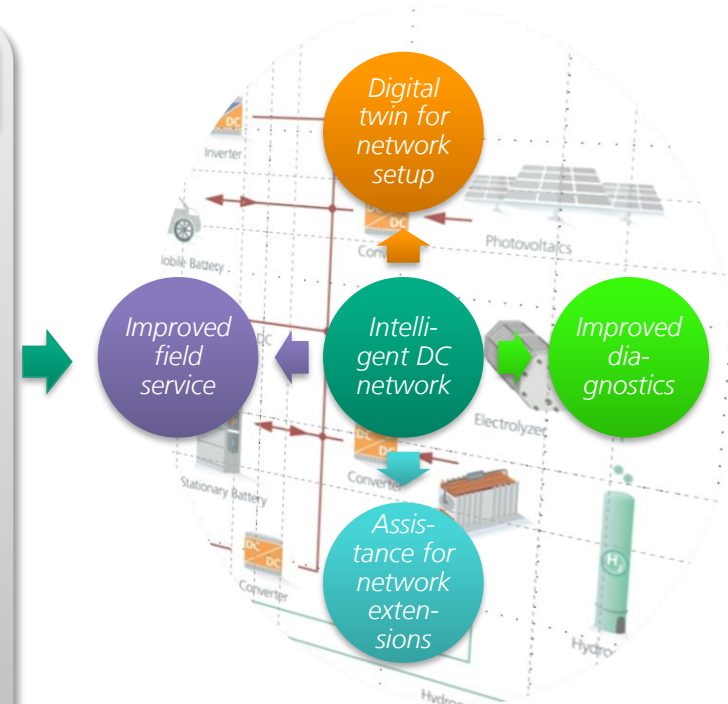


Acknowledgments: This work was supported by the Bavarian Ministry of Economic Affairs, Regional Development and Energy through the Center for Analytics – Data – Applications (ADA-Center) within the framework of „BAYERN DIGITAL II“ (20-3410-2-9-8)

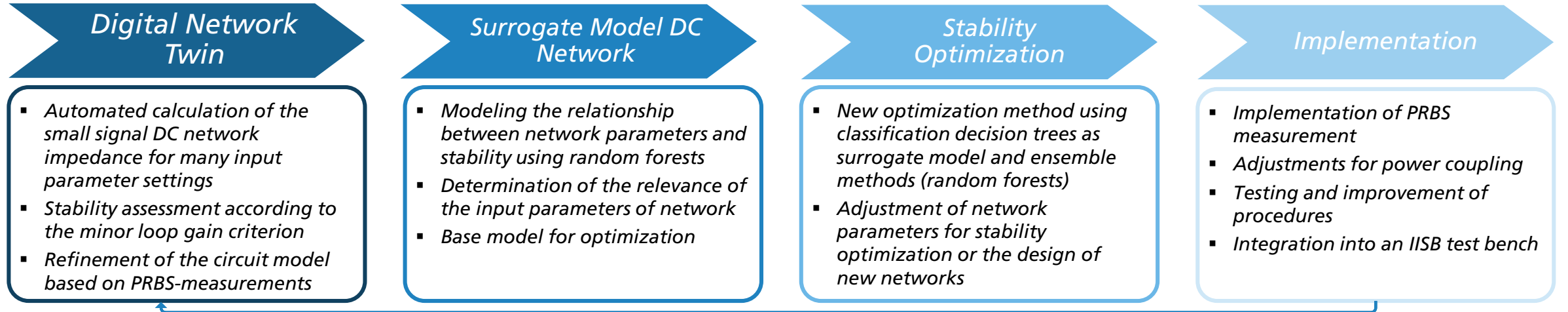
Stabilization of DC Networks Applying Artificial Intelligence




SPICE Model

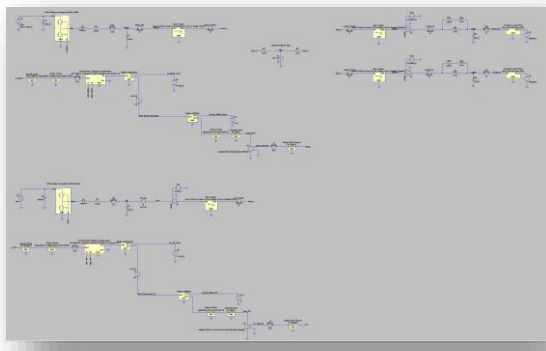

Random Forest Model

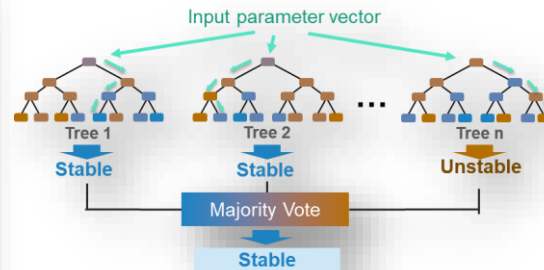

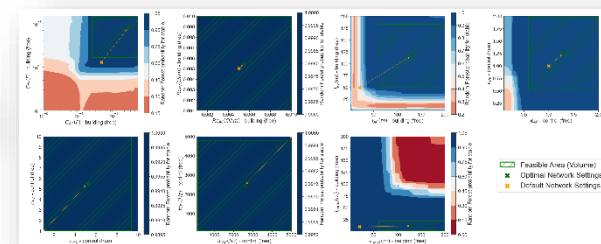New Optimization Algorithm for Classification Models



Test Bench



Summary

- *DC-Microgrids*
 - *Power electronics dominated*
 - *Droop-controlled*
 - *Decentral load sharing*
- *Droop-Control*
 - *Current controlled converter*
 - *Droop curves can be linear or nonlinear*
 - *Constant-power converters have negative droop resistances*
- *Stability*
 - *Passivity-Criterion*
 - *MLGC-Criterion*
- *Bode 100 Testbench*
 - *Bode 100*
 - *Wide band amplifier*
 - *Coupling transformer*
- *PRBS*
 - *Injection of bit streams*
 - *Multiple frequencies in one measurement*
- *Data-Analytics & AI*
 - *Digital Twin*
 - *Stability optimization*
 - *Intelligent DC-Microgrid*