



PSRR – Why Measure It, the Measurement Errors and How to Correct Them

Steven M. Sandler - Picotest

12th Power Analysis & Design Symposium 2023 (VIRTUAL)
March 15, 2023


Submitted Abstract

Modern distributed systems are noise sensitive. Power rail noise is one of the most significant sources of jitter in high-speed systems, phase noise in RF systems, and noise in A/D and D/A converters. Recommendations abound, from adding ferrite beads and ceramic caps, to LDOs to clean the power supply rails. The most basic of measurements is the frequency domain PSRR measurement. Many manufacturers include data for their components, but in the system, they act very differently than they do in isolation. Measuring PSRR challenges the best of test engineers' ability, making us question even the manufacturers' data. This presentation discusses the major PSRR measurement errors and how to correct them. That's the key to getting accurate PSRR results.

Why Measure PSRR?



Even Tiny Noise Gets Into Sensitive Circuits

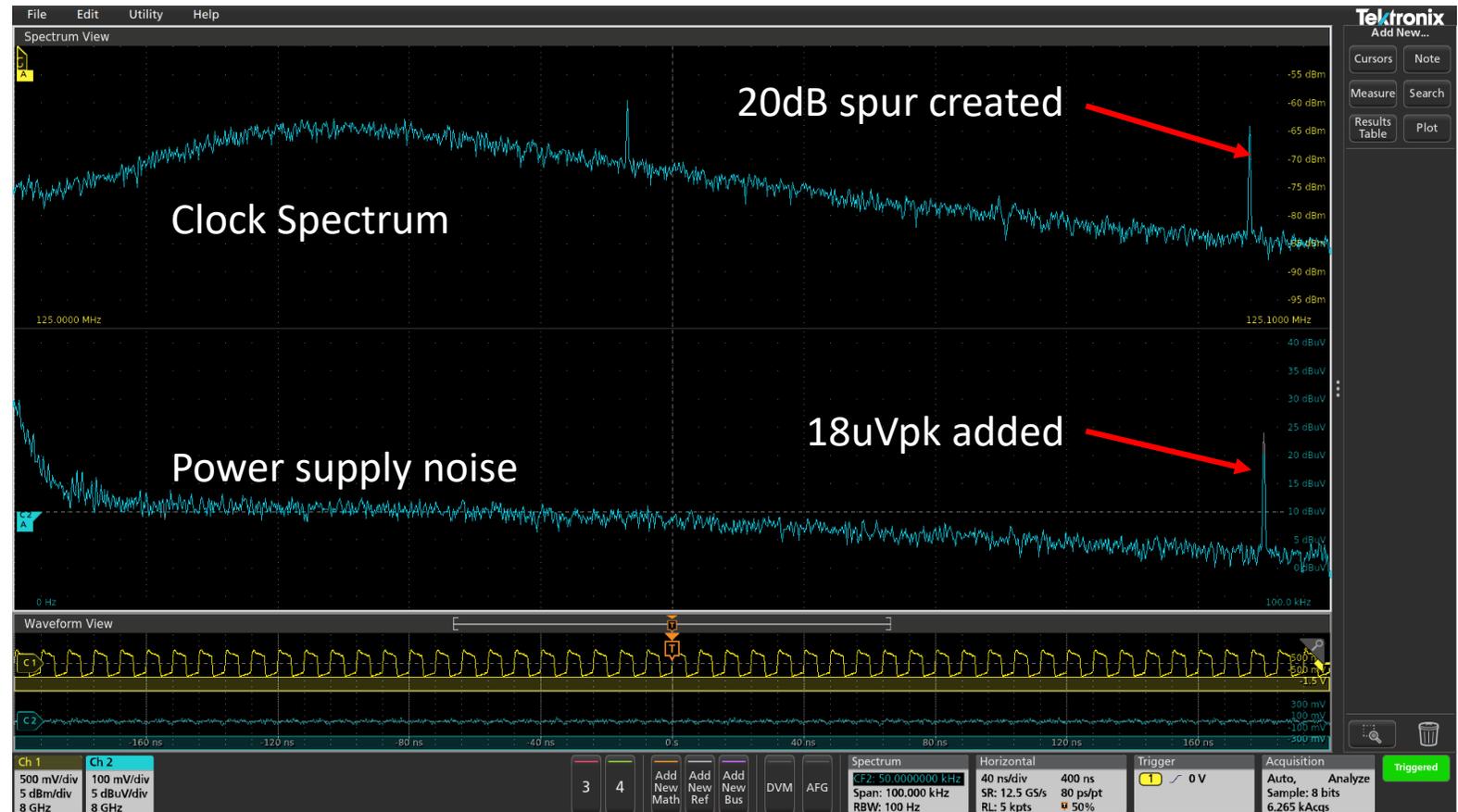One common method of assessing the phase noise - jitter relationship is through the Power Supply Modulation Ratio (PSMR) test, where this sensitivity is measured at many frequencies and a noise mask is developed to verify the system level performance



Measuring the Direct Impact on Phase Noise

Jitter
 1.528 ps
 6.603 ps
 21.968 ps

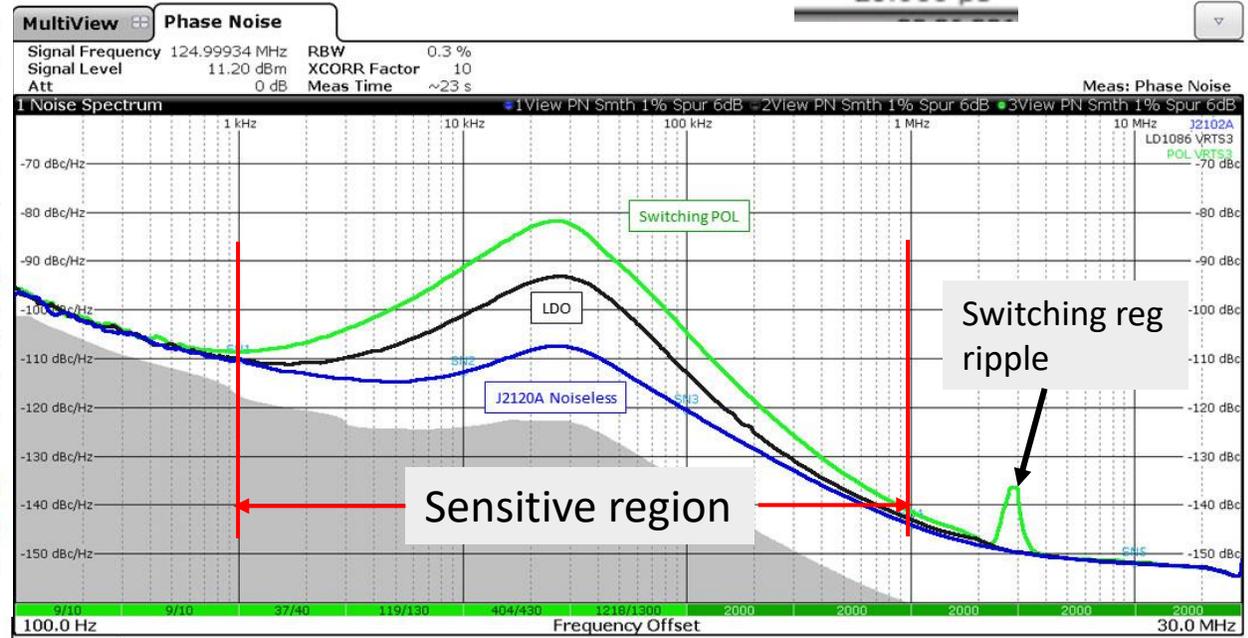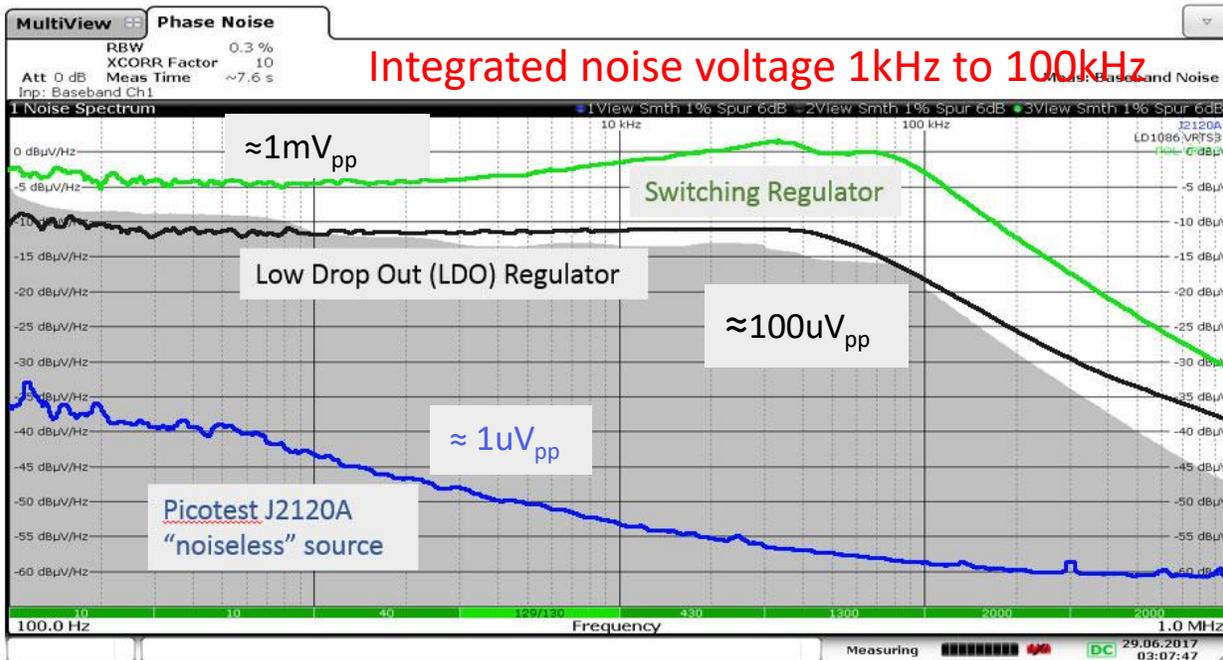

2 Integrated Measurements

Range	Trace	Start Offset	Stop Offset	Weighting	Int Noise	PM	FM	Jitter
1	1	100.000 Hz	30.000 MHz		-61.43 dBc	68.76 m°/1.20 mrad	2.832 kHz	1.528 ps
2	2	100.000 Hz	30.000 MHz		-48.71 dBc	297.12 m°/5.19 mrad	2.905 kHz	6.603 ps
3	3	100.000 Hz	30.000 MHz		-38.27 dBc	988.54 m°/17.25 mrad	2.964 kHz	21.968 ps

Date: 29 JUN.2017 03:07:47

Date: 29 JUN.2017 03:47:07

Reducing It to a Simpler Form

Table 2: Recommended Operating Conditions⁽¹⁾⁽²⁾ (Cont'd)


Symbol	Description	Min	Typ	Max	Units	
V _{CCBATT} ⁽¹¹⁾	Battery voltage	1.0	–	1.89	V	
GTX and GTH Transceivers						
V _{MGTAVCC} ⁽¹²⁾	Analog supply voltage for the GTX/GTH transceiver QPLL frequency range ≤ 10.3125 GHz ⁽¹³⁾⁽¹⁴⁾	0.97	1.0	1.08	V	110mVpp
	Analog supply voltage for the GTX/GTH transceiver QPLL frequency range > 10.3125 GHz	1.02	1.05	1.08	V	30mVpp
V _{MGTAVTT} ⁽¹²⁾	Analog supply voltage for the GTX/GTH transmitter and receiver termination circuits	1.17	1.2	1.23	V	30mVpp
V _{MGTVCCAUX} ⁽¹²⁾	Auxiliary analog Quad PLL (QPLL) voltage supply for the transceivers	1.75	1.80	1.85	V	50mVpp
V _{MGTAVTTRCAL} ⁽¹²⁾	Analog supply voltage for the resistor calibration circuit of the GTX/GTH transceiver column	1.17	1.2	1.23	V	30mVpp

As the amplitude of the noise should be limited to less than 10 mVpp, the power supply filter should be designed to attenuate the noise from the switching regulator to meet this requirement

https://support.xilinx.com/s/question/0D54U00005VU9noSAD/power-supply-for-mgt-groups-of-virtex-7-fpga-xc7vx690tffg19272?language=en_US


System “Components” Also Effect PSRR

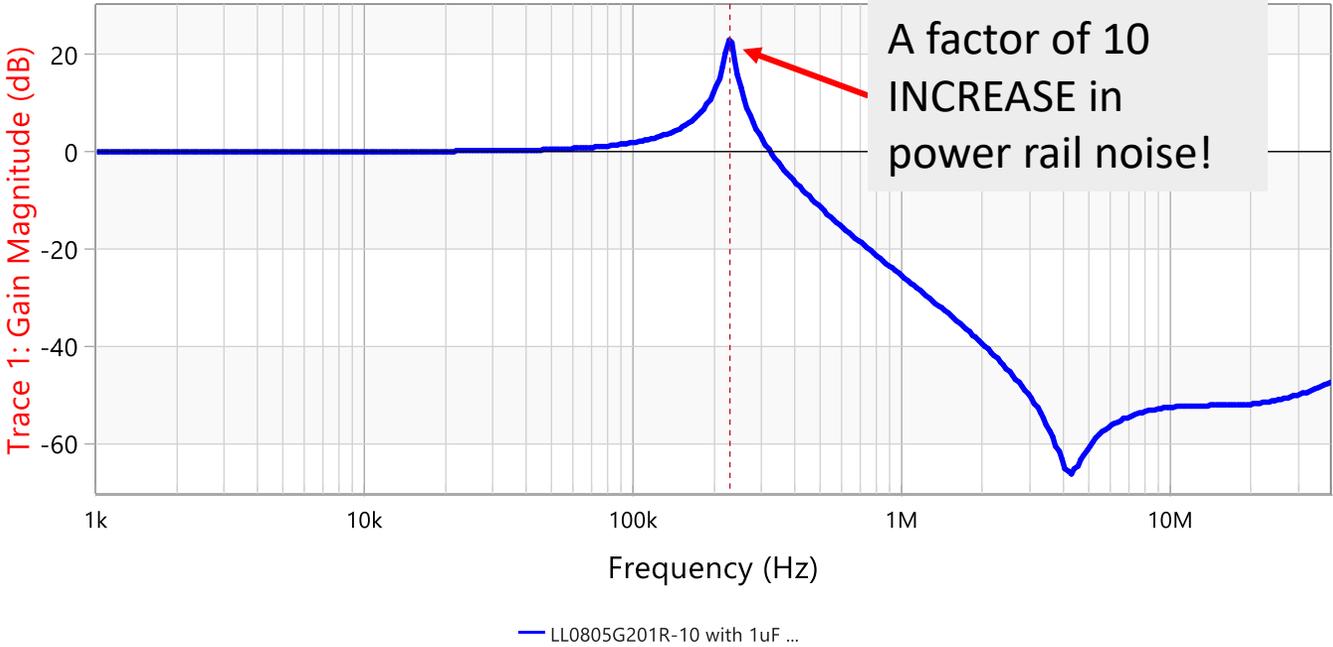Ferrite Bead “Attenuation”- Not Everywhere!



Florian Hämmerle showed the effects of a ferrite bead in a USB oscilloscope during OMICRON Lab Symposium 7

PSRR vs Phase Margin

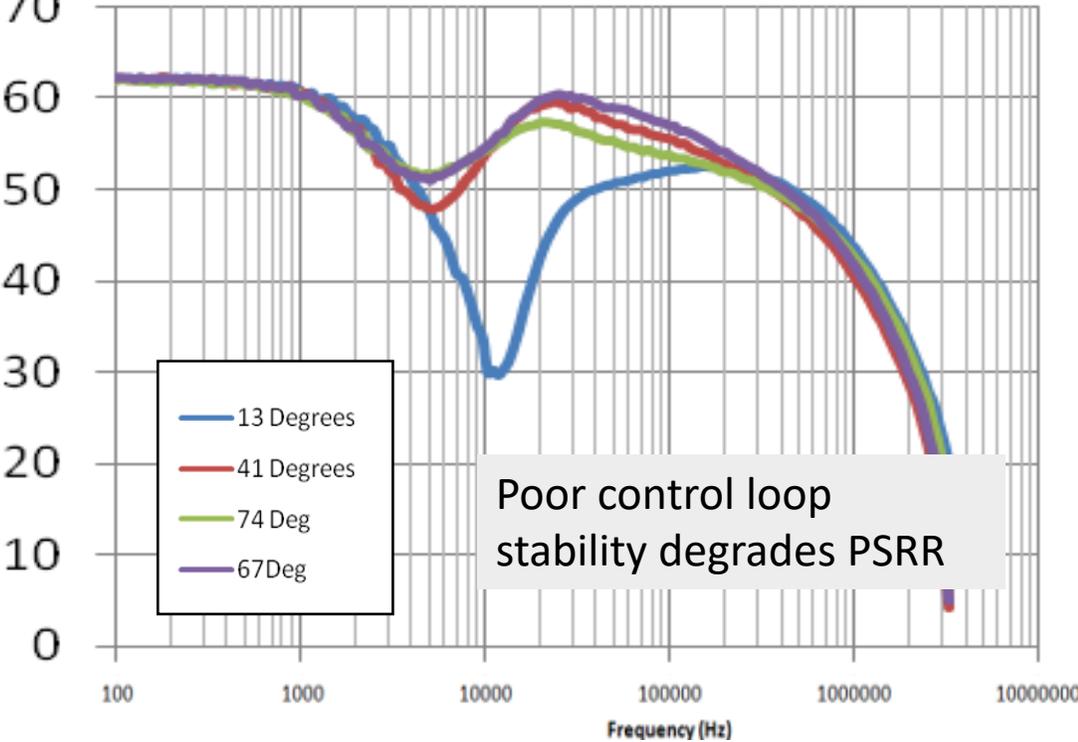

And Even Slope Compensation Impacts PSRR


In my presentation "Measurement-based Modelling and Simulation of DC-DC Converters" at Electronica 2018, I showed the impact of current mode control slope compensation on PSRR

Clearly, PSRR is an important consideration as it impacts the load, and it's impacted by many parameters by the voltage regulator, the PCB components, and the sensitivity of the load

This is why it is so important for us to measure it, preferably in-system, at the system level

PARAMETER SWEEP
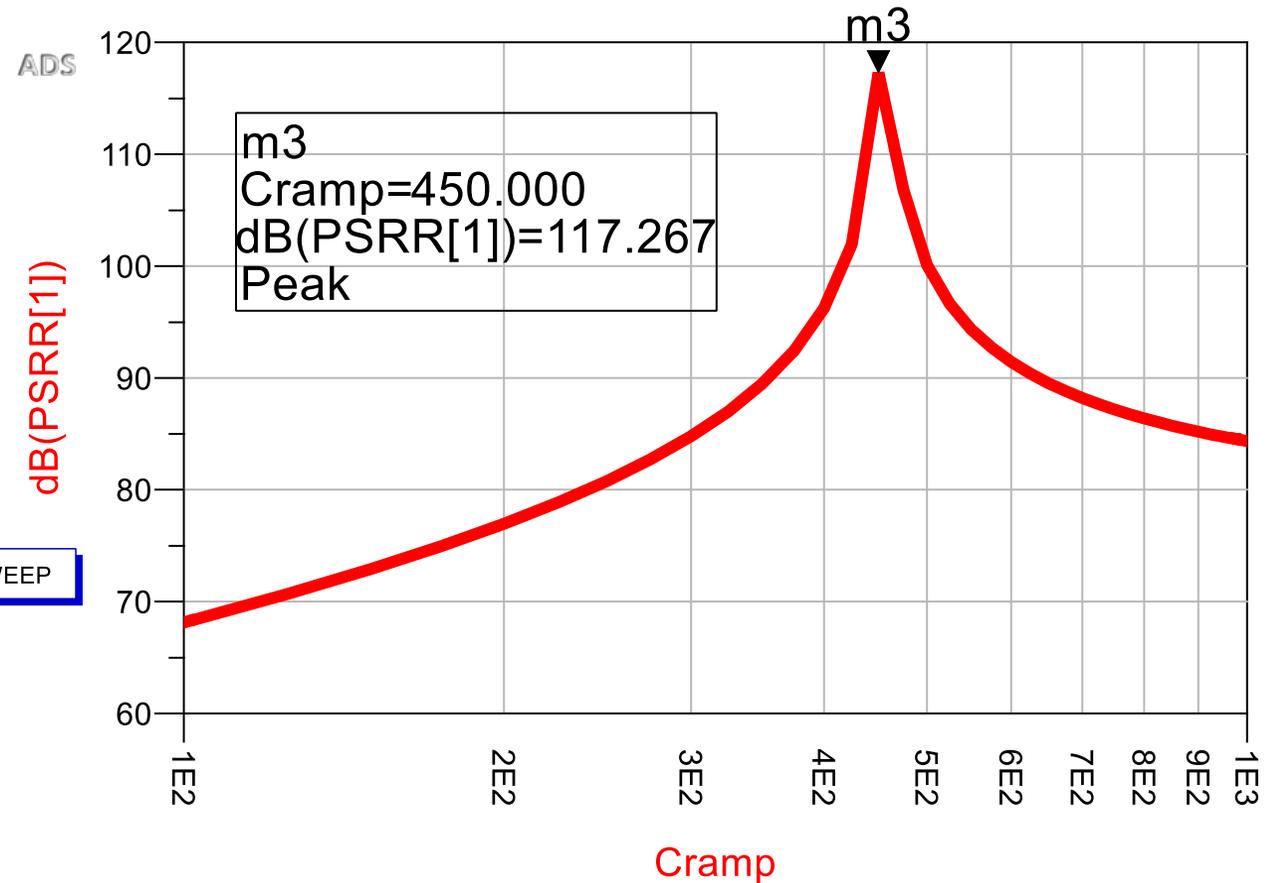
```
ParamSweep
Sweep1
SweepVar="Cramp"
SimInstanceName[1]="AC1"
SimInstanceName[2]=
SimInstanceName[3]=
SimInstanceName[4]=
SimInstanceName[5]=
SimInstanceName[6]=
Start=100
Stop=1000
Step=25
```




It's Abundantly Clear Why We Must Measure PSRR

- Many loads are extremely sensitive to power supply noise. Increased power rail noise can cause Bit Error Rate failures due to phase noise/jitter
- Filters comprised of ferrite beads and ceramic capacitors are often recommended, but these WILL significantly INCREASE noise if not properly damped
- VRM control loop stability can be degraded by the PCB effects and decoupling capacitors. This can degrade PSRR, resulting in higher noise
- Slope compensation of switching regulator also impacts PSRR and so can be optimized for the best PSRR

<https://www.signalintegrityjournal.com/articles/573-designing-power-for-sensitive-circuits>

The PSRR Measurement Setup


Inject noise here

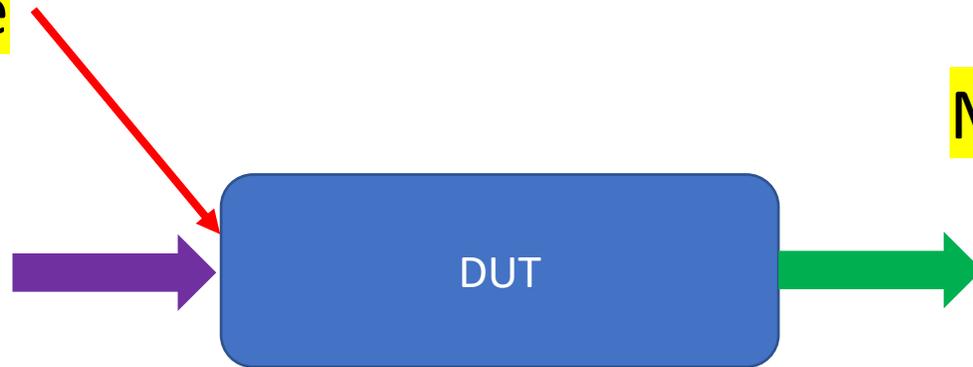

Measure performance here


Noise Injection Methods

Bias Tee

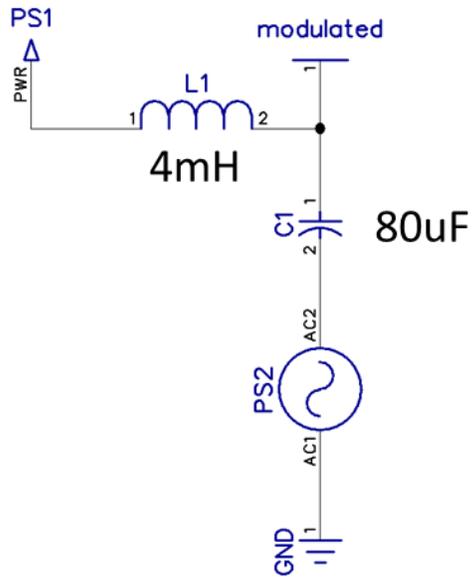


Very poor bandwidth
Really small signals

Power Amp

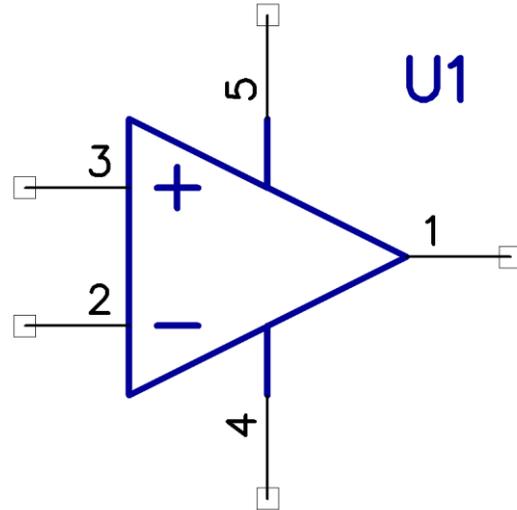


Poor bandwidth
Stability issues
Low power

Line Injector
(open loop summer)

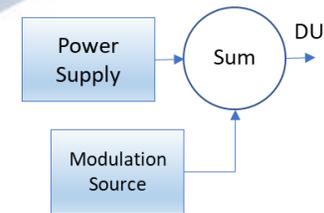


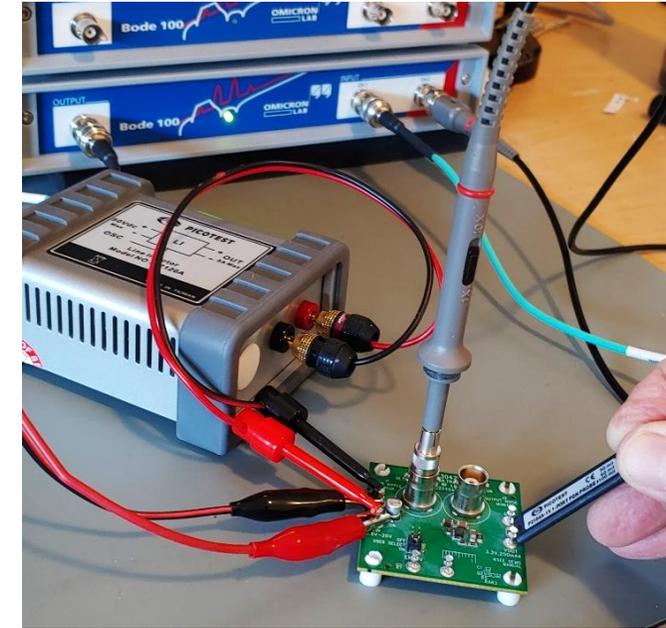Wide Bandwidth
No loop – no stability issue
Low power to high power
Variable voltage drop (remote sense filter)



The power supply modulation setup is the same for PSRR, PSMR, and PSNR

The PSRR Test

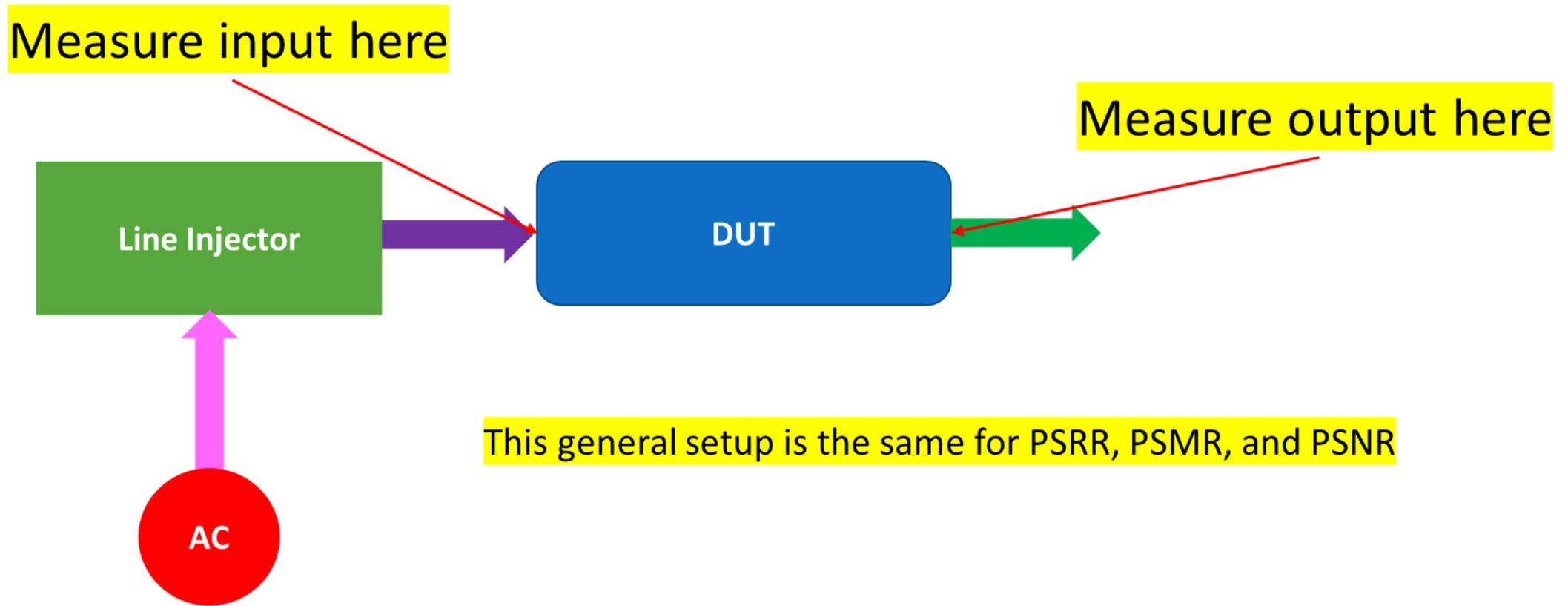


Measuring a 100dB Attenuator

Before measuring something that you don't know, measure something you DO know


With uV sensitivities required by sensitive circuits, many new high performance Linear Regulators and LDOs can provide 100dB PSRR

At low frequency, the error is 694% but it corrects itself at higher frequency

WHY???

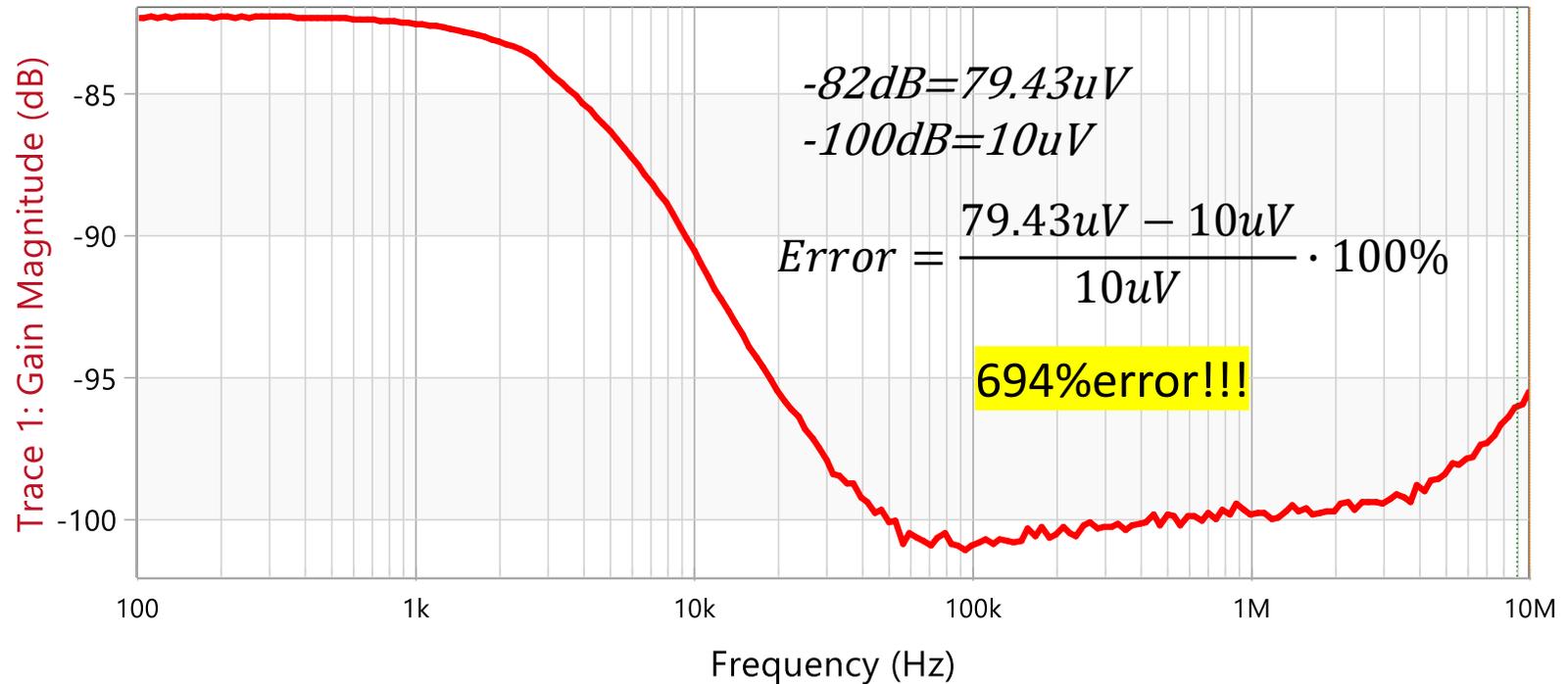

This Isn't as Easy as It Looks!

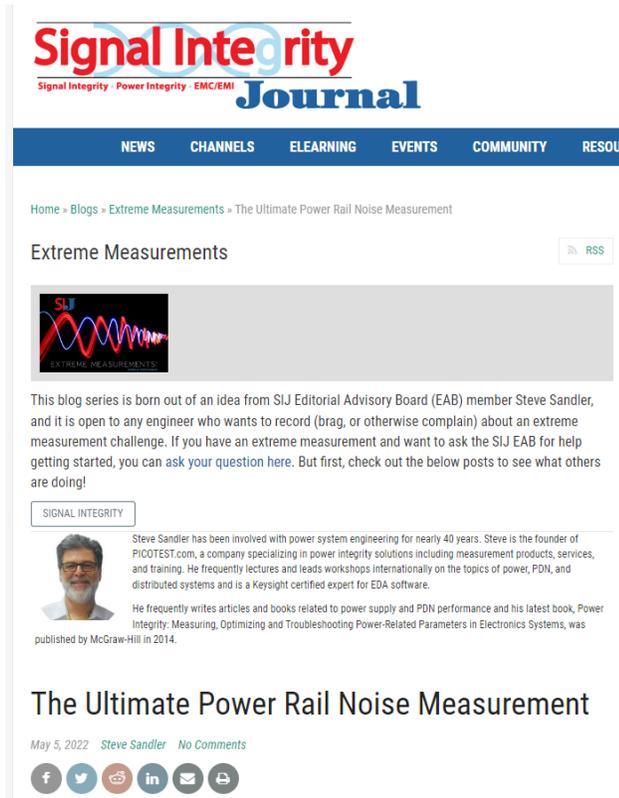

The screenshot shows the Signal Integrity Journal website. The header includes the journal's name and navigation links for News, Channels, Elearning, Events, Community, and Resources. The main content area features a blog post titled "The Ultimate Power Rail Noise Measurement" by Steve Sandler, dated May 5, 2022. The post includes a small image of a waveform and a bio for Steve Sandler, who is the founder of Picotest.com and a Keysight certified expert for EDA software.

- The output signals can be really tiny (like micro-Volts)
- Measured in one instrument? Ground loop error
- Differential probe? Too noisy
- Injecting high frequency?
- Interconnects in the way




[This Photo](#) by Unknown Author is licensed under [CC BY-SA](#)

<https://www.signalintegrityjournal.com/blogs/15-extreme-measurements/post/2484-the-ultimate-power-rail-noise-measurement>


What Causes the Error??

The AC modulation current flows through the resistance of both cable shields, providing a shield voltage (similar to ground bounce)
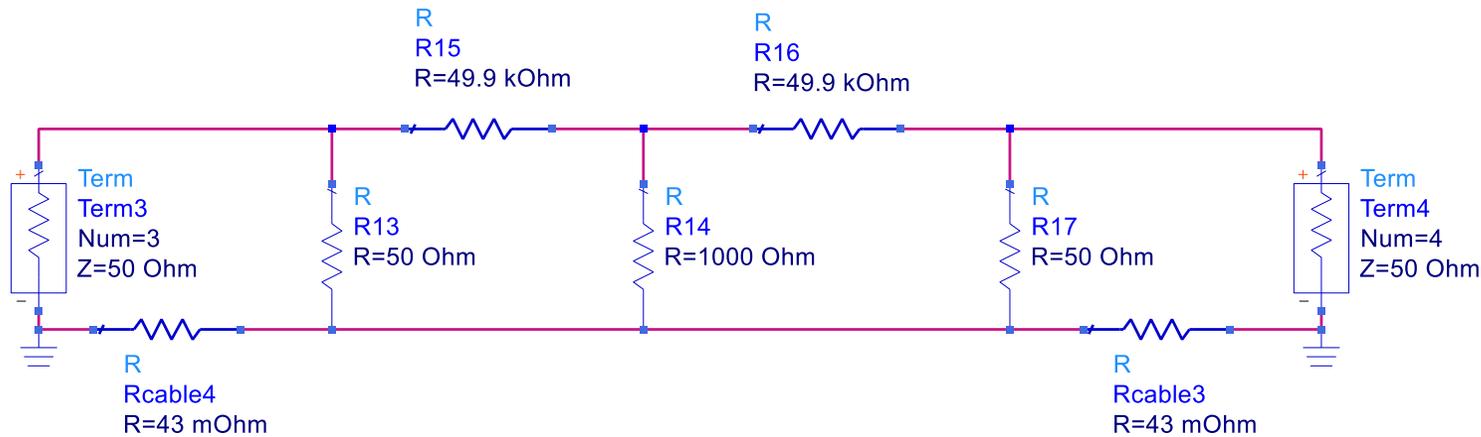
<https://www.picotest.com/measurements/2-port.html>



Include the cable shield resistance

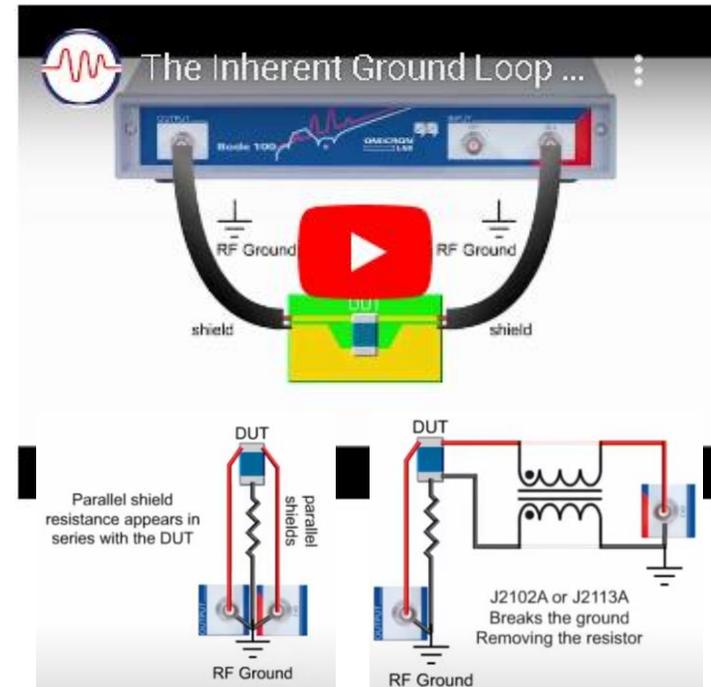

There Ya Go

Vin := 2
 Rsource := 50
 R_atten_in := 49.9

Rshield1 := 0.0001
 Rshield2 := 0.0001

Atten := 100000
 Atten_dB := 20·log(Atten) = 100

The voltage across the shield is:

$$V_{shield} := \frac{V_{in} \cdot \frac{R_{shield1} \cdot R_{shield2}}{R_{shield1} + R_{shield2}}}{R_{source} + R_{atten_in} + \frac{R_{shield1} \cdot R_{shield2}}{R_{shield1} + R_{shield2}}}$$


$$V_{shield} = 1.001 \times 10^{-6}$$

$$V_{atten_in} := \frac{V_{in} \cdot R_{atten_in}}{R_{source} + R_{atten_in} + \frac{R_{shield1} \cdot R_{shield2}}{R_{shield1} + R_{shield2}}}$$

$$V_{atten_in} = 9.99 \times 10^{-1}$$

$$V_{out} := \frac{V_{atten_in} \cdot 2}{Atten} + V_{shield} = 2.098 \times 10^{-5}$$
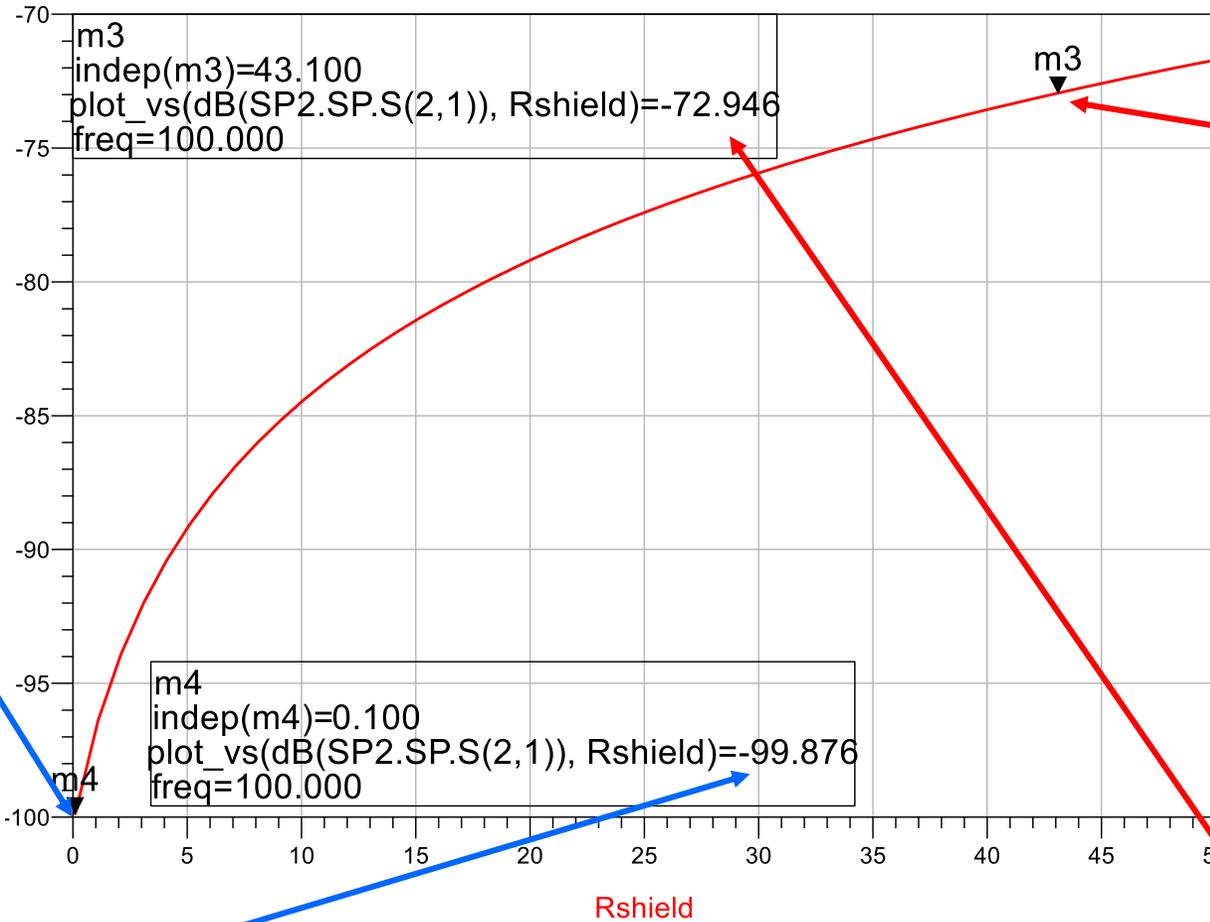
$$Atten_measured := 20 \cdot \log\left(\frac{V_{out}}{V_{in}}\right) = -99.584$$



Vin := 2
 Rsource := 50
 R_atten_in := 49.9

Rshield1 := 0.043
 Rshield2 := 0.043

Atten := 100000
 Atten_dB := 20·log(Atten) = 100

The voltage across the shield is:

$$V_{shield} := \frac{V_{in} \cdot \frac{R_{shield1} \cdot R_{shield2}}{R_{shield1} + R_{shield2}}}{R_{source} + R_{atten_in} + \frac{R_{shield1} \cdot R_{shield2}}{R_{shield1} + R_{shield2}}}$$

$$V_{shield} = 4.303 \times 10^{-4}$$

$$V_{atten_in} := \frac{V_{in} \cdot R_{atten_in}}{R_{source} + R_{atten_in} + \frac{R_{shield1} \cdot R_{shield2}}{R_{shield1} + R_{shield2}}}$$

$$V_{atten_in} = 9.988 \times 10^{-1}$$


$$V_{out} := \frac{V_{atten_in} \cdot 2}{Atten} + V_{shield} = 4.503 \times 10^{-4}$$

$$Atten_measured := 20 \cdot \log\left(\frac{V_{out}}{V_{in}}\right) = -72.95$$

Including the Cables


- Cable shield resistance creates the low frequency error
- Different cables have different shield resistance
- At higher frequencies, the cable coupling starts to correct it

PDN CABLE

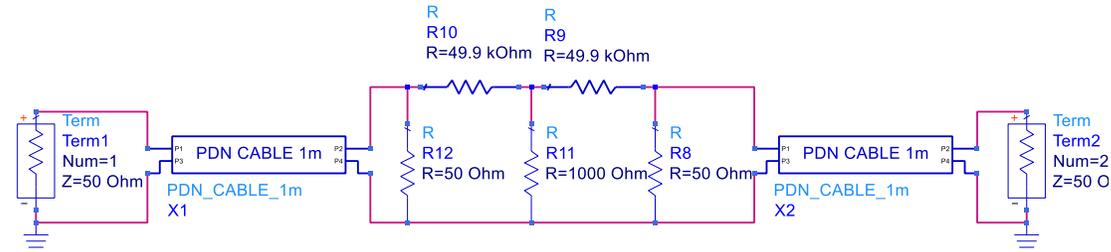

S-PARAMETERS

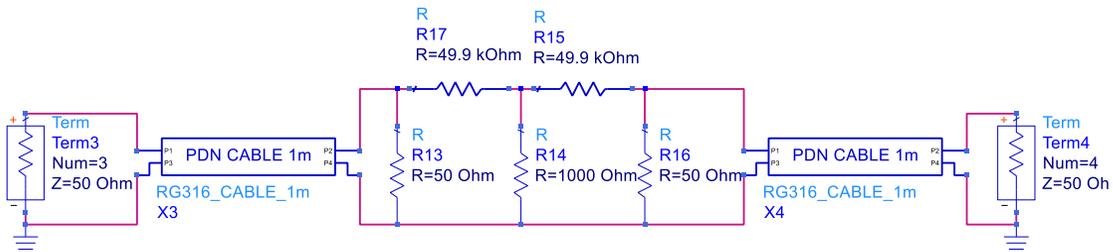
S_Param
SP1
Start=100 Hz
Stop=100 kHz
Step=



RG316 CABLE


dB(S(4,3))

dB(S(2,1))

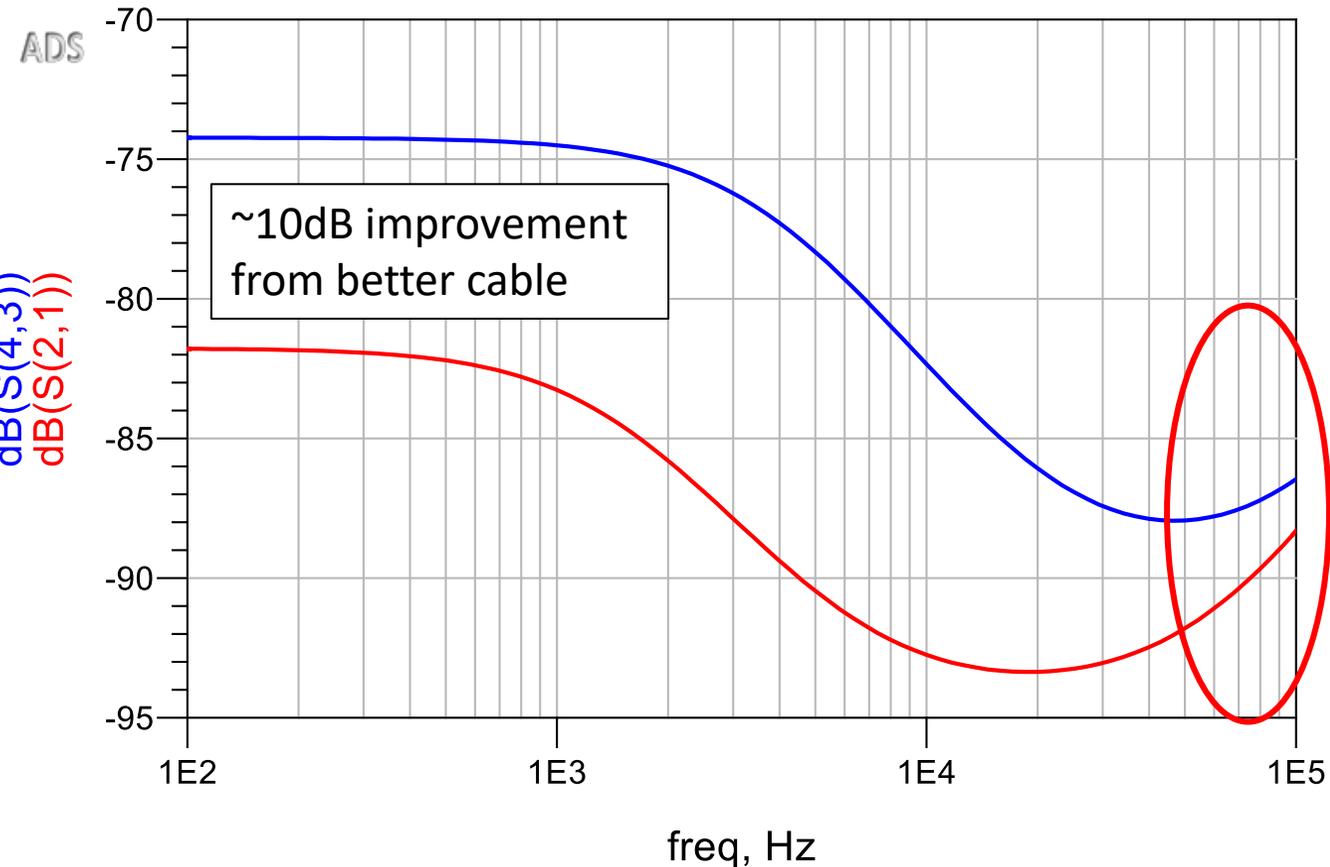


So How Do We Fix It??

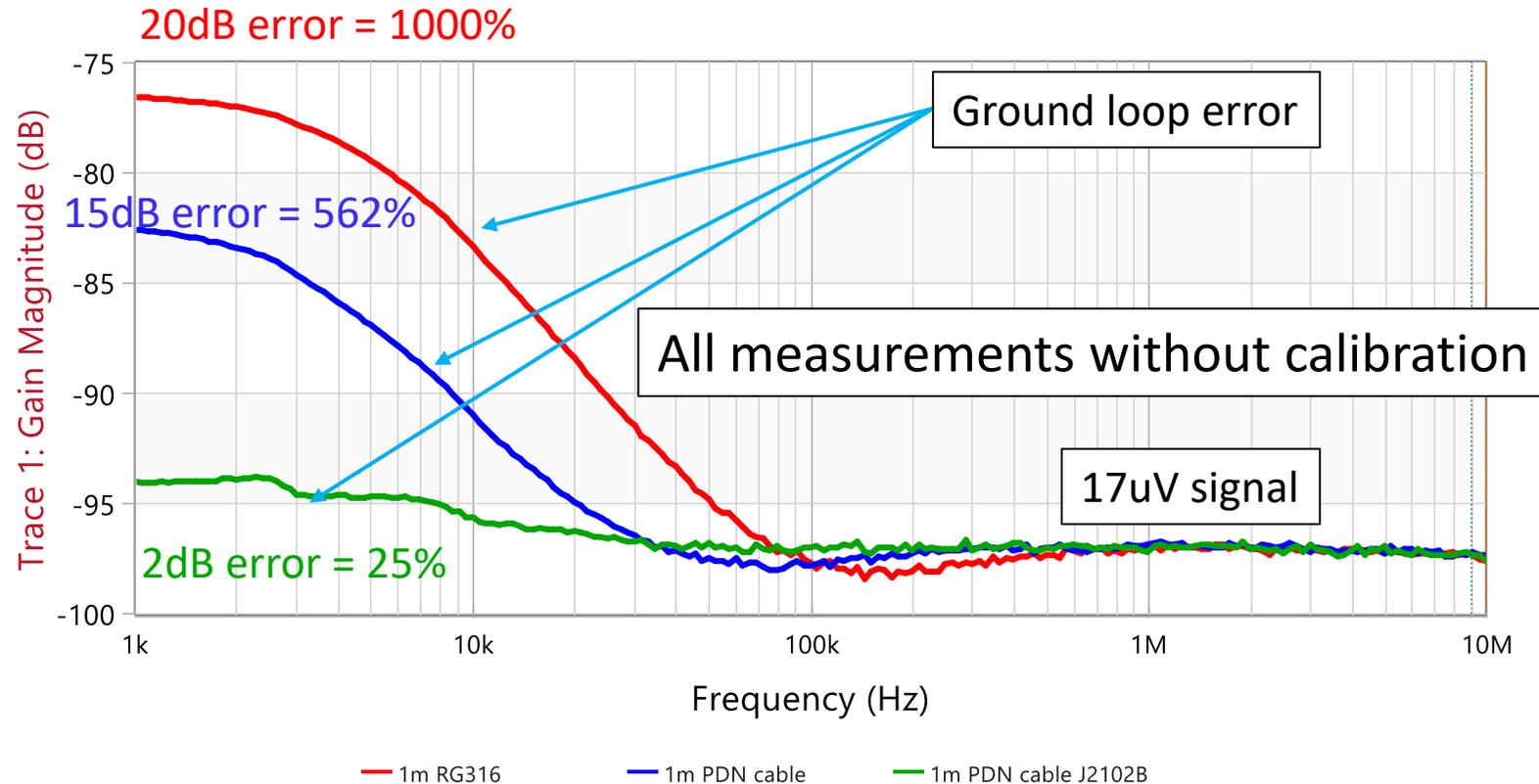- Cables matter. Use low shield resistance cables
- Improve the coupling on the output side by adding a high CMRR coaxial isolator
- Calibrate the SHORT whenever possible
- While it seems like a differential probe will help, it won't. They are very noisy



The Ideal Setup

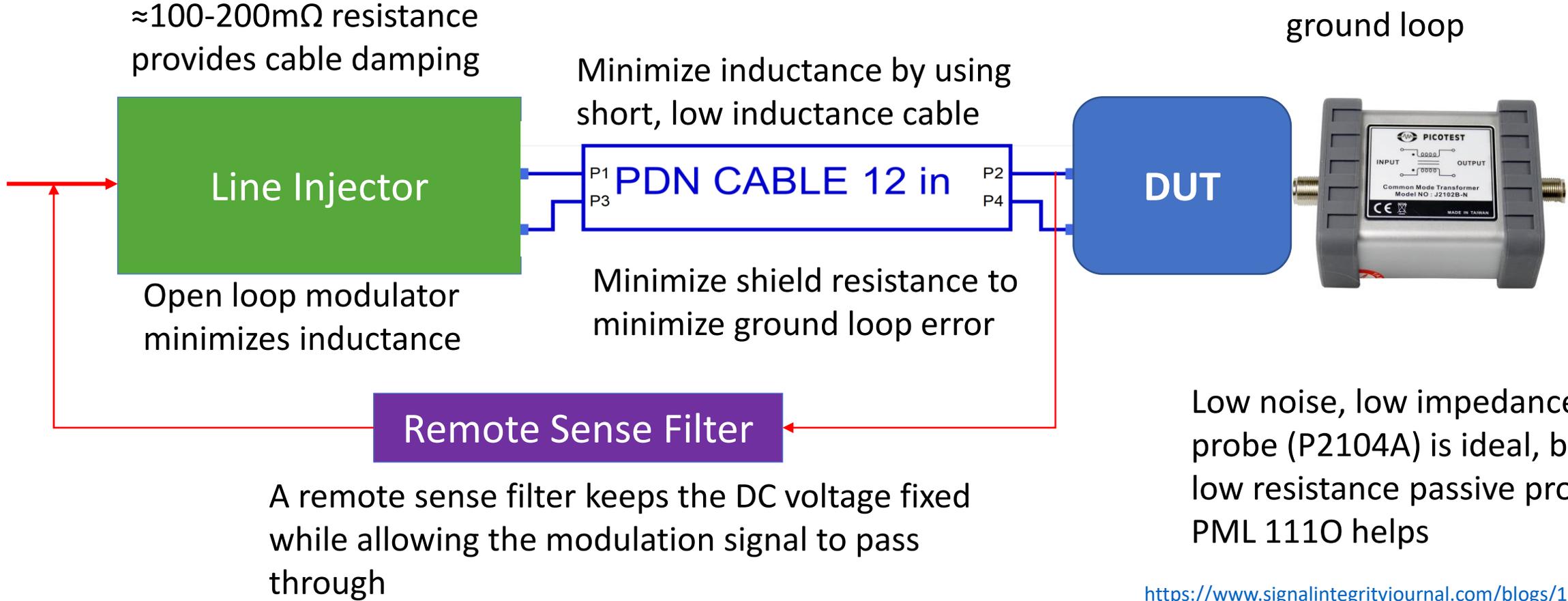

<https://www.picotest.com/images/download/AppNoteRemoteSenseVer05Final.pdf>

<https://www.signalintegrityjournal.com/blogs/15-extreme-measurements/post/2484-the-ultimate-power-rail-noise-measurement>

Not Done Yet – the Capacitors!!

- The interconnecting cable inductance and the modulator resistance form a low pass filter with the DUT capacitors
- Many high-speed specifications recognize this and require their removal for testing purposes
- Yes, THRU calibration at the capacitors can correct this, but the received signals at the output will likely be too small to measure

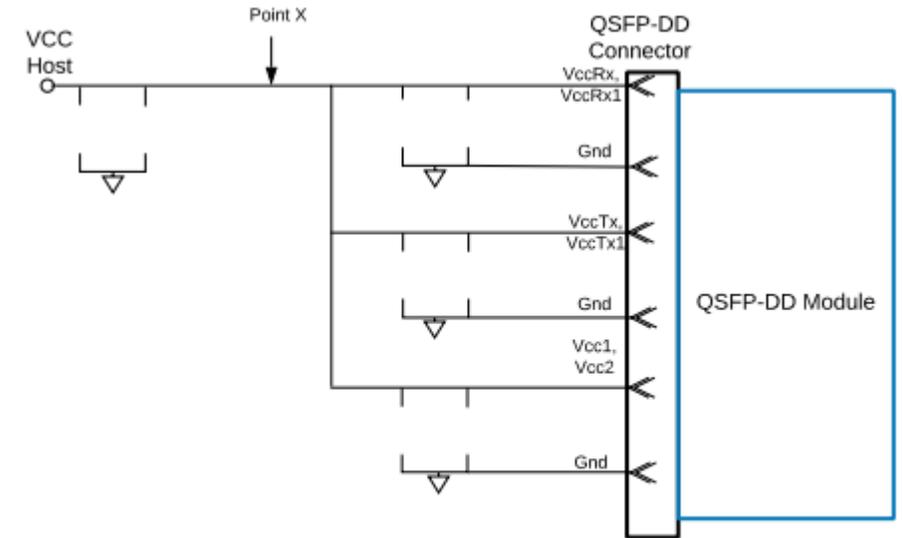


Figure 11: Module Noise Output Measurement


Extreme Measurement

- Even after removing the capacitors, some loads present a very low resistance
- This can be due to a low input voltage, high power switching regulator (which is negative resistance at low frequency)
- Many high-speed circuits such as transceivers also present a very low resistance, typically on the order of 0.5 Ohms
- In this case, the impedance of the interconnect quickly degrades the bandwidth
- **We can correct this by eliminating the interconnect!**




Moving the modulator into a probe head removes the interconnect! Problem solved!!

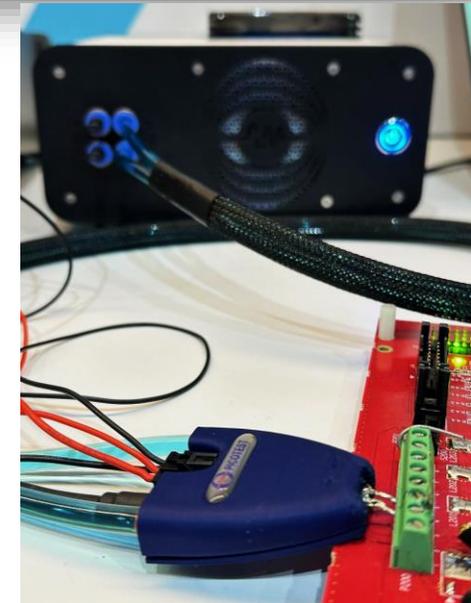Well, almost. There is still power loss to contend with, so you can see this probe is water-cooled!!



The End Result

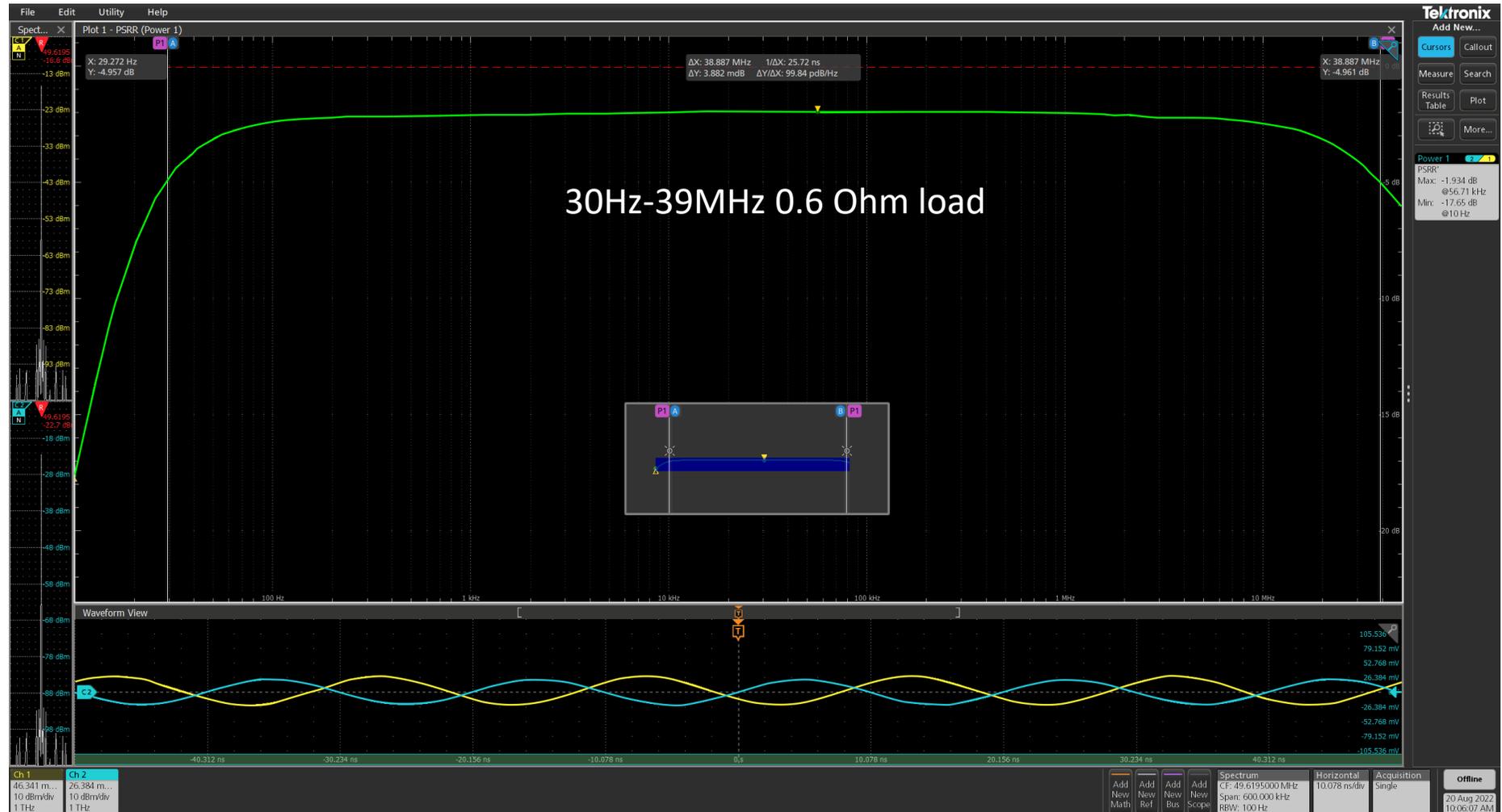Moving the modulator into a probe head eliminated the interconnect, allowing modulation up to 39MHz (-3dB) or even higher into the low resistance load!!



Thank You for Attending!

Learn more about the products and accessories we discussed today by visiting:

- www.picotest.com
- www.omicron-lab.com
- Picotest PSRR Solution page: <https://www.picotest.com/measurements/PSRR.html>

Stay Connected! Follow Picotest on LinkedIn: <https://www.linkedin.com/company/picotest>

Check out Picotest's online Forum for questions and answers from Steve and the community:
<https://www.picotestonline.com/forum>

Email info@picotest.com with any other questions