

Inductor Resonances and EMI

OMICRON 14th Power Analysis & Design Symposium

Organized by,



Arturo Mediano
Founder & EMI/EMC magician
HF MAGIC LAB S.L.
amediano@hfmagiclab.com




Prof. Arturo Mediano
I3A, UNIVERSITY OF ZARAGOZA (SPAIN)
amediano@unizar.es

2025

April 9th, 2025



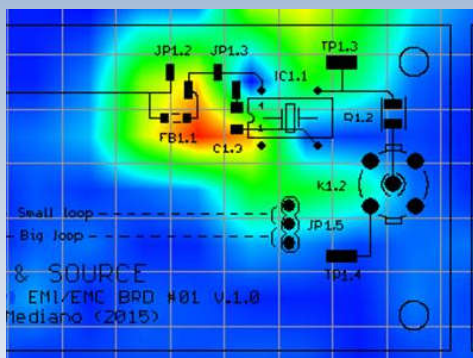A High Frequency Lab for design, diagnostic, troubleshooting and training



Interferences (EMI)
Electromagnetic Compatibility (EMC)
Signal Integrity (SI)
Radiofrequency (RF)

Contact: Arturo Mediano
HF MAGIC LAB S.L.

Bari, 31. Edificio TechnoCenter. Oficinas 216-217
50197 Zaragoza (Spain)
amediano@hfmagiclab.com

About the speaker ...

ARTURO MEDIANO – HF MAGIC LAB S.L.



- Faculty member at the University of Zaragoza (SPAIN) for 30 years
- Founder HF Magic Lab S.L.
- Senior Member IEEE
- Chair IEEE EMC-S Spain Chapter
- Past Chair IEEE MTT-S Technical Committee 17
- amediano@unizar.es



© A. Mediano · HF MAGIC LAB S.L. · amediano@hfmagiclab.com

Outline ...

- 1. Introduction inductors everywhere.**
- 2. Let's work with inductors in the ideal way.**
- 3. Using cores.**
- 4. Example Buck converter**
 - Ideal design and simulation
 - Prototype
 - EMI results
 - Inductor characterization and model
 - Using LTSPICE to analyze the problems
- 5. Conclusions**




© A. Mediano · HF MAGIC LAB S.L. · amediano@hfmagiclab.com



Inductors ... a common component

INDUCTORS EVERYWHERE

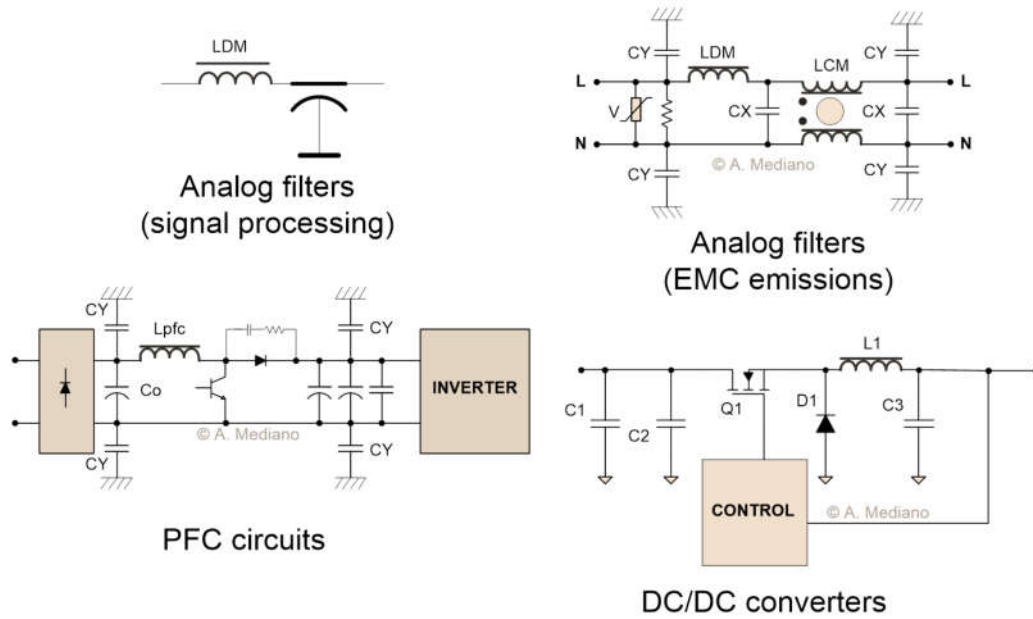


© A. Mediano · HF MAGIC LAB S.L. · amediano@hfmagiclab.com



Inductors ... ideal way.

How to work with inductors IDEAL MODEL

Take a wire and create a simple model:

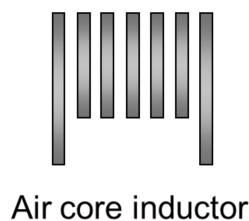

© A. Mediano · HF MAGIC LAB S.L. · amediano@hfmagiclab.com



Inductors ... they are not ideal

The ideal behavior of an inductor is a **fantasy**.
Its parasitics define your EMI/EMC reality.





© A. Mediano · HF MAGIC LAB S.L. · amediano@hfmagiclab.com




Inductors ... using core.

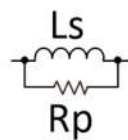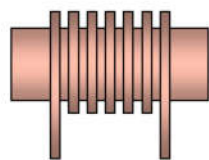
A core is used for a higher inductance without the need for big sized inductors.




Core losses

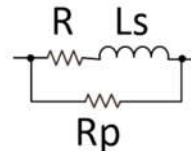

Core and wire losses

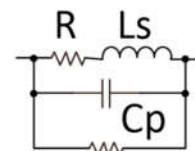

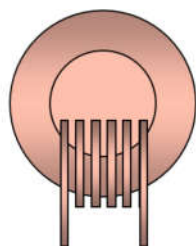
Adding stray capacitance (high frequency)



© A. Mediano · HF MAGIC LAB S.L. · amediano@hfmagiclab.com



Inductors ... commercial example

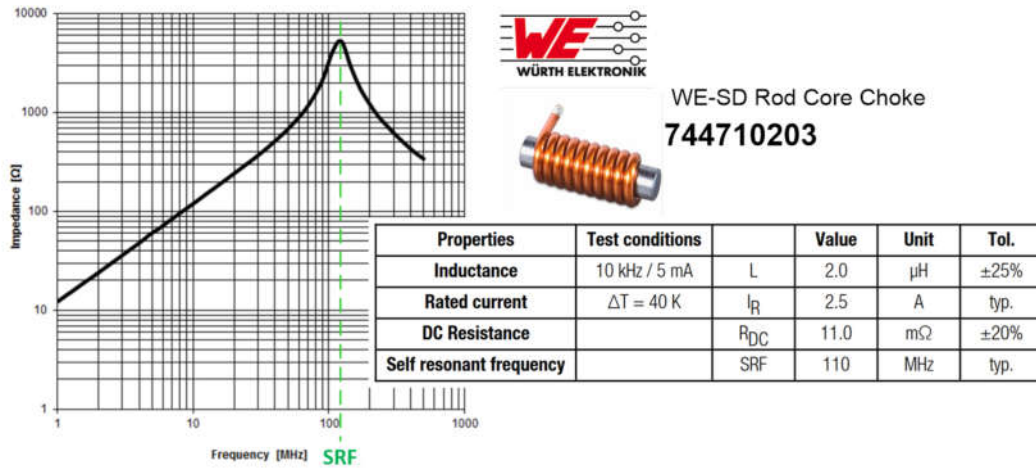


© A. Mediano · HF MAGIC LAB S.L. · amediano@hfmagiclab.com



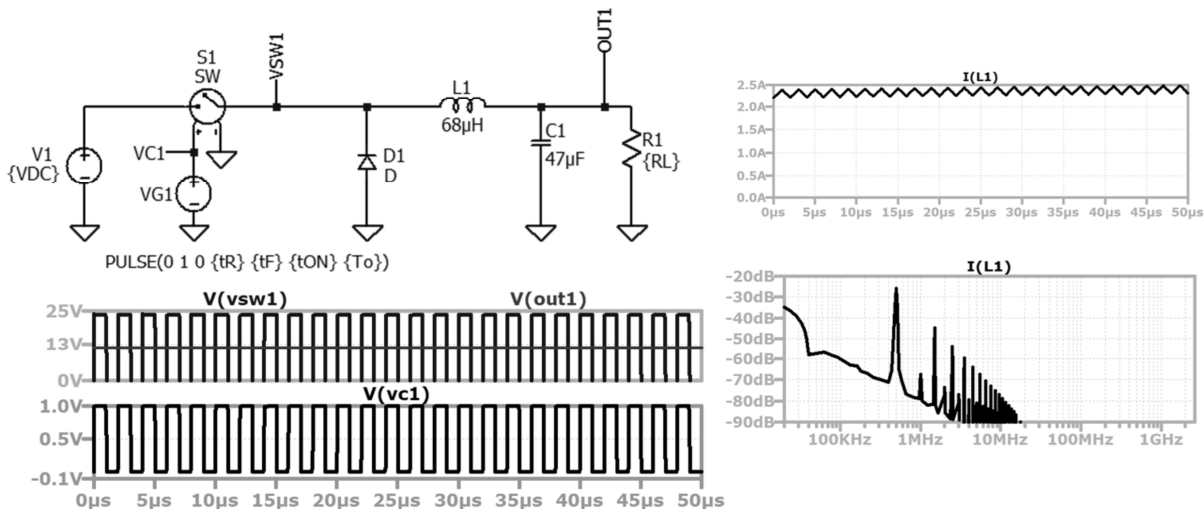Example: Buck converter


A Buck converter is designed for $V_{in}=24V$, $V_{out}=12V$ and $R_L=50\Omega$



© A. Mediano · HF MAGIC LAB S.L. · amediano@hfmagiclab.com

Example: Buck converter and EMC


A prototype is built ...

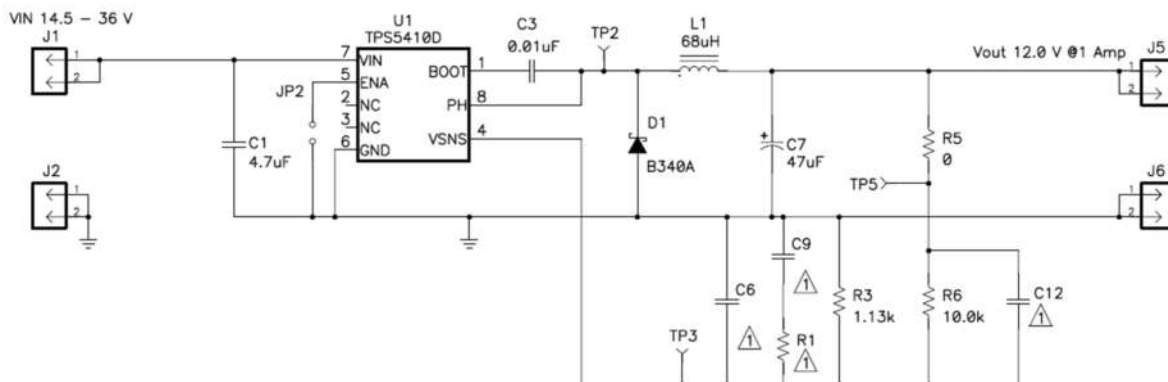

© A. Mediano · HF MAGIC LAB S.L. · amediano@hfmagiclab.com

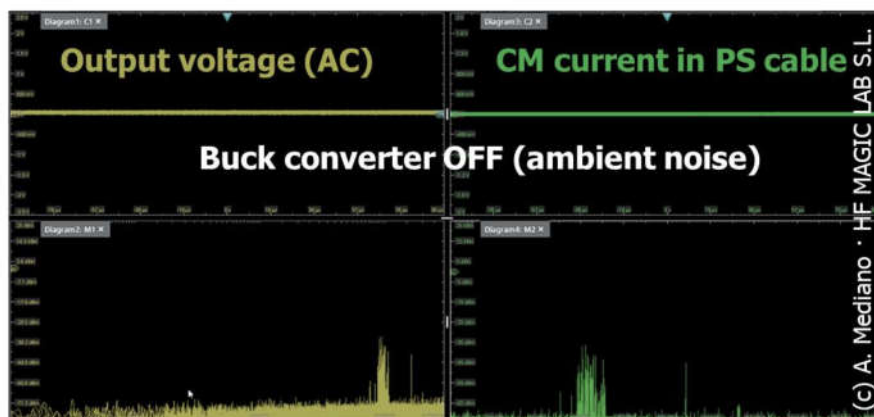Example: Radiated emissions


Let's measure output voltage and CM current in power supply cable:



© A. Mediano · HF MAGIC LAB S.L. · amediano@hfmagiclab.com

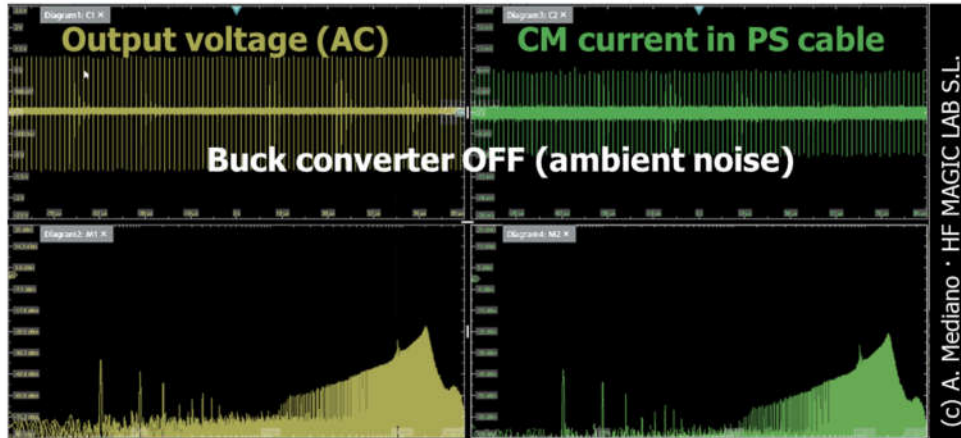Example: Radiated emissions


Turn ON buck converter and radiated emissions fail in VHF because CM current in input voltage cable:



© A. Mediano · HF MAGIC LAB S.L. · amediano@hfmagiclab.com

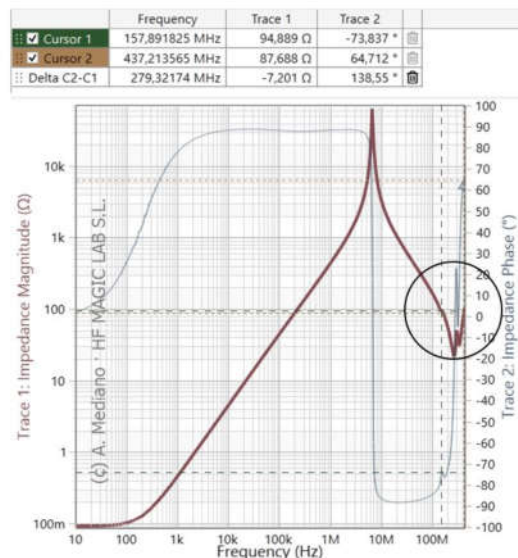Example: Inductor characterization

Let's measure response of our inductor (INDUCTOR #1):



© A. Mediano · HF MAGIC LAB S.L. · amediano@hfmagiclab.com

Example: Inductor model

Let's calculate inductor #01 model:


Equivalent circuit model

Network structure: Parallel

Pole count (1-20): Automatic

01 Inductor 1 model.fit

R_0	-4,841 k Ω
C_0	1,73 pF
R_1	108,33 m Ω
L_1	66,309 μ H
R_{p2}	4,533 k Ω
R_{s2}	25,365 Ω
L_2	43,839 nH
C_2	6,383 pF

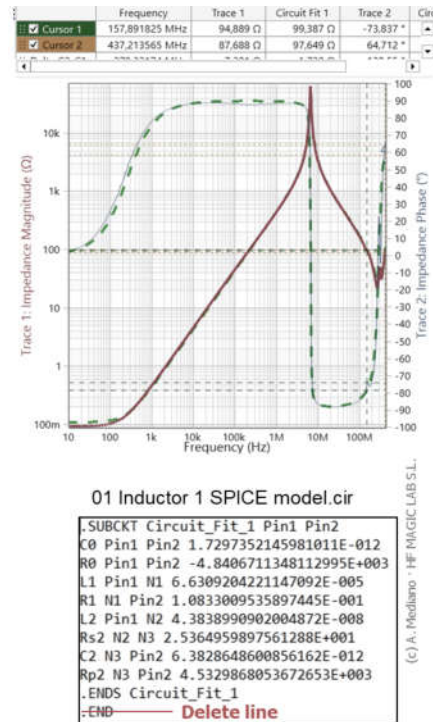

© A. Mediano · HF MAGIC LAB S.L. · amediano@hfmagiclab.com


Example: Inductor model

Open the .CIR file with LTSPICE:

```

LTspice XVII - [01 Inductor 1 SPICE model.cir]
File Edit View Simulate Tools Window Help
. . . . .
01 Inductor 1 SPICE model.cir 01 Models test.asc
.SUBCKT Circuit_Fit_1 Pin1 Pin2
C0 Pin1 Pin2 1.7297352145981011E-012
R0 Pin1 Pin2 -4.8406711348112995E+003
L1 Pin1 N1 6.6309204221147092E-005
R1 N1 Pin2 1.0833009535897445E-001
L2 Pin1 N2 4.3838990902004872E-008
Rs2 N2 N3 2.5364959897561288E+001
C2 N3 Pin2 6.3828648600856162E-012
Rp2 N3 Pin2 4.5329868053672653E+003
.ENDS Circuit_Fit_1
    
```

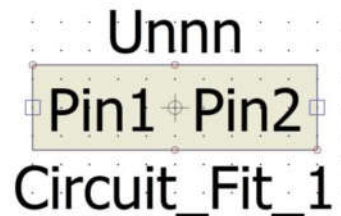
Use click+right mouse button for crating symbol and save in project folder:



© A. Mediano · HF MAGIC LAB S.L. · amediano@hfmagiclab.com


Example: Test model in simulation

Check model with LTSPICE:

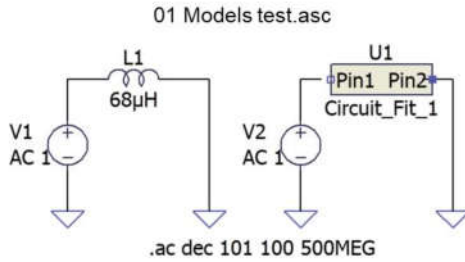

```
.ac dec 101 100 500MEG

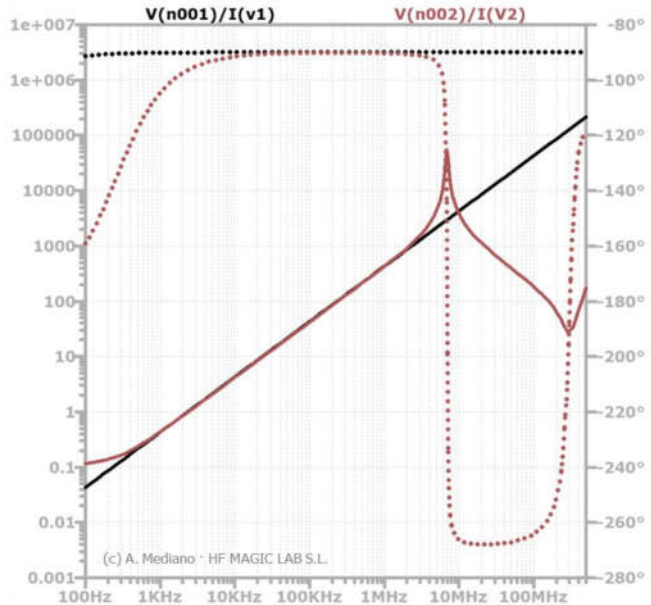.SUBCKT Circuit_Fit_1 Pin1 Pin2
C0 Pin1 Pin2 1.7297352145981011E-012
R0 Pin1 Pin2 -4.8406711348112995E+003
L1 Pin1 N1 6.6309204221147092E-005
R1 N1 Pin2 1.0833009535897445E-001
L2 Pin1 N2 4.3838990902004872E-008
Rs2 N2 N3 2.5364959897561288E+001
C2 N3 Pin2 6.3828648600856162E-012
Rp2 N3 Pin2 4.5329868053672653E+003
.ENDS Circuit_Fit_1
```




© A. Mediano · HF MAGIC LAB S.L. · amediano@hfmagiclab.com

Example: Test model in simulation



Create a model of the DC/DC converter with the "real" inductor:

02 Buck demo.asc

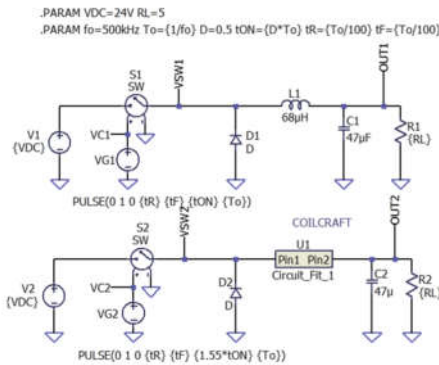

```
.PARAM VDC=24V RL=5
.PARAM fo=500kHz To=(1/fo) D=0.5 tON=(D*To) tR=(To/100) tF=(To/100)

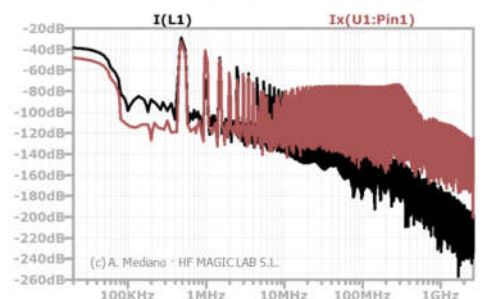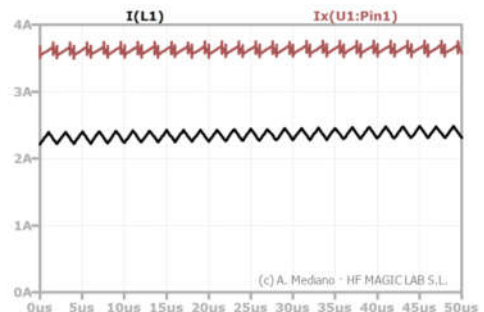.SUBCKT Circuit_FR_1 Pin1 Pin2
C0 Pin1 Pin2 1.7297352145981011E-012
R0 Pin1 Pin2 -4.8406711348112995E+003
L1 Pin1 N1 6.6309204221147092E-005
R1 N1 Pin2 1.0833009535897445E-001
L2 Pin1 N2 4.3838990902004872E-008
Rs2 N2 N3 2.5364959897561288E+001
C2 N3 Pin2 6.3828648600856162E-012
Rp2 N3 Pin2 4.5329868053672653E+003
.ENDS Circuit_FR_1
```



© A. Mediano · HF MAGIC LAB S.L. · amediano@hfmagiclab.com

THANK YOU!



Arturo Mediano
Founder & EMI/EMC magician
HF MAGIC LAB S.L.
amediano@hfmagiclab.com



Prof. **Arturo Mediano**
I3A, **UNIVERSITY OF ZARAGOZA (SPAIN)**
amediano@unizar.es

