

# Hands-On Challenges and Solutions in Bidirectional GaN Switch Design



# Speaker



**Milan Marjanovic**

[milan@electronicdesign-marjanovic.com](mailto:milan@electronicdesign-marjanovic.com)

[www.electronicdesign-marjanovic.com](http://www.electronicdesign-marjanovic.com)



# Content overview

High Voltage Switches- Overview

Bidirectional Switches- what is that?

Gate Driving

Placement-Layout

Modern Packages- New Challenges

Appendix- Measurements




# Detailed Comparison of High-Voltage Power Switch Technologies

Technology	Key Specs & Features	Technical Pros	Technical Cons
Silicon (SJ / IGBT)	600 – 1700 V Freq < 250 kHz Gate 0 – 15 V JEDEC & AEC-Q101	Mature, low-cost Avalanche/short-circuit robust Easy drive	High switching loss Large die Low frequency efficiency No bi-directional capability
SiC MOSFET	650 – 1700 V Freq up to 500 kHz Gate +15 V to +18 V/-4 V JEDEC & AEC-Q101	High efficiency High immunity: 100 V/ns High Tj (175 °C) No tail current	Costly Needs bipolar voltage bias driver High 3rd quadrant losses (w/o co-diode) No bi-directional capability
Cascode GaN (D-Mode + Si MOSFET)	650 V Gate 0 – 12 V Top-cooled TOLT JEDEC & AEC-Q101	Rugged gate Low Qrr Easy drive Bi-directional operation	Two-chip solution Small Rds(on) penalty No avalanche capability
E-Mode GaN	650 V* p-GaN Gate +6/-2 V Freq ≤ 2 MHz JEDEC & some AEC-Q101	Ultra-fast (+100 V/ns) No Qrr Smallest die Bi-directional operation	Fragile gate (6 V max) No avalanche capability Needs tight layout Lower power density when used on the primary side
Integrated E-Mode GaN	650 V* Built-in driver ~2 MHz Top-cooled JEDEC; AEC-Q101 in progress	Simplifies design OCP/OTP, UVLO Compact	Higher cost Limited scalability – good up to medium power Heat density high Lower power density when used on the primary side No 2nd source
Direct-Drive D-Mode GaN	650 V Integrated driver 150 V/ns adj. slew Top-cooled QFN JEDEC	Direct control (no cascode) ZCD, cycle OC, temp monitor 2 MHz capable	Costly Supply complexity Startup sequencing No 2nd source



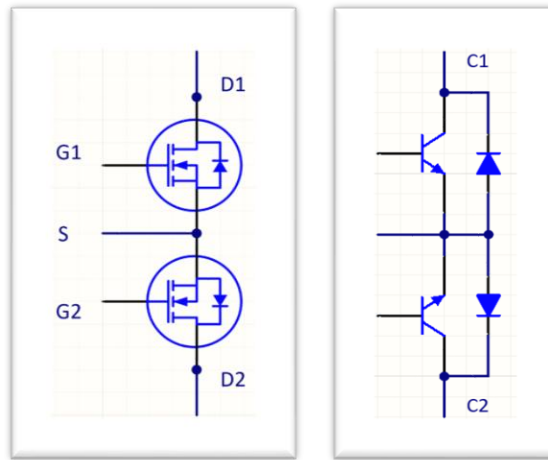
# Bidirectional Switches- what is that?

- The idea is not new, and there are various ways to build a bidirectional switch.
- Common Drain, Common Source, FET, IGBT, GaN



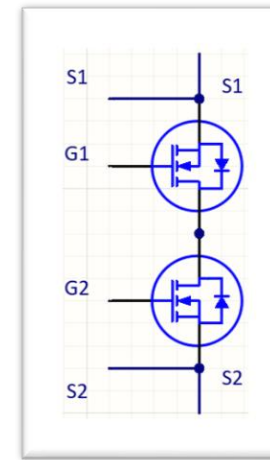*Common Source/Emitter Topology  
Control is simpler—the number of  
isolated AUX supplies is lower.*




*Common Drain Topology  
The control system is more  
complex and costly.  
Integration at chip level is  
easier.*



# E-Mode FQS: GaN-on-QST


## Dual-Gate Bidirectional Switch (BDS)

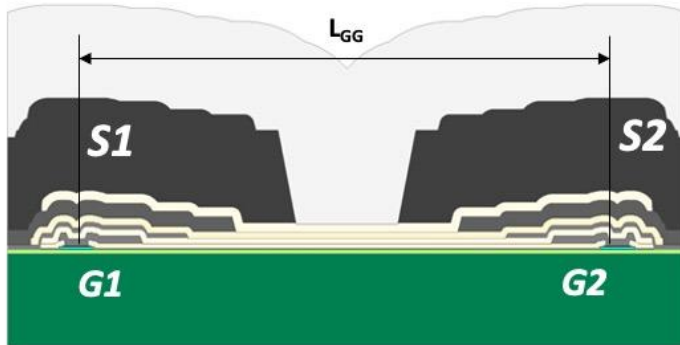

Depending on the bias at the two gates, four operation modes can be defined:


Mode	Current direction	G1	G2
ON-state	S1 $\leftrightarrow$ S2	ON	ON
Frw. diode mode	S1 $\leftarrow$ S2	ON	OFF
Rev. diode mode	S1 $\rightarrow$ S2	OFF	ON
OFF-state	S1 $\times$ S2	OFF	OFF

**ON state**

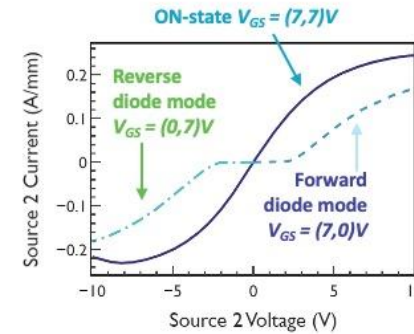


Typical values for reference $L_{GG}$	
$V_{TH}$ (gate 1 and 2)	2 V
$R_{ON}$ , ON-state	18 $\Omega$ mm
$R_{ON}$ diode modes	34 $\Omega$ mm
$V_{offset}$ diode modes	2.5 V

**OFF state**

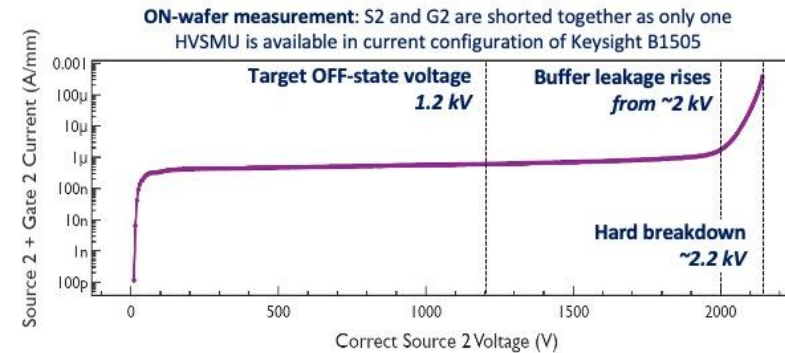

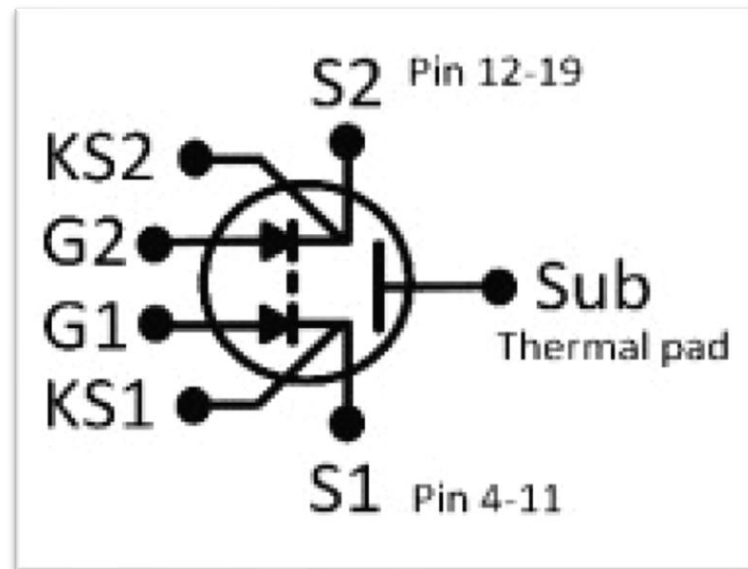
# Bidirectional GaN Switches?

- Bidirectional GaN switches are very new to the market.
- Manufacturers: very few on the market



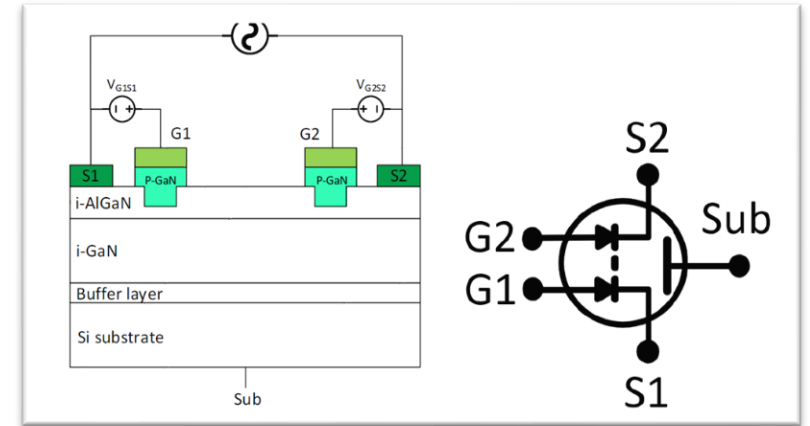
# Bidirectional GaN Switches?

- It is a common drain tap with a double gate structure based on Infineon's gate injection transistor (GIT) technology. The CoolGaN™ BDS is a five-terminal device with two gates, two sources, and one substrate. There are four operating modes:
- the traditional on/off modes
- two diode modes in which the switch can be actively controlled to behave like a diode that can block voltages in both directions



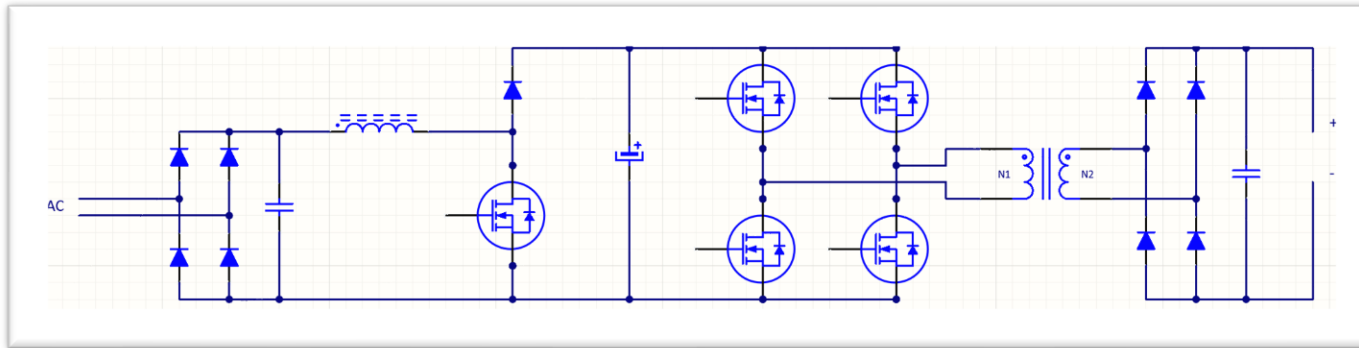
# What is this good for?

- Standard Topologies- PFC+DC/DC
- Single stage topology: AC/DC without intermediate circuit capacitor



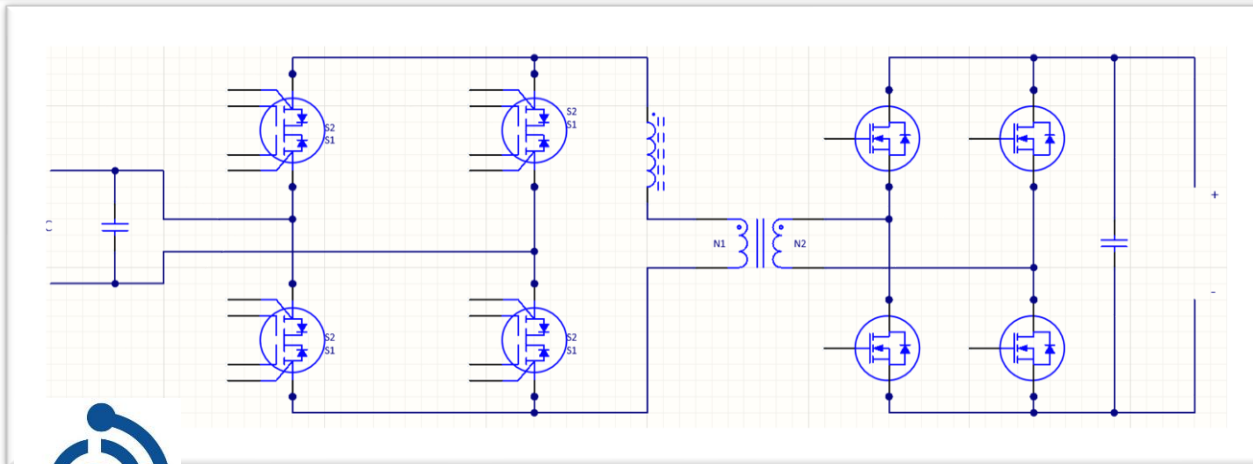
- *Standard Topologies*
- *Analog/Digital Control*
- *Availability*
- *Number of components*
- *Efficiency*
- *Electrolytes, service life*
- *Operating temperatures*



- *New topologies*
- *Complex [digital] control*
- *Availability*
- *Number of components*
- *Efficiency*
- *Service life*
- *Operating temperatures*




# Gate Driving?

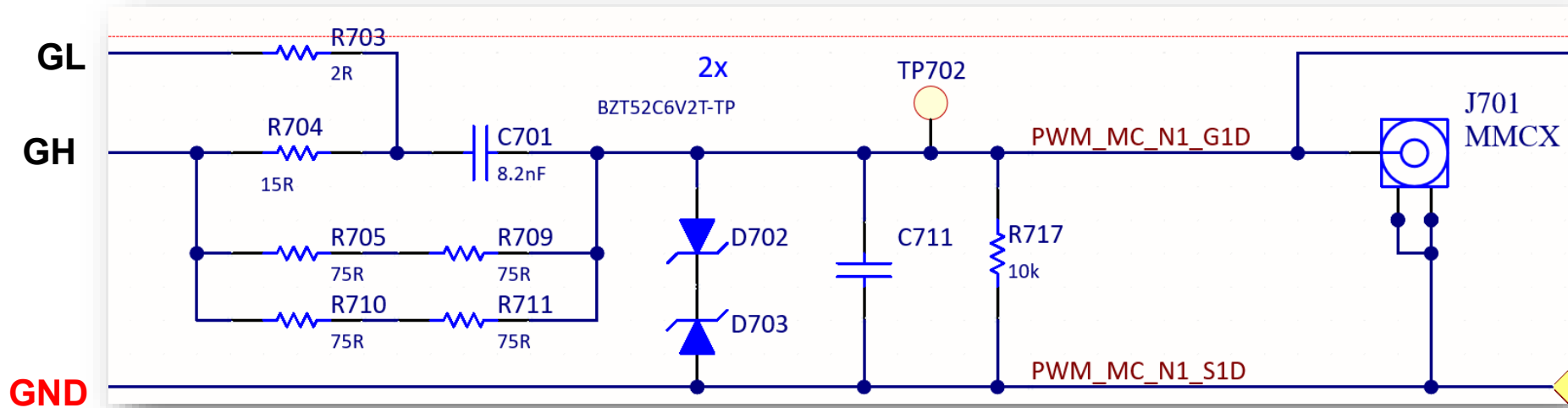
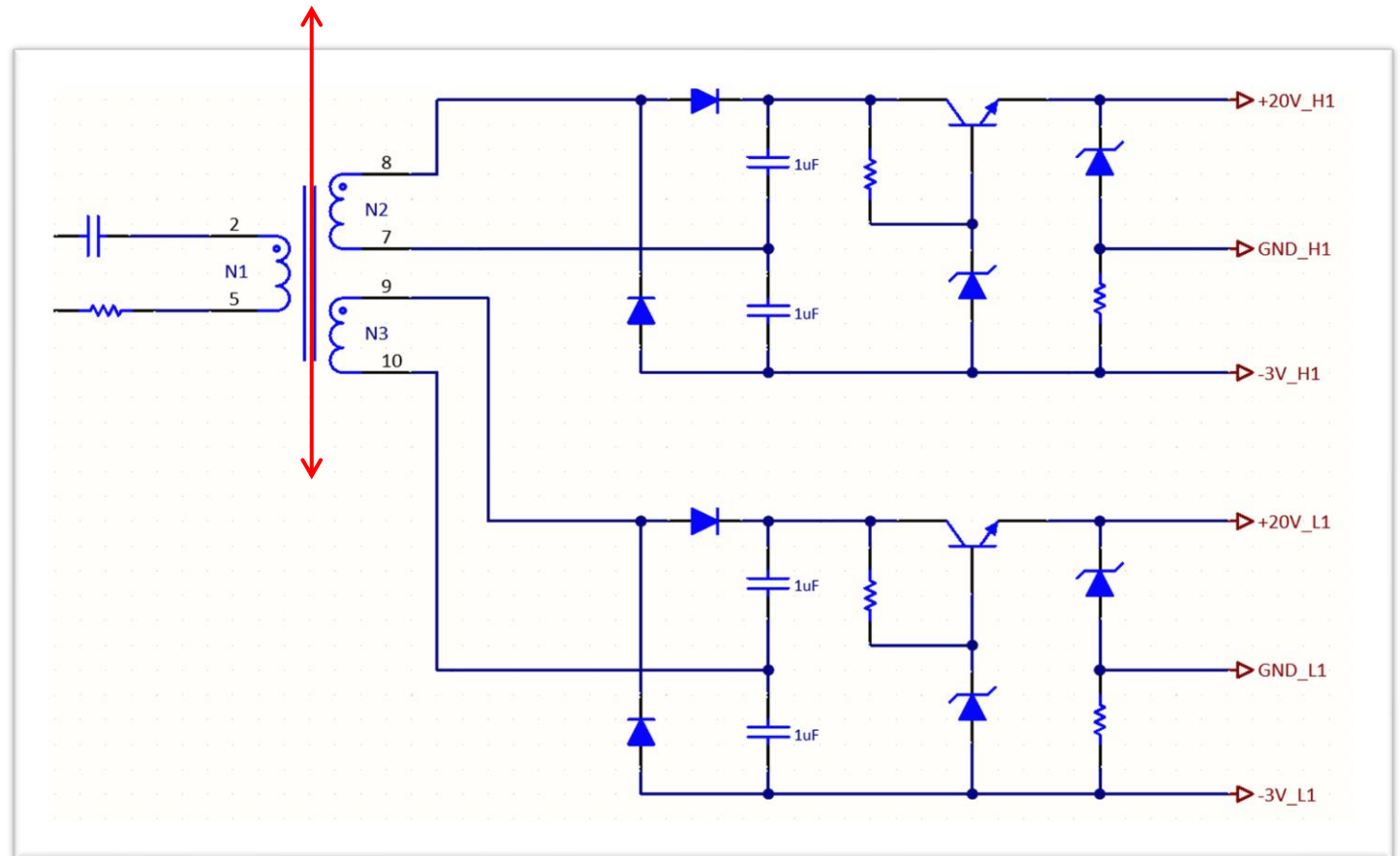
# Gate Driving?

- Component selection
- Gate Drivers,
- Isolation,
- Placement, Layout





- *Important- Very good decoupling  $C_p \sim 1\text{pF}$*
- *Gate drivers with high CMTI,  $>100\text{V/ns}$*



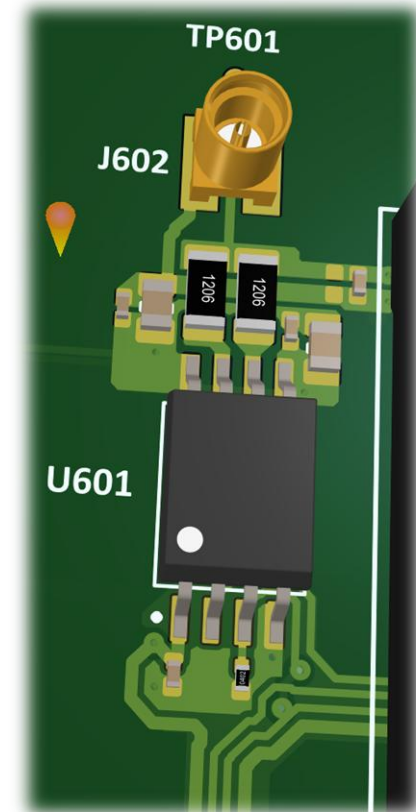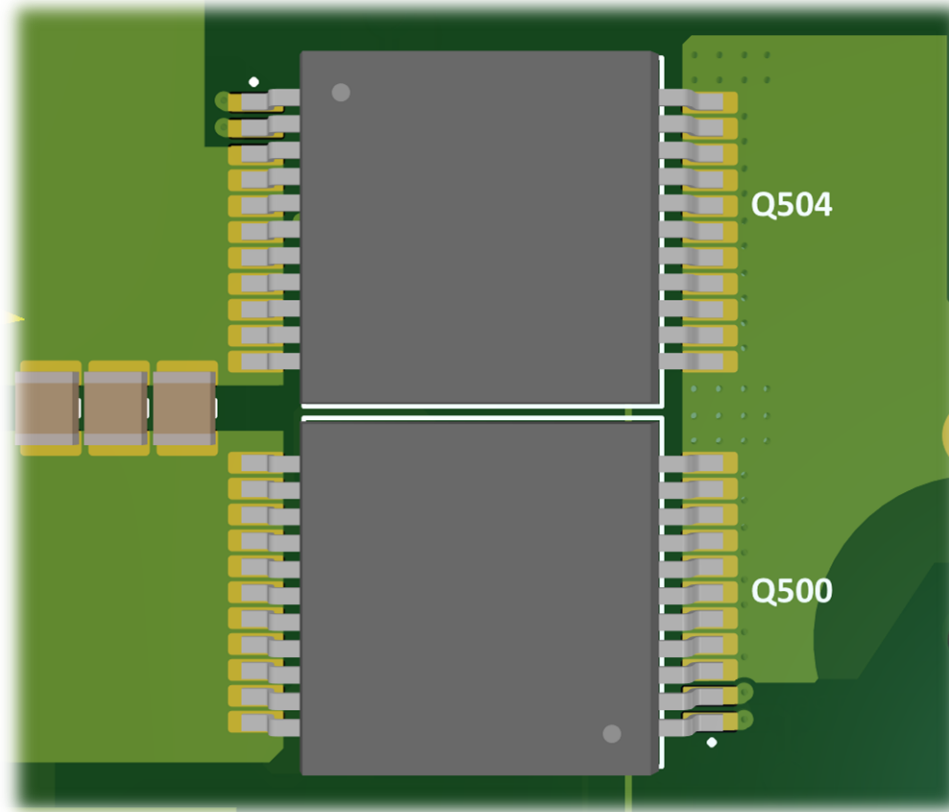
# Placement- Layout?

- Placement
- Layout
- Component selection
- Measurement Techniques




# Cooling- System integration?

- Placement
- Layout
- Mechanics

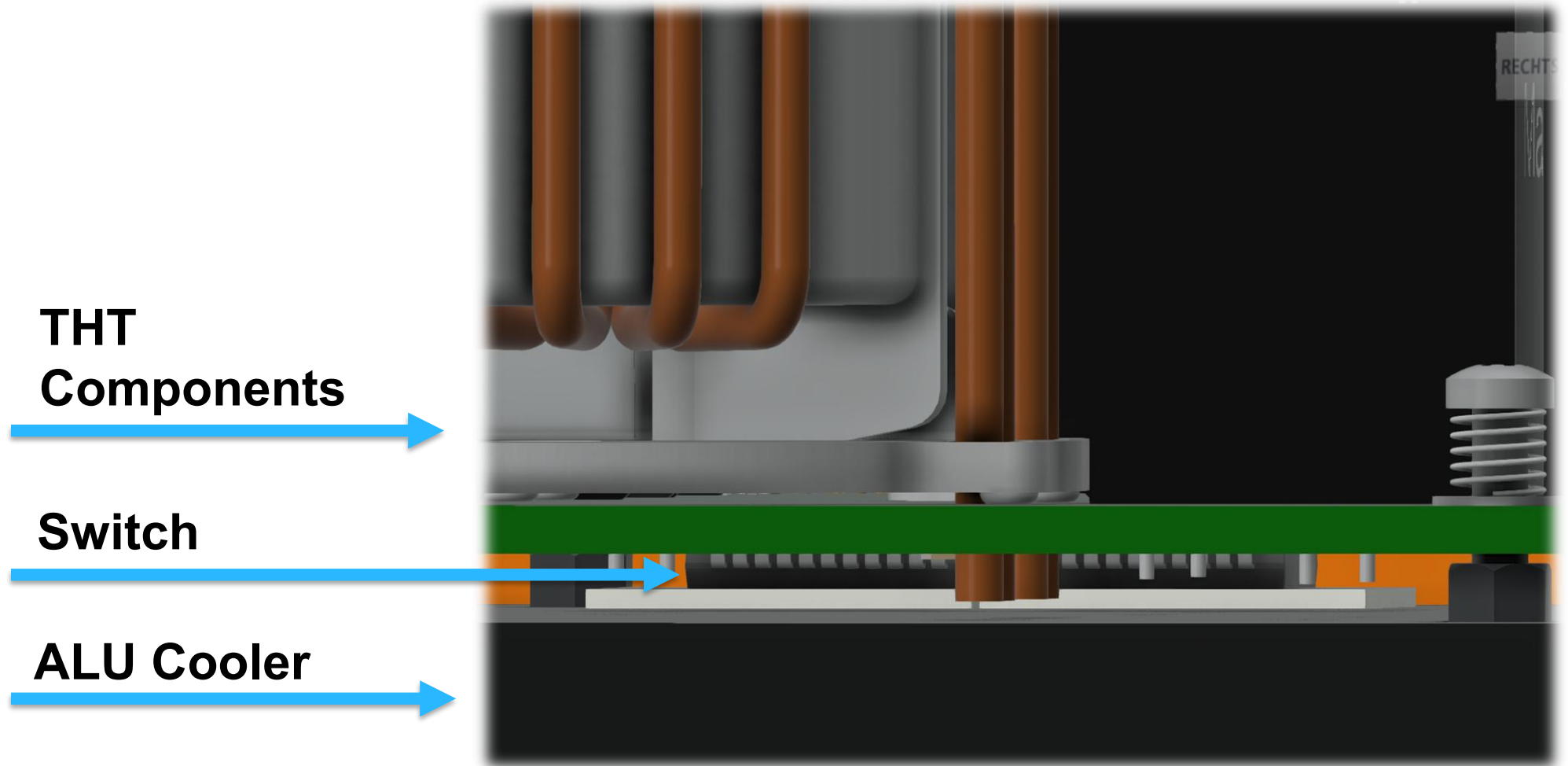
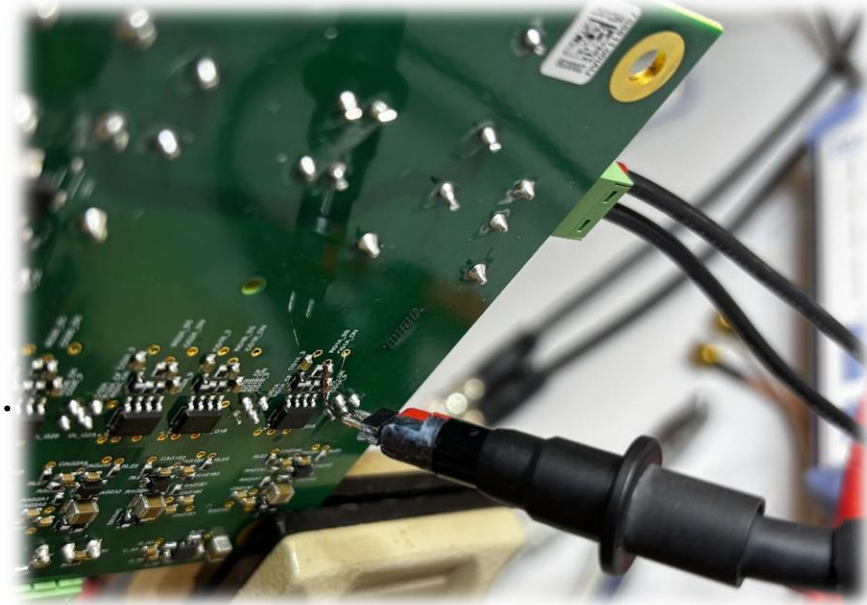
# Practical challenges- Measurement

- Modern high-speed Scopes, 1GHz
- Probes and probing techniques
- HF connectors (MMCX and compensated tips)
- There's no room for improvisation with the tips anymore.



- 8CH Scopes, Optical Isolated Probes, HV Diff Probes, High speed current probes



# Practical challenges- Control

Virtual validation with C-HIL and P-HIL de-risks every step from model to a HW design.



**Speedgoat Performance**  
Simulink Real-Time target



**Plexim RT Box 3**  
PLECS C-HIL / P-HIL



**Typhoon HIL 404**  
Ultra-high-fidelity C-HIL



**OPAL-RT OP4510**  
FPGA + CPU real-time sim



**dSPACE SCALEXIO**  
Modular automotive HIL

**Concept & Model**  
System-level design

**C-HIL**  
Controller in the loop  
signal-level I/O

**P-HIL**  
Power stage in the loop  
real currents & voltages

**Prototype**  
Validated HW + FW

- ▶ **Switched / sampled models** — resolve every switching event; verify PWM, dead-time, protection, and control bandwidth at sub- $\mu$ s time steps.
- ▶ **Averaged models** — abstract the switching action; ideal for slow outer loops, system-level dynamics and long simulations with larger time steps.
- ▶ **Pick per objective** — averaged for architecture exploration, sampled for firmware-accurate HIL validation.
- ▶ **Hybrid flow** — move from averaged to sampled inside the same environment to keep the model investment.



- ▶ **Find bugs before physical prototype** — firmware, protections, and fault handling are exercised without risking real power hardware.
- ▶ **Shorter debug cycles** — deterministic, repeatable tests beat one-off bench sessions.
- ▶ **Safer commissioning** — hardware arrives with a controller already battle-tested against representative plants.
- ▶ **Automation & coverage** — regression suites on HIL cover corner cases real HW rarely reaches.
- ▶ **Seamless handoff** — same model reused from concept → C-HIL → P-HIL → field prototype.



# Appendix




# Vgs- Emode GaN- direct vs. compensated

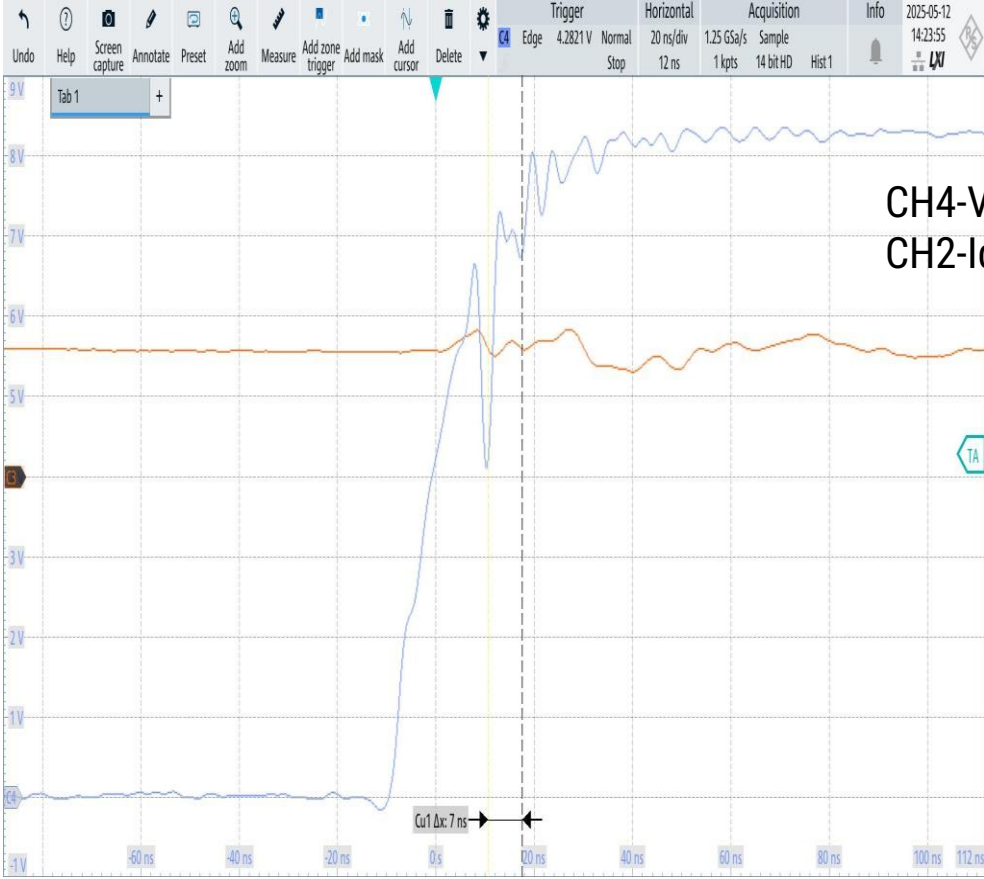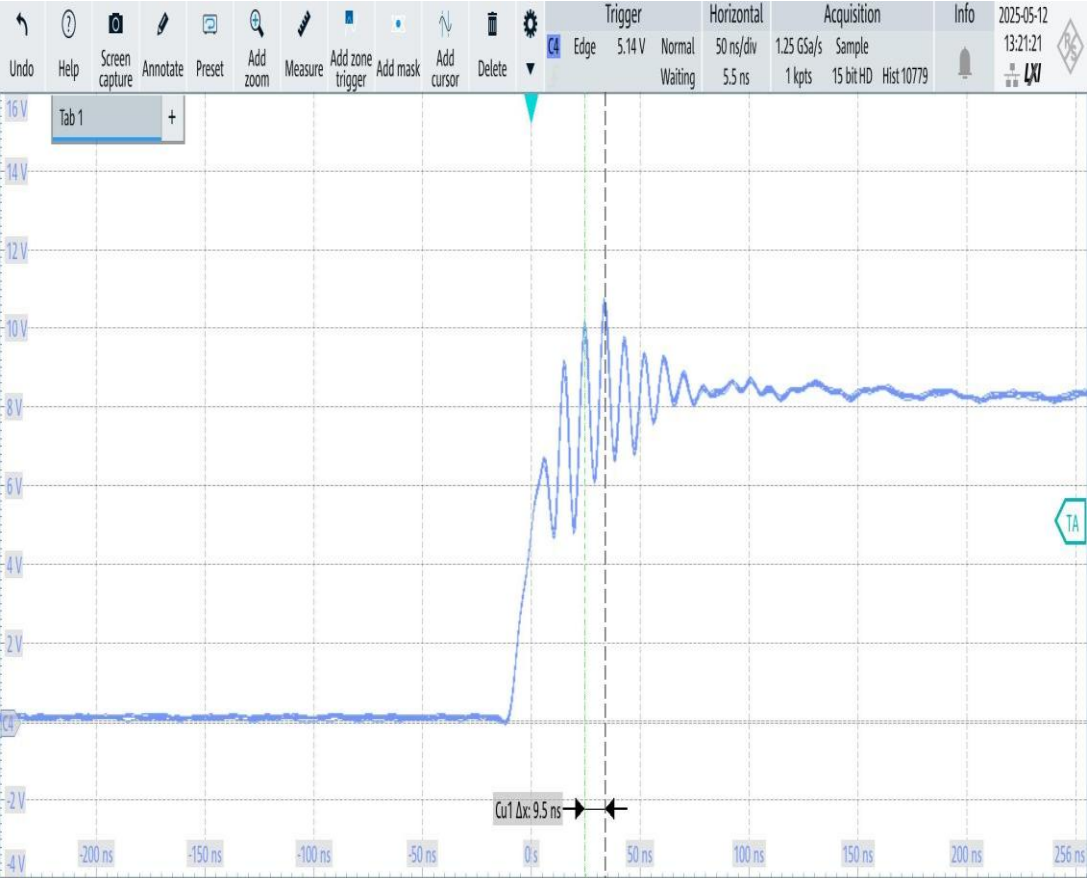

CH4-Vgs ZISO Probe  
CH2-Id current probe



# Vgs- Comparison measurement using different probe techniques

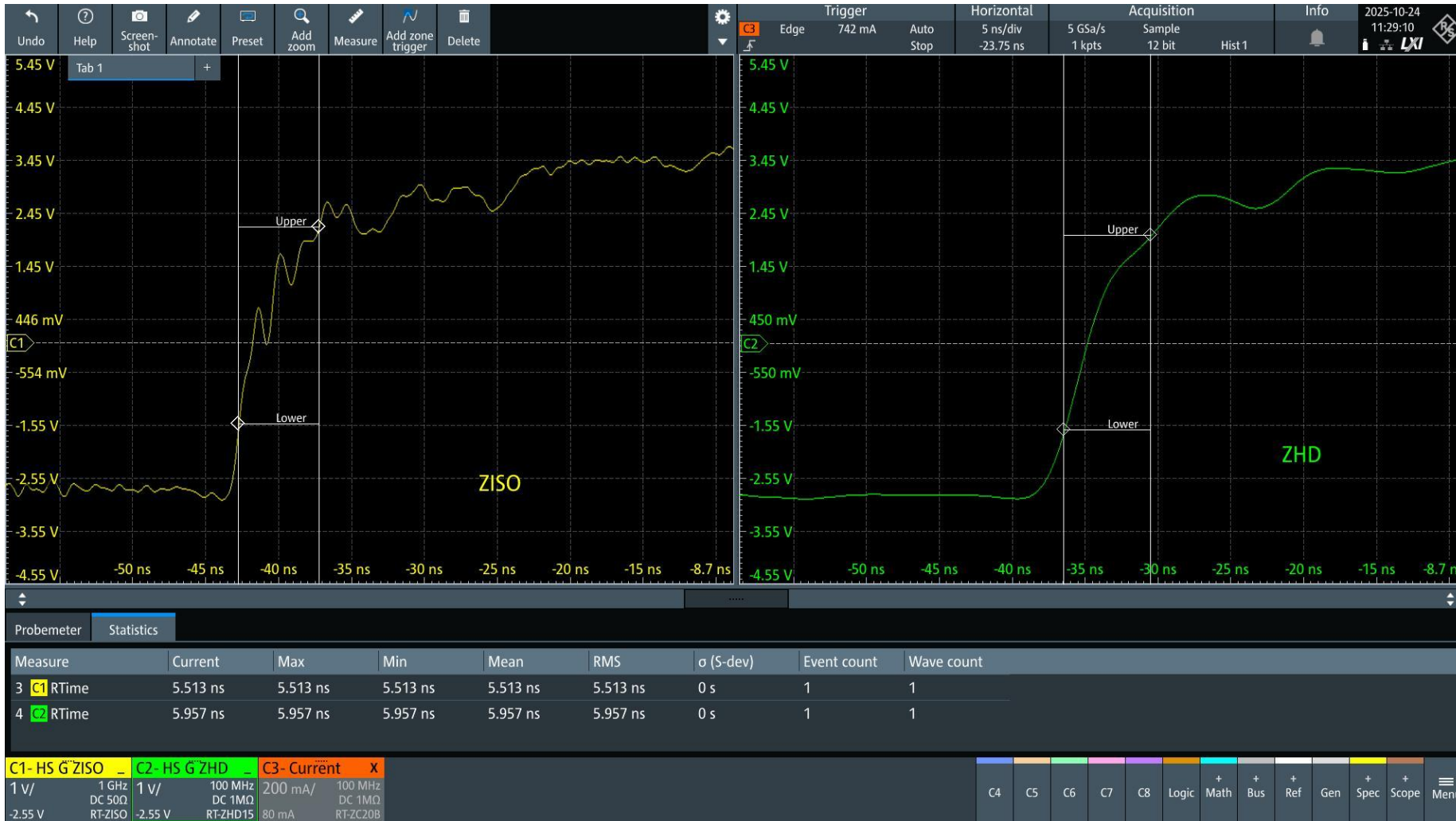

CH1-ZISO Probe  
CH2-ZHD probe




# Efficient AC-AC Power Conversion measurement



CH2- Vss Voltage  
CH3- Choke current


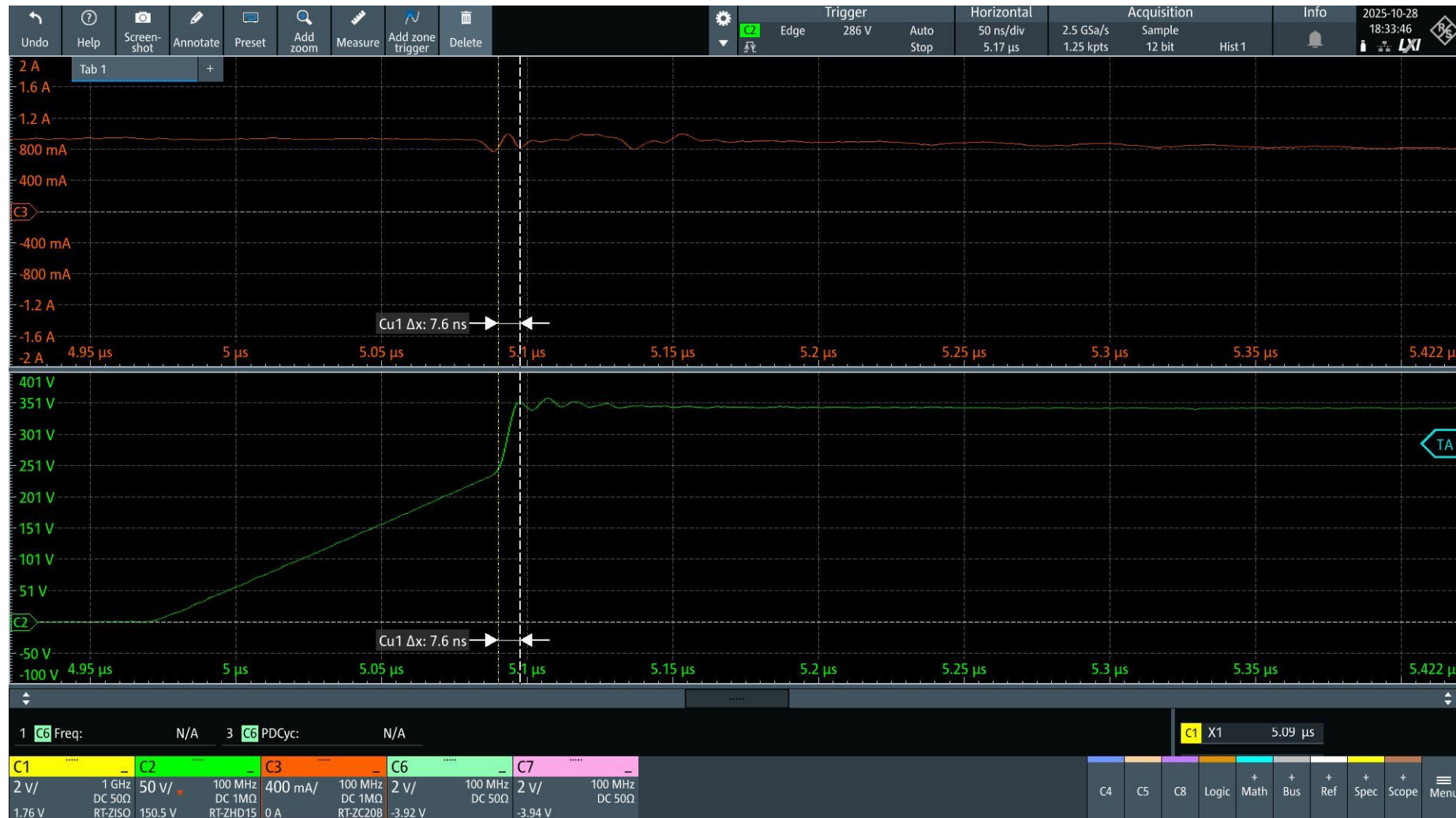
# Efficient AC-AC Power Conversion- Measurement at ZVS



# Gate driving performance



CH1-Vgs  
CH2-Vss voltage  
CH3-Switch current



# Conclusion

- Bidirectional GaN switches are emerging as a notable innovation in modern power electronics,
- They are offering a more compact and efficient alternative to traditional back-to-back unidirectional MOSFET/IGBT configurations.
- Current market offerings: medium-voltage devices (e.g., ~40 V), high-voltage types (e.g., 650 V devices suitable for converters, inverters, EV charging, and renewable systems)
- They actively block voltage and current in both directions and simplify designs while improving efficiency and reducing component count and PCB area.
- Although commercial bidirectional GaN products are still concentrated around established vendors.
- Research and advanced prototypes (e.g., 1200 V GaN bidirectional switches) indicates ongoing development toward higher blocking voltages and broader adoption in grid, EV, and industrial applications.
  
- Overall, **\*\*bidirectional GaN switches represent a growing class of power devices\*\*** that are helping designers to achieve:
  - **higher power density,**
  - **lower losses,**
  - **simpler topologies across a range of markets.**



# Q&A



# Thank You!

For more information, please visit our website



Electronicdesign Marjanovic  
[www.electronicdesign-marjanovic.com](http://www.electronicdesign-marjanovic.com)

