



Output Impedance

OMICRON Lab Webinar Series 2020

2020-04-29

Webinar Hints

Open the Q&A function



The screenshot displays a webinar interface. On the left, a slide features an image of an OMICRON LAB Bode 100 device. The slide text reads: "We will record the presentation such that you can view it again later", "OMICRON Lab Webinar Series 2020", and "2020". The OMICRON LAB logo is in the bottom right of the slide. On the right, a video feed shows two men, with the host labeled "Tobias-Schuster (Host)". A Q&A panel is open, showing "All (0)" questions and an "Ask:" dropdown menu set to "All Panelists". A "Send" button is visible. A blue callout bubble points to the Q&A panel with the text "Send questions to the presenters".

We will record the presentation such that you can view it again later

OMICRON Lab Webinar Series 2020

2020

OMICRON LAB

Q&A

All (0)

Ask: All Panelists


Select a panelist in the Ask menu first and then type your question here.

Send

Send questions to the presenters


Florian Hämmerle

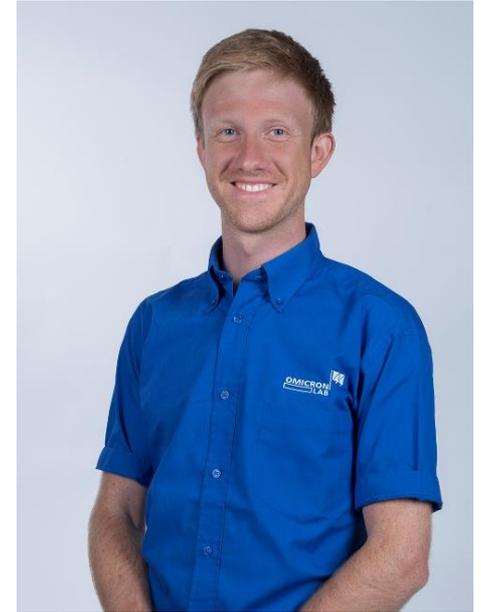- Studied Mechatronics at Vorarlberg University of Applied Sciences
- Working at OMICRON Lab since 2010 in:
 - Technical Support & Applications
 - Product management
- Contact:
 - florian.haemmerle@omicron-lab.com
 - <https://meet-omicron.webex.com/meet/florian.haemmerle>



Tobias Schuster

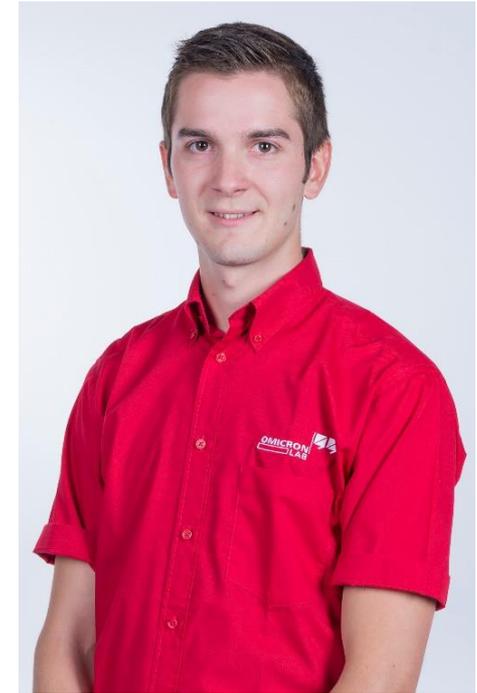- Completed electrical engineering college in 2013
- Studied Industrial Engineering and Management
- Working at OMICRON Lab since 2015 focusing on:
 - Technical Support
 - Applications
 - Sales
- Contact:
 - tobias.schuster@omicron-lab.com
 - <https://meet-omicron.webex.com/meet/tobias.schuster>



Agenda


- DC voltage source (ideal vs. real)
- Output Impedance of VRM
- NISM (Non-Invasive Stability Measurement)
- From the power to the load
- Measuring Output Impedance
- Examples




DC Voltage Source

Two-terminal device that can maintain a fixed DC voltage.


Ideally:

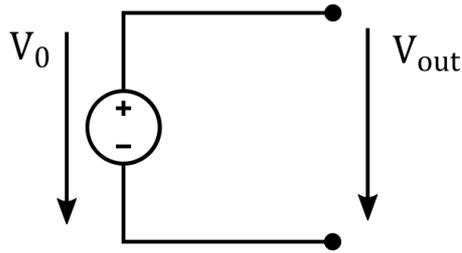

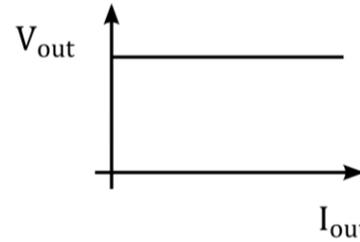
$$R_{out} = 0 \rightarrow V_{out} = V_0$$




In reality:

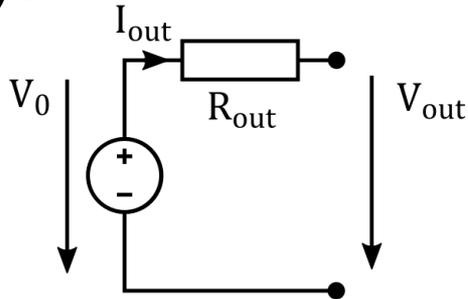
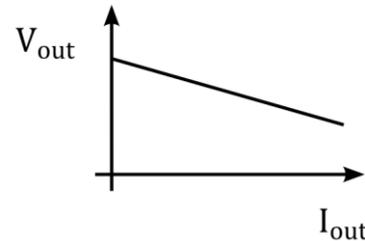
$$R_{out} \neq 0 \rightarrow V_{out} = V_0 - I_{out}R_{out}$$



Stabilizing Output via Voltage Feedback

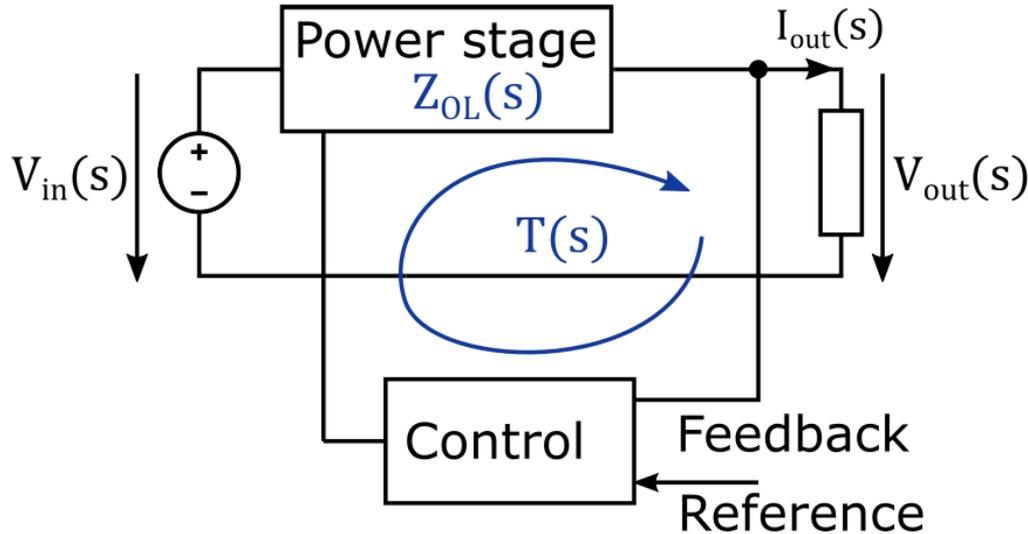

- Closing the loop changes the output impedance to:

$$Z_{out}(s) = \frac{Z_{OL}(s)}{1 + T(s)}$$

$T(s)$...Loop Gain


$Z_{OL}(s)$...Open-Loop Output Impedance

$Z_{out}(s)$...Closed-Loop Output Impedance

Closed-Loop Output Impedance


$$Z_{out}(s) = \frac{Z_{OL}(s)}{1 + T(s)}$$

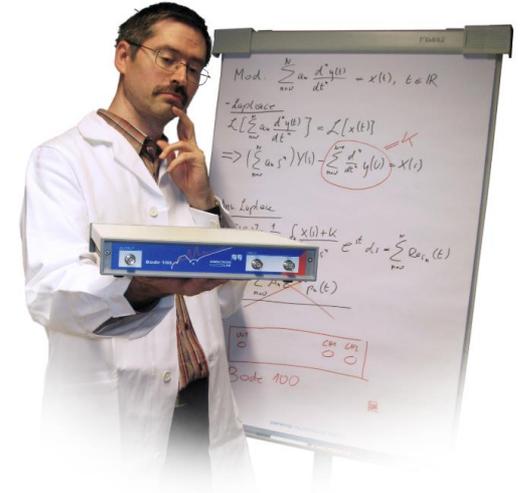- If $T(s) \gg 1$ then $Z_{out}(s) \ll Z_{OL}(s)$
 - If $T(s) \ll 1$ then $Z_{out}(s) = Z_{OL}(s)$
 - If $T(s) = 1$ then $Z_{out}(s) = \frac{1}{2} Z_{OL}(s)$
- High loop gain results in low output impedance



Loop Gain

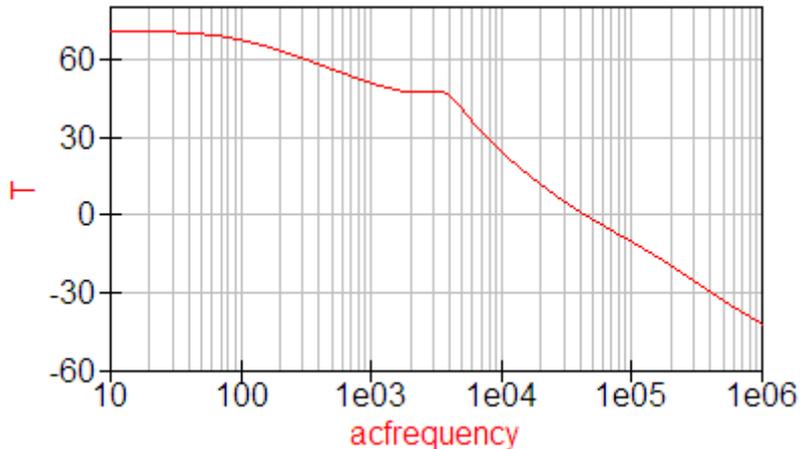- Loop Gain at DC is not $\infty \rightarrow R_{out} \neq 0$
- Control loop is not infinitely fast \rightarrow Loop Gain reduces with f
- Loop Gain crosses 0 dB line at some crossover frequency f_c
- Control loop affects Z_{out} mainly below f_c
- Above f_c the feedback has nearly no effect: $Z_{out}(s) = Z_{OL}(s)$



Simulation example (Linearized Buck)


$f_c \approx 40$ kHz

$\varphi_m \approx 30^\circ$

DC Gain limited to roughly 70dB


Buck Output Impedance Simulation

Closed-Loop:

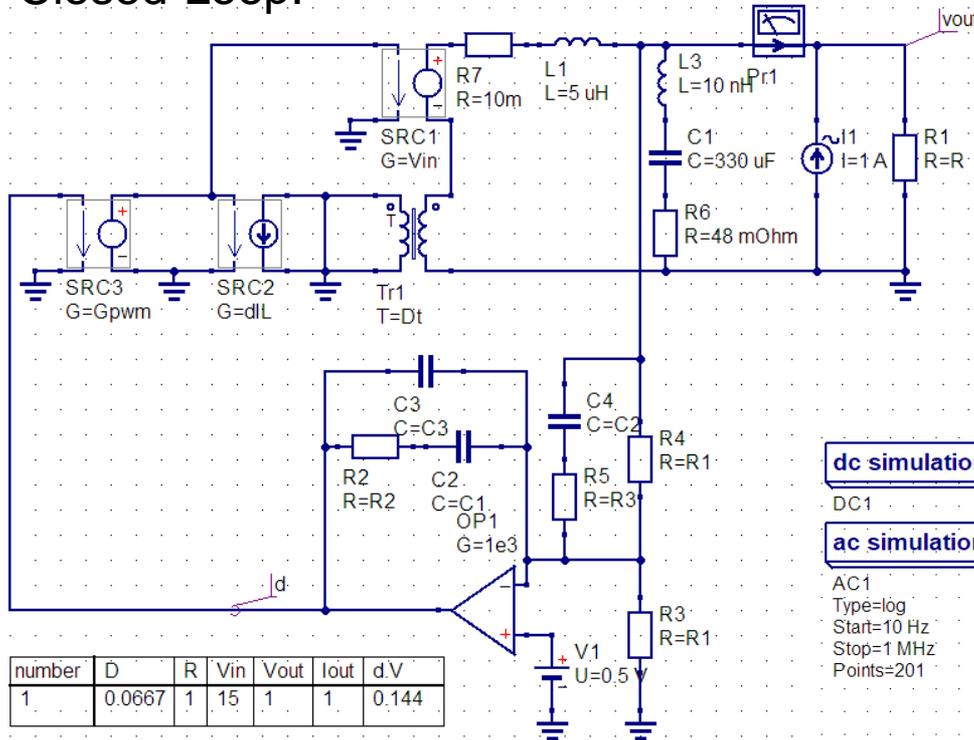

number	D	R	Vin	Vout	Iout	dV
1	0.0667	1	15	1	1	0.144

Open-Loop:

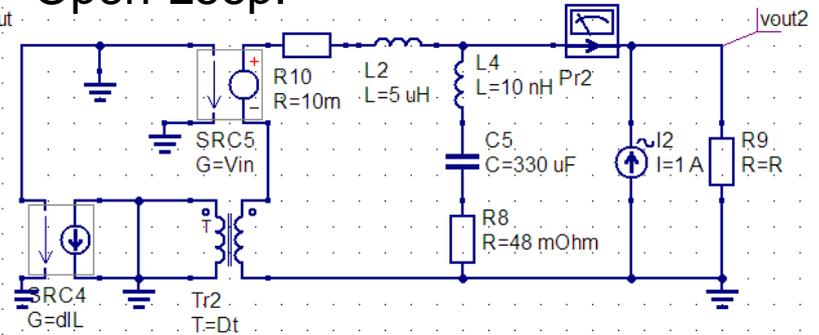

dc simulation

DC1

ac simulation

AC1
Type=log
Start=10 Hz
Stop=1 MHz
Points=201

Equation

Input1
Vin=15
Vout=1
D=Vout/Vin
R=1
Iout=Vout/R
Dt=1/D
IL=Iout
dVin=-Vin
Vramp=2.14
Gpwm=1/Vramp

Equation

Compensator70
R1=2k
R2=3.641k
R3=1.278k
C1=11.16n
C2=12.4n
C3=88.11p

Equation

Compensator30
R1=1k
R2=20.48k
R3=0.358k
C1=2.208n
C2=2.96n
C3=1.19n


Equation

Result1
Zout=vout/v-Pr1.i
magZout=abs(Zout)
argZout=180*arg(Zout)/pi

Equation

CalculateLoopGain
Tcalc=(Zol/Zout)-1
magTcalc=20*log10(mag(Tcalc))
argTcalc=180*(arg(Tcalc))/pi

Output Impedance

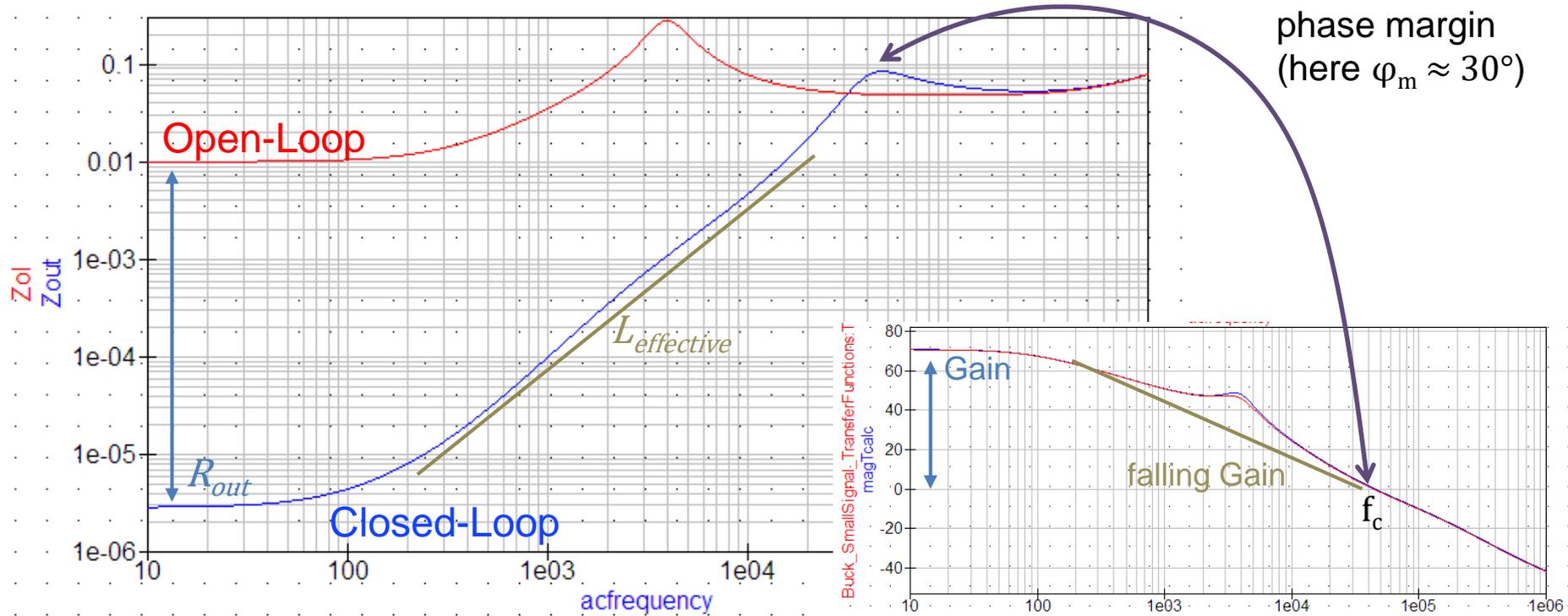

➤ Output Impedance contains information about Loop Gain (Stability)!


$$Z_{out}(s) = \frac{Z_{OL}(s)}{1+T(s)} \rightarrow T(s) = \frac{Z_{OL}(s)}{Z_{out}(s)} - 1$$

NISM (Non-Invasive Stability Measurement)




- Q correlates to Phase Margin φ_m
- Peak in Z_{out} correlates to the Q of the closed loop system

Trace 1: Impedance Magnitude (Ω)

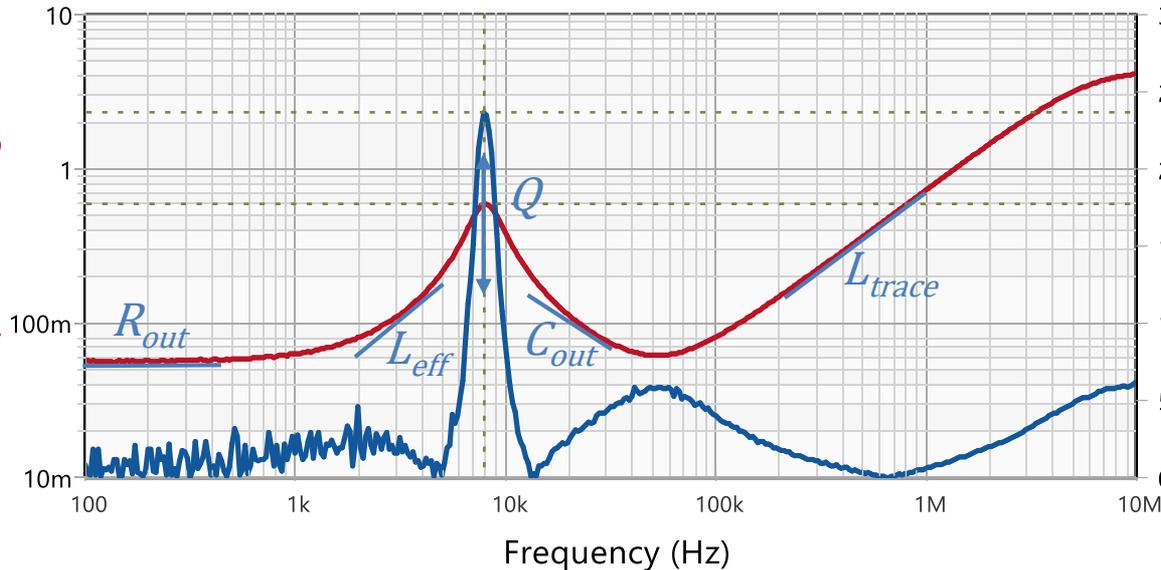


Trace 2: Impedance Q(Tg)
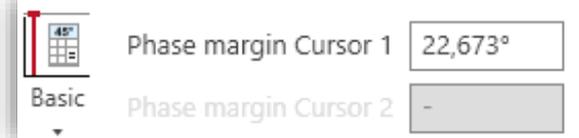
$$Q = \frac{\sqrt{\cos(\varphi_m)}}{\sin(\varphi_m)}$$




There is more from the VRM to the Load

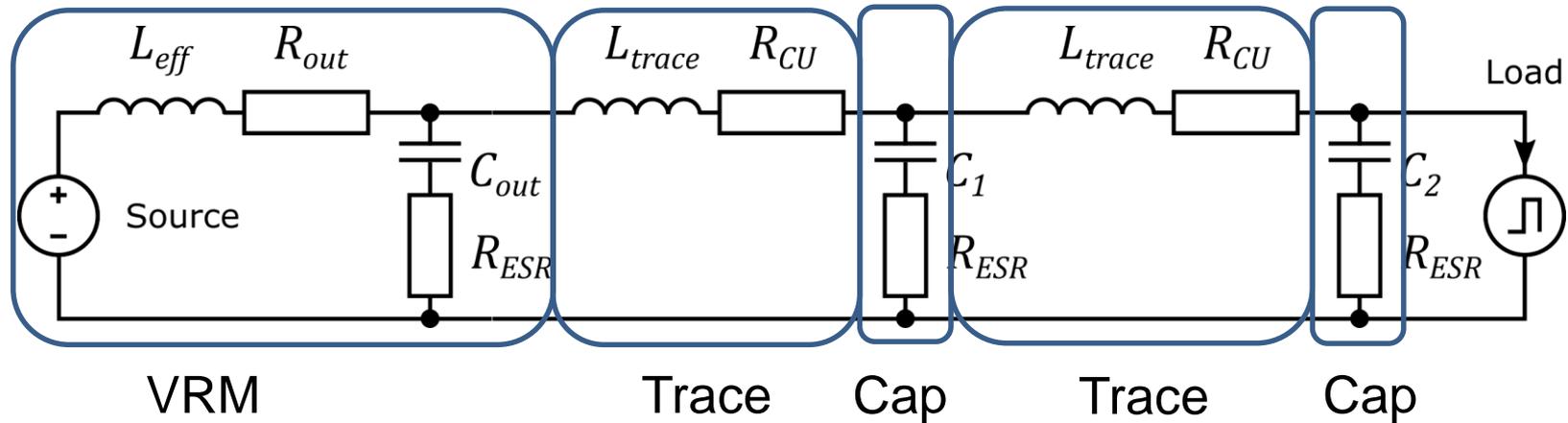


- Multiple L-C resonance circuits
 - Ceramic caps have generally very low ESR values
 - Ferrites have generally low resistance
 - The Q of the resonances can be high

A Simulation Example

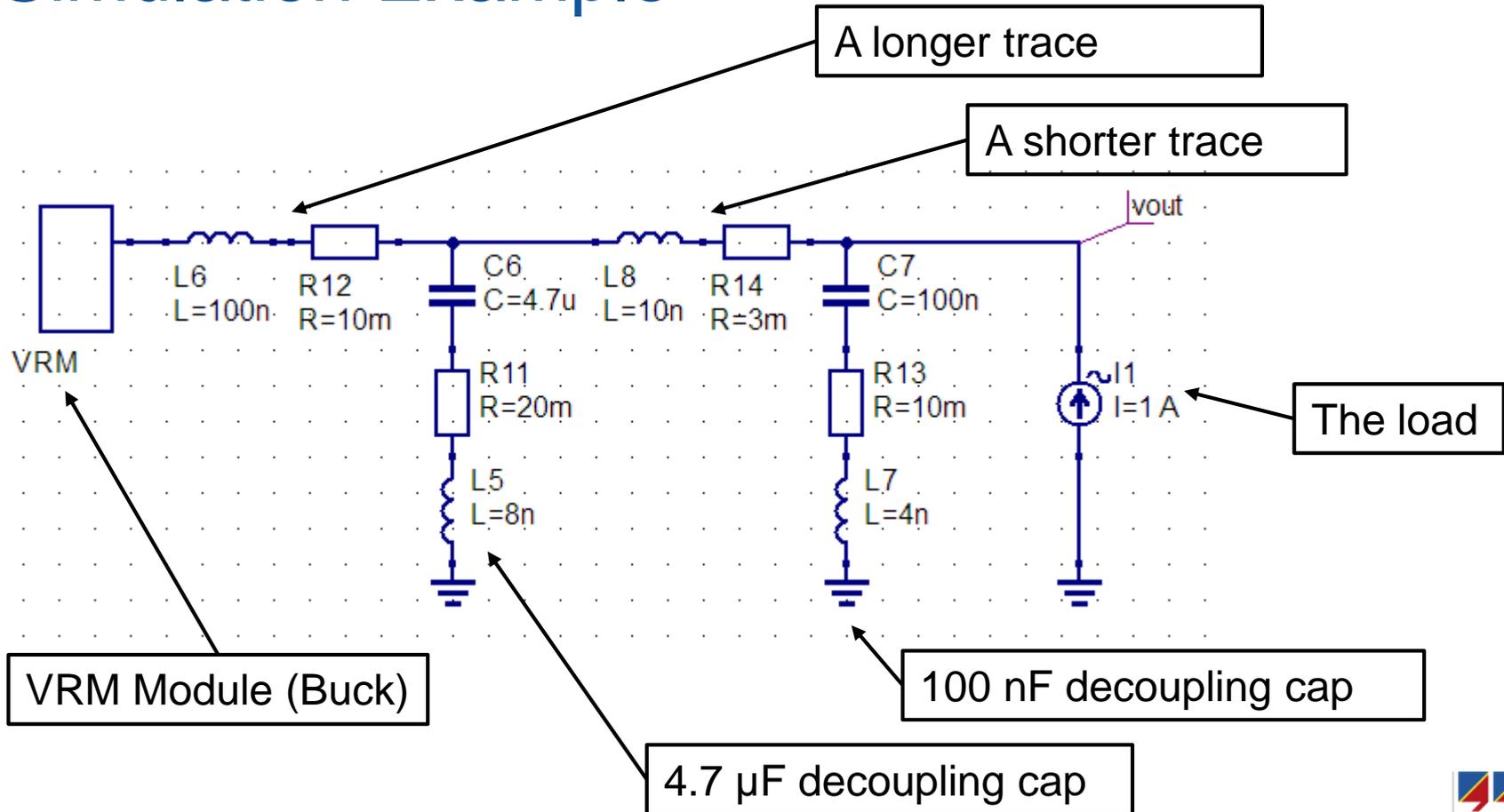

This is what the load sees:

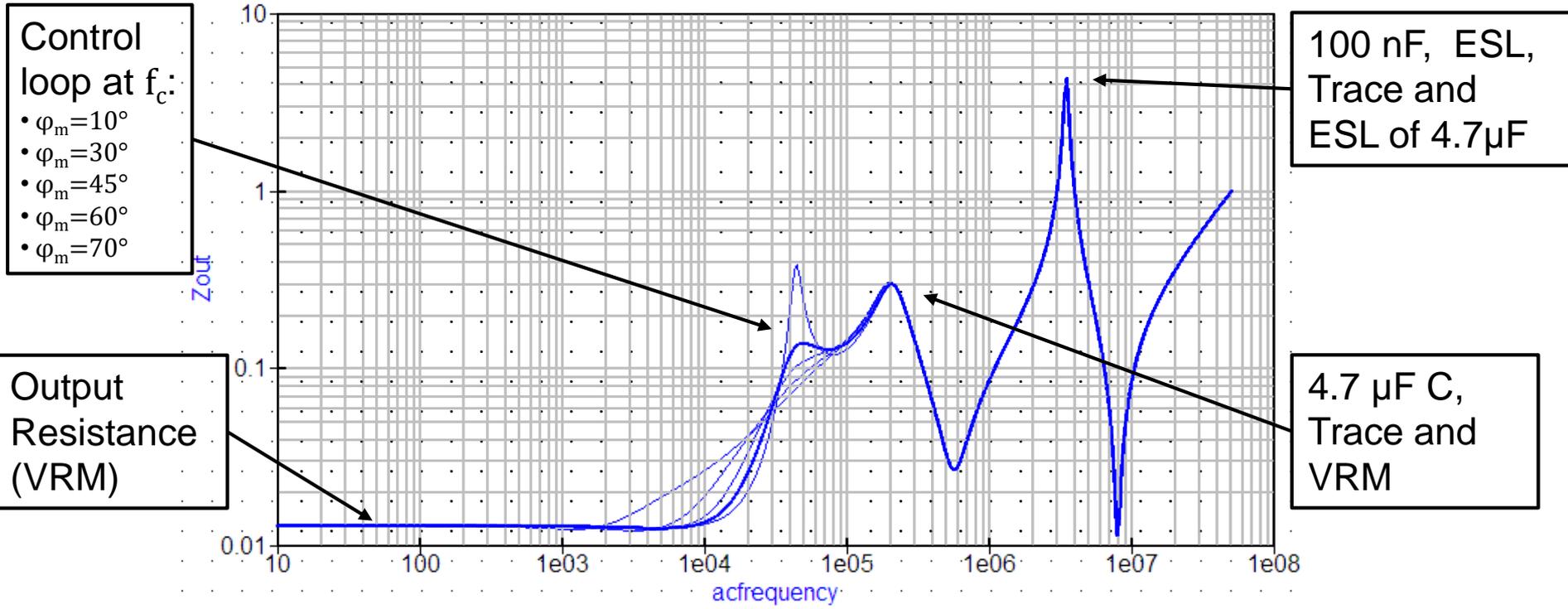


- 200 kHz load current \rightarrow 300 m Ω source impedance
- 3 MHz load current \rightarrow 3 Ω source impedance
- 1 A load current causes 0.3V / 3 V drop

Supply Impedance Peaks

- High impedance increases the risk of coupling noise to the supply voltage ($V = \sqrt{P \cdot R}$)
- Noise on the supply voltage can degrade performance of:
 - Oscillators (Jitter)
 - ADCs
 - Reference voltages
 - Low-Noise amplifiers
 - etc...

Risk of Rogue Waves

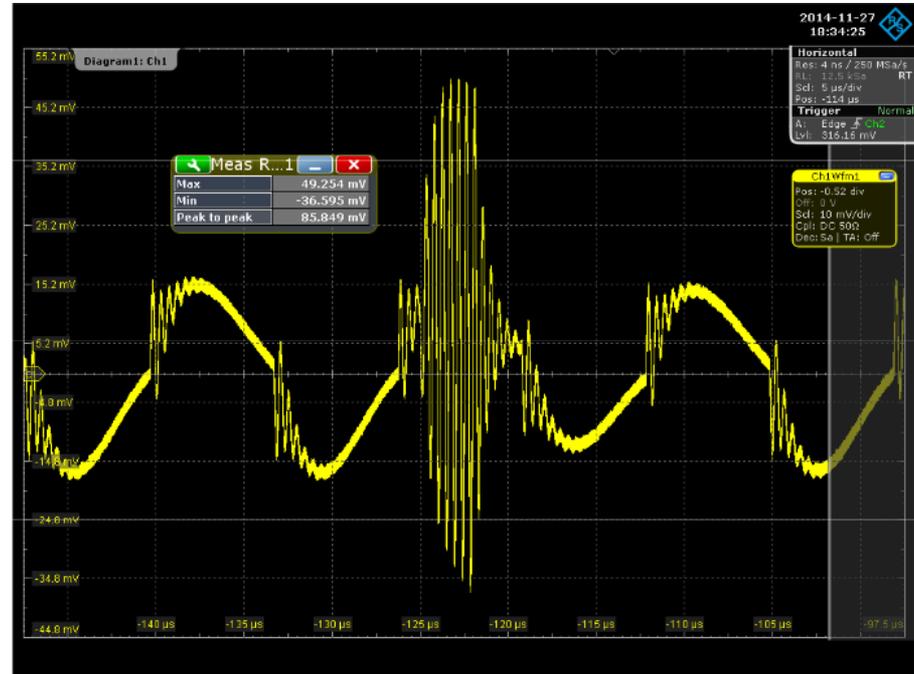
- Dynamic load currents or load current patterns at multiple frequencies can superimpose
- Worst case scenario is a **rogue wave**



The Flat-Impedance Approach



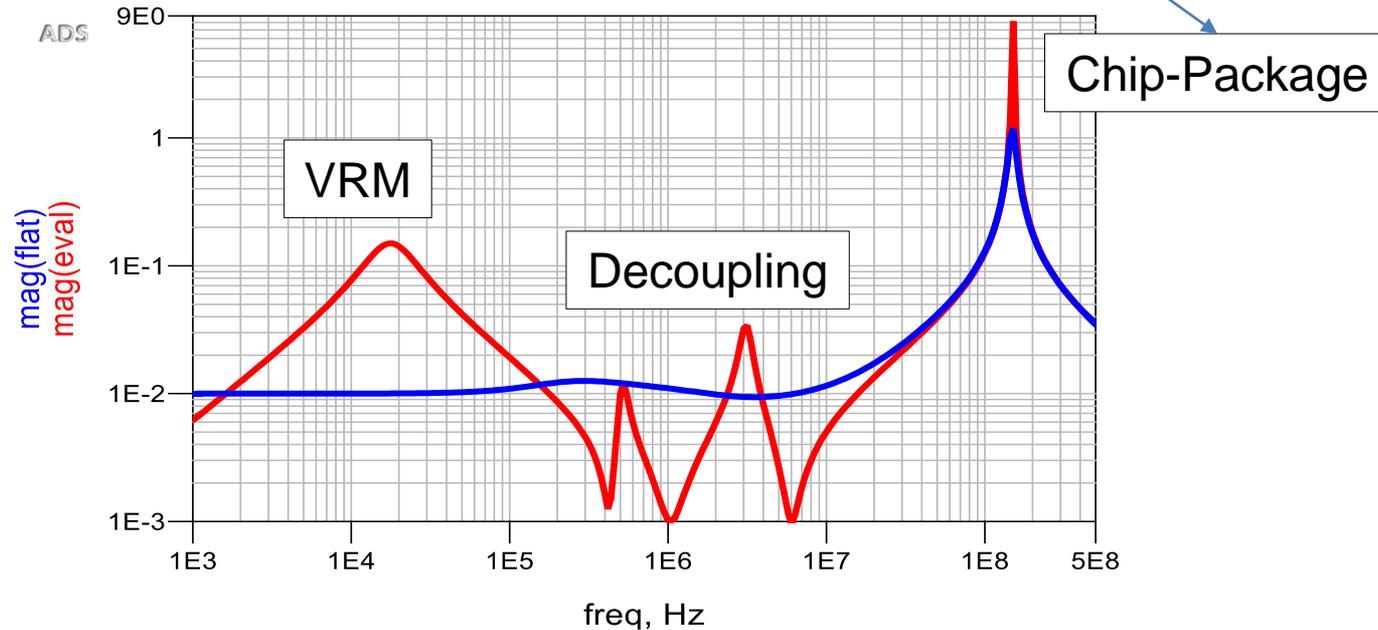- The only reliable way to avoid resonances
- Represents a constant source resistance to the load
- Reduces the height of the “Bandini Mountain”



The Output Impedance Plot

1. Contains information about the stability (oscillation tendency) of the voltage regulator
2. Reveals resonance frequencies of the decoupling network
3. The resonance peaks can cause performance degradation of the supplied load


➤ Let's measure it!
(it sounds more difficult than it is)



Measuring Output Impedance $\leq 3.3\text{VDC}$


- No special precautions needed. Bode 100 Signal Source and $50\ \Omega$ inputs can withstand the voltage.
- Possible Measurement Methods:
 1. One-Port impedance measurement
 2. Shunt-Thru measurement (recommended for very low Z)
 3. J2111A current injector
 4. Alternative load modulation

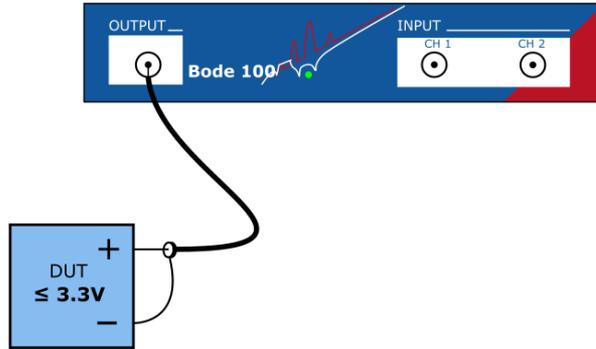Measuring Output Impedance $\leq 3.3\text{VDC}$



One-Port Method:

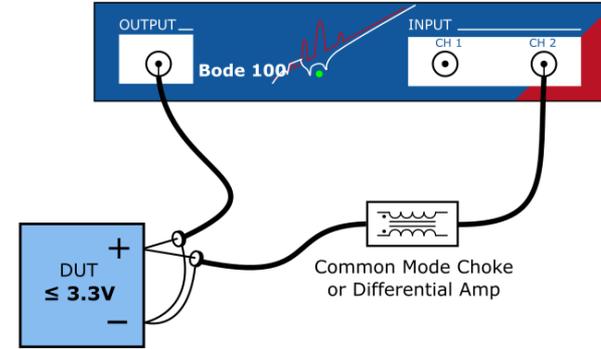- Simplest setup providing quick results
- Not really suitable for $\text{m}\Omega$ measurements



2-Port Shunt-Thru:


- Best suitable for $\text{m}\Omega$ measurements
- Take care of the GND-loop!
- Use amplifier to get more signal

➤ Both methods can also measure OFF-State impedance

Measuring Output Impedance $\leq 42\text{VDC}$


- Bode 100 Signal Source and $50\ \Omega$ must be AC coupled!
- Possible Measurement Methods:
 1. J2111A current injector
 2. One-Port impedance measurement **with DC Block**
Note: Use calibration to remove the impedance of the DC Block
 3. Shunt-Thru measurement with **2 DC Blocks**
Note: Use calibration to remove the impedance of the DC Block
 4. Shunt-Thru measurement with series-resistance
Note: Use thru-calibration to remove the resistor influence
 5. Alternative load modulation

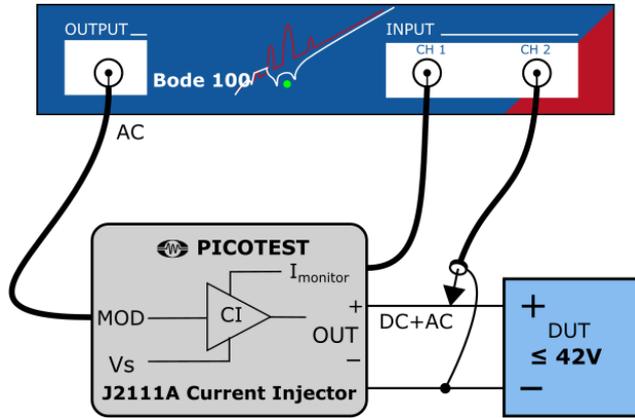Measuring Output Impedance $\leq 42\text{VDC}$



Current Injector:

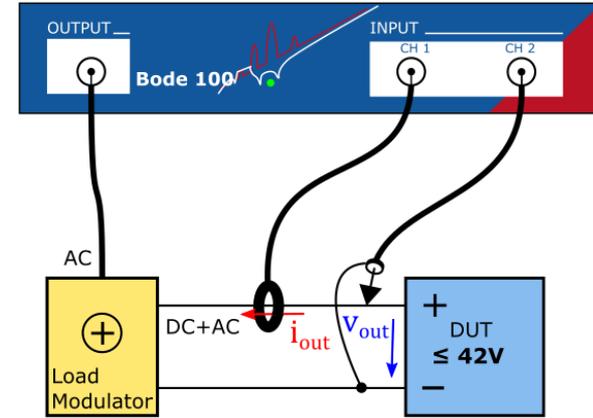- Simple setup
- Sinks 25 mA DC load current + AC current (10mA/V)




Dynamic Load:


- AC or AC+DC current
- Current probe & voltage probe

Measuring Output Impedance $\geq 42\text{VDC}$

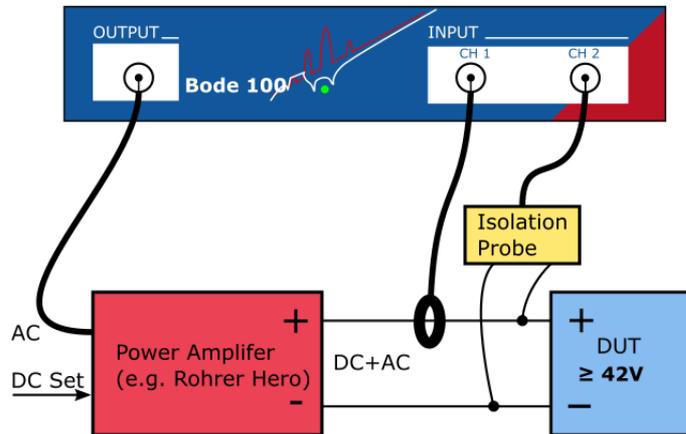- Bode 100 must be protected from high voltages!
- Possible Measurement Methods:
Voltage/Current method using a power amplifier




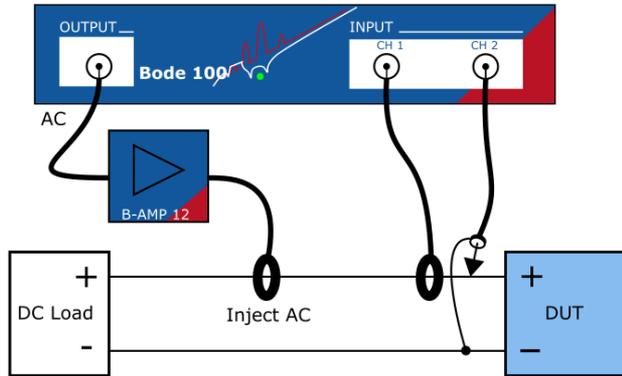Alternative Load Modulation Possibilities



Inductive injection


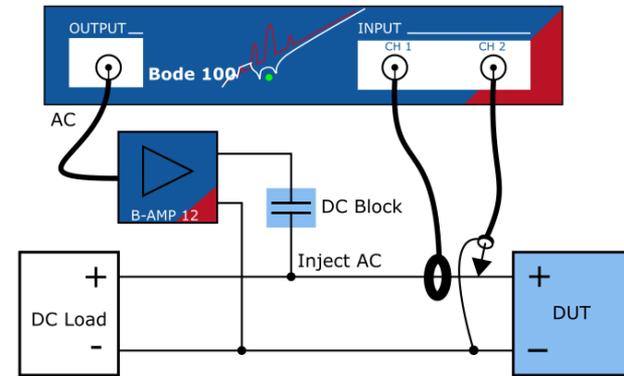
- Provides galvanic isolation
- Requires big transformer that does not saturate at DC
- Use an amplifier to get more signal




Capacitive injection

- Requires big capacitor at low frequencies
- Use amplifier to get more signal

Hands-On Example VRTS 1.5

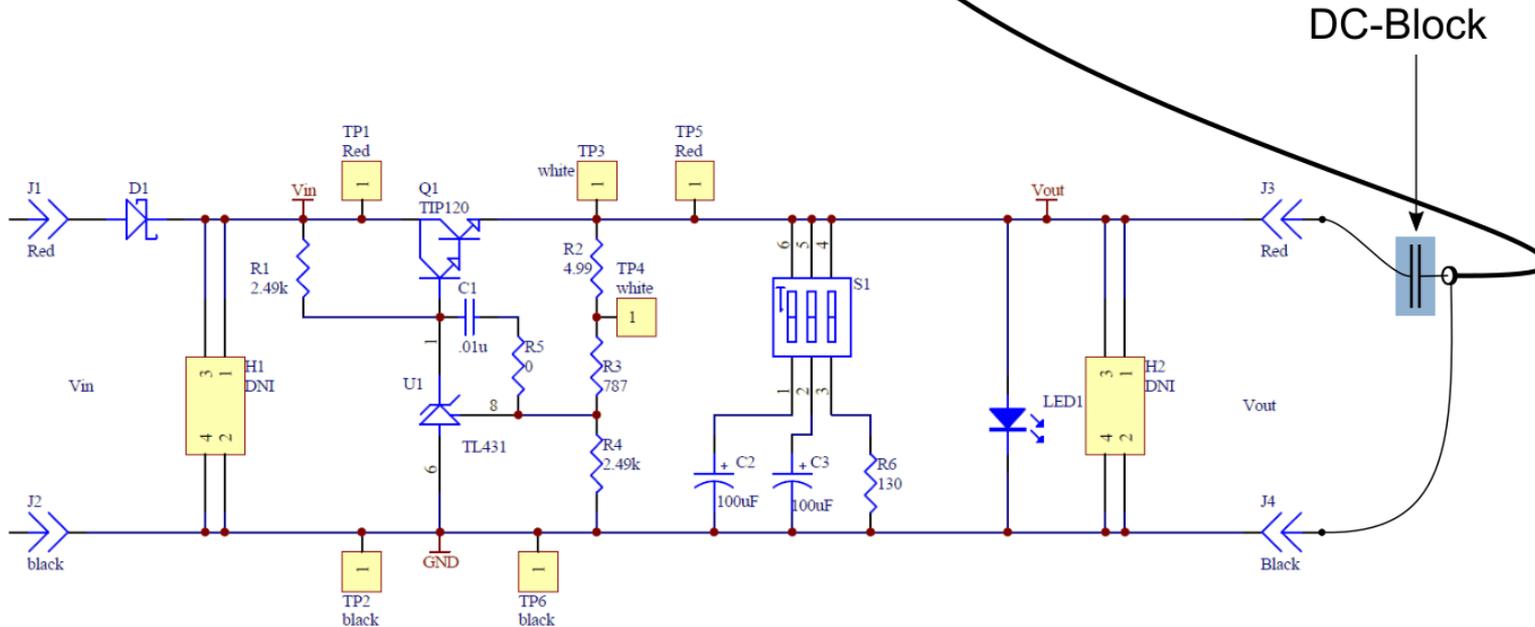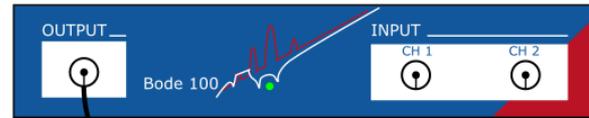

Hands-On Example SEPIC

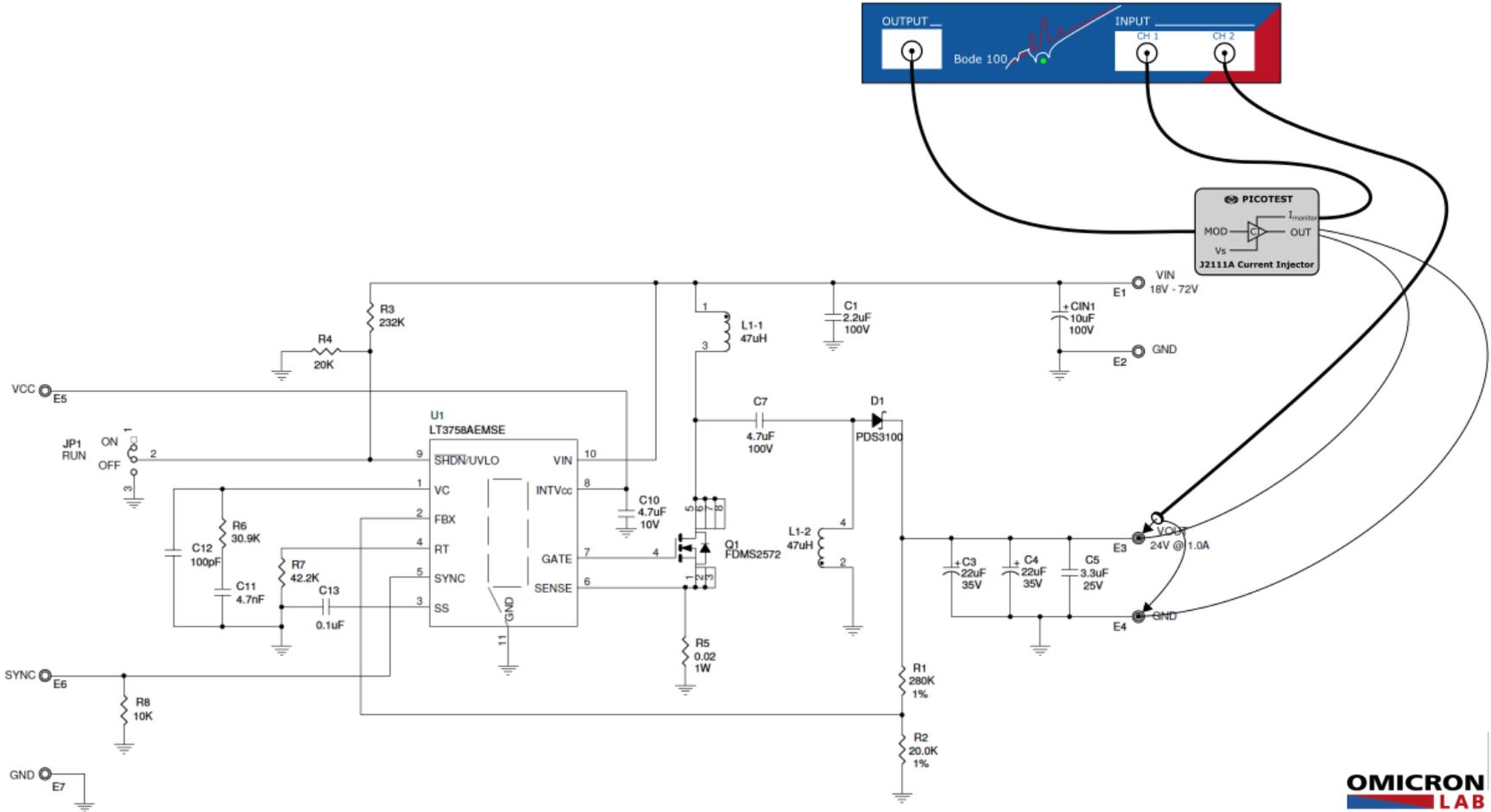

System-Example: USB Scope



CH1

CH2

ADC


LDO

61053712


QC
03

012-05573BH

ADC Power Supply

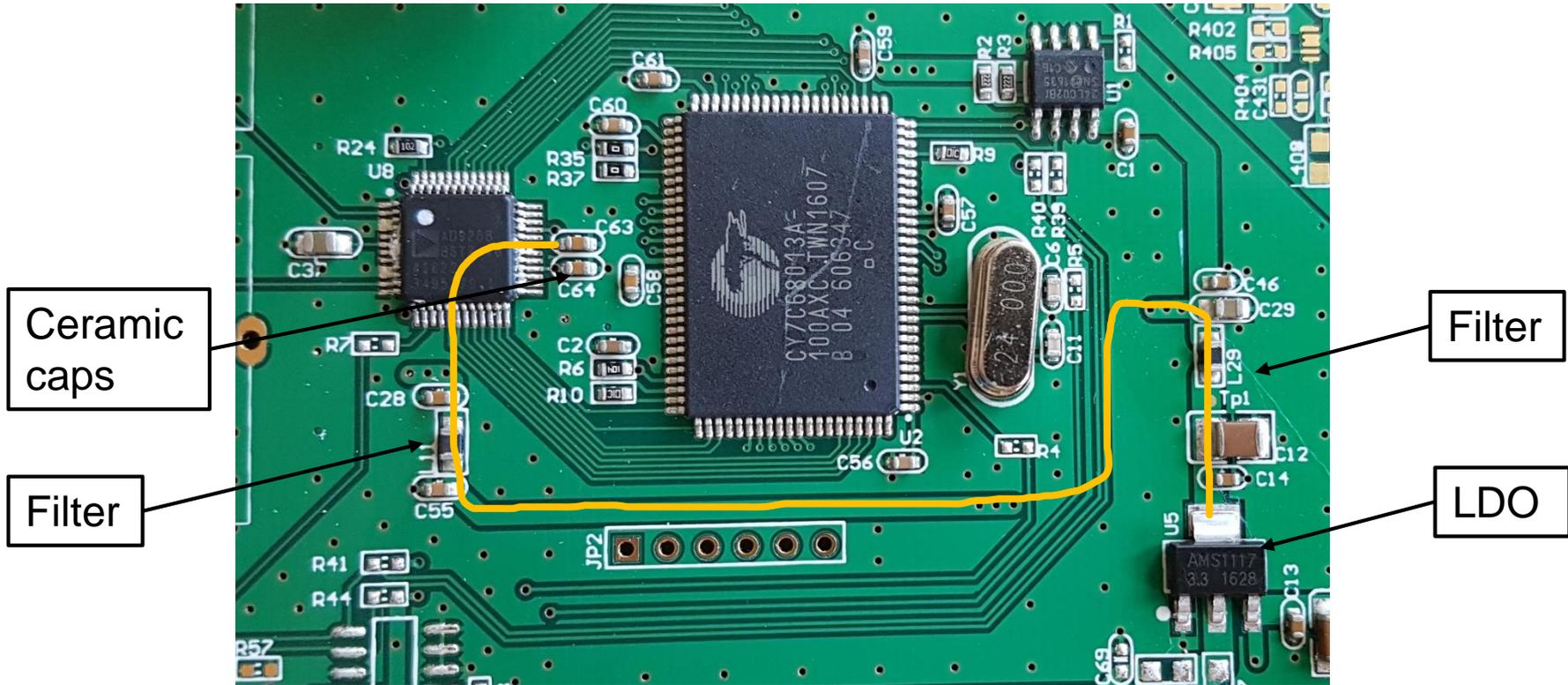



Measuring Supply Output Impedance

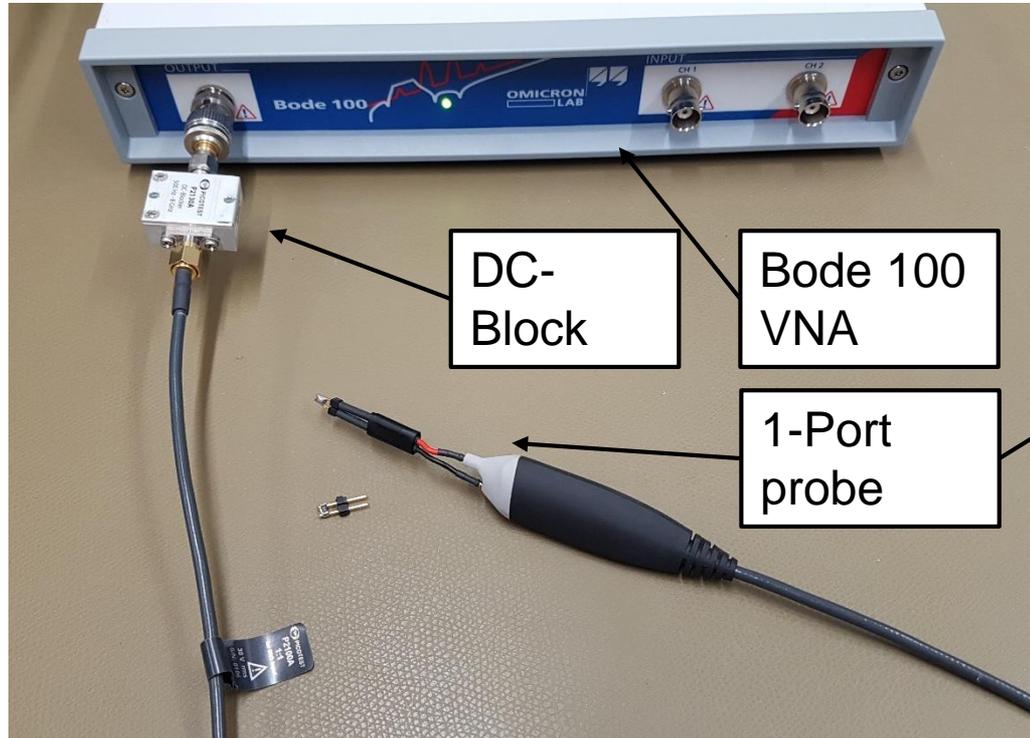


Measurement Result

High resonance peak at 300...400 kHz
Caused by SMC ferrite and ceramic caps.

Trace 1: Impedance Magnitude (Ω)

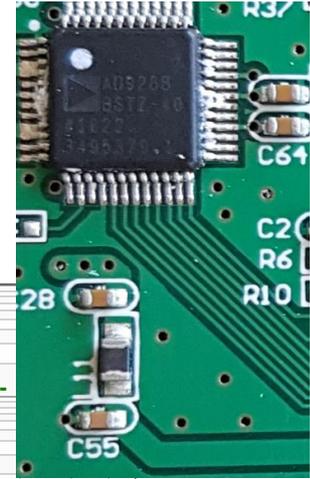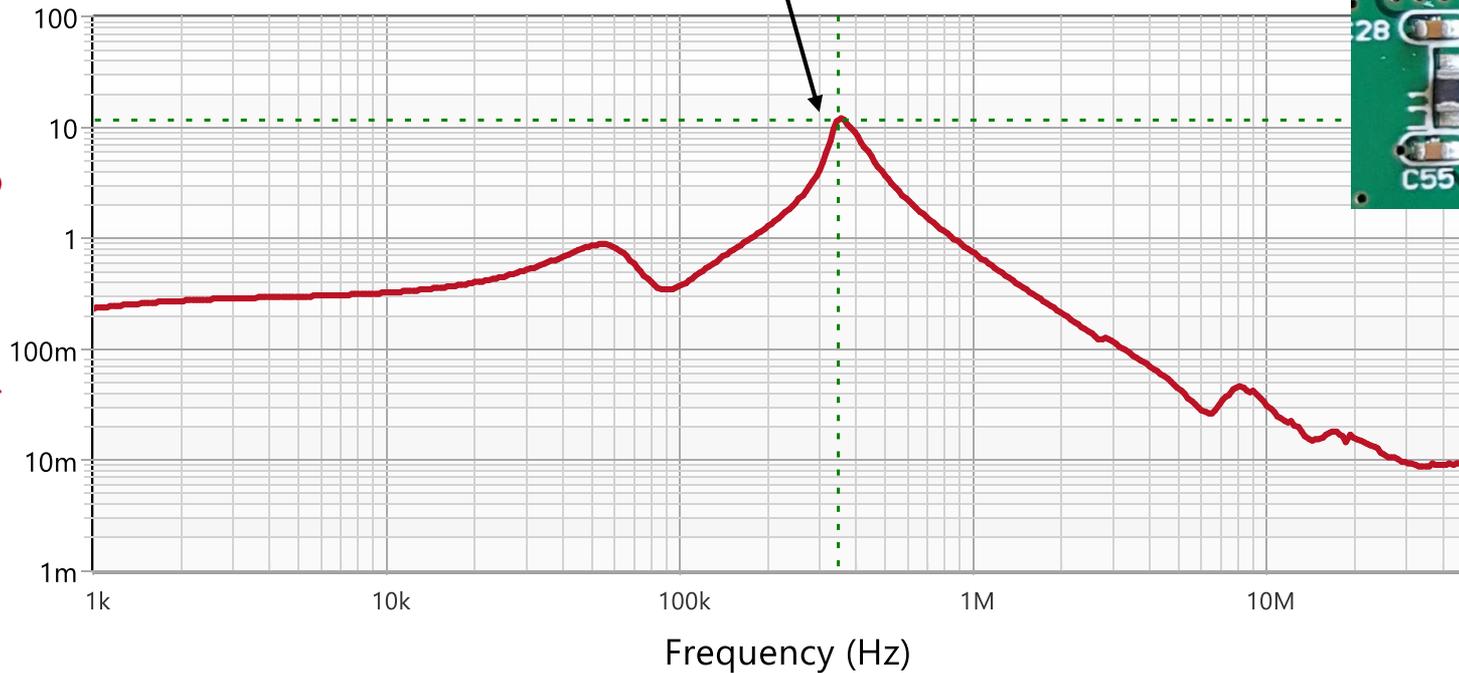


400 kHz Disturbance (inductively coupled)

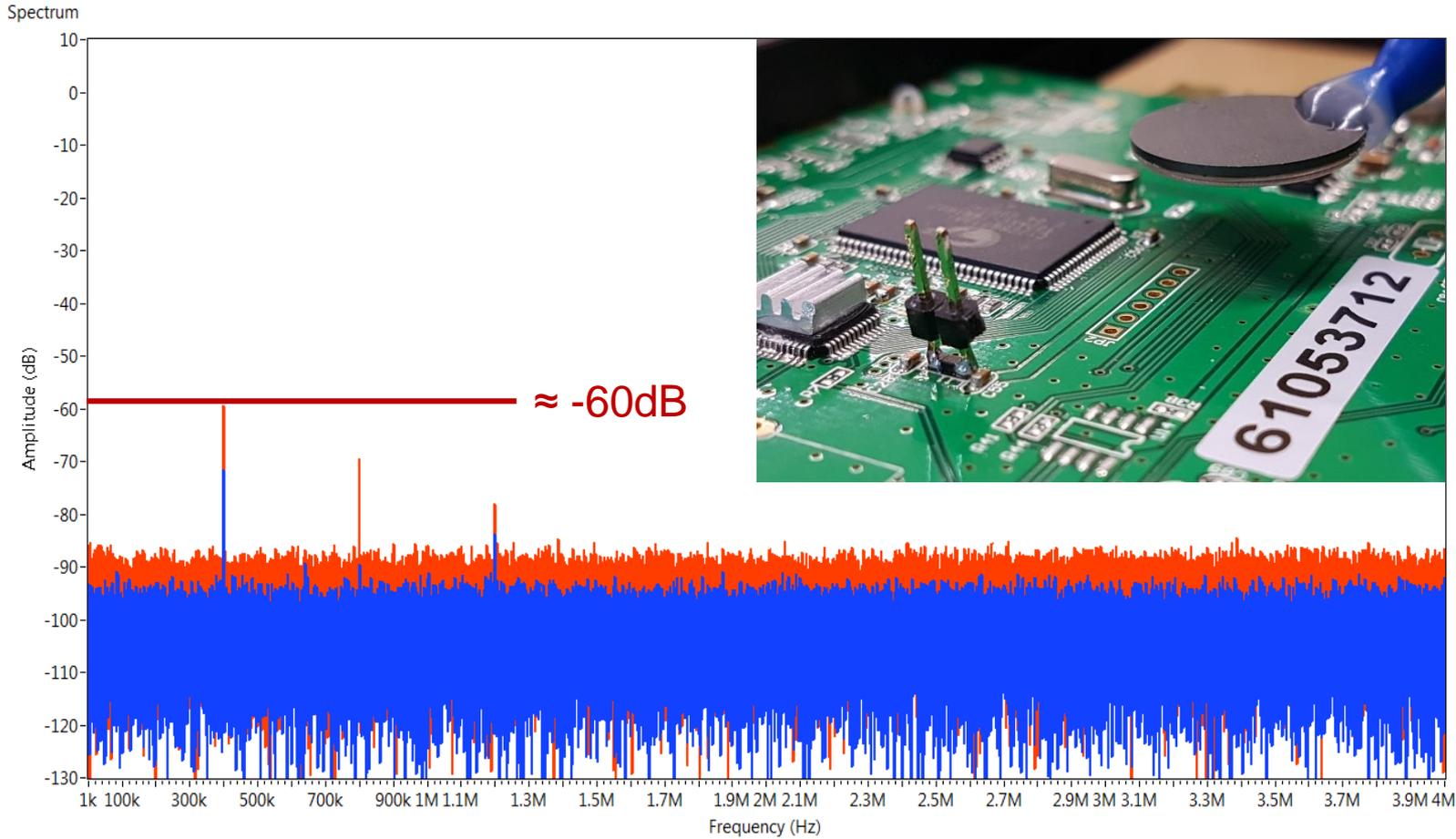


CH1
CH2



Shorting the Ferrite Bead

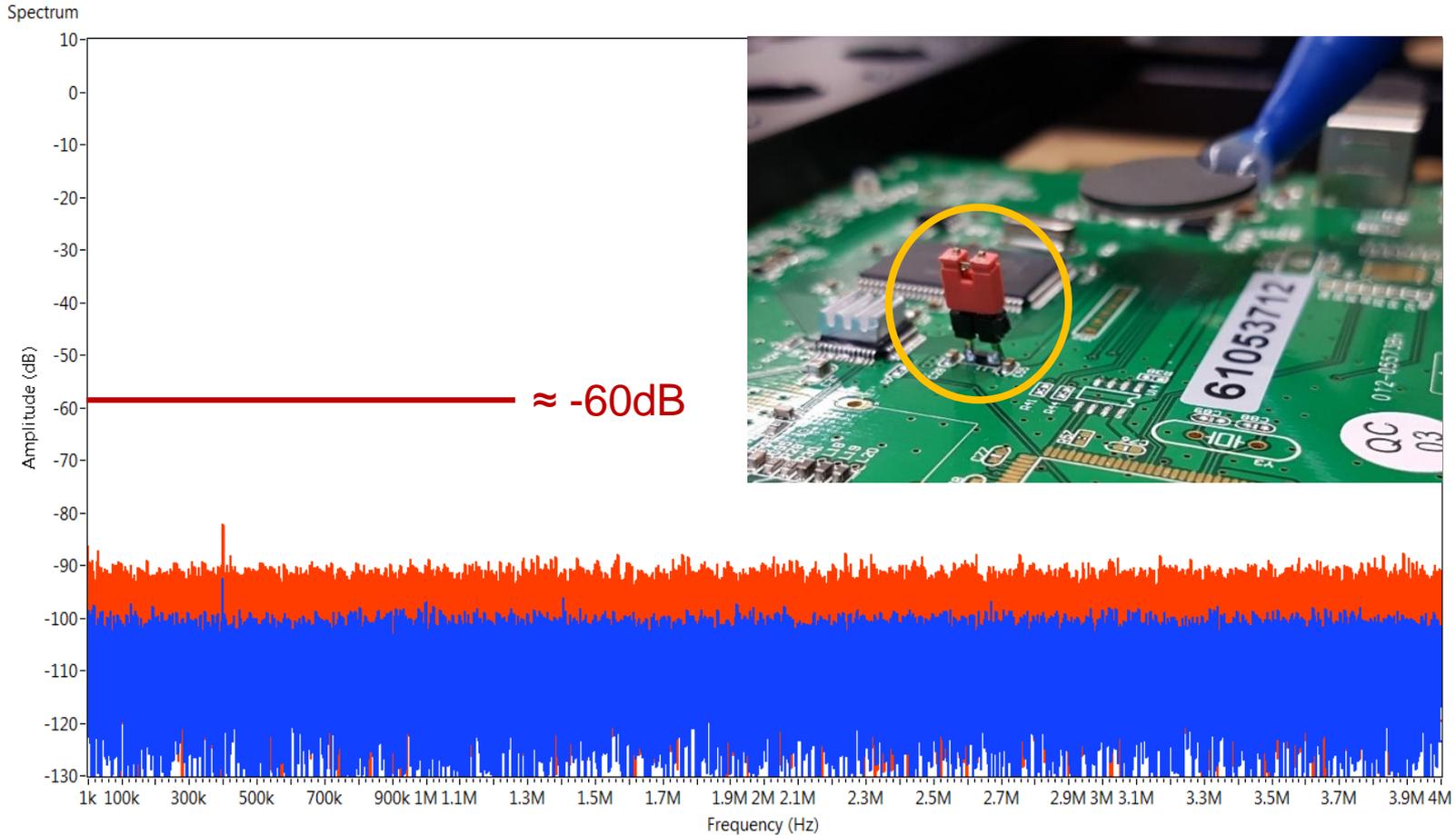

What has Changed in Output Impedance?

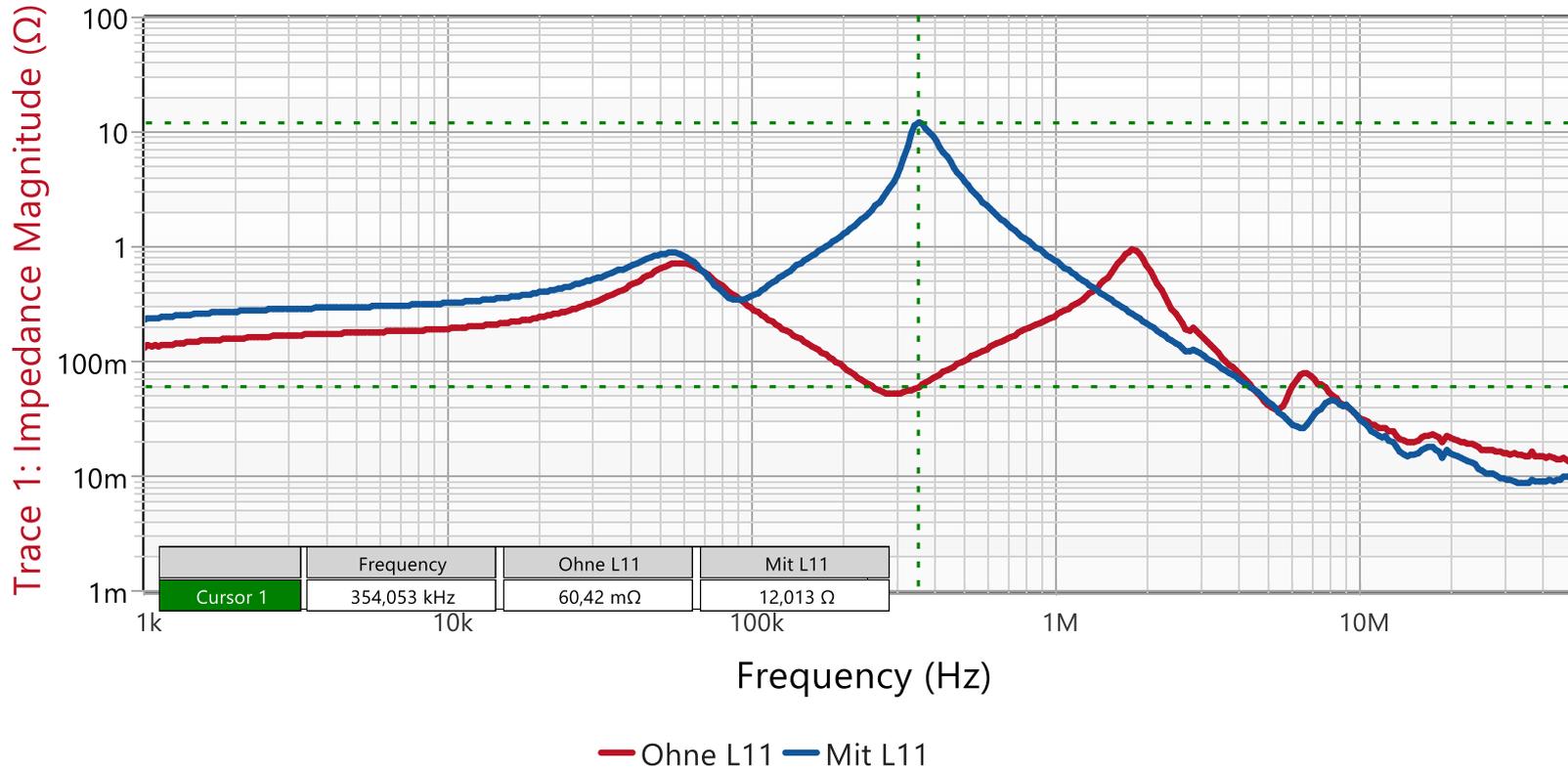

Summary

- Output impedance reveals information about
 - Control loop stability
 - Resonance frequencies in the supply line
- Measuring output impedance is simple
 - The output capacitors are nearly always accessible
 - The control loop must not be broken
- A flat impedance guarantees optimum damping at all frequencies
- Lower output impedance results in less noise

References and further information:

- [1] R. W. Erickson and D. Maksimovic, *Fundamentals of Power Electronics*, 2nd ed. 2001. Norwell, Mass: Springer, 2001.
- [2] Sandler, S., *The inductive nature of voltage-control loops*, EDN (www.edn.com), 2015.
- [3] Sandler, S., *Designing Power for Sensitive Circuits*, EDICon, 2017
- [4] Sandler, S., *Target Impedance and Rogue Waves*, DesignCon, 2016
- [5] Sandler, S., *Power Integrity*, Mc Graw Hill Education Ltd, 2014
- [6] Yuri Panov and Milan Jovanovic, *Practical Issues of Input/Output Impedance Measurements in Switching Power Supplies and Application of Measured Data to Stability Analysis*, Delta Power Electronics Laboratory



Feel free to ask questions via the Q&A function...

If time runs out, please send us an e-mail and we will follow up.
You can contact us at: info@omicron-lab.com

Thank you for your attention!