



Bode 100 as Impedance Analyzer

OMICRON Lab Webinar Series 2020

2020-05-05

Webinar Hints

Open the Q&A function



The screenshot shows a webinar interface. On the left, a slide displays an OMICRON LAB Bode 100 device. The slide text reads: "We will record the presentation such that you can view it again later", "OMICRON Lab Webinar Series 2020", and "2020". The OMICRON LAB logo is in the bottom right of the slide. On the right, a video feed shows two men, with the host labeled "Tobias-Schuster (Host)". A Q&A panel is open, showing "All (0)" questions and a form to ask a question. The form includes a dropdown menu set to "All Panelists" and a "Send" button. A blue callout bubble points to the Q&A panel with the text "Send questions to the presenters".

We will record the presentation such that you can view it again later

OMICRON Lab Webinar Series 2020

2020

OMICRON LAB

Q&A

All (0)

Ask: All Panelists


Select a panelist in the Ask menu first and then type your question here.

Send

Send questions to the presenters


Florian Hämmerle

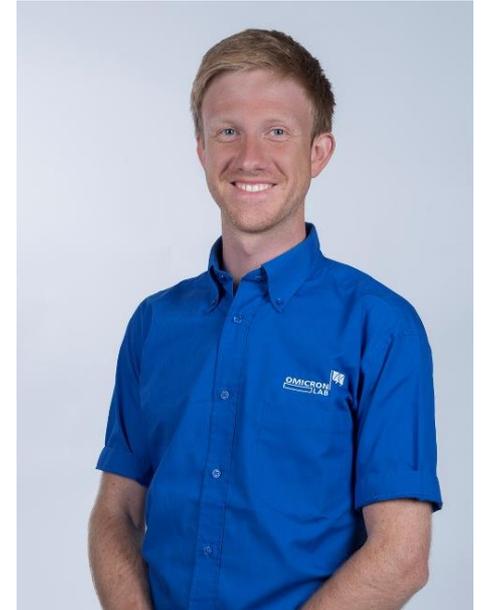- Studied Mechatronics at Vorarlberg University of Applied Sciences
- Working at OMICRON Lab since 2010 in:
 - Technical Support & Applications
 - Product management
- Contact:
 - florian.haemmerle@omicron-lab.com
 - <https://meet-omicron.webex.com/meet/florian.haemmerle>




Tobias Schuster

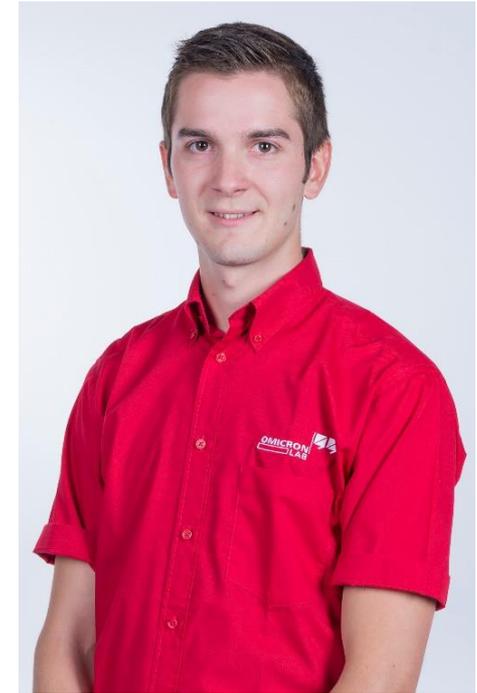- Completed electrical engineering college in 2013
- Studied Industrial Engineering and Management
- Working at OMICRON Lab since 2015 focusing on:
 - Technical Support
 - Applications
 - Sales
- Contact:
 - tobias.schuster@omicron-lab.com
 - <https://meet-omicron.webex.com/meet/tobias.schuster>



Agenda

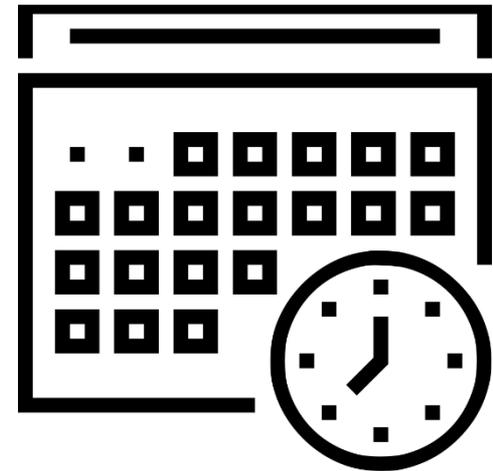- Passive components & equivalent circuits
- Bode 100 impedance measurement methods
- Calibration (user- & full-range)
- Why is it important to measure Cs
 - Live comparison measurement
- Why should we measure Ls
 - Live comparison measurement
 - Leakage inductance
- Additional hands-on live measurements



Passive Components

- Essential parts in analog circuits
- Inductor and capacitor used e.g. to store energy or to create filter circuits



$$\text{Inductor: } v(t) = L \frac{di(t)}{dt} \quad X_L = \omega L \quad \frac{V}{I} = Z_L = j\omega L$$



$$\text{Capacitor: } i(t) = C \frac{dv(t)}{dt} \quad X_C = \frac{-1}{\omega C} \quad \frac{V}{I} = Z_C = \frac{1}{j\omega C}$$

Theory and Reality

- Theoretically inductor and capacitor are purely **reactive** elements → No resistive behavior and therefore **lossless**
- In reality **parasitics** can strongly influence the real behavior especially at higher frequencies

Examples:

Inductor:

- Wire has resistance
- Windings form electric field
- Core is not lossless



Capacitor:


- Plates are resistive
- Rolling of foils creates inductance
- Insulator not lossless




Equivalent Circuits

- Are used to model the real behavior of the components
- Different complexity of models
 - 1st order models are valid at one particular frequency
 - Fixed Frequency measurement shows R, L and C at one frequency


Series equivalent circuit

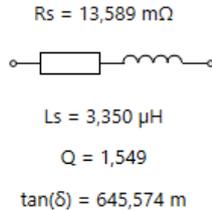

Parallel equivalent circuit

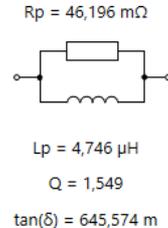

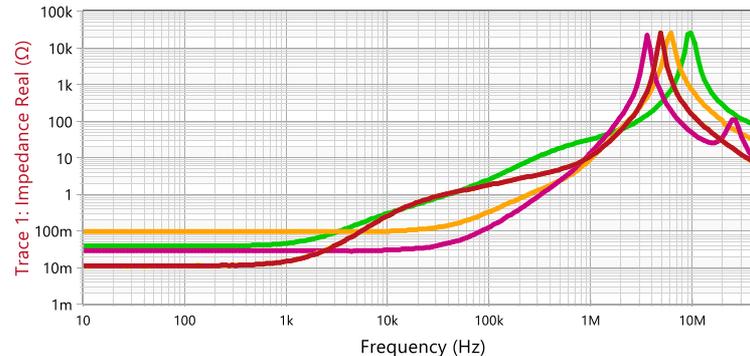- Frequency Sweep calculates R, L and C over frequency




Equivalent Circuits



- Higher complexity models are valid for a frequency range
 - 2nd Order equivalent circuits for inductor and capacitor



≅

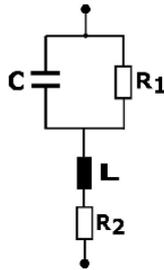

≅

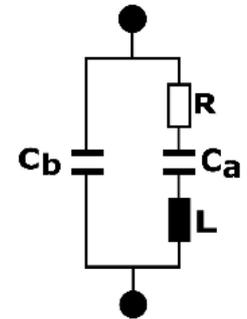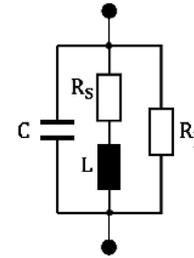

- 3rd Order models (e.g. quartz crystal or piezo element)

see Application Note:



Equivalent Circuit Analysis of Quartz Crystals


<https://www.omicron-lab.com/application-notes/>

- Parameter identification requires manual work or e.g. curve-fitting procedure


Bode 100 Impedance Measurement Methods

- One-Port Reflection
- Impedance Adapter (3-port technique)
- Shunt-Thru (2-port technique)
- Shunt-Thru with series resistance (similar to Shunt-Thru)
- Series-Thru (2-port technique)
- Voltage-Current Gain (3-port technique)
- External bridge (e.g. high impedance bridge)

Impedance Range Overview

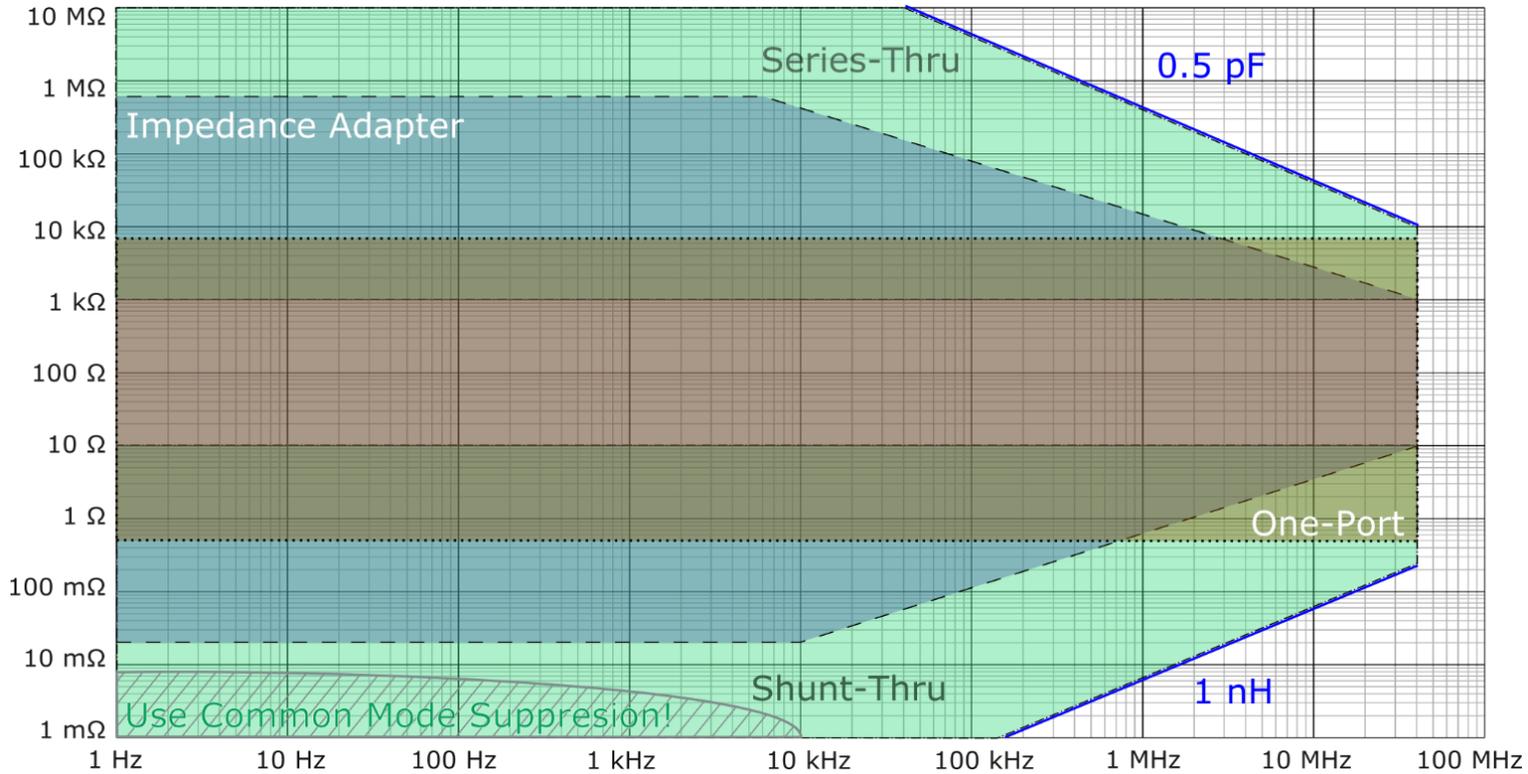

One-Port

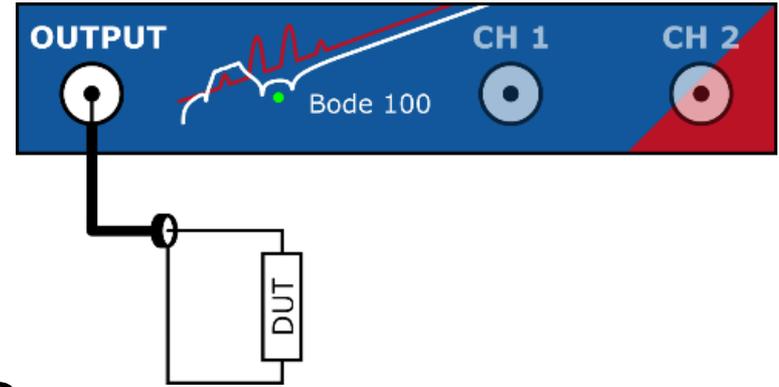

- Optimum range $\approx 0.5 \Omega - 10 \text{ k}\Omega$
- Impedance/Reflection measurement at the output port
- One point is GND
- Can be calibrated with Open/Short/Load (O/S/L)

One-Port (Measurement Setup)

- Solder to BNC connector




One-Port (Measurement Setup)


- Use BNC to 4 mm adapter



Impedance Adapter

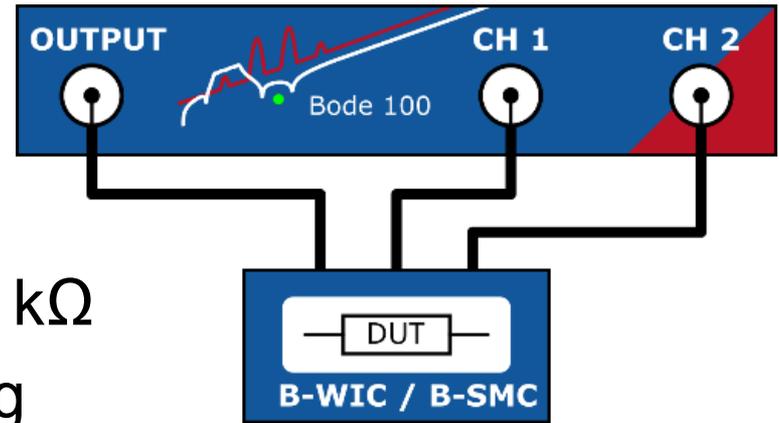

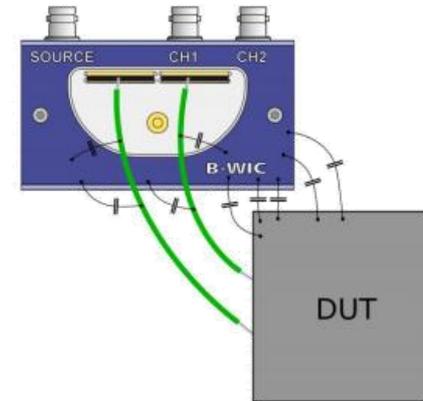
- Optimum range $\approx 20 \text{ m}\Omega - 600 \text{ k}\Omega$
- Impedance measurement using the impedance adapters B-WIC or B-SMC
- DUT must not be connected to GND
- Must be calibrated with O/S/L
- Not for physically big components or long leads



Impedance Adapter (Measurement Setup)




Shunt-Thru

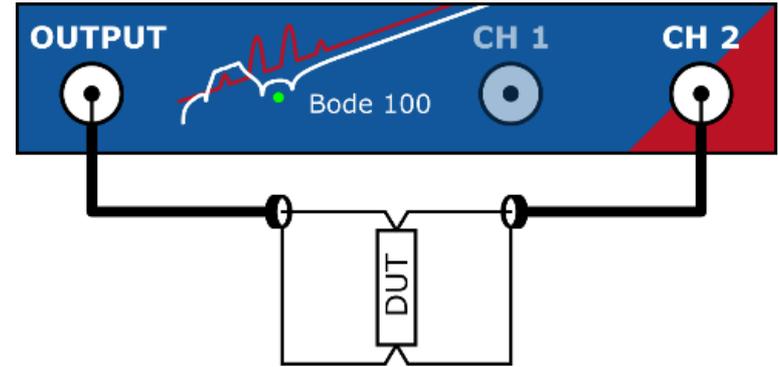

- Optimum range $\approx 1 \text{ m}\Omega - 100 \Omega$
- Measure impedance using a 2 port shunt-thru setup in the 50Ω system
- One point is GND
- Can be calibrated with Thru or O/S/L
- Attention: Ground-loop!


Shunt-Thru (Measurement Setup)

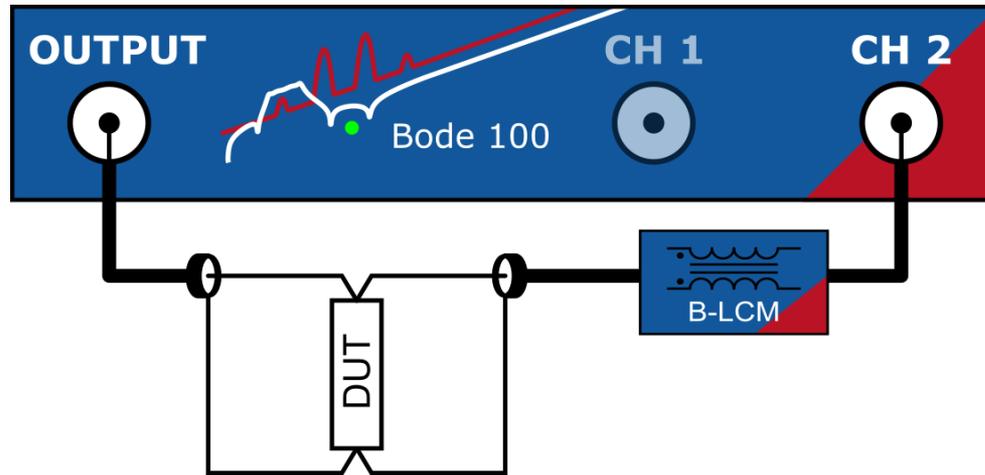- with the B-LCM to suppress ground-loop error at low frequencies (< 10 kHz to 100 kHz)




Shunt-Thru (Measurement Setup)

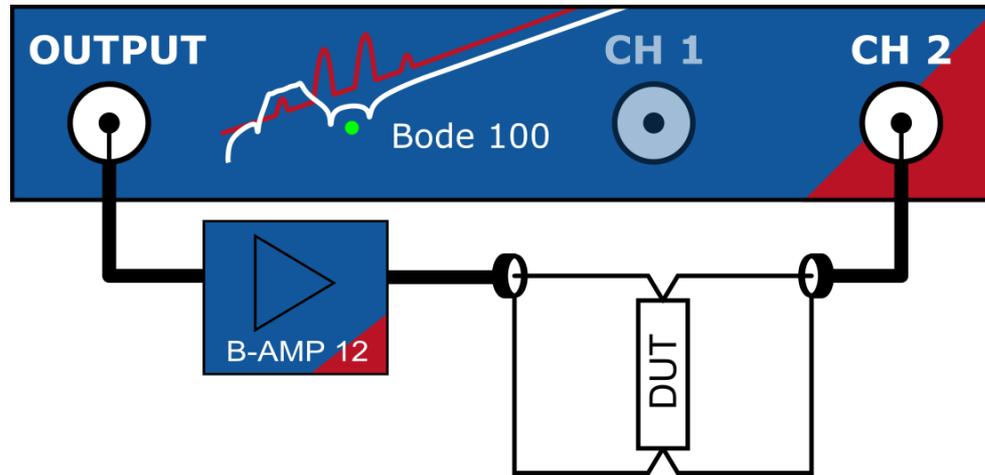- with the B-AMP 12 to amplify the output signal of the Bode 100 up to 25 dBm





Shunt-Thru (Measurement Setup)

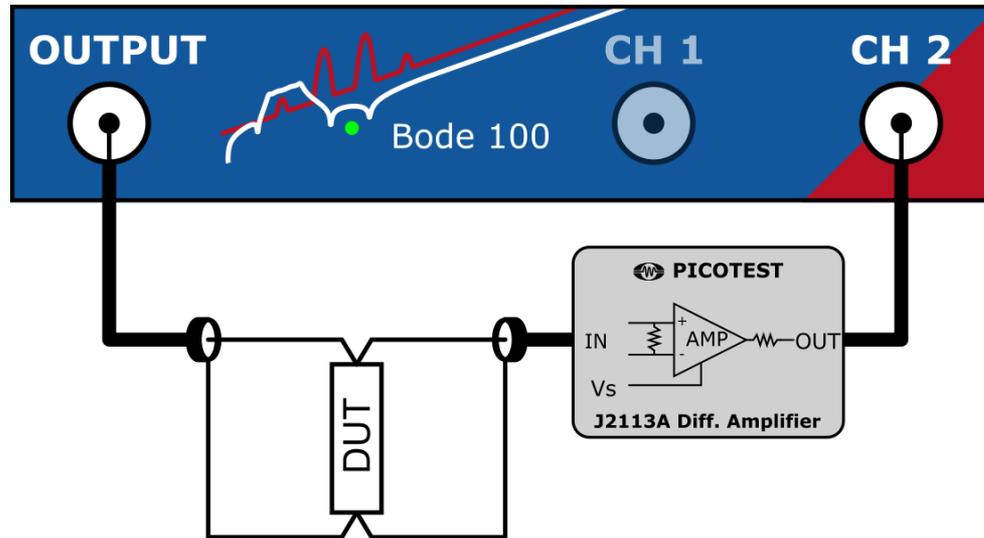- with the Picotest J2113A differential amplifier to suppress ground-loop error at low frequencies




Shunt-Thru (Measurement Setup)

- with B-AMP12 and B-LCM

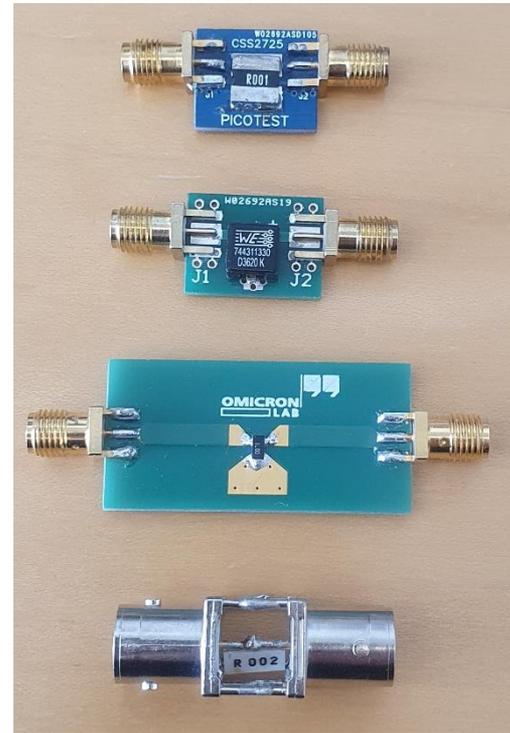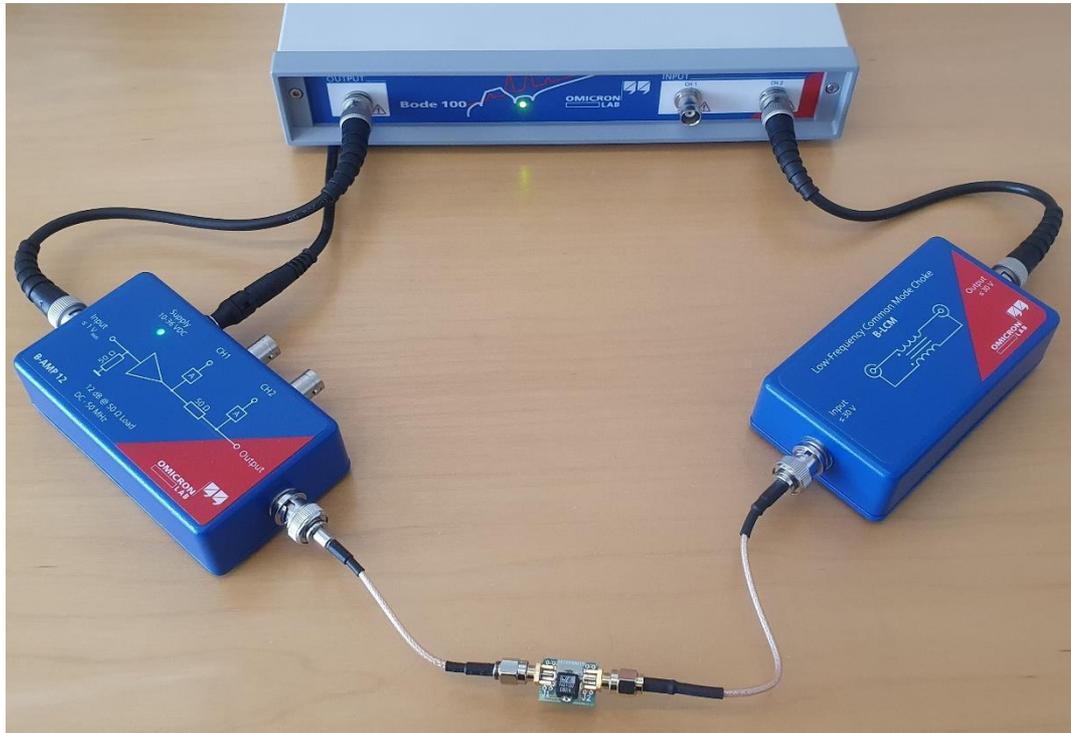

Shunt-Thru with series resistance

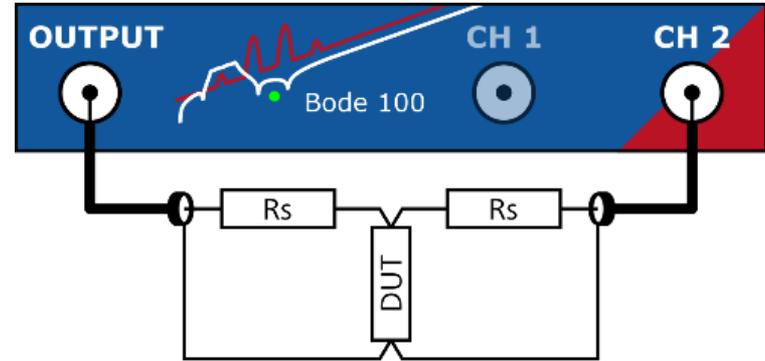

- Optimum range depends on series resistors


$R_s = 200 \Omega$ \rightarrow $5 \text{ m}\Omega - 1125 \Omega$

$R_s = 499 \Omega$ \rightarrow $11 \text{ m}\Omega - 2480 \Omega$


- One point is GND
- Must be calibrated
- Higher DC voltages possible
- Attention: Ground-loop!

Shunt-Thru with series resistance (Measurement Setup)

- using Picotest PITK01 boards

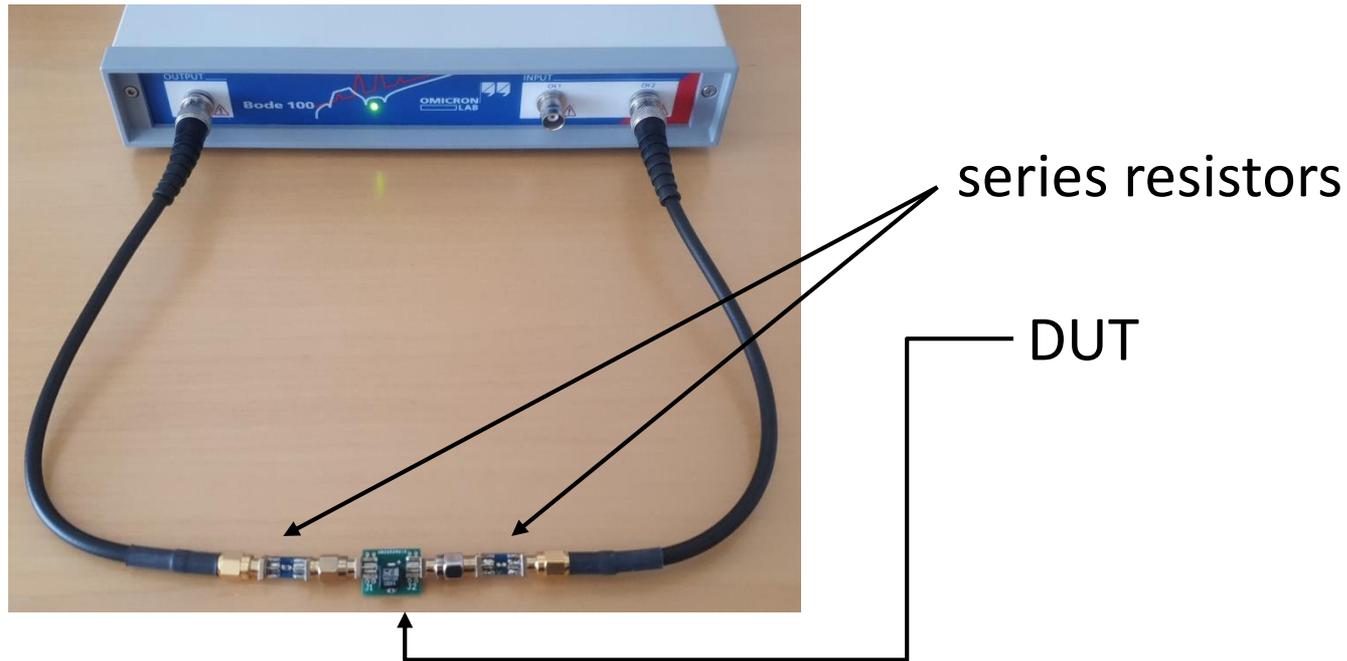



Series-Thru

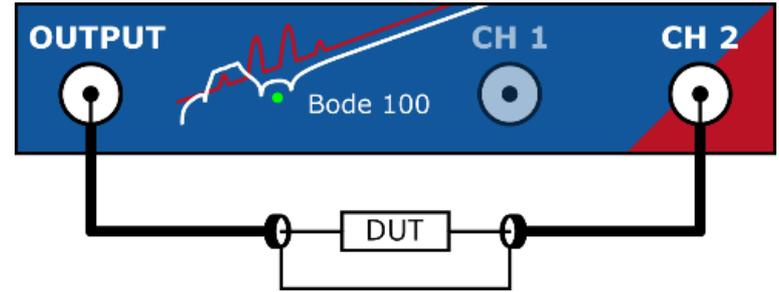


- Optimum range $\approx 1 \text{ k}\Omega - 1 \text{ M}\Omega$
- Measure impedance using a 2 port series-thru setup in the 50Ω system
- DUT must not be connected to GND
- Can be calibrated with Thru or O/S/L

Series-Thru (Measurement Setup)

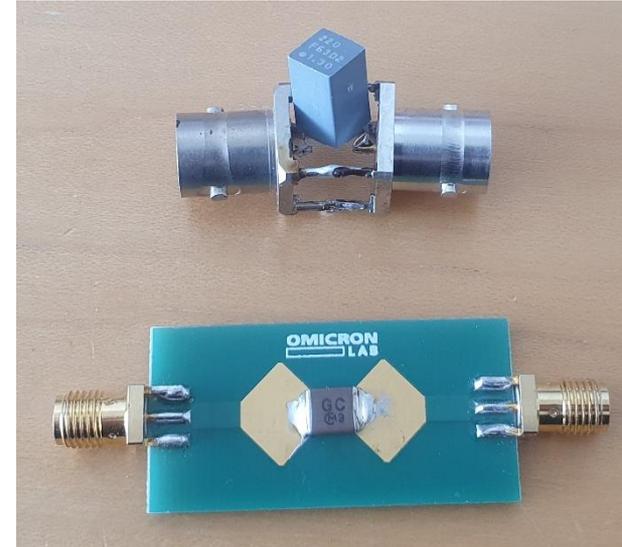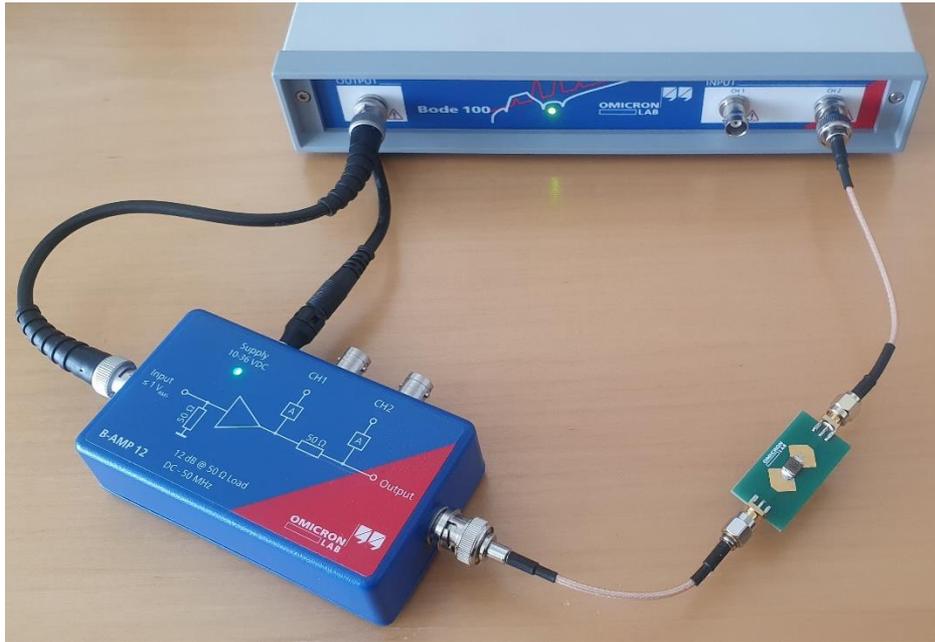- with the B-AMP 12 to amplify the output signal of the Bode 100 up to 25 dBm




Voltage / Current

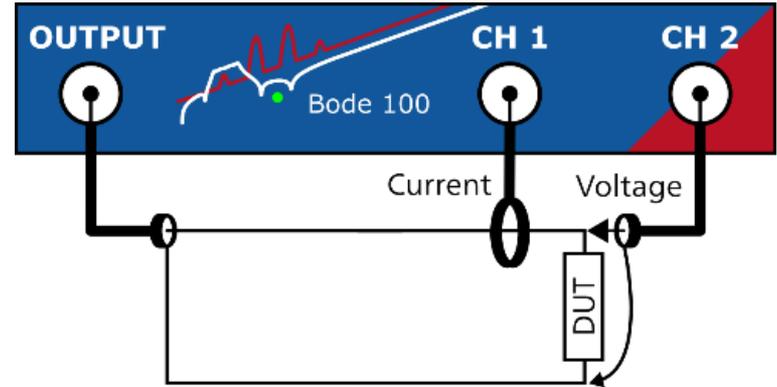


- Range depends on probes
- Measure impedance by using a voltage probe at CH2 and a current probe at CH1
- Can be calibrated with Thru or O/S/L

Voltage / Current (Measurement Setup)

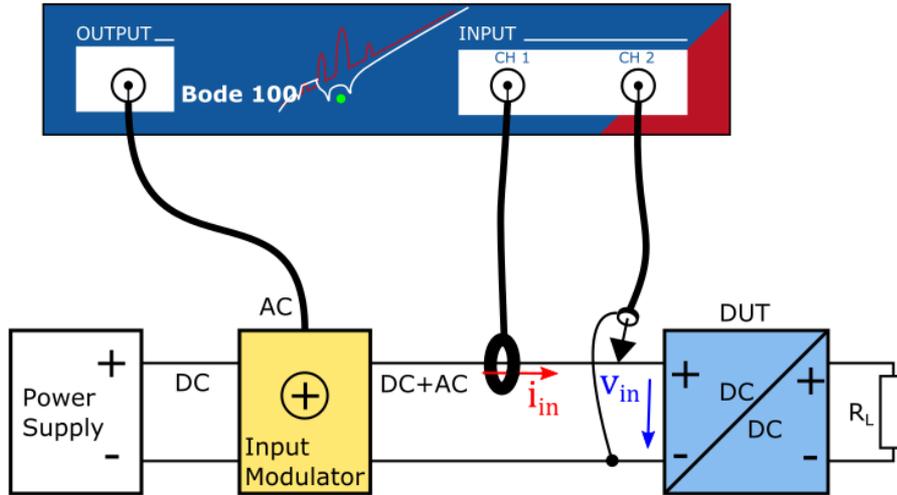- e.g. for input or output impedance measurement




External Bridge

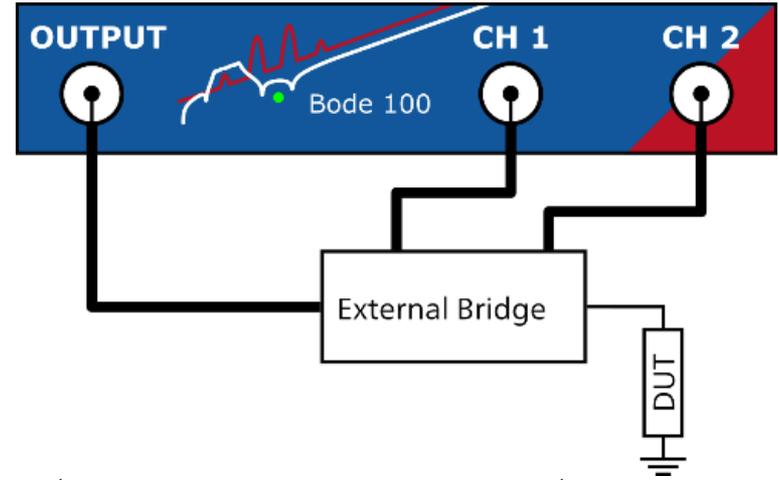

- Range is variable
- Measure impedance using a custom measurement bridge
- Must be calibrated with O/S/L

External Bridge (Measurement Setup)

- high impedance bridge

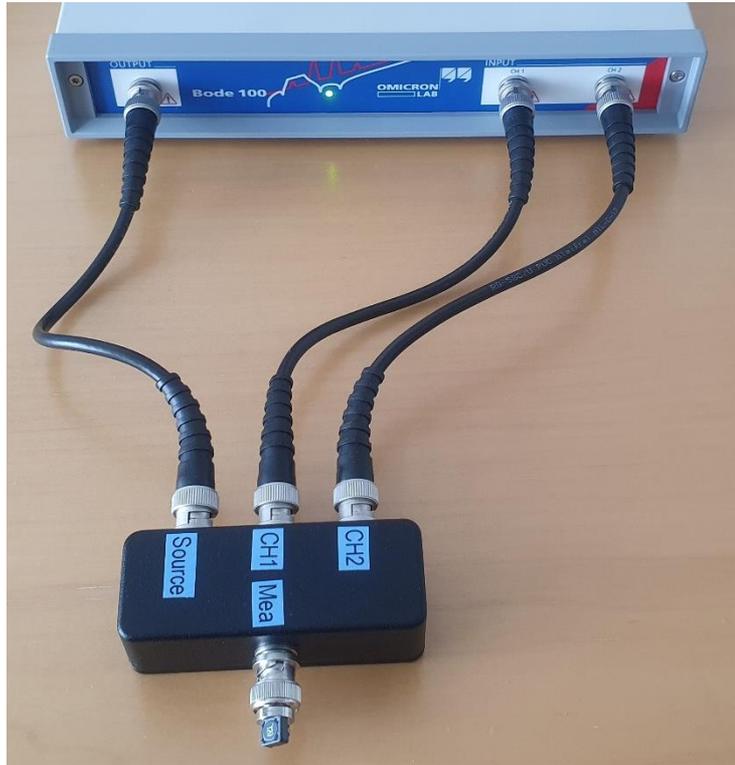


User-Range / Full-Range Calibration

- User Range Calibration

Calibrates at exactly the frequencies that are currently measured

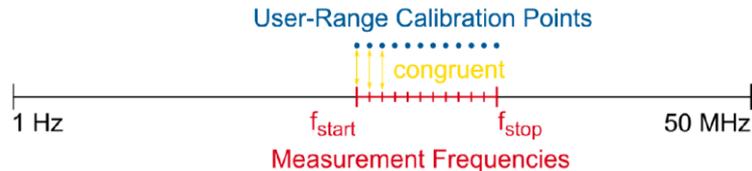
+ No interpolation → suitable for narrowband probes



- Full-Range Calibration


calibrates at pre-defined frequencies and interpolates in-between

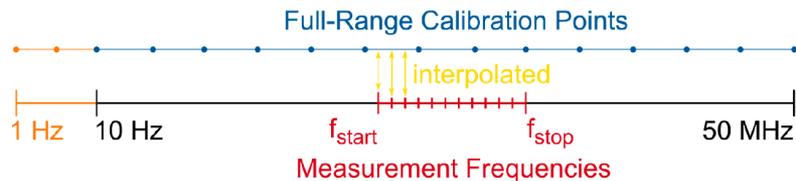+ Calibration does not get lost when frequency range is changed




Why is it important to measure capacitors?

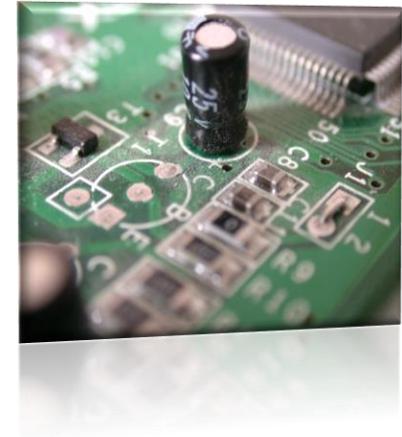- A capacitor is **NEVER** just a capacitor
- Capacitor ESR influences the phase margin of power supplies
- Capacitor ESR influences the output ripple at the switching frequency of a SMPS
- ESR can change over Frequency
- Capacitors are inductors above their resonance frequency



What does the data sheet tell us?

220 μ F aluminum capacitor

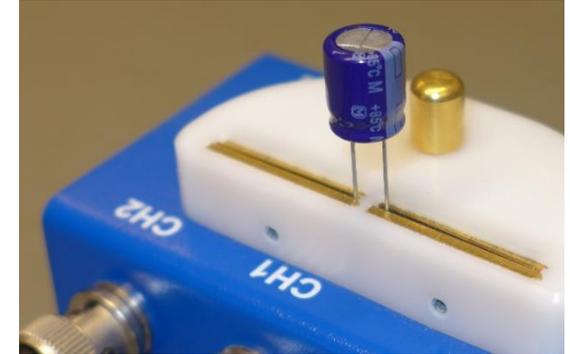





■ Standard Products

W.V.	Cap. ($\pm 20\%$)	Case size		Specification		Lead Length			Part No.	Min. Packaging Q'ty		
		Dia.	Length	Ripple Current (120 Hz) (+85 °C)	$\tan \delta$ (120 Hz) (+20 °C)	Lead Dia.	Lead Space			Straight Leads	Taping	
							Straight	Taping *B				Taping *i
(V)	(μ F)	(mm)	(mm)	(mA r.m.s.)		(mm)	(mm)	(mm)				
	220	10	12.5	400	0.12	0.6	5.0	5.0	ECA1HM221()	200	500	

$$C = 220\mu\text{F} (\pm 20\%)$$

$$ESR = \frac{\tan(\delta)}{\omega C} = \frac{0.12}{2\pi \cdot 120\text{Hz} \cdot 220\mu\text{F}} = 720 \text{ m}\Omega @ 120 \text{ Hz}$$


This is what the measurement tells us

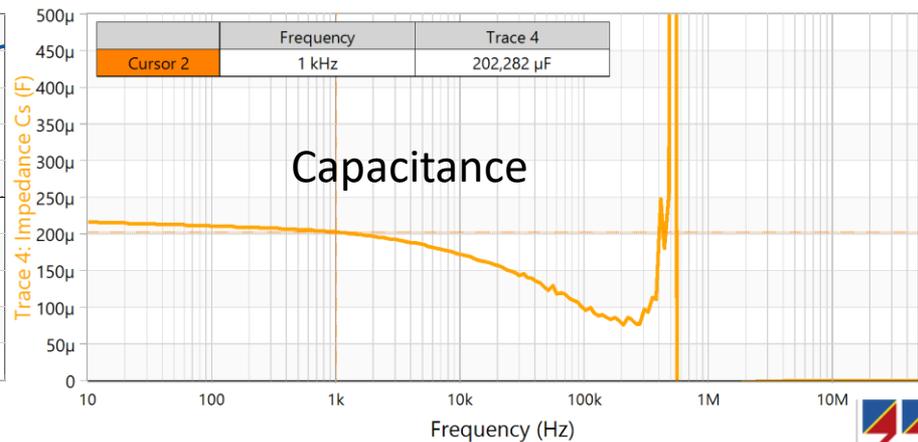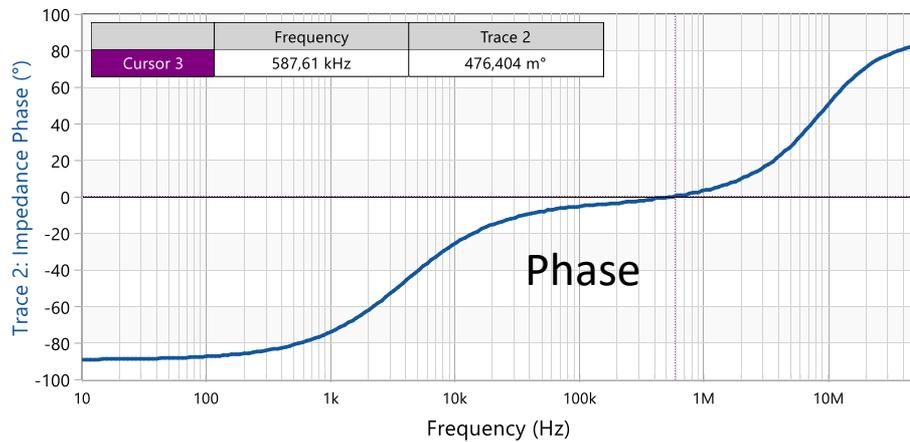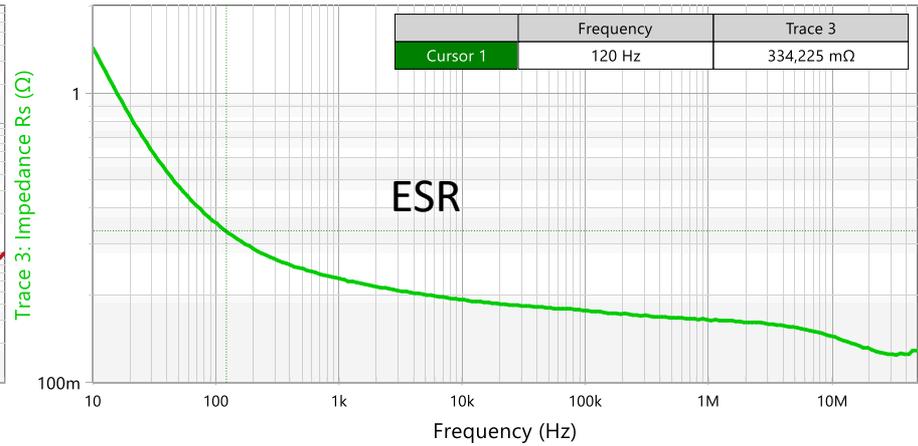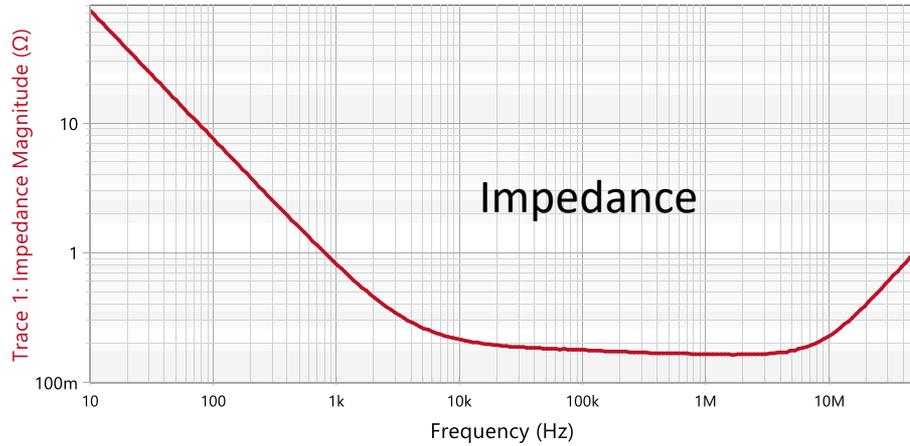

Live Comparison Measurement

Measurement of different types of 10 μF capacitors

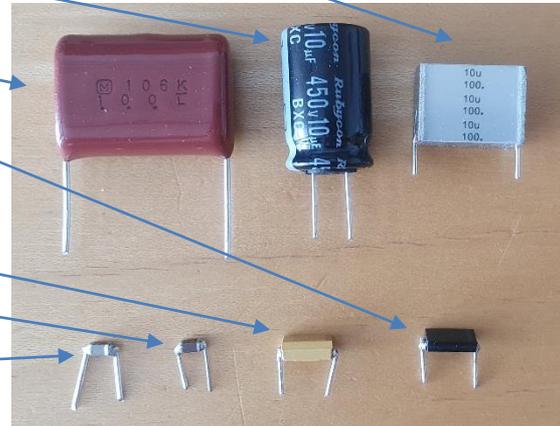- film (MKT / PET)
- aluminum
- film (PET)
- aluminum polymer
- tantalum
- ceramic (X5R)
- ceramic (X7R)



Why should we measure inductors?

- An inductor is **NEVER** just an inductor
- AC resistance \leftrightarrow DC resistance
 - skin effects
 - “Eddie Currents”
- Inductors have resonance frequencies
- Inductors with magnetic cores can have core losses

What does the data sheet tell us?

33 μH shielded power inductor

Properties	Test conditions		Value	Unit	Tol.
Inductance	1 kHz/ 250 mV	L	33	μH	$\pm 20\%$
Rated current	$\Delta T = 40 \text{ K}$	I_R	2.68	A	max.
Saturation current	$ \Delta L/L < 10\%$	I_{sat}	3.00	A	typ.
DC Resistance	@ 20°C	R_{DC}	0.049	Ω	typ.
DC Resistance	@ 20°C	R_{DC}	0.057	Ω	max.
Self resonant frequency		f_{res}	11	MHz	typ.







$H = 33\mu\text{H} (\pm 20\%) @ 1 \text{ kHz}$

$R_{\text{DC}} = 0,049 \Omega (\text{typ.})$

$R_{\text{DC}} = 0,057 \Omega (\text{max.})$

$f_{\text{res}} = 11 \text{ MHz}$


This is what the measurement tells us:

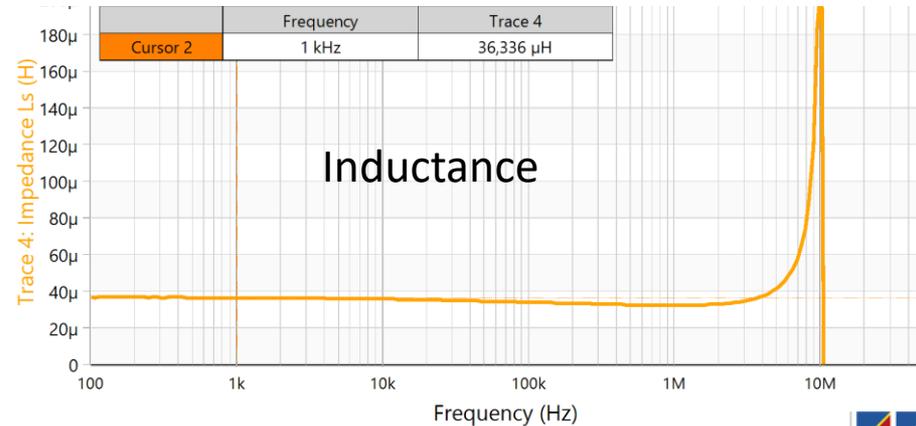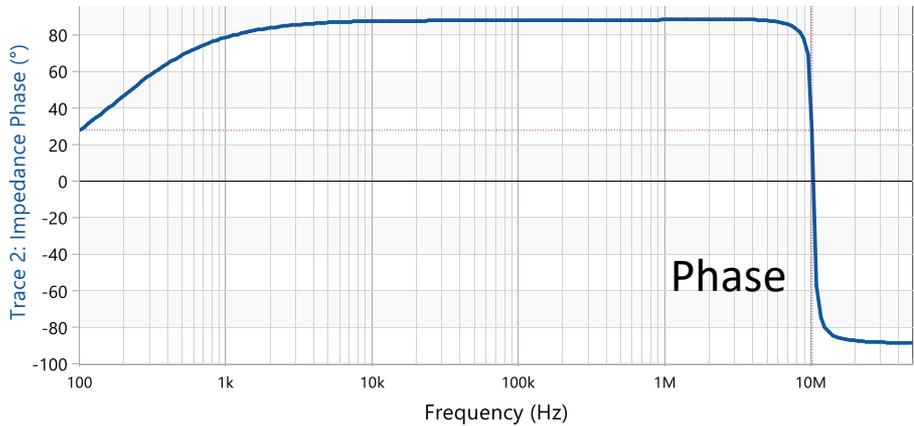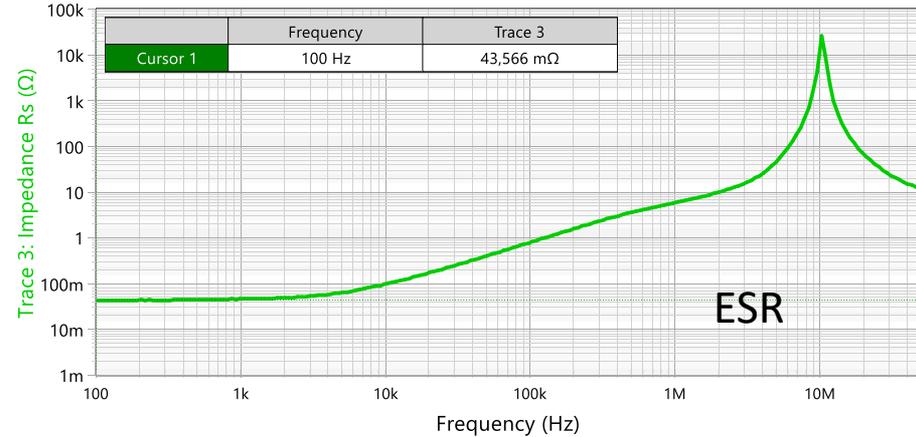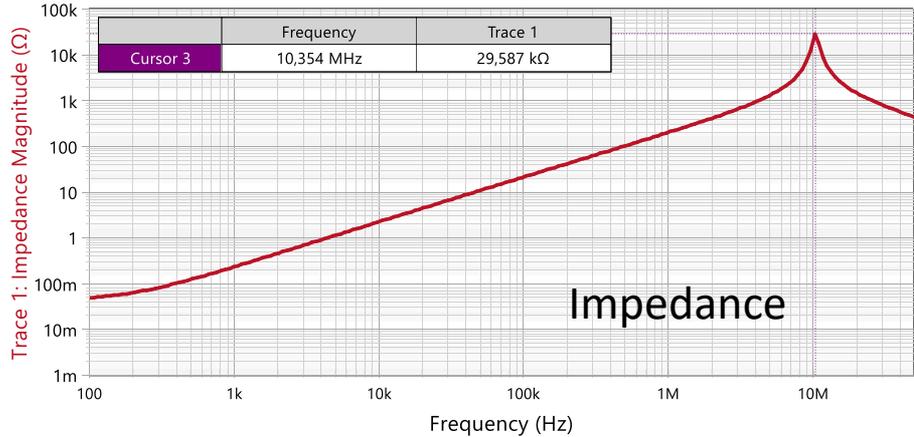

Live Comparison Measurement


Measurement of different types of 100 μH inductors

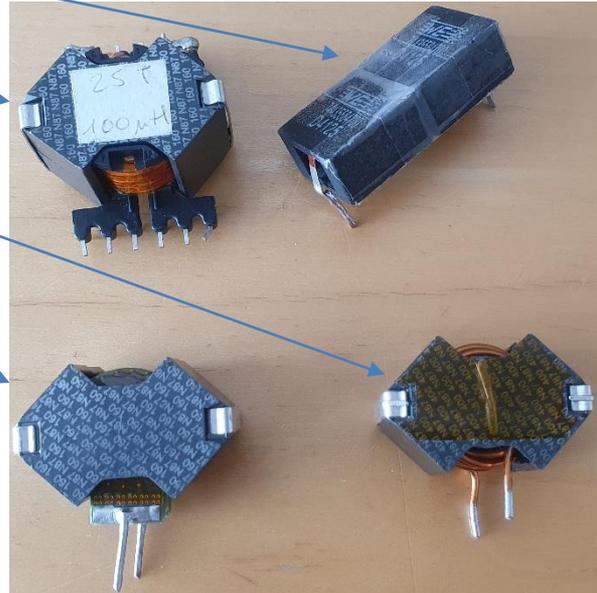- SMD flat band
- litz wire
- copper wire
- planar coils
(PCB winding structure)




Flyback Transformer Leakage Inductance

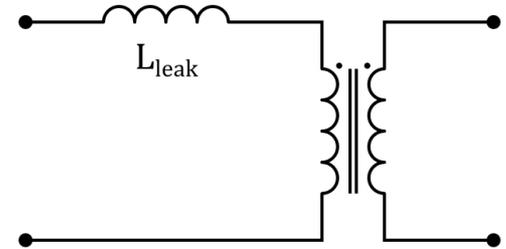- Not all flux generated by the primary winding is coupled to the secondary winding
 - some flux leaks
 - some contributes to core losses
- Represented by a series inductance in the circuit
- Leakage inductance creates a voltage spike when turning off current through primary side (flyback converter)



Measuring Leakage Inductance

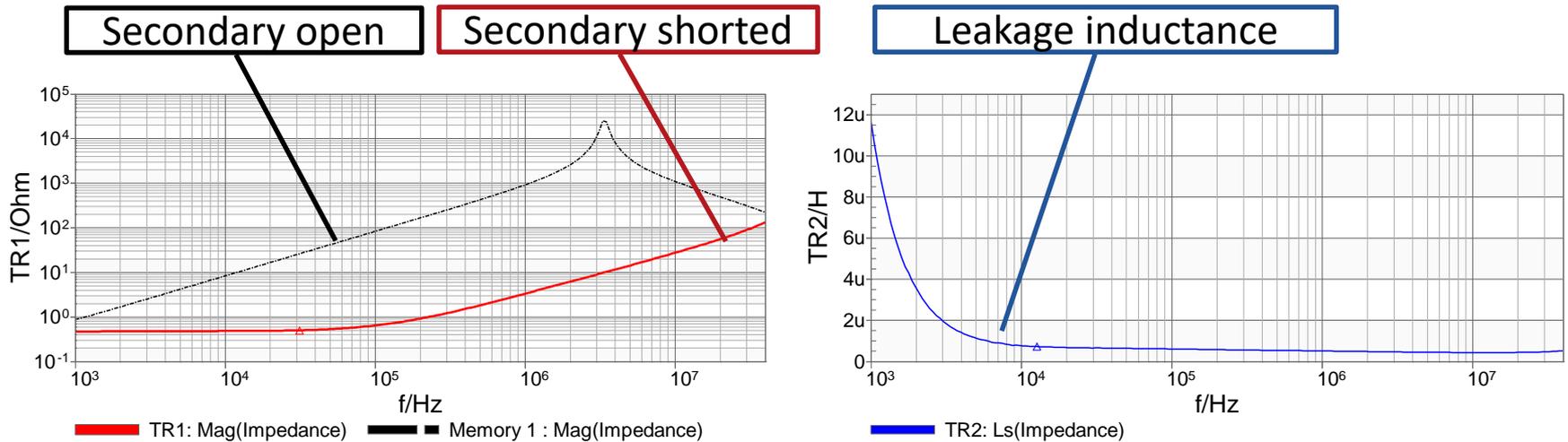Leakage inductance is measured by shorting all other windings except the primary winding



→ Leakage inductance is not constant over frequency

Additional Hands-On Live-Measurements

- Shunt-Thru measurement of
 - $m\Omega$ resistor
 - low ESR capacitor

- Series-Thru measurement

Summary

- Component parasitics are important to understand real life circuit behavior
- Models considering parasitics allow better simulation
- Measuring components can tell us more than the data sheet says



References and Further Reading

- [1] OMICRON Lab, Bode 100 User Manual, <https://www.omicron-lab.com/downloads/vector-network-analysis/bode-100/>
- [2] OMICRON Lab, Impedance Measurement Application Notes, <https://www.omicron-lab.com/applications/vector-network-analysis/application-notes/#cuid1:pathGroup=.cuid10>



Feel free to ask questions via the Q&A function...

If time runs out, please send us an e-mail and we will follow up.
You can contact us at: info@omicron-lab.com

Thank you for your attention!